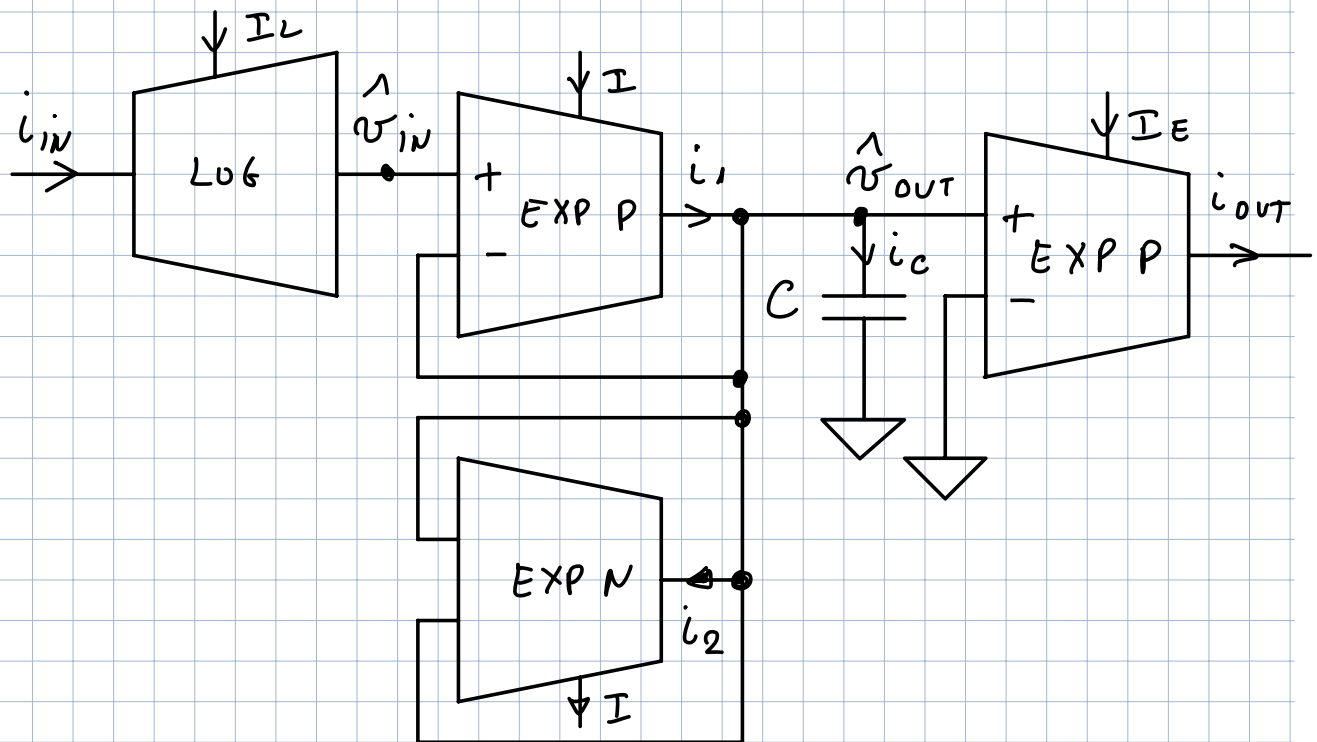


LABORATOR 6



$$i_c = C \frac{d \hat{v}_{out}}{dt}$$

$$i_c = i_1 - i_2$$

$$i_1 = I \exp\left(\frac{\hat{v}_{in} - \hat{v}_{out}}{2V_T}\right) - I$$

$$i_2 = I \exp\left(\frac{\hat{v}_{out} - \hat{v}_{out}}{2V_T}\right) - I$$

$$C \frac{d \hat{v}_{out}}{dt} = I \exp\left(\frac{\hat{v}_{in} - \hat{v}_{out}}{2V_T}\right) - \cancel{I} - I \exp\left(\frac{\hat{v}_{out} - \hat{v}_{out}}{2V_T}\right) + \cancel{I}$$

$$C \frac{d \hat{v}_{out}}{dt} = I \exp\left(\frac{\hat{v}_{in} - \hat{v}_{out}}{2V_T}\right) - I \exp\left(\frac{\hat{v}_{out} - \hat{v}_{out}}{2V_T}\right)$$

$$C \frac{d\hat{v}_{out}}{dt} \exp\left(\frac{\hat{v}_{out}}{2V_T}\right) = I \exp\left(\frac{\hat{v}_{in}}{2V_T}\right) - I \exp\left(\frac{\hat{v}_{out}}{2V_T}\right)$$

$u'(t) \cdot \exp(u(t))$

$$2V_T \cdot C \frac{d}{dt} \left(\exp\left(\frac{\hat{v}_{out}}{2V_T}\right) \right) = I \exp\left(\frac{\hat{v}_{in}}{2V_T}\right) - I \exp\left(\frac{\hat{v}_{out}}{2V_T}\right)$$

$$\frac{d}{dt} \left(\exp\left(\frac{\hat{v}_{out}}{2V_T}\right) \right) = \frac{I}{2V_T \cdot C} \exp\left(\frac{\hat{v}_{in}}{2V_T}\right) - \frac{I}{2V_T \cdot C} \exp\left(\frac{\hat{v}_{out}}{2V_T}\right)$$

$$\Delta \exp\left(\frac{\hat{v}_{out}}{2V_T}\right) + \frac{I}{2V_T \cdot C} \exp\left(\frac{\hat{v}_{out}}{2V_T}\right) = \frac{I}{2V_T \cdot C} \exp\left(\frac{\hat{v}_{in}}{2V_T}\right)$$

$$\exp\left(\frac{\hat{v}_{out}}{2V_T}\right) \left(\Delta + \frac{I}{2V_T \cdot C} \right) = \exp\left(\frac{\hat{v}_{in}}{2V_T}\right) \cdot \frac{I}{2V_T \cdot C}$$

$$\frac{\exp\left(\frac{\hat{v}_{out}}{2V_T}\right)}{\exp\left(\frac{\hat{v}_{in}}{2V_T}\right)} = \frac{\frac{I}{2V_T \cdot C}}{\Delta + \frac{I}{2V_T \cdot C}}$$

$$\hat{v}_{out} = 2V_T \ln\left(\frac{i_{in}}{I_L}\right) \quad \Bigg| \quad i_{in} = i_{in} + I_L$$

$$\hat{v}_{in} = 2V_T \ln\left(\frac{i_{out}}{I_E}\right) \quad \Bigg| \quad i_{out} = i_{out} + I_E$$

$$\frac{\exp\left(\frac{2V_T \ln\left(\frac{i_{OUT}}{I_E}\right)}{2V_T}\right)}{\exp\left(\frac{2V_T \ln\left(\frac{i_{IN}}{I_L}\right)}{2V_T}\right)} = \frac{\frac{I}{2V_T \cdot C}}{\Delta + \frac{I}{2V_T \cdot C}}$$

$$\frac{\exp\left(\ln\left(\frac{i_{OUT}}{I_E}\right)\right)}{\exp\left(\ln\left(\frac{i_{IN}}{I_L}\right)\right)} = \frac{1}{\frac{\Delta}{\frac{I}{2V_T \cdot C}} + 1}$$

$$\frac{i_{OUT}}{i_{IN}} = \frac{\frac{I_E}{I_L}}{1 + \frac{\Delta}{\frac{I}{2V_T \cdot C}}} = H(\omega) = \frac{A_0}{1 + \frac{\omega}{\omega_0}}$$

$$A_0 = \frac{I_E}{I_L}$$

$$\omega_0 = \frac{I}{2V_T \cdot C}$$