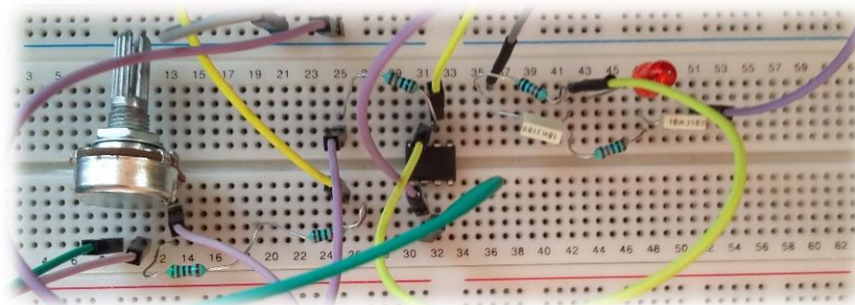




ELECTRONIC DEVICES

Assoc.prof. Laura-Nicoleta IVANCIU, Ph.D.

C1 – Introduction. Fundamentals.



Contents

- Course presentation
- Desired outcome. Evaluation.
- Fundamentals

Course presentation

Fundamentals

- Electrical signals
- Relations and laws for electrical circuits
- RC circuits – time and frequency response

Diodes (D)

- Types, operating principle, characteristic, parameters
- Diode circuits
- Zener diodes, LEDs


Operational Amplifiers (OpAmps)

- Ideal OpAmp, operating principle, characteristics, parameters, operating modes
- OpAmp comparators
- OpAmp amplifiers
- Applications with OpAmp


Transistors (T)

- Types, operating principles, characteristics, parameters
- Bipolar junction transistors (BJTs)
- Field-effect transistors (MOSFET)

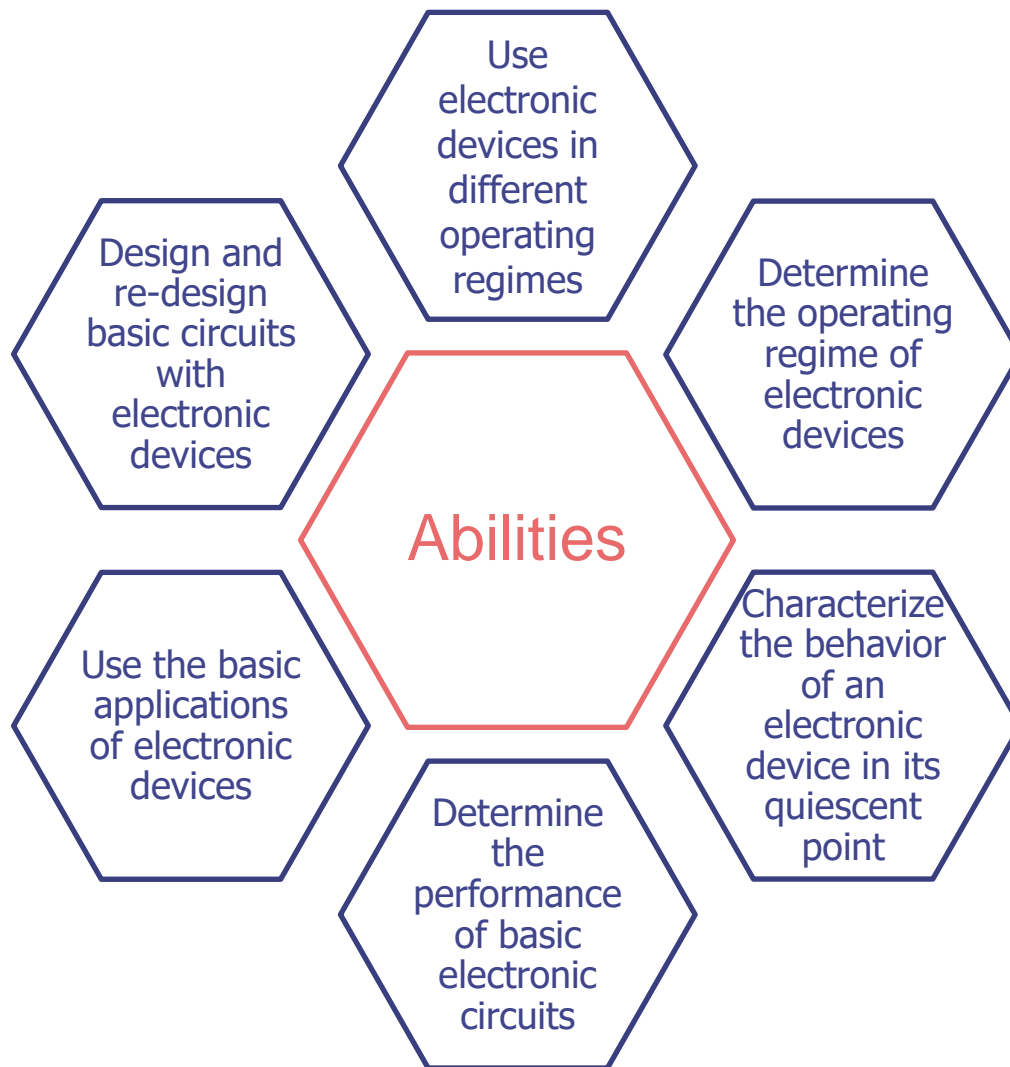At the end of the semester, you will be able to



Provided that you spend

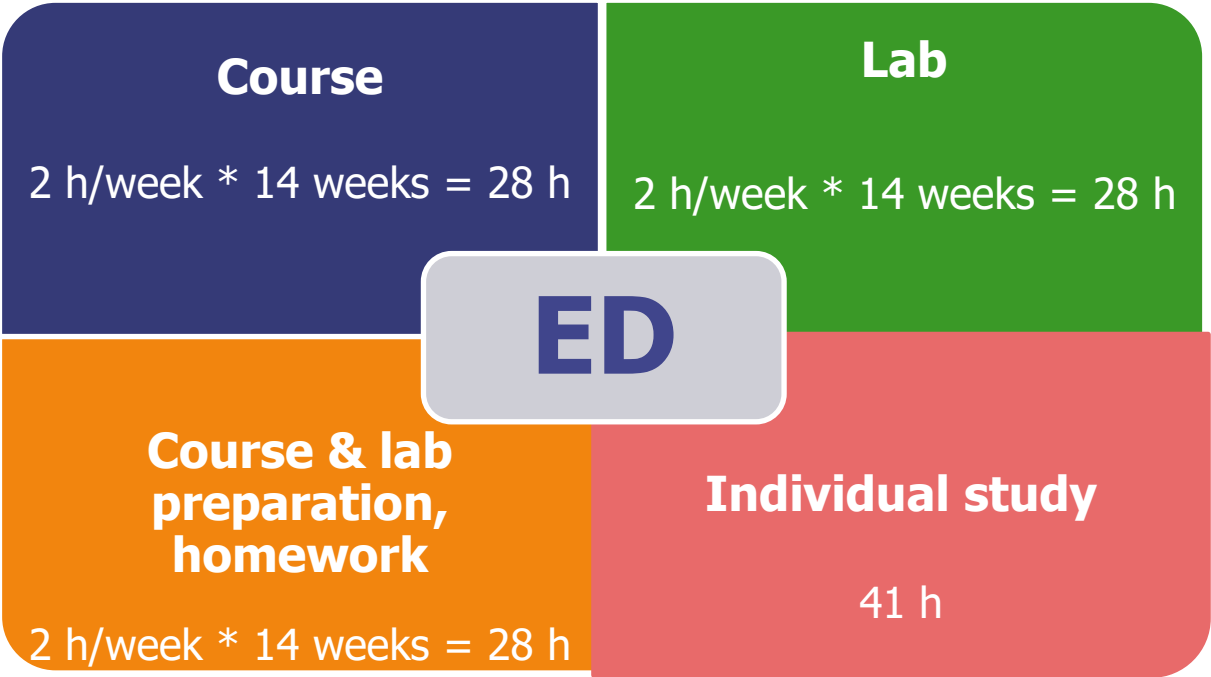

www.bel.utcluj.ro/dce/didactic/ed/



Activities - weekly

- Course – optional attendance
Tuesday, 10-12, room 41

Reasons to attend:

- complete solutions for examples
- not everything is on the slides
- inside jokes and memes

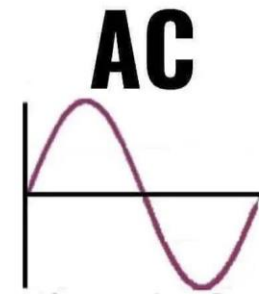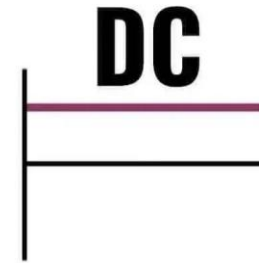- Lab – **mandatory** attendance
as scheduled, room BT 1.03



Evaluation

Written exam (**E**)
0...10 points


- problem solving

Laboratory (**L**)
0...10 points

- full attendance
- activity
- practical test

Course homework (**H**)
0...1 point

- problems - optional

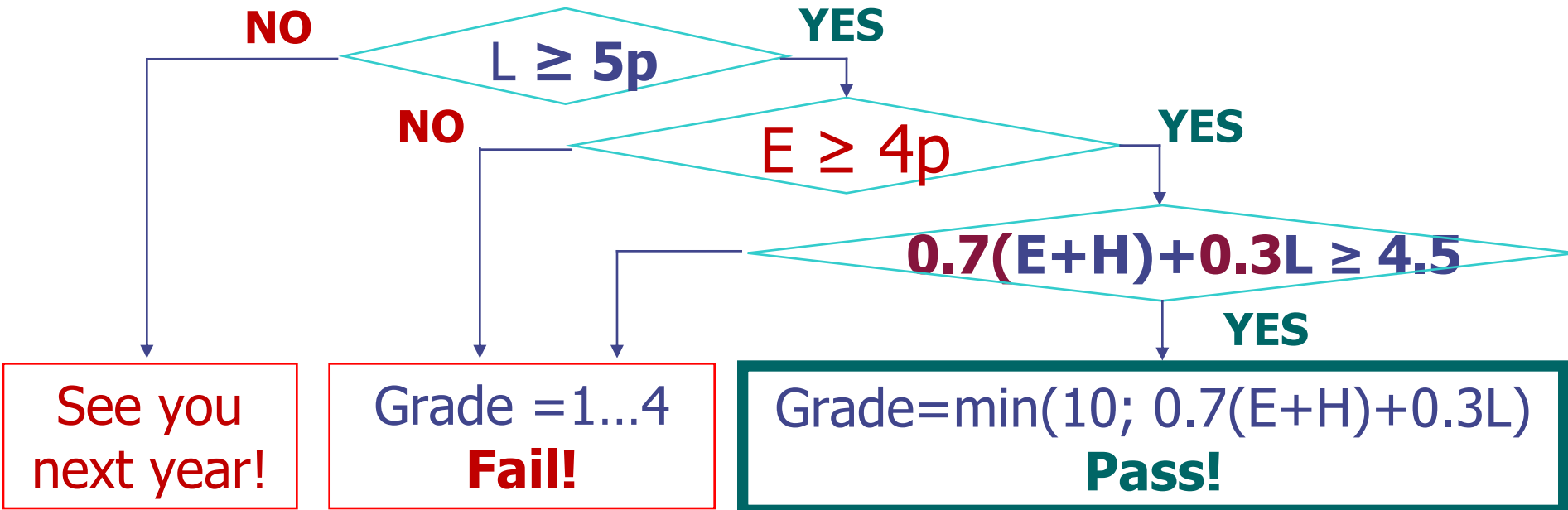


Fundamentals

➤ Electrical signals



a)

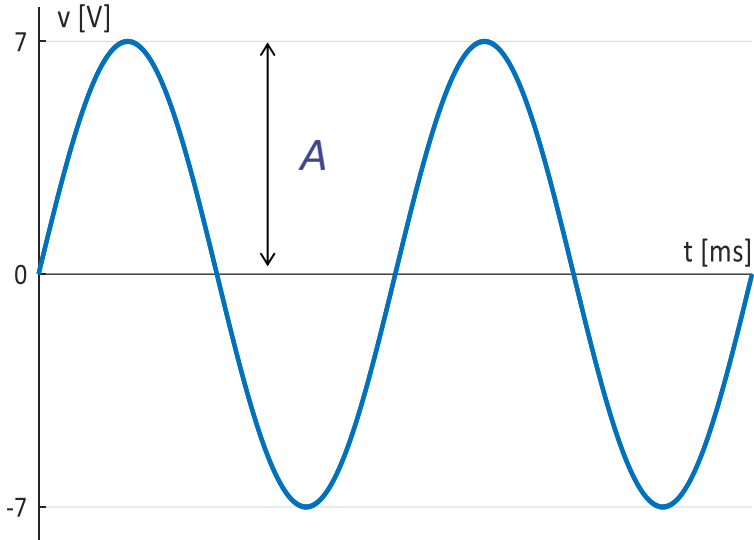

b)


Time variation of a:

a) continuous voltage (dc);


b) sinusoidal voltage (ac)

Fundamentals


➤ Sources. Notations.

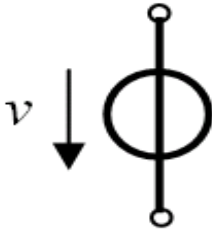


ac voltage

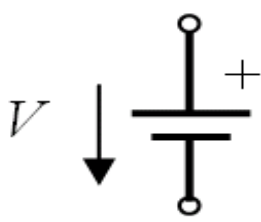

dc voltage

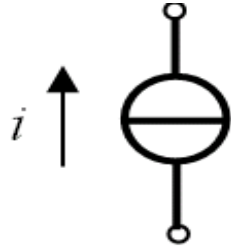


current

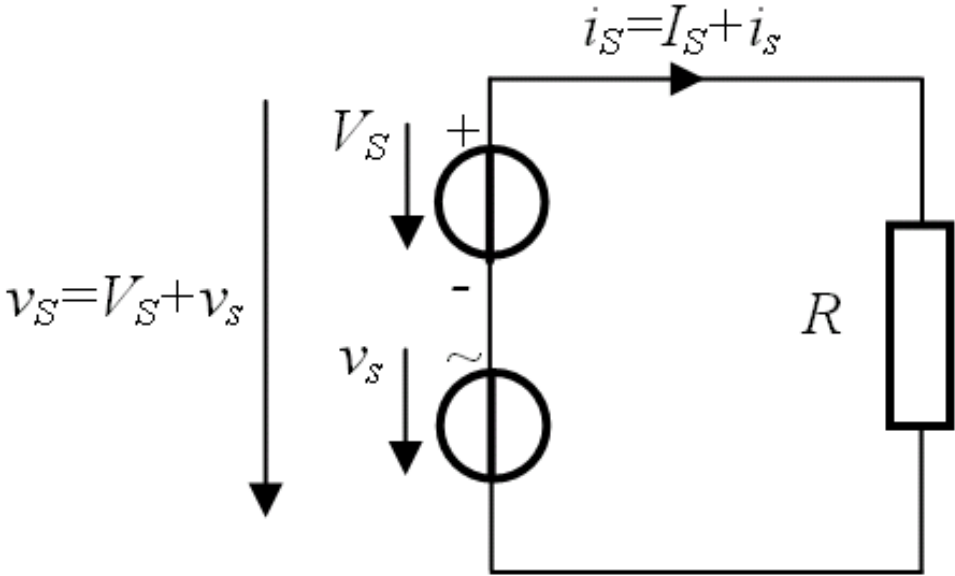


Fundamentals

➤ Ohm's law. Kirchhoff's laws.

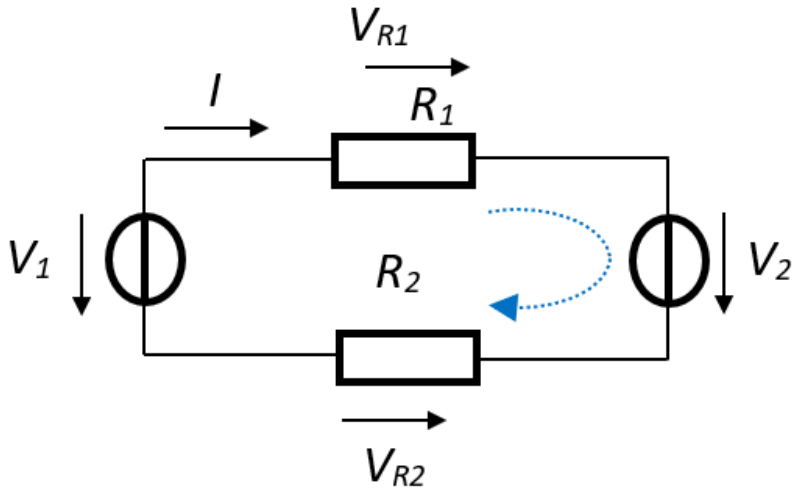

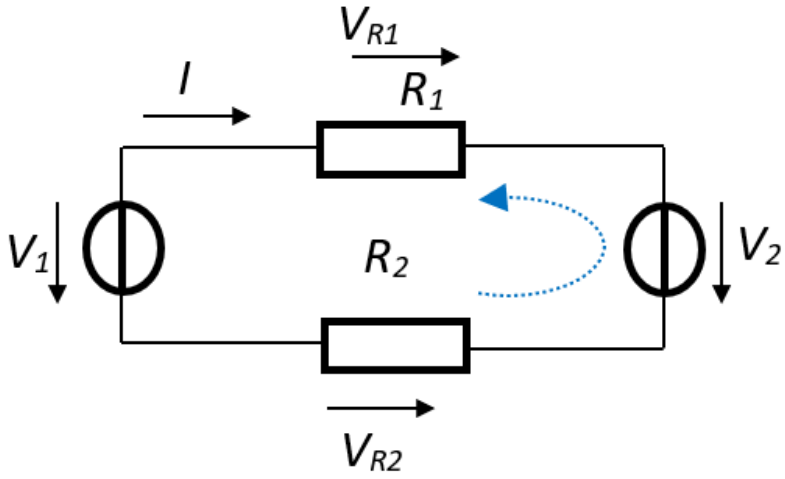
$$-V_1 + R_1 \cdot I + V_2 - R_2 \cdot I = 0$$



$$V_1 - R_1 \cdot I - V_2 + R_2 \cdot I = 0$$

Fundamentals

➤ Resistive divider

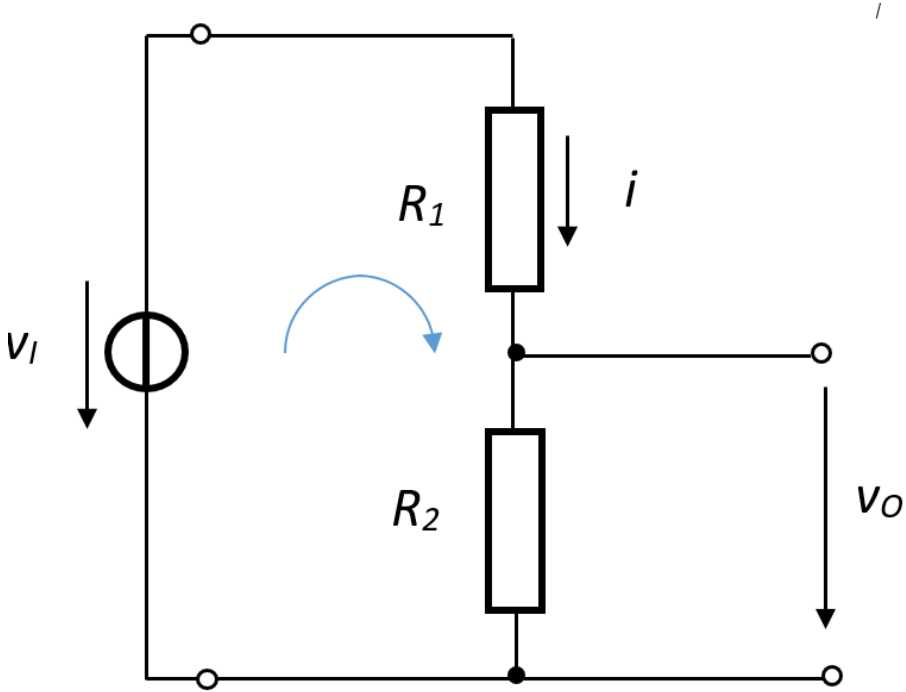


$$i = \frac{V_1}{R_1 + R_2}$$


$$V_0 = i \cdot R_2 = \frac{R_2}{R_1 + R_2} \cdot V_1$$

Fundamentals

➤ Adjustable resistive divider

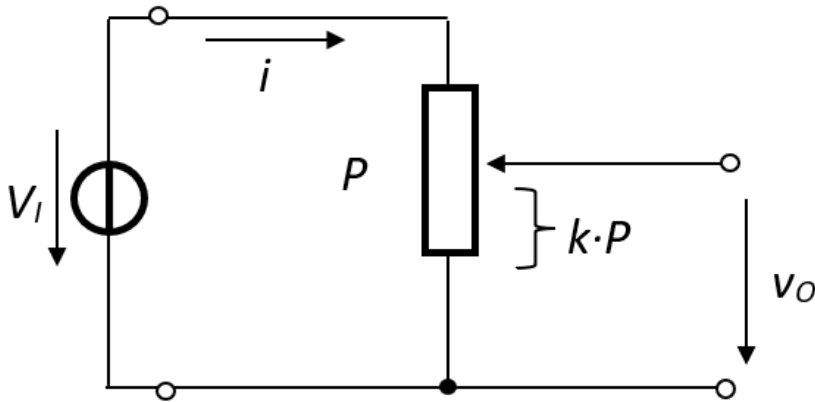
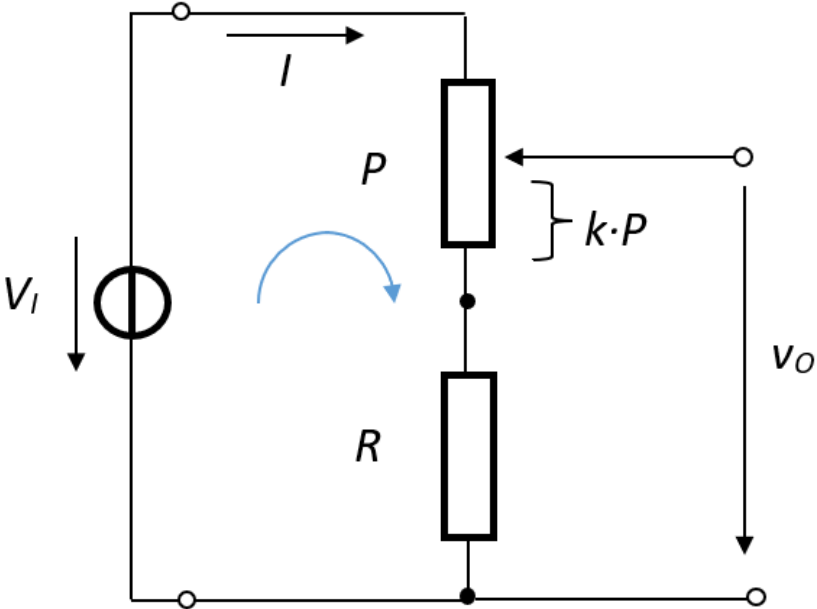
$$V_O = \frac{k \cdot P}{P} V_I = k \cdot V_I$$




$$V_O = \frac{k \cdot P + R}{P + R} \cdot V_I$$



$$V_O \text{ min/max} = ?$$

Fundamentals

➤ Superposition method

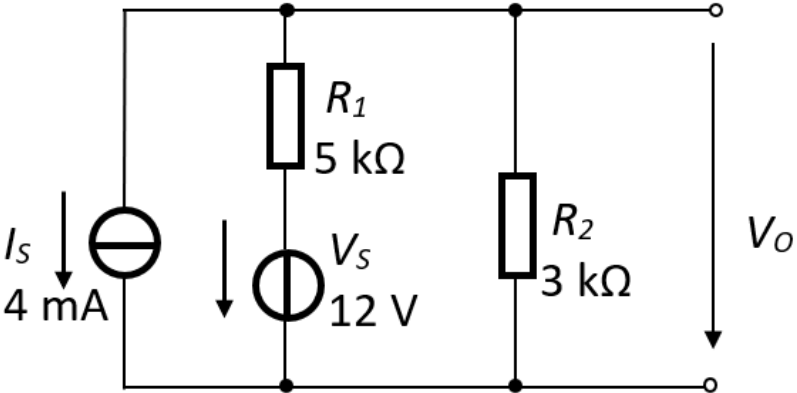


$$V_o = V_{o1} + V_{o2}$$

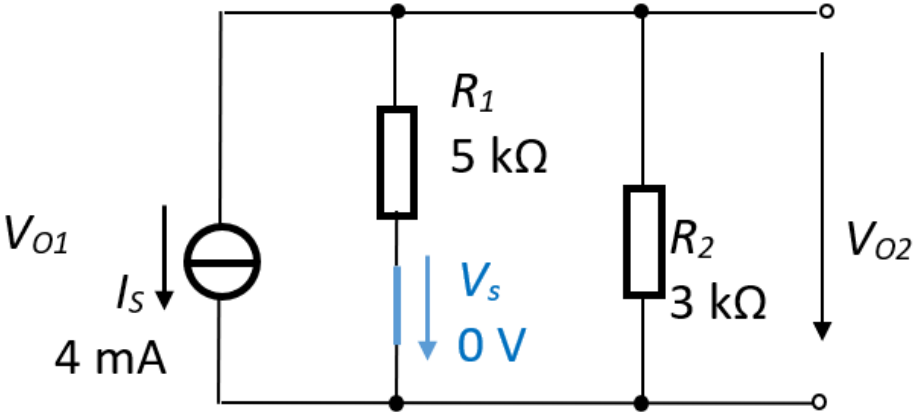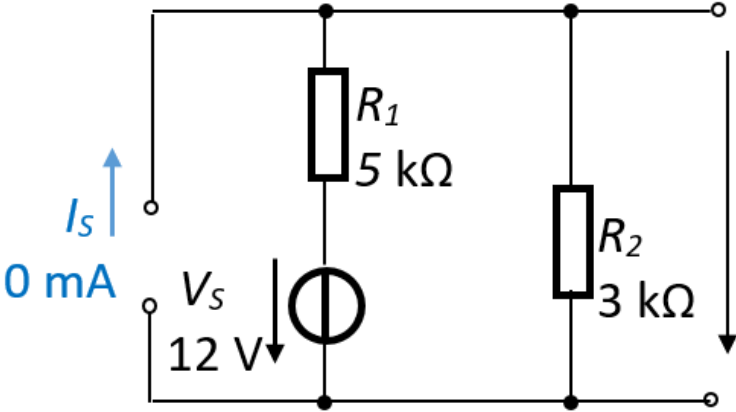

Fundamentals

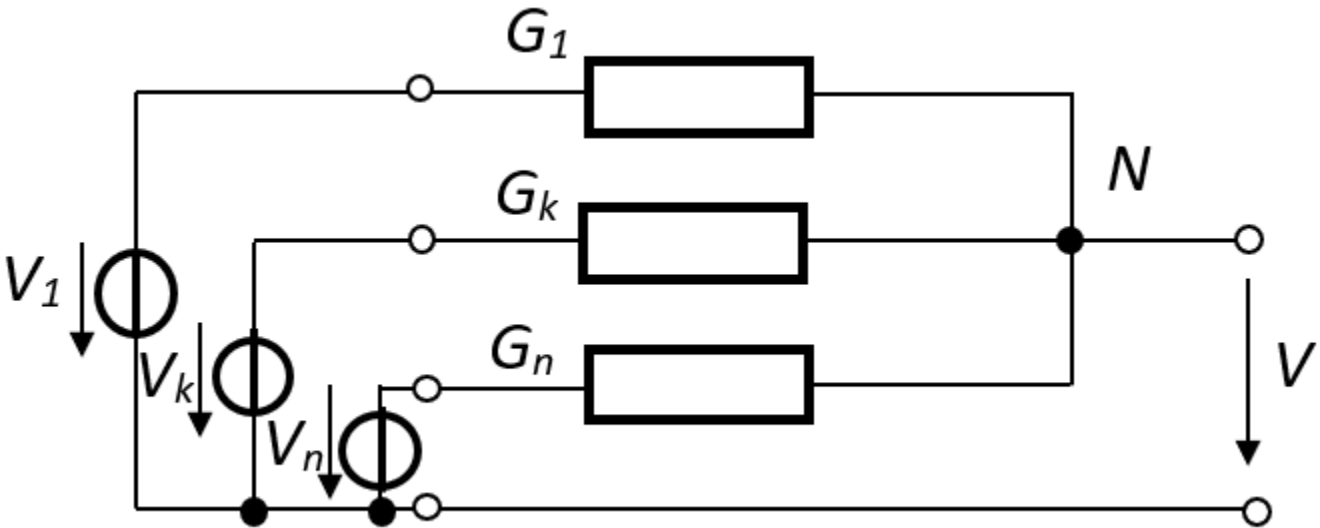
➤ Millman's theorem (nodes potential theorem)



$$V = \frac{\sum_{k=1}^n V_k \cdot G_k}{\sum_{k=1}^n G_k} = \frac{\sum_{k=1}^n V_k \cdot \frac{1}{R_k}}{\sum_{k=1}^n \frac{1}{R_k}}$$

Fundamentals

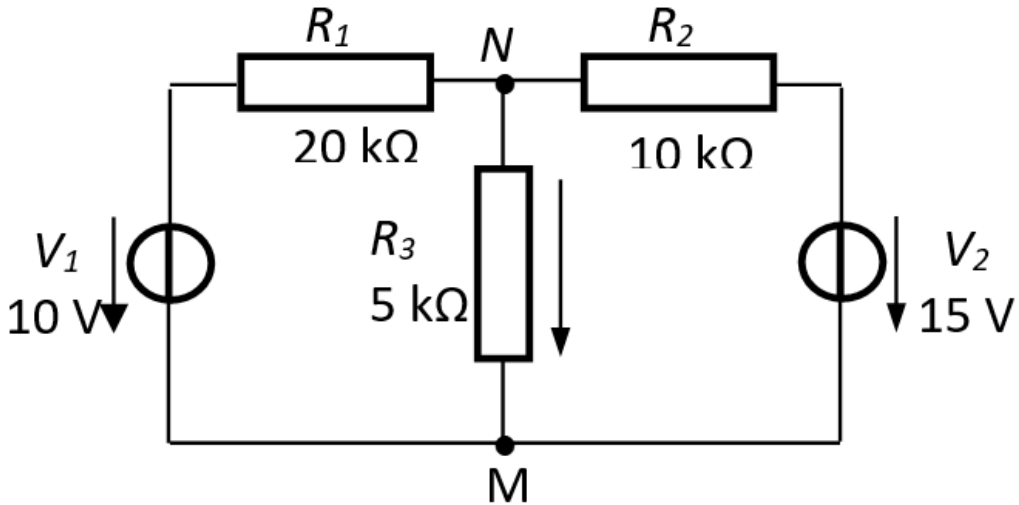➤ Millman's theorem (nodes potential theorem)




M - the reference point (ground)

$$V_N = \frac{V_1 \cdot G_1 + V_2 \cdot G_2 + 0 \cdot G_3}{G_1 + G_2 + G_3} = \frac{V_1 \cdot \frac{1}{R_1} + V_2 \cdot \frac{1}{R_2} + 0 \cdot \frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{10}{20} + \frac{15}{10}}{\frac{1}{20} + \frac{1}{10} + \frac{1}{5}} = 5.71 \text{ V}$$

Fundamentals

➤ Power. Power transfer.

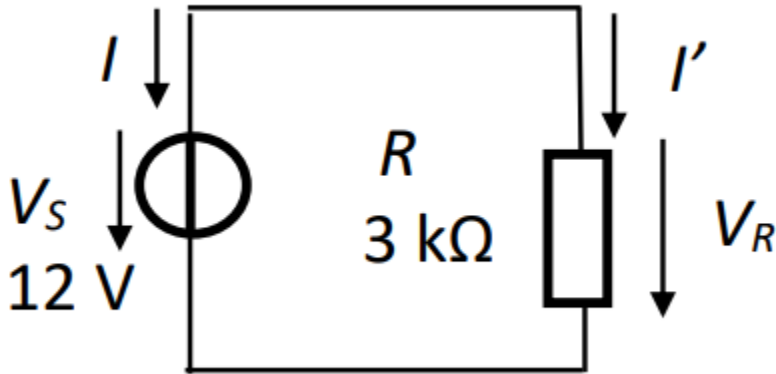


$$I = -\frac{V_S}{R} = -3\text{ mA}$$
$$I' = -I = 3\text{ mA}$$

$P_S = V_S I = 12\text{V} \cdot (-3\text{mA}) = -36\text{mW}$; the power is **generated** by the source.

$P_R = V_R I' = 12\text{V} \cdot 3\text{mA} = 36\text{mW}$; the power is **dissipated** by the resistor.

Fundamentals

➤ RC circuits

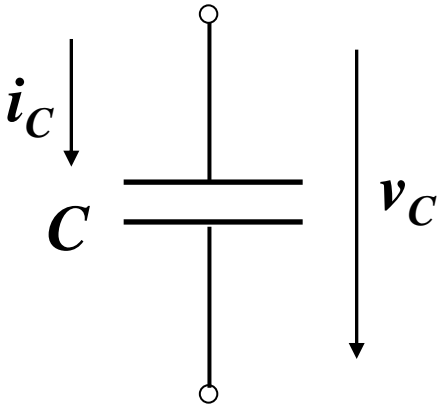

Relation between current and voltage:

$$Cdv_C(t) = i_C(t)dt$$


Assuming finite variations:

$$C\Delta v_C = i_C\Delta t$$

Fundamentals

➤ RC circuits – time domain analysis

RC circuit with a dc voltage source

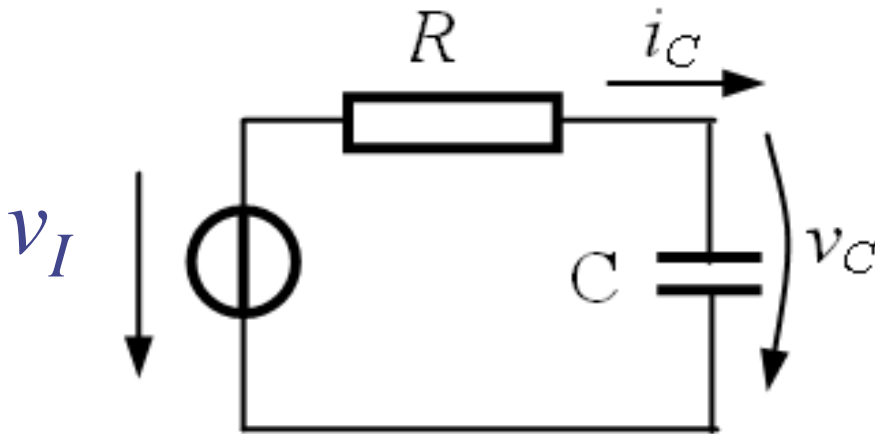

$$Ri_C(t) + v_C(t) = v_I(t)$$

$$Cdv_C(t) = i_C(t)dt$$

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_I(t)$$


$\tau = RC$ time constant of the circuit

$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$



Fundamentals

➤ RC circuits – time domain analysis

RC circuit with a dc voltage source

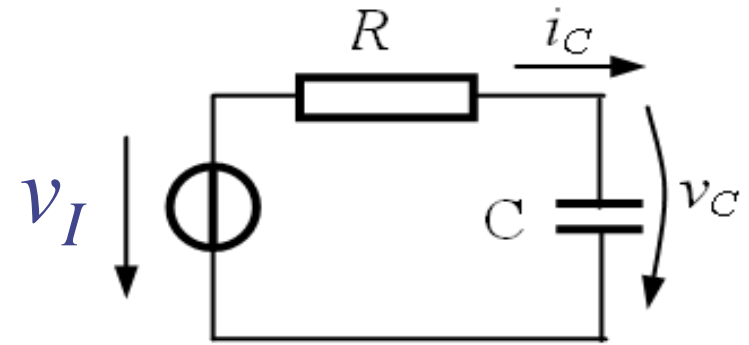

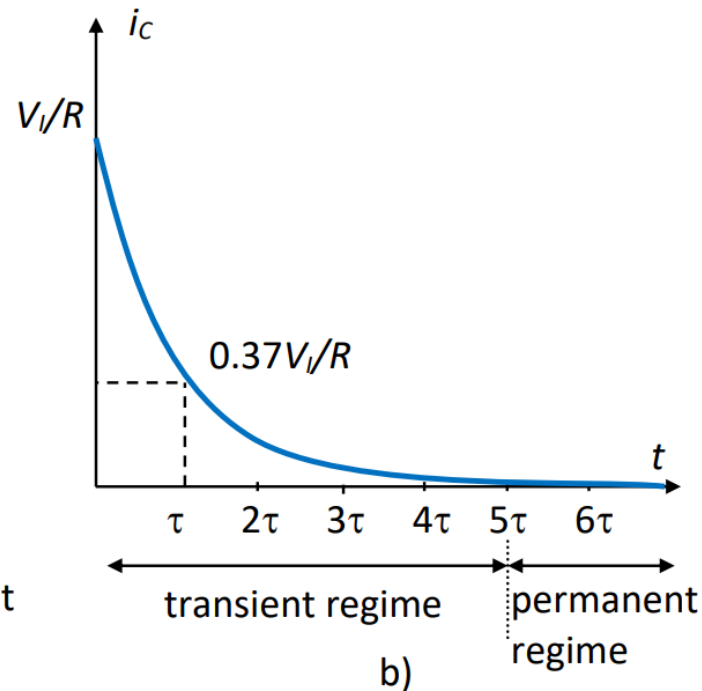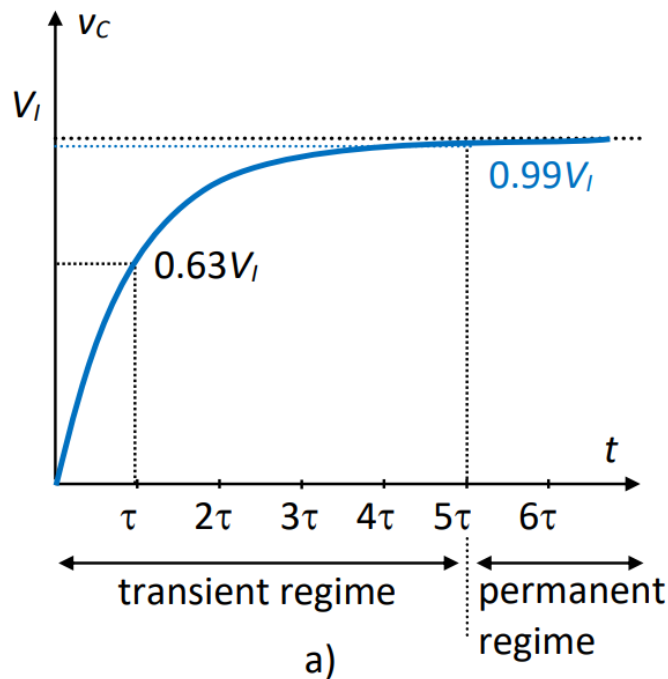
$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$





Fundamentals

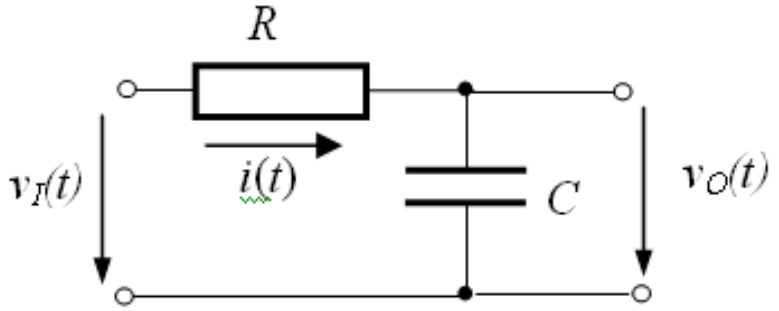- RC circuits – time domain analysis
- RC circuit with an ac voltage source


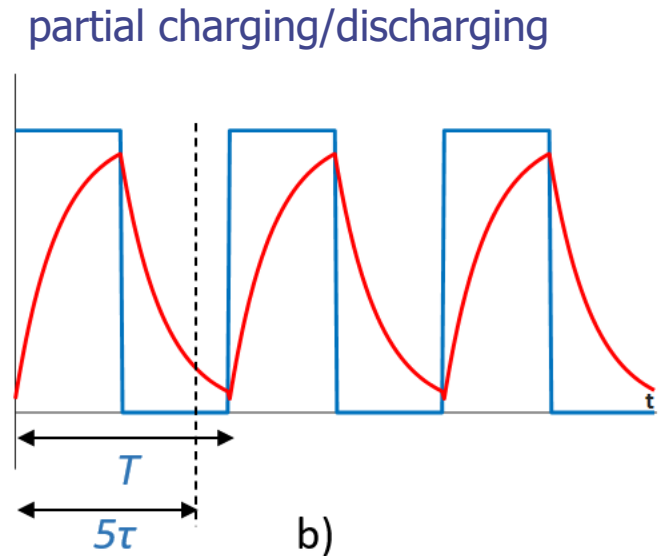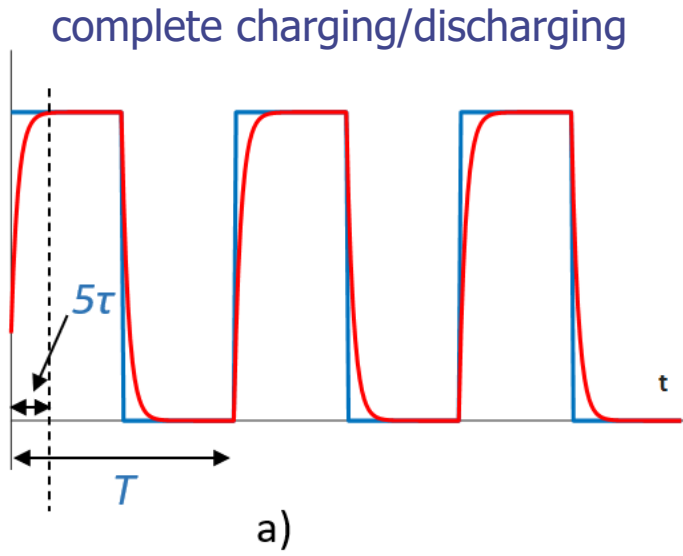
$$v_C(t) = v_C(0)e^{-\frac{t}{\tau}} + (1 - e^{-\frac{t}{\tau}})v_C(\infty)$$




Fundamentals

- Capacitor charging under a constant current

$$Cdv_c(t) = i_c(t)dt$$


$$v_c(t) = \frac{1}{C} \int_0^t i_c(t)dt + v_c(0)$$

$$v_c(t) = \frac{1}{C} It + v_c(0)$$

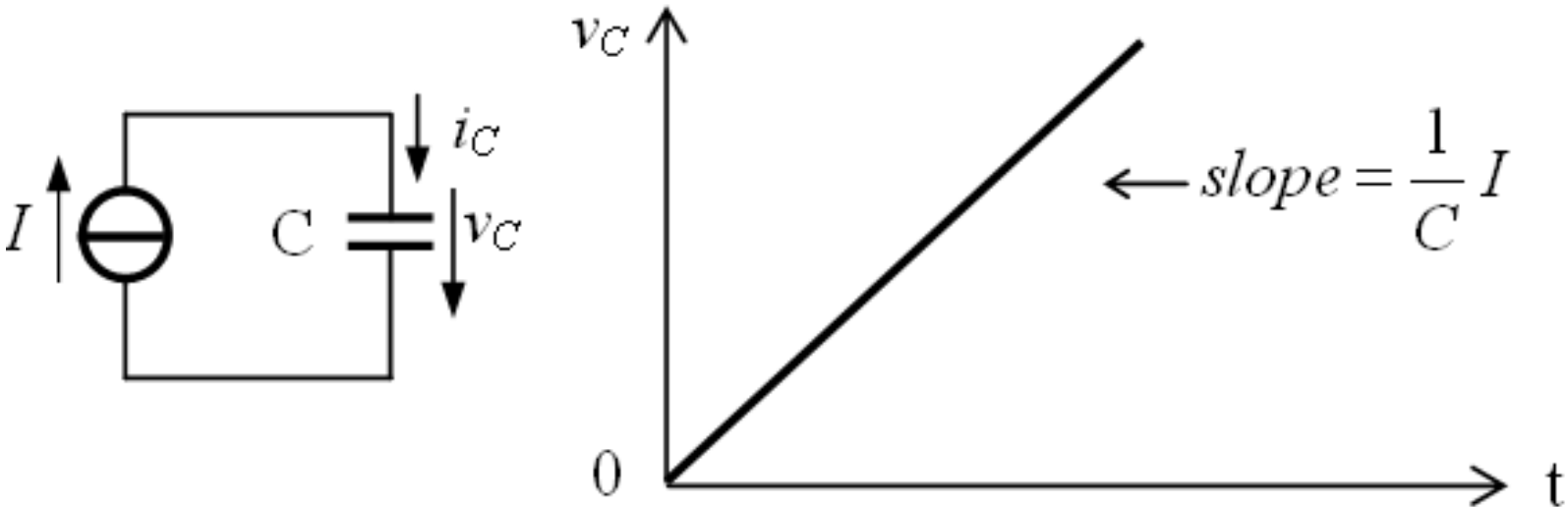

Fundamentals

➤ RC circuit – frequency response

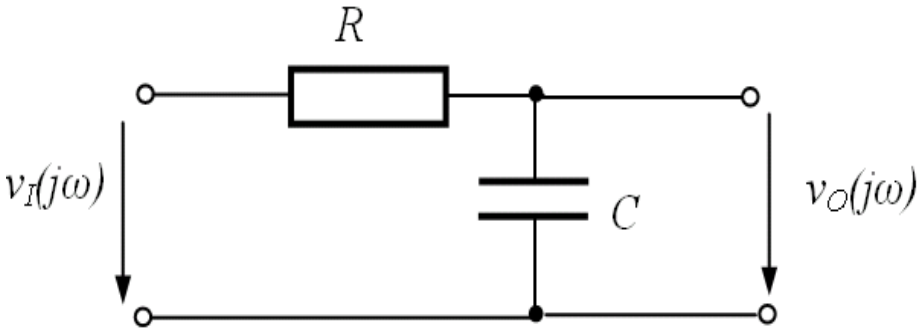

$$Z_C = \frac{1}{j\omega C}$$

Low frequency:

$f \rightarrow 0$; $Z_C \rightarrow \infty$; output \rightarrow open circuit; $v_O(j\omega) \rightarrow v_I(j\omega)$ **pass**


High frequency:

$f \rightarrow \infty$; $Z_C \rightarrow 0$; output \rightarrow short-circuit; $v_O(j\omega) \rightarrow 0$ **don't pass (reject)**

First order, passive, low-pass filter (LPF)

Fundamentals

➤ RC circuit – frequency response

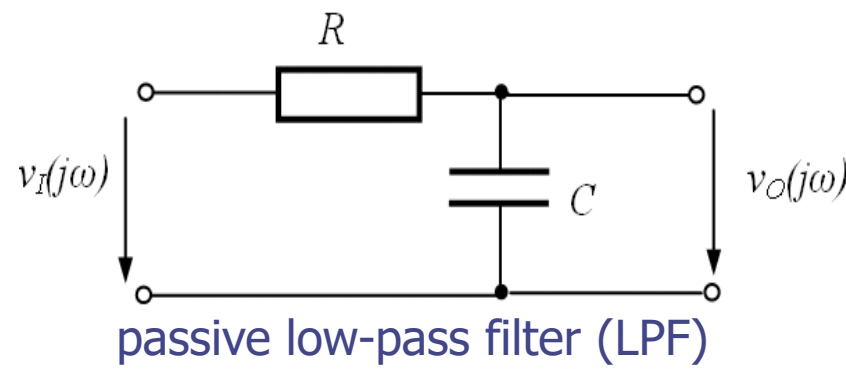

Transfer function

$$F(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{1}{1 + j\omega RC}$$

$$|F(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\Phi(\omega) = -\text{arctg}(\omega RC)$$

f – very low; $|F(j\omega)| \approx 1$

f – high; $|F(j\omega)| \approx \frac{1}{\omega RC}$



$$1 = \frac{1}{\omega_0 RC} \Rightarrow \omega_0 = \frac{1}{RC} \Rightarrow$$

$$f_0 = \frac{1}{2\pi RC}$$


Cut-off frequency

Fundamentals

➤ RC circuit – frequency response

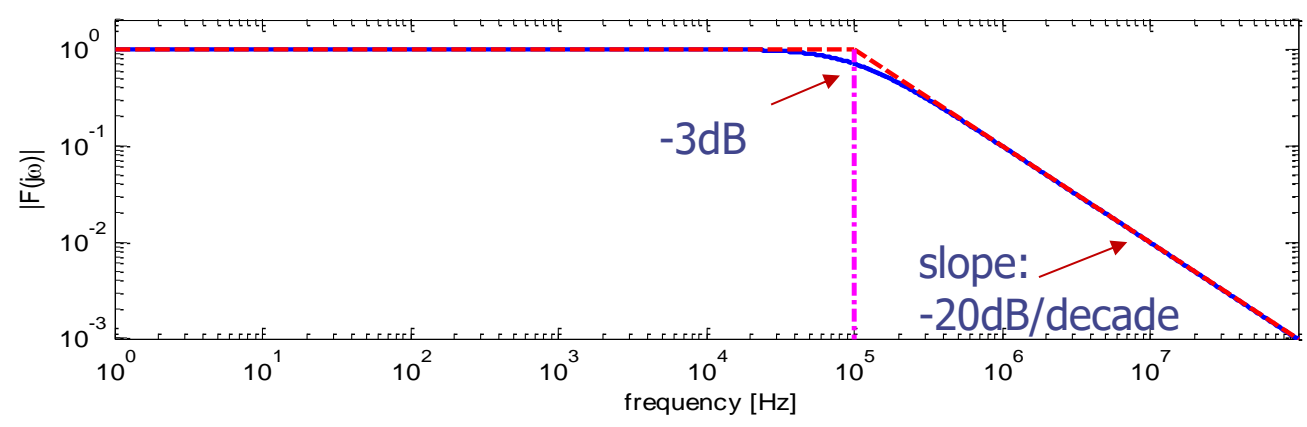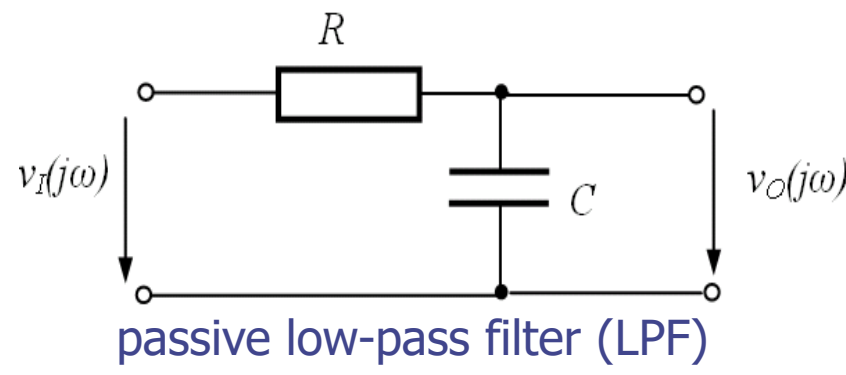


magnitude response (log-log plot)

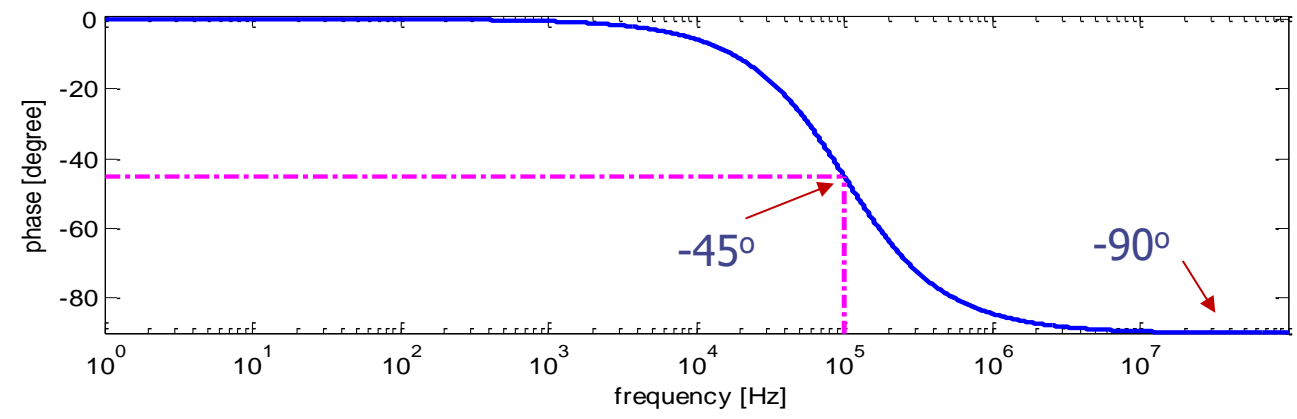

phase response (lin-log plot)

Fundamentals

➤ RC circuit – frequency response

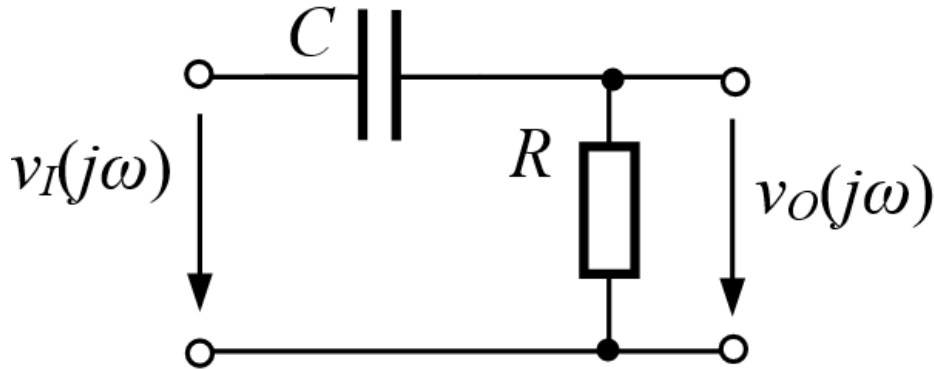

$$Z_C = \frac{1}{j\omega C}$$

Low frequency:

$f \rightarrow 0$; $Z_C \rightarrow \infty$; input – output \rightarrow open circuit; $v_O(j\omega) \rightarrow 0$ **don't pass (reject)**


High frequency:

$f \rightarrow \infty$; $Z_C \rightarrow 0$; input – output \rightarrow short-circuit; $v_O(j\omega) \rightarrow v_I(j\omega)$ **pass**

First order, passive, high-pass filter (HPF)

Fundamentals

➤ RC circuit – frequency response

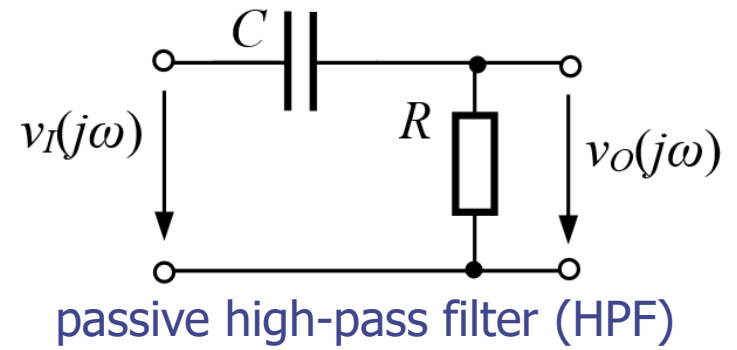

Transfer function

$$F(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{j\omega RC}{1 + j\omega RC}$$

$$|F(j\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\Phi(\omega) = 90^\circ - \text{arctg}(\omega RC)$$



f – very low; $|F(j\omega)| \approx \omega RC$

f – high; $|F(j\omega)| \approx 1$


$$\omega_0 RC = 1 \Rightarrow \omega_0 = \frac{1}{RC} \Rightarrow f_0 = \frac{1}{2\pi RC} \quad \text{Cut-off frequency}$$

Fundamentals

➤ RC circuit – frequency response

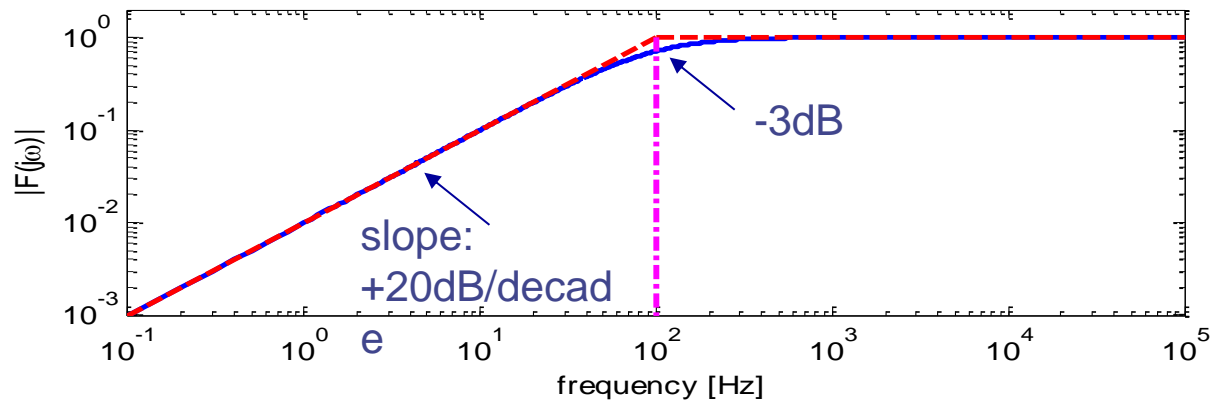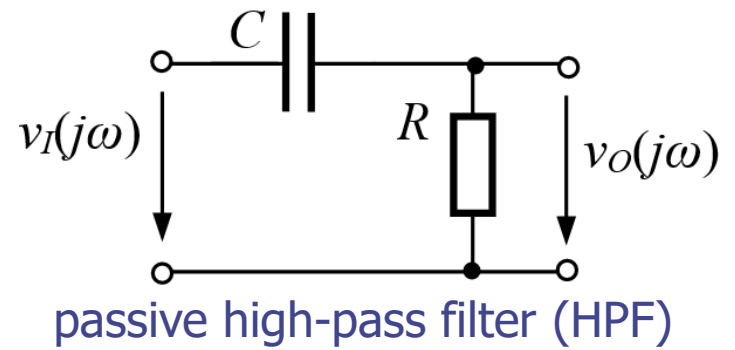


magnitude response (log-log plot)

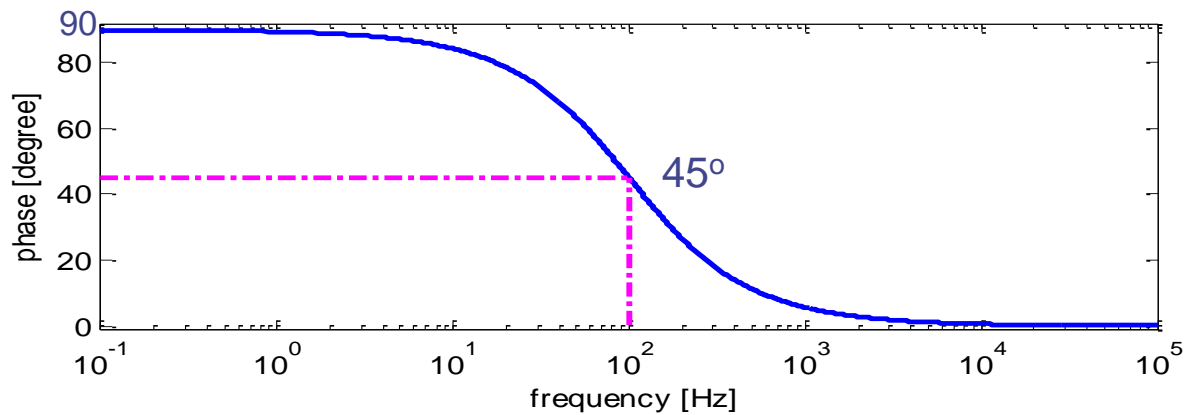

phase response (lin-log plot)

Fundamentals

➤ RC circuit – frequency response

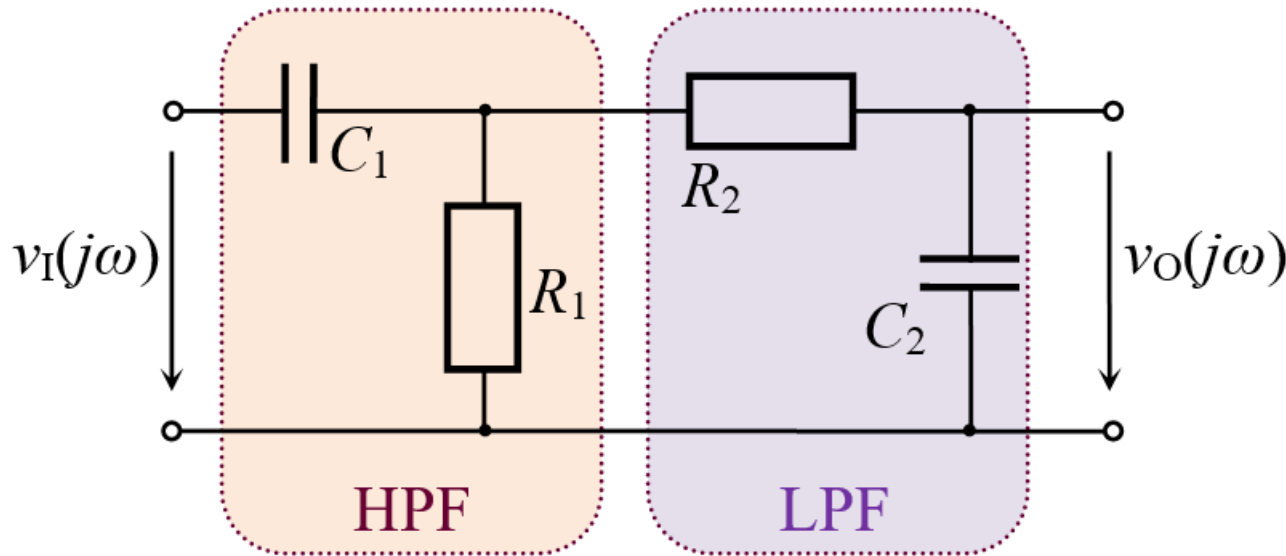


$$Z_C = \frac{1}{j\omega C}$$

Second order, passive, band-pass filter (BPF)

Fundamentals

➤ RC circuit – frequency response

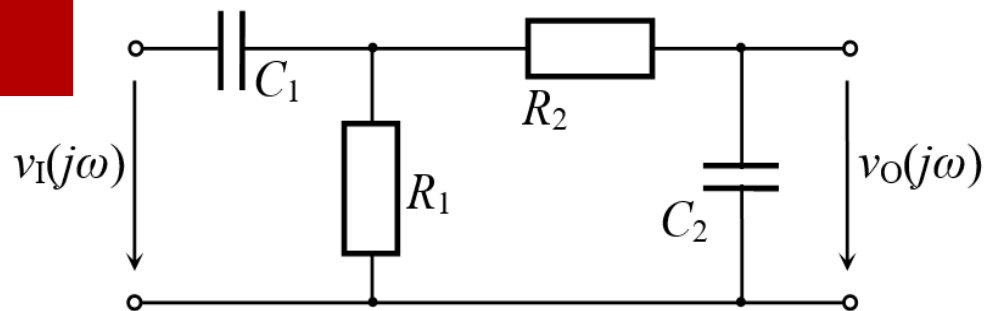

passive band-pass filter (BPF)

Transfer function

$$F(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{j\omega R_1 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

$$|F(j\omega)| = \frac{\omega R_1 C_1}{\sqrt{1 + (\omega R_1 C_1)^2} \sqrt{1 + (\omega R_2 C_2)^2}}$$

$$\Phi(\omega) = 90^\circ - \text{arctg}(\omega R_1 C_1) - \text{arctg}(\omega R_2 C_2)$$

Cut-off frequencies


$$f_L = \frac{1}{2\pi R_1 C_1} \quad f_H = \frac{1}{2\pi R_2 C_2}$$

Bandwidth


$$B = f_H - f_L$$

Fundamentals


➤ RC circuit – frequency response

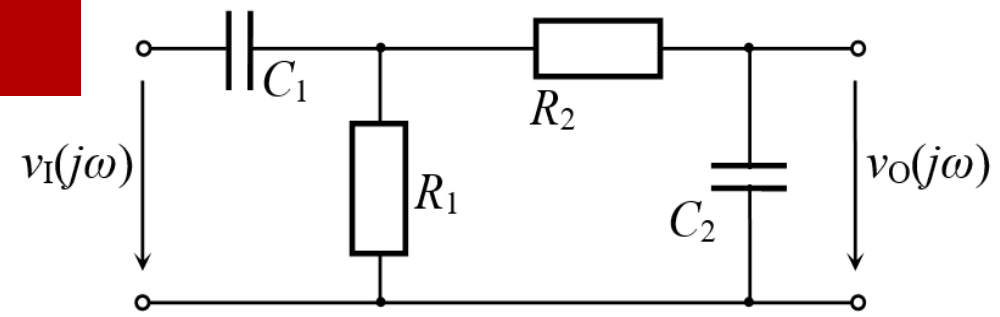

passive band-pass filter (BPF)

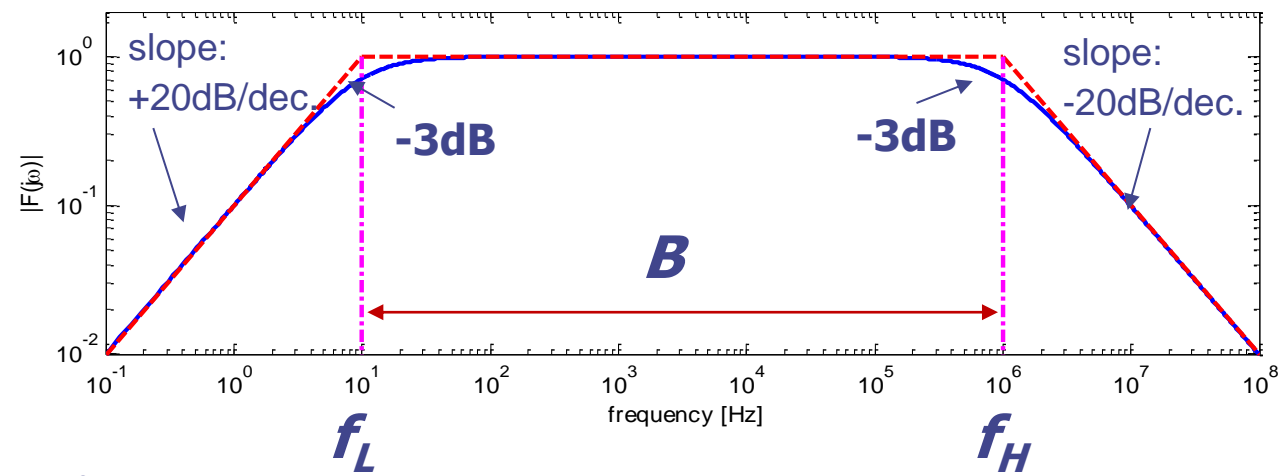

magnitude response (log-log plot)

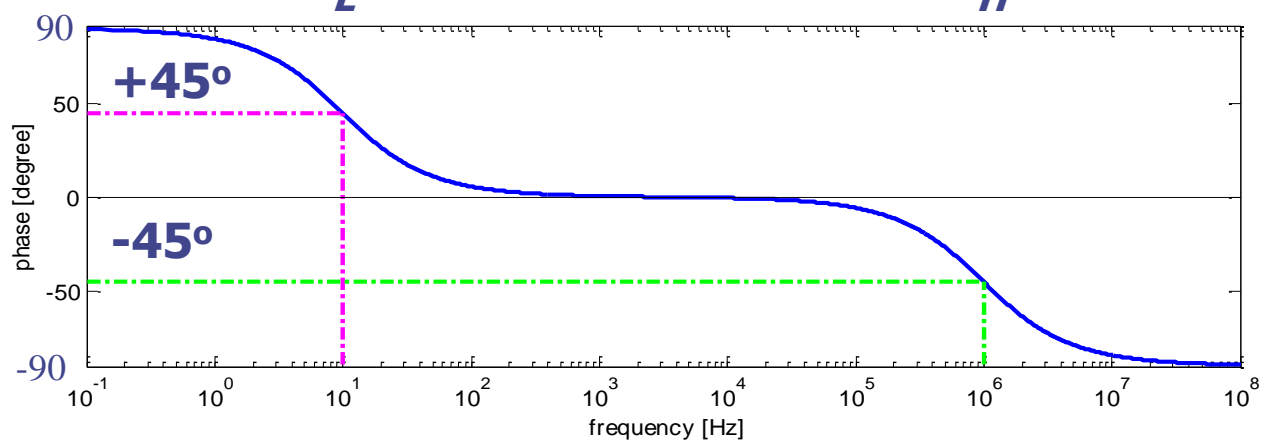

phase response (lin-log plot)

Summary

The trip down memory lane revived knowledge about:

- Electrical signals, sources
- Ohm's law
- Kirchhoff's law
- Resistive divider
- Superposition method
- Millman's theorem
- RC circuits – time and frequency domain behaviors, filters

Next week: Diodes. DR circuits.