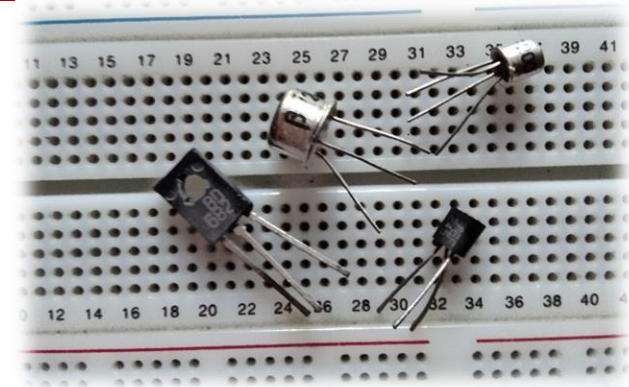




ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C11 – Transistors. BJTs.



Contents

- Types of transistors
- Operating principle. Operating regions.
- n-type transistors. Transfer characteristics.
- p-type transistors. Transfer characteristics.
- Bipolar junction transistors (BJTs)

Transistors



- 1926 - JE Lilienfeld (physicist, engineer)
first patent of a field effect transistor – could not be built
- 1947, Bell Labs, USA - J Bardeenn, W Brattain, W Shockley
first built transistor
- 1956 J Bardeenn, W Brattain, W Shockley
Nobel prize in physics

The invention of the transistor in 1947 is included on the [list of IEEE milestones](#)

But what is a transistor?

Transistors

= **active** semiconductor devices, with three terminals

- used to amplify or switch signals
- essential components of electronic circuits
- discrete or integrated

Operating principle:

The **voltage** applied between two terminals (command) controls the **current** through the third terminal

transistors \equiv **voltage-controlled current sources**

Transistors

= **active** semiconductor devices, with three terminals

- used to amplify or switch signals
- essential components of electronic circuits
- discrete or integrated

“Putting sixty-four transistors on a chip allowed people to dream of the future.
Putting four million transistors on a chip actually gave them the future.”

- Malcolm Gladwell

Intel 4004, 1971, 10 μ , 14 mm², **2,300 transistors**

Pentium 4, 2006, 65 nm, 90 mm², **184,000,000 transistors**

Core i7 Haswell-E, 8-core, 2014, 22 nm, 355 mm², **2,600,000,000 transistors**

Xeon_Broadwell-E5, 22-core, 2016, 14 nm, 456 mm², **7,200,000,000 transistors**

Apple M2 Max 12-core, 2023, 5 nm, **67,000,000,000 transistors**


Transistors

Moore's Law: The number of transistors on microchips doubles every two years


Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.



Transistor count

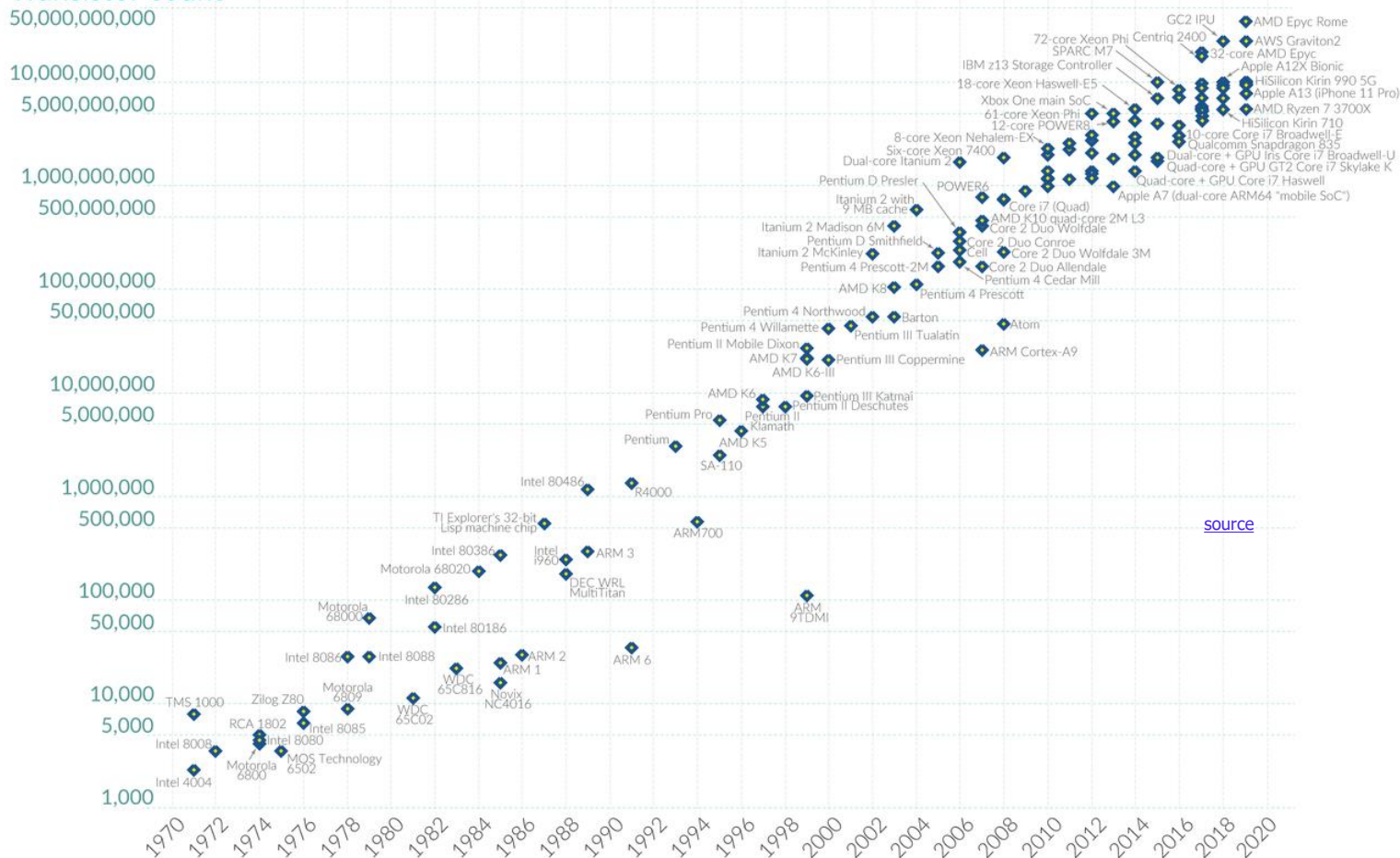

source

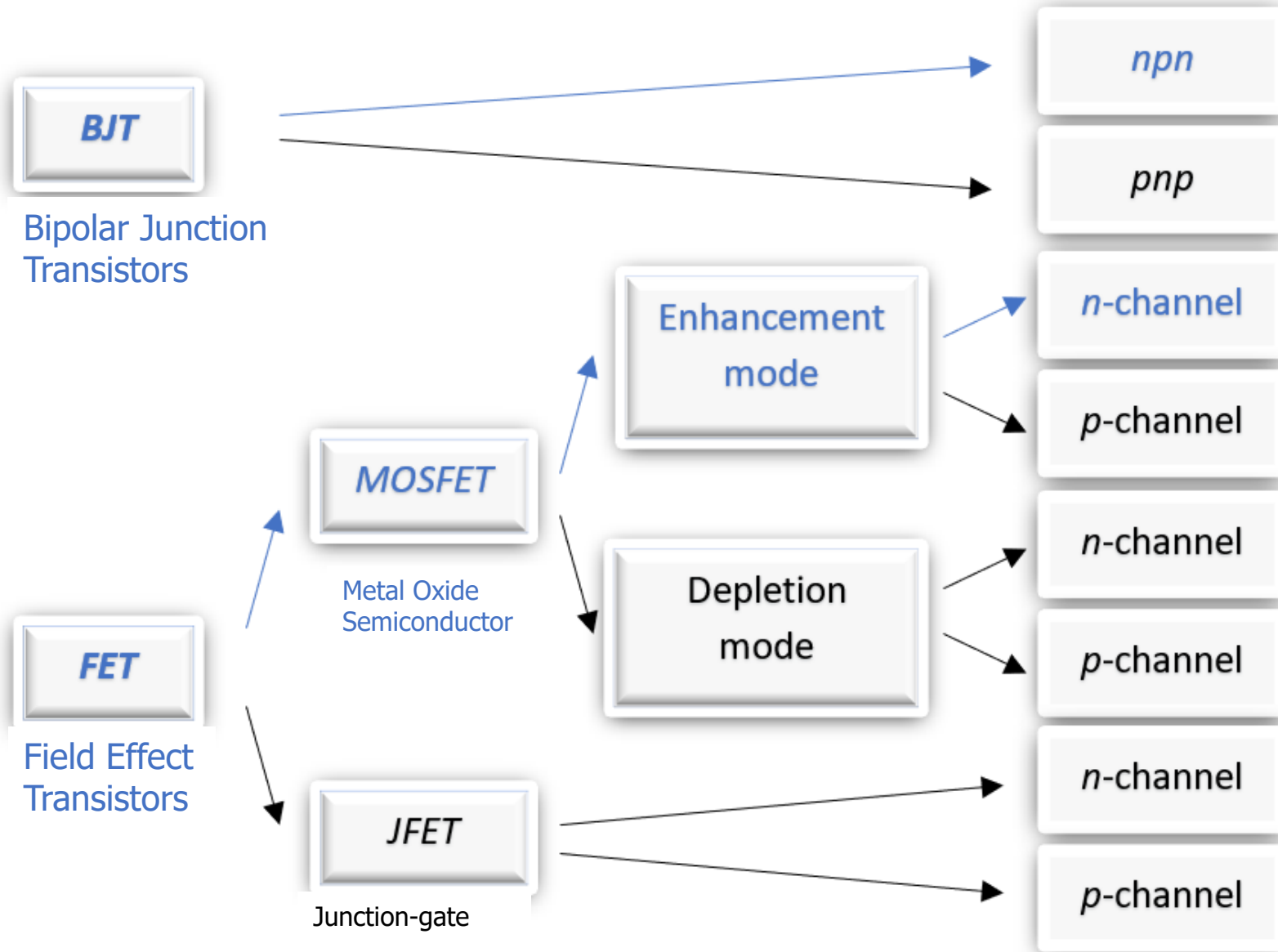


➤ Operating principle

transistors \equiv non-linear **voltage-controlled current sources**

square – MOSFET; exponential – BJT

n-type


- n-channel MOSFET
- npn BJT

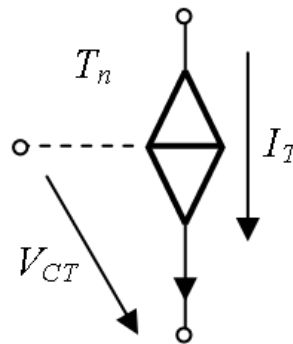

dc model – ideal VCCS

p-type


- p-channel MOSFET
- pnp BJT

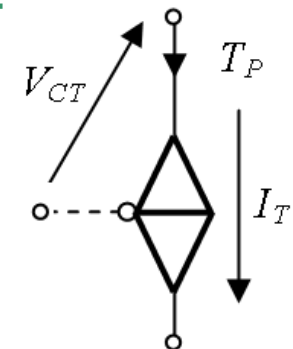

➤ Operating regions


transistors \equiv non-linear **voltage-controlled current sources**

n-type

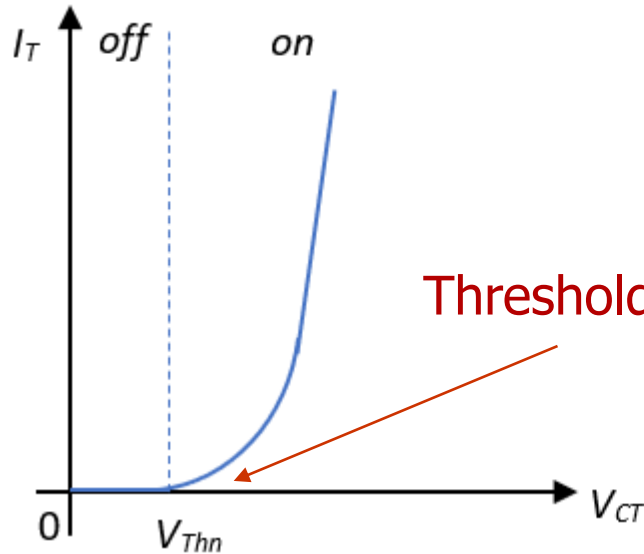

- $V_{CT} < V_{Thn}, T_n - \text{off}, I_T = 0$
- $V_{CT} > V_{Thn}, T_n - \text{on}, I_T > 0$

p-type

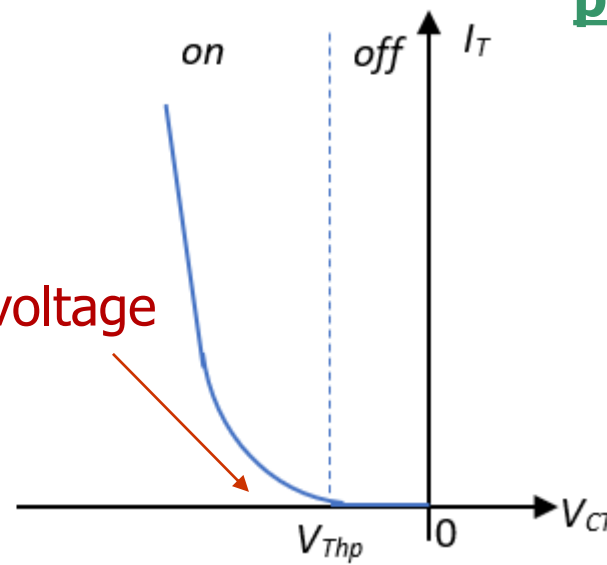

- $V_{CT} > V_{Thp}, T_p - \text{off}, I_T = 0$
- $V_{CT} < V_{Thp}, T_p - \text{on}, I_T > 0$

➤ n-type transistors


Using the n-type transistor, T_n , in a circuit

- series supply – voltage source
- parallel supply – current source

Output quantities: I_O , V_O

Transfer characteristics: $I_O(V_{CT})$, $V_O(V_{CT})$

$$I_T = I_O$$

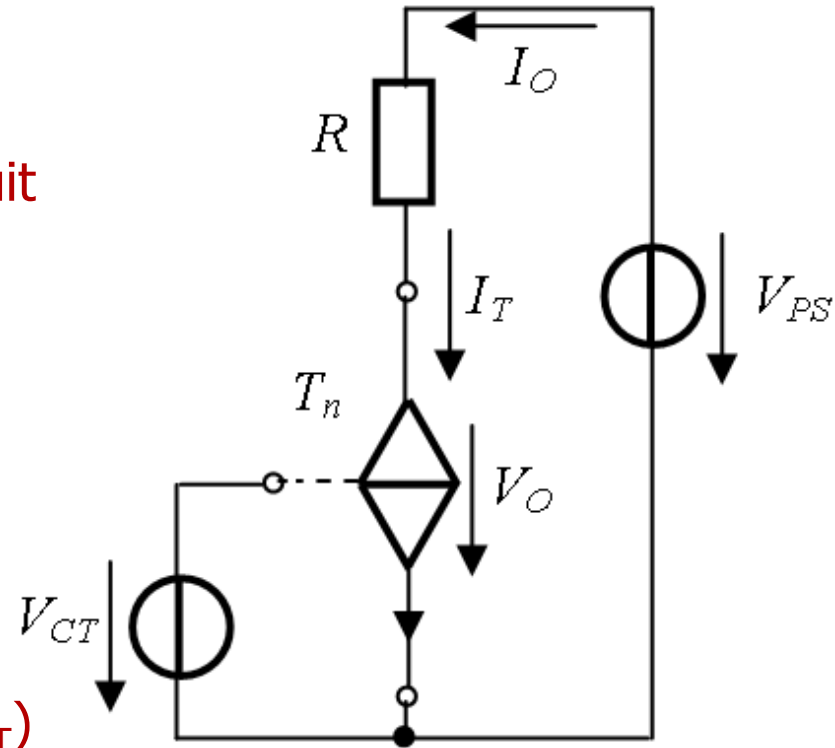

Why is R necessary?

➤ Transfer characteristics

- $V_{CT} < V_{Thn}$, T_n – off, $I_O = I_T = 0$
- $V_{CT} > V_{Thn}$, T_n – on, $I_O = I_T > 0$

$$V_{PS} = RI_O + V_O$$


$$V_O = V_{PS} - RI_O$$

$$V_{CT} \uparrow, I_O \uparrow, V_O \downarrow$$

$$V_{O,min} = 0$$

$$I_{Oex} = \frac{V_{PS}}{R}$$


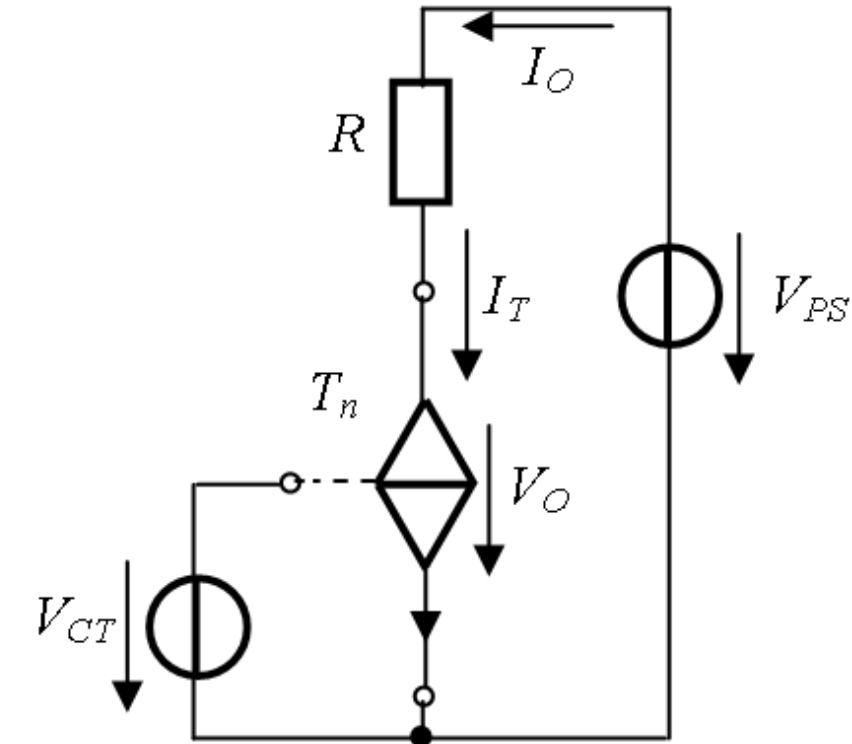
I_{Oex} – maximum possible value of I_O , in the given circuit



Plots for $I_O(V_{CT})$, $V_O(V_{CT})$?

➤ Transfer characteristics

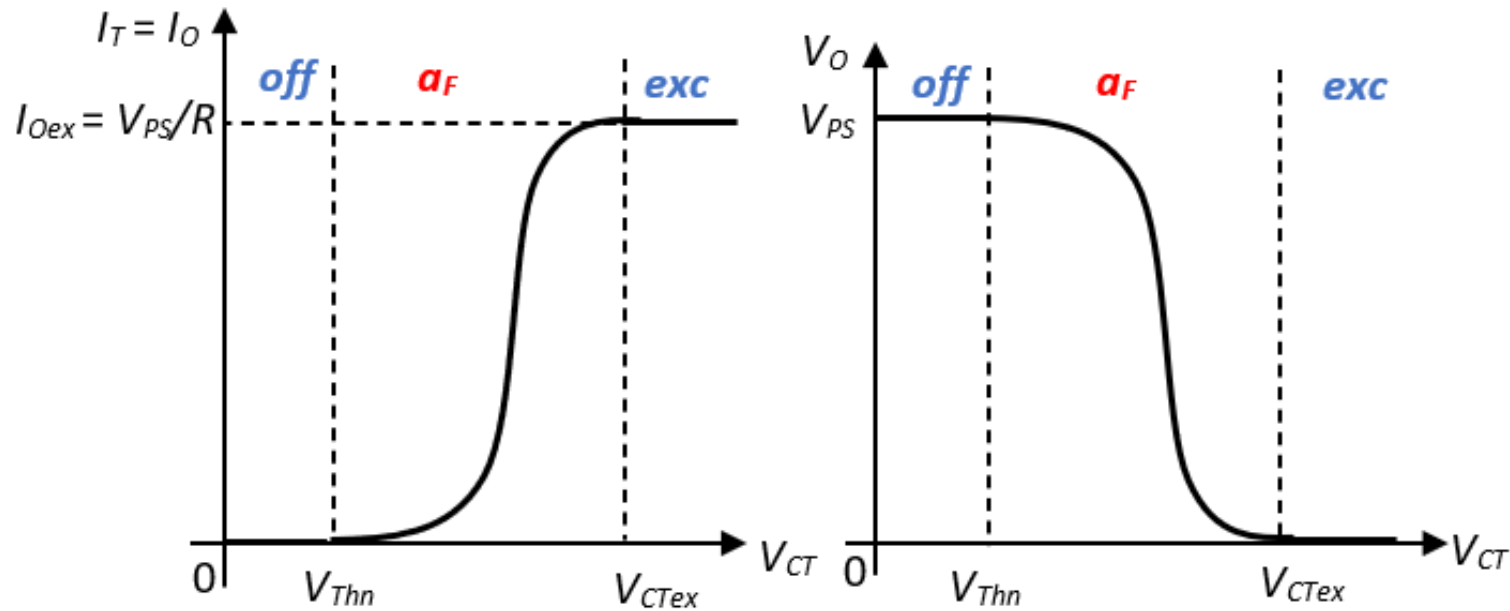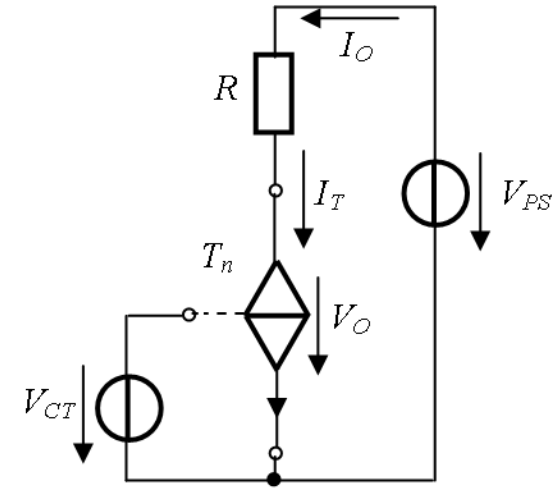- $V_{CT} < V_{Thn}$, T_n – off, $I_O = I_T = 0$
- $V_{CT} > V_{Thn}$, T_n – on, $I_O = I_T > 0$



➤ Transfer characteristics

- Two extreme regions, **passive**:

- **cutoff (off)**

$I_O = 0; V_O > 0$; ideal switch in **off** state

- **extreme conduction (exc)**

$I_O = I_{Oex}; V_O = 0$; ideal switch in **on** state



$V_{CT} < V_{Thn}$ or $V_{CT} > V_{CTex}$ - **switching transistor**

- An intermediate region, **active**:

active forward region (**a_F**)

$V_{Thn} < V_{CT} < V_{CTex}$ - **permanent conduction**

(amplifier)

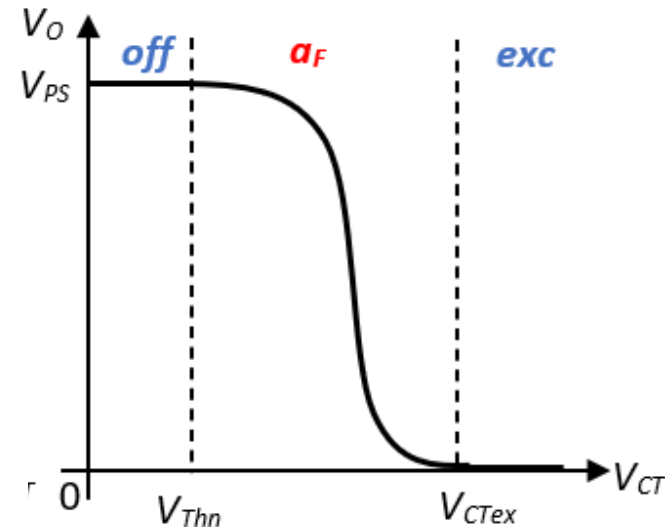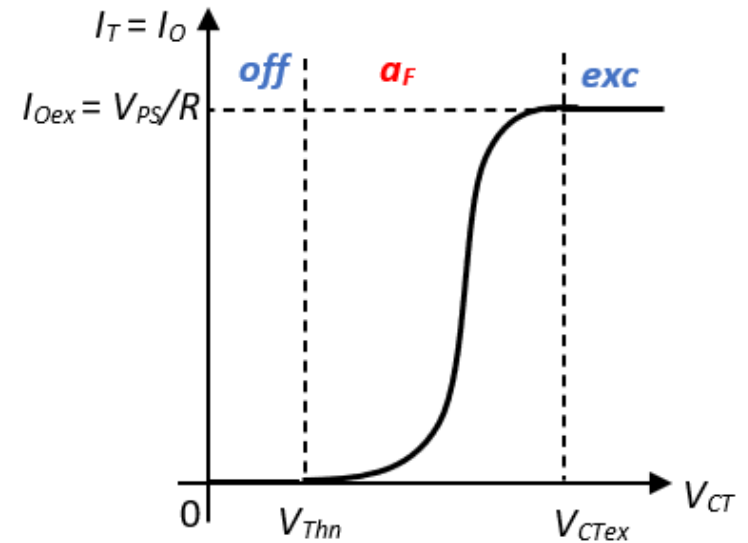

➤ p-type transistors


Using the p-type transistor, T_p , in a circuit

- series supply – voltage source
- parallel supply – current source



Output quantities: I_O , V_O

Transfer characteristics: $I_O(V_{CT})$, $V_O(V_{CT})$

$$I_T = I_O$$


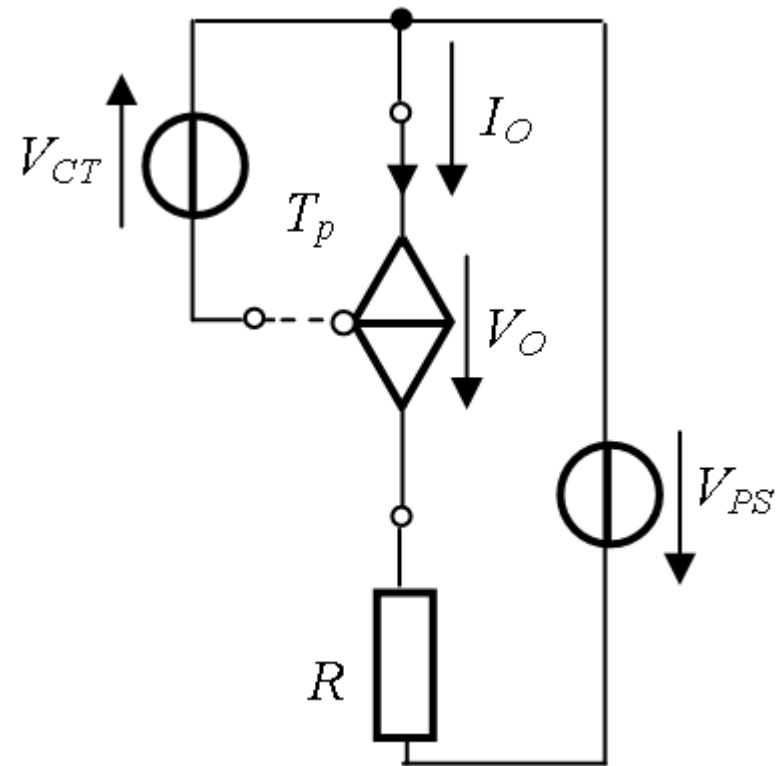


➤ Transfer characteristics

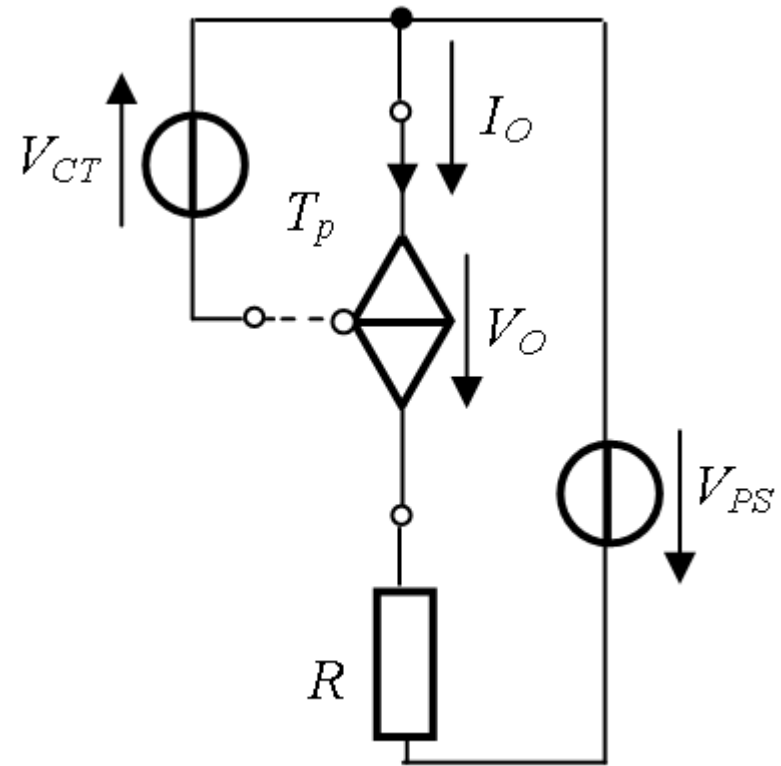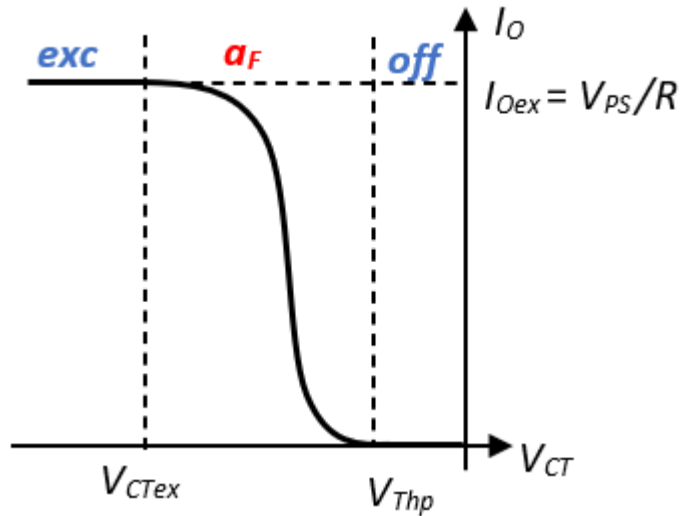

- **cutoff (off)** $V_{CT} > V_{Thp}$
- **extreme conduction (exc)** $V_{CT} < V_{CTex}$
- **active region (a_F)** $V_{CTex} < V_{CT} < V_{Thp}$

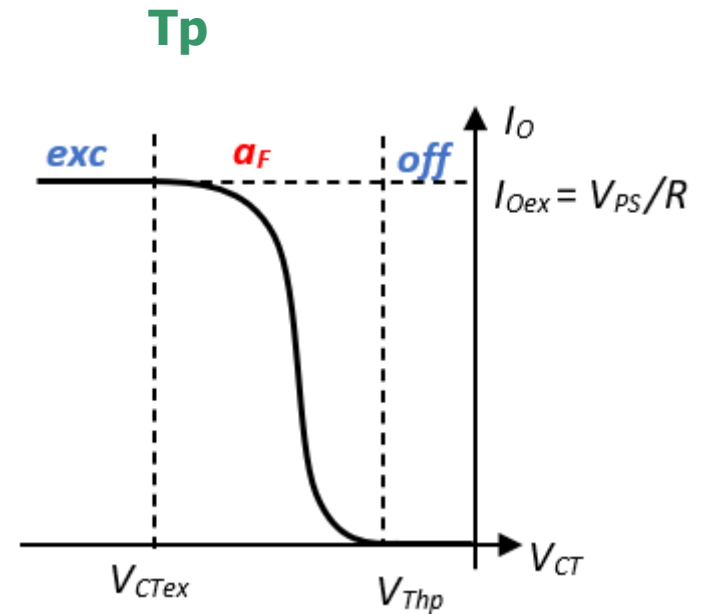
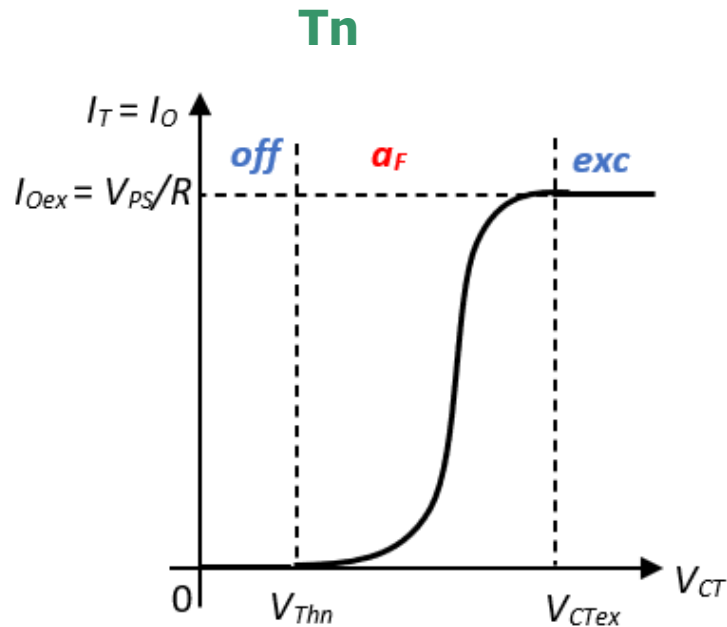
➤ Who determines the boundaries between operating regions?



- border (off) - (a_F), $V_{CT} = V_{Th}$: the **transistor** (by its V_{Th})
- border (a_F) - (exc), $V_{CT} = V_{CTex}$:
transistor (by means of $I_O(V_{CT})$)
R and **V_{PS}** (by I_{Oex})

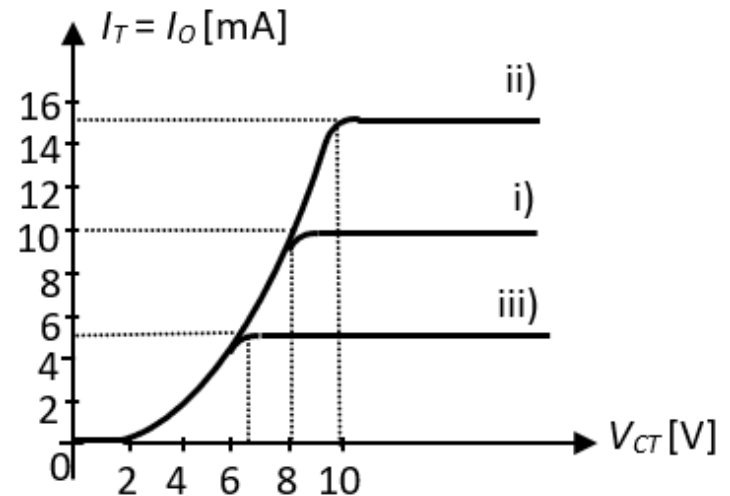
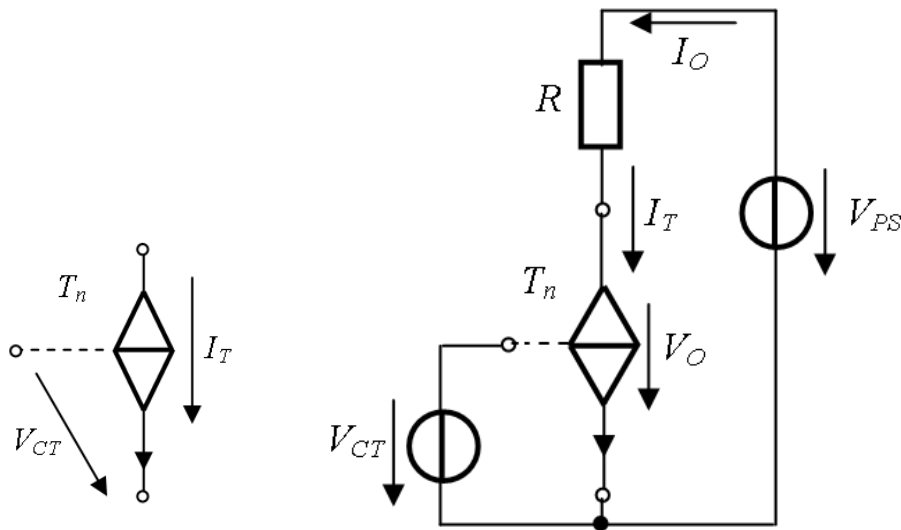
Example

- Determine the boundaries between the operating regions of T and compute I_{Oex} and V_{CTex} for:
 - $V_{PS} = 10V$; $R = 1\text{ k}\Omega$
 - $V_{PS} = 15\text{ V}$; $R = 1\text{ k}\Omega$
 - $V_{PS} = 10\text{ V}$; $R = 2\text{ k}\Omega$
- Resize the circuit so that $I_{Oex} = 20\text{ mA}$.



➤ Bipolar junction transistors (BJTs)

Circuit symbols

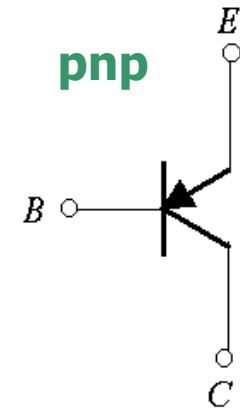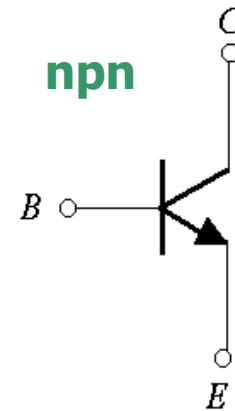

B – base

C – collector





E – emitter

The arrow on the emitter terminal indicates the direction of the positive current.

➤ Bipolar junction transistors (BJTs)

An ohmmeter's view

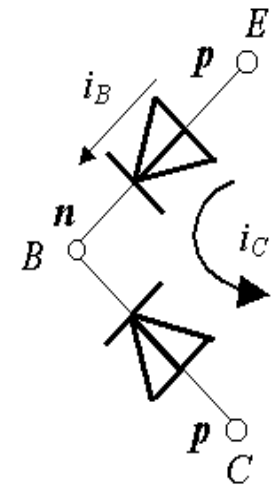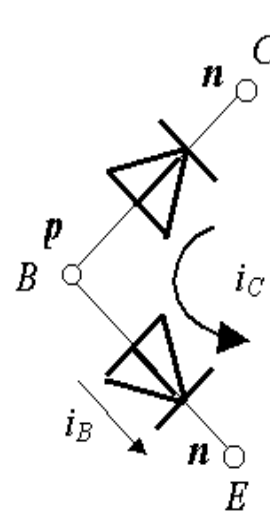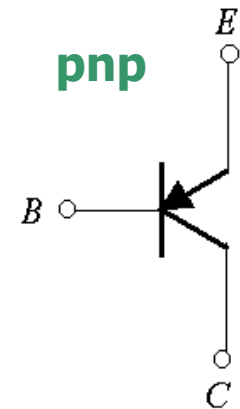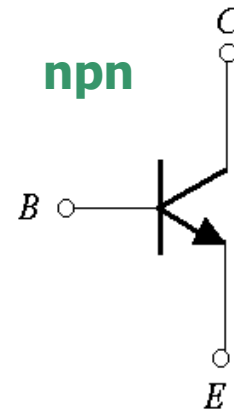!There are interactions between the two junctions!



Summary

Looks like transistors are not that scary, after all! Their fundamental features were revealed today:

- Types of transistors
- Operating principle. Operating regions.
- n-type transistors. Transfer characteristics.
- p-type transistors. Transfer characteristics.
- Bipolar junction transistors (BJTs)

Next week: BJT operation

To do: Find out what used to be called **Transistor** in the pre-Internet, pre-TV era 😊