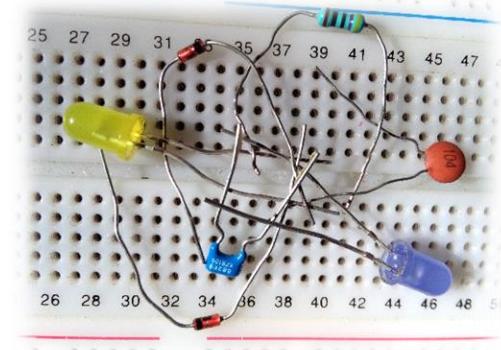




# ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

**C4 – DR rectifiers.  
DRC rectifiers. LEDs.  
Photodiodes.**




# Contents

- DR rectifiers – half-wave and full-wave
- DRC rectifiers (power supply filtering)
- LEDs and photodiodes
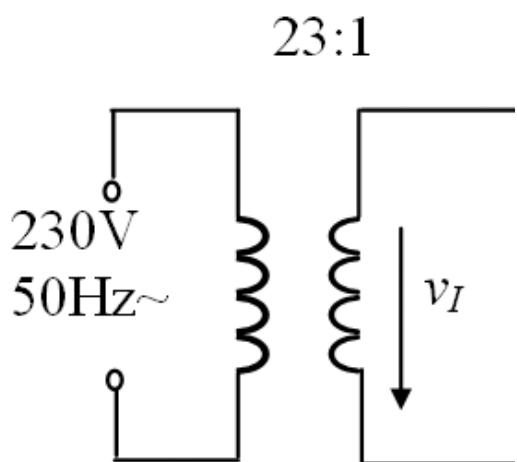
## ► DR rectifiers

The input voltage is obtained from the secondary winding of a transformer




$$\widehat{V}_I = \frac{\widehat{V}_S}{n}, \text{ n-transformer ratio}$$


$$\widehat{V}_I = \frac{230\sqrt{2}}{23} = 14.1V$$

Shape of  $v_I$ ?


## ➤ Half-wave DR rectifier

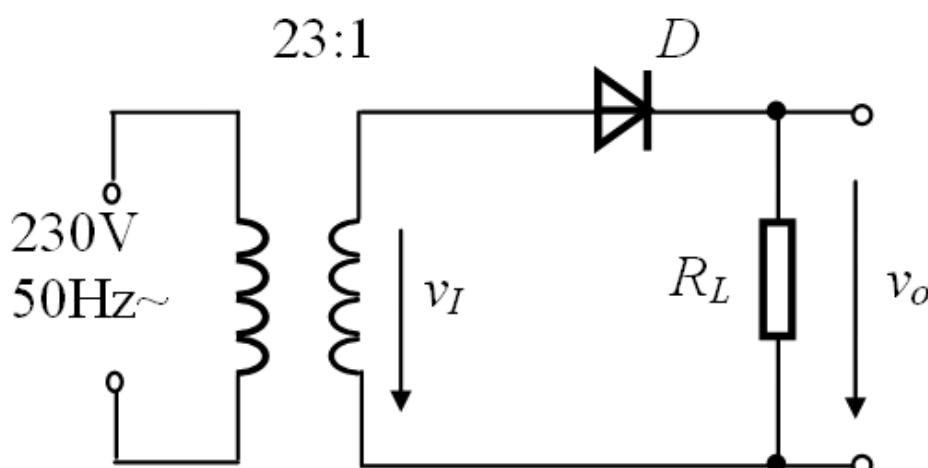

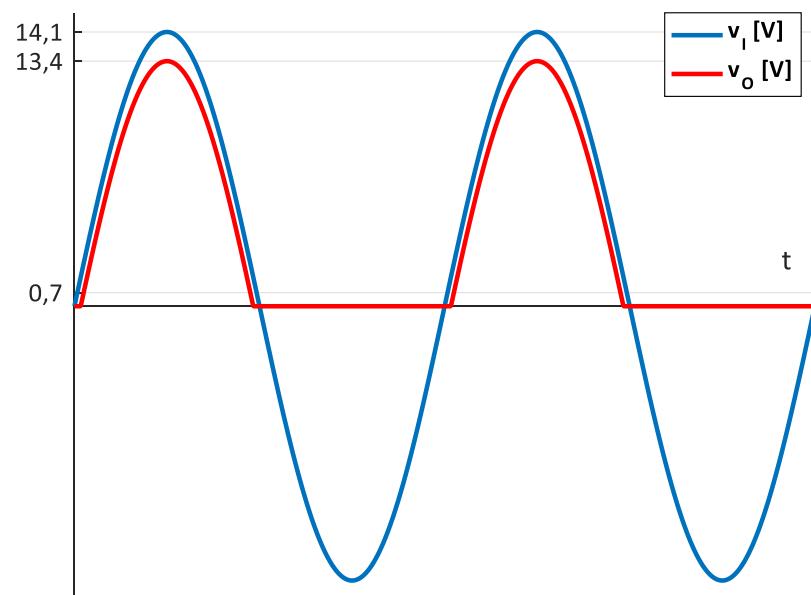
$$\widehat{v_I} = \frac{230\sqrt{2}}{23} = 14.1V$$



➤ Full-wave DR rectifier – diode bridge

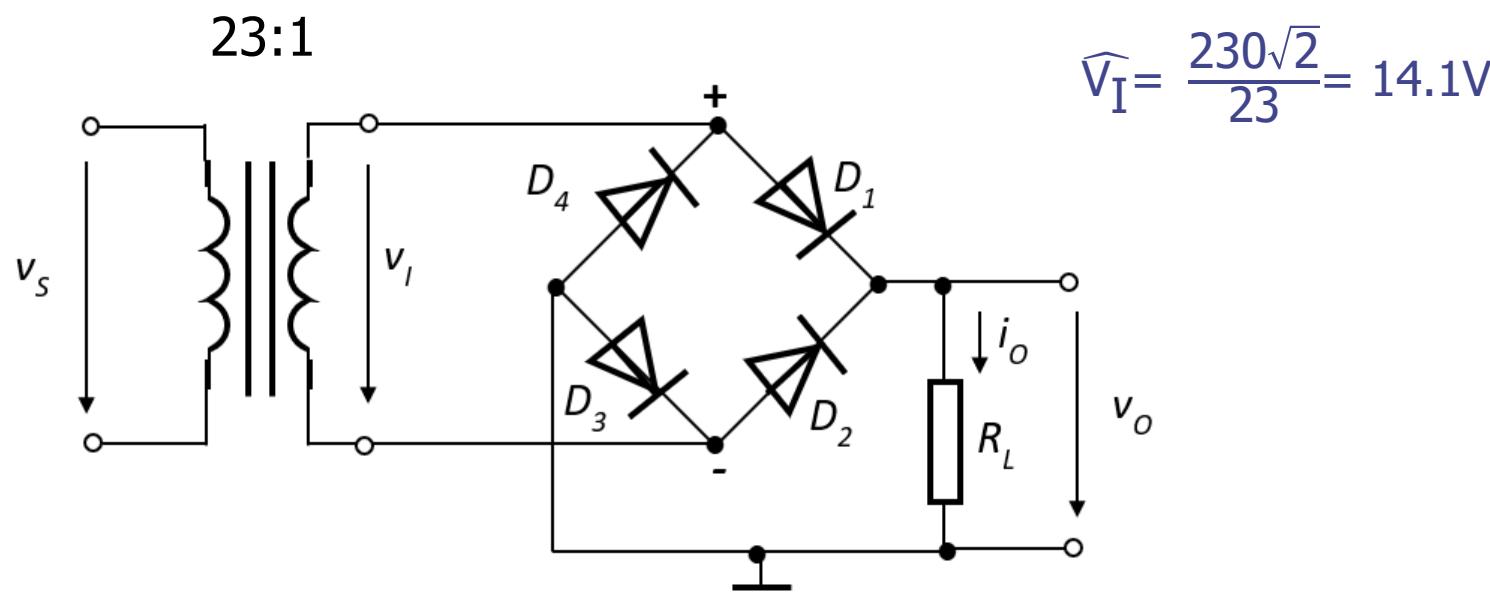
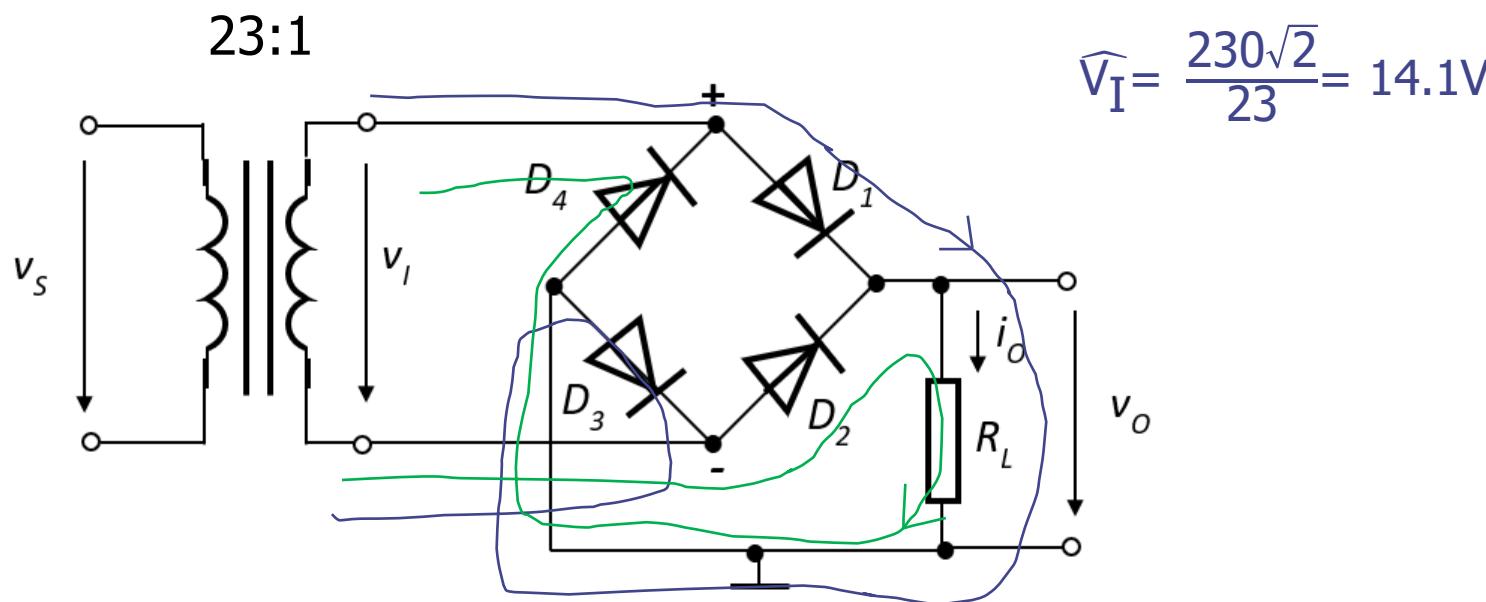
## ➤ Full-wave DR rectifier – diode bridge



➤ positive half,  $v_I > 1.4 V$

**D<sub>1</sub>, D<sub>3</sub> – (on)**


D<sub>2</sub>, D<sub>4</sub> – (off)

➤ negative half,  $v_I < -1.4 V$



D<sub>1</sub>, D<sub>3</sub> – (off)

**D<sub>2</sub>, D<sub>4</sub> – (on)**
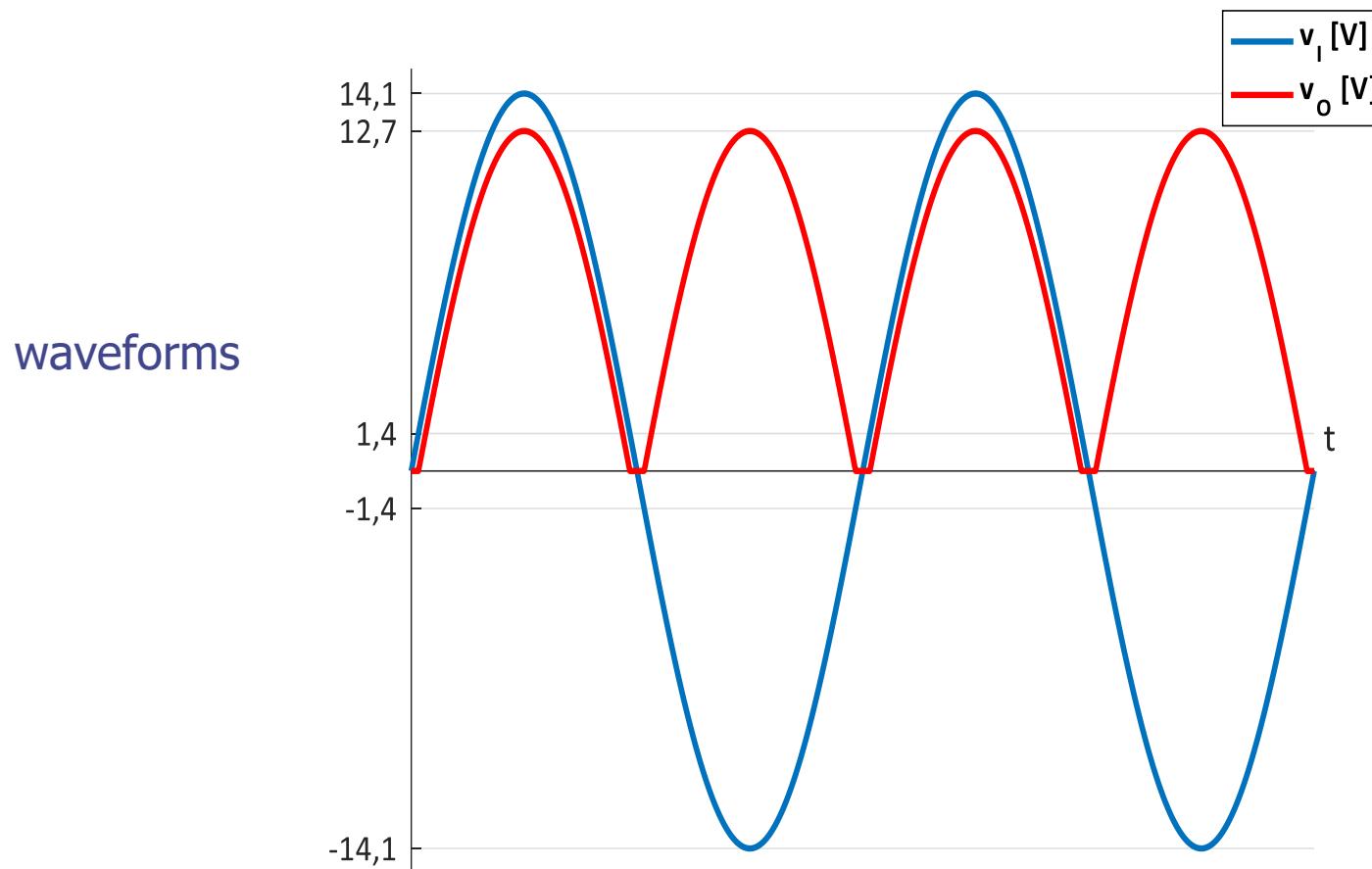
## ➤ Full-wave DR rectifier – diode bridge




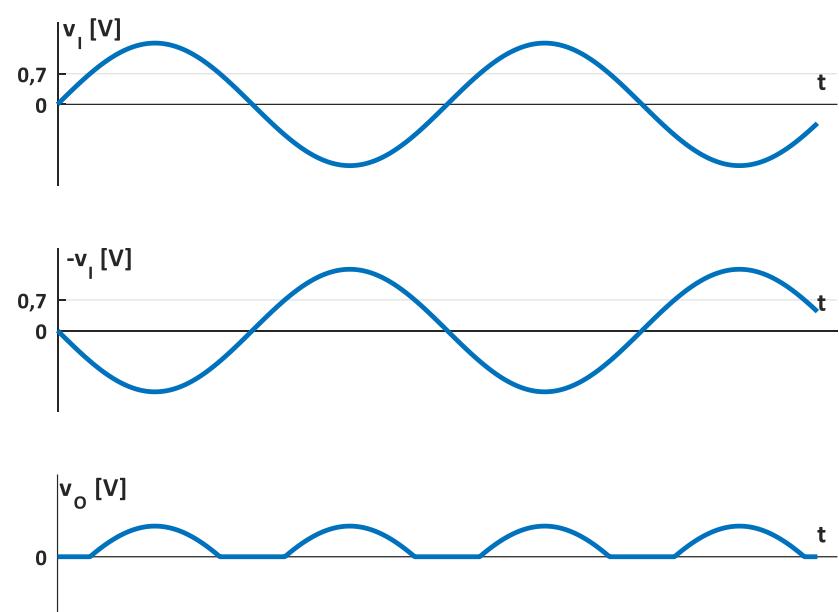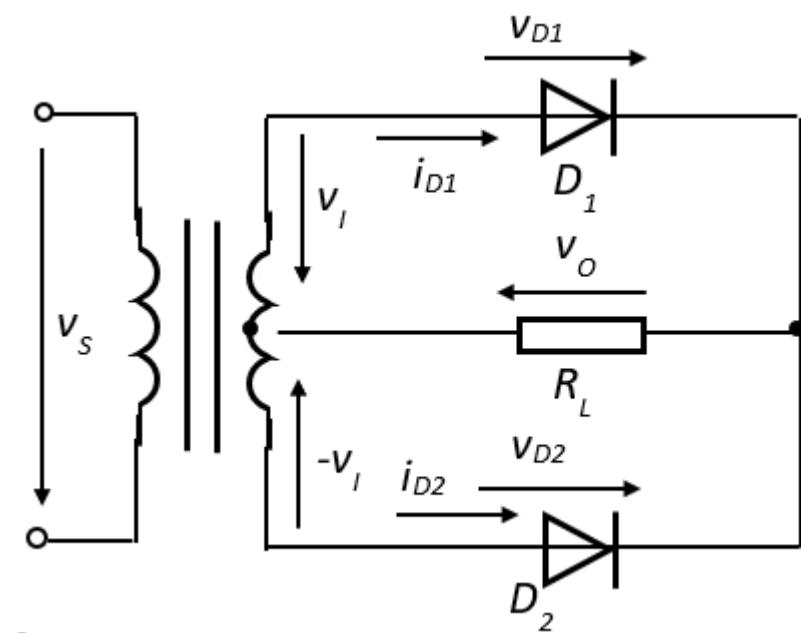➤ Full-wave DR rectifier – center-tapped transformer



## Example

$$v_I(t) = \hat{V}_I \sin \omega t$$

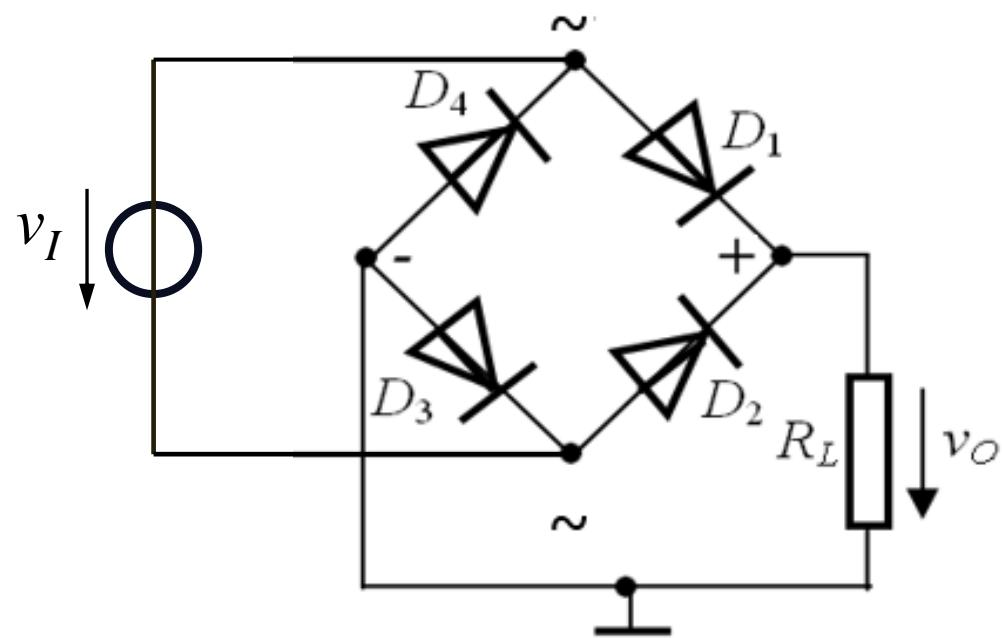


For the circuit in the figure,  $R_L = 50 \Omega$ . Assume  $\hat{V}_I = 5 \text{ V}$ .


- Plot  $v_I(t)$ ,  $v_O(t)$  and  $i_O(t)$ .
- Compute the values of the maximum reverse voltage  $v_{DR}$  across each diode and the maximum forward current through each diode.
- Repeat a) and b) assuming  $\hat{V}_I = 100 \text{ V}$ .

➤ Half-wave DRC rectifier w/ capacitive filter  
(loaded positive peak detector)

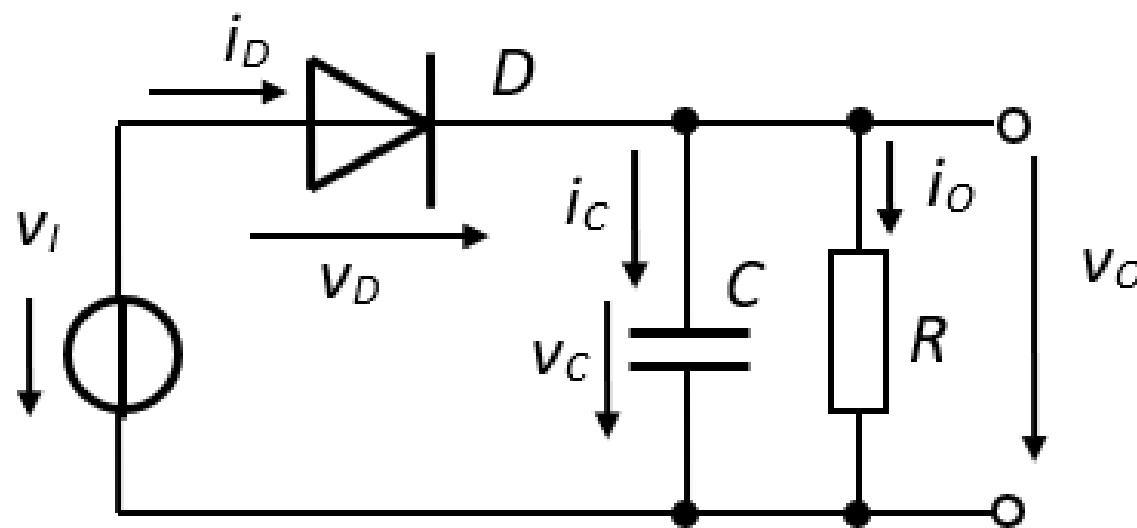- $v_I$  is the voltage in the secondary winding of a step-down line transformer
- How can the output voltage (on a load resistor) be almost dc?



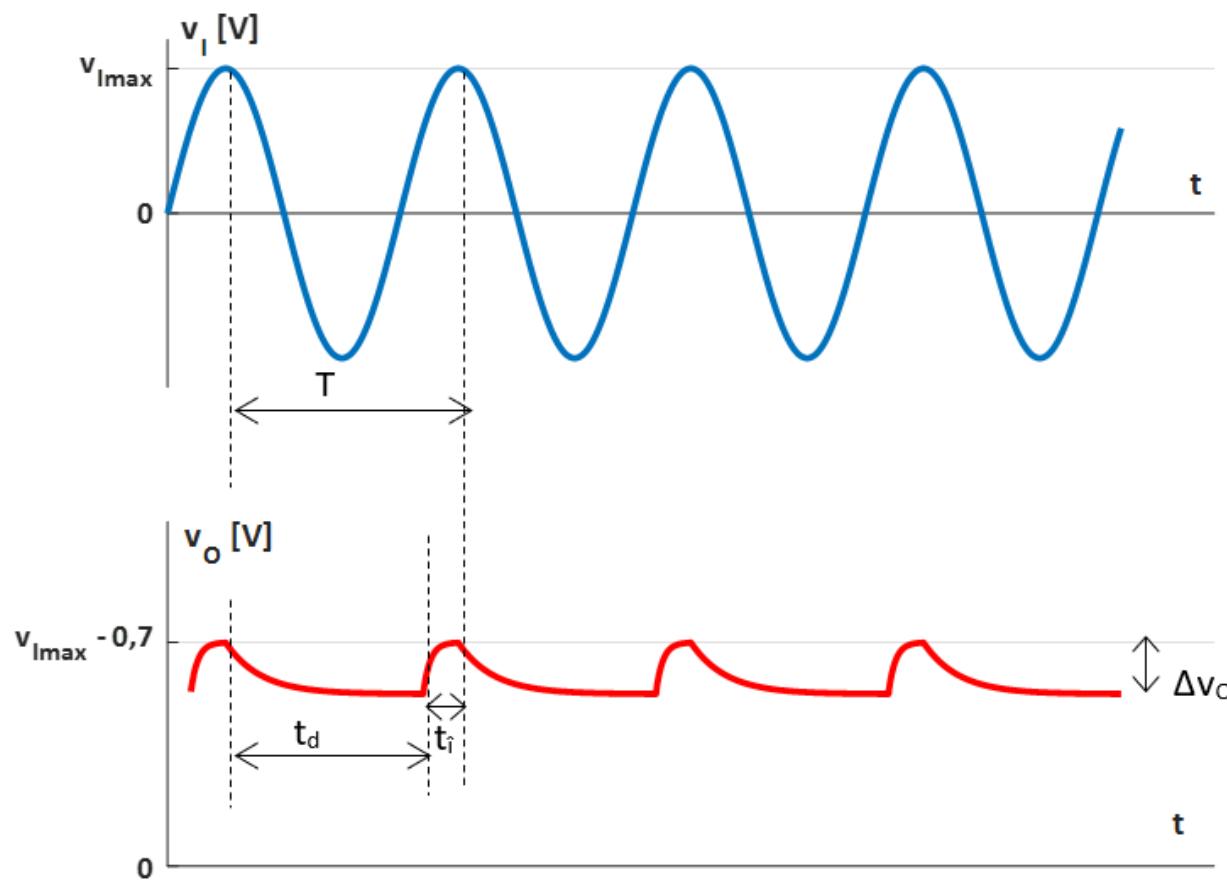- Half-wave DRC rectifier w/ capacitive filter  
(loaded positive peak detector)



## ➤ Half-wave DRC rectifier w/ capacitive filter (loaded positive peak detector)

Between two successive voltage peaks, D – (off) and discharges through R

$$v_c(t) = e^{-\frac{t}{\tau}} \cdot V_C(0) + \left( 1 - e^{-\frac{t}{\tau}} \right) \cdot V_C(\infty)$$

$$\begin{aligned} V_C(0) &= V_{Omax} \\ V_C(\infty) &= 0 \text{ V} \end{aligned}$$

If  $RC \gg T \Rightarrow$  the capacitor discharge during  $t_d$  can be approximated with a linear variation of the output voltage (across the capacitor)

$$e^{-\frac{T}{\tau}} \cong 1 - \frac{T}{\tau}$$

$$V_{Omin} \cong \left( 1 - \frac{T}{\tau} \right) \cdot V_{Omax}$$

$$V_{Omax} - \Delta v_O \cong V_{Omax} - \frac{T}{\tau} \cdot V_{Omax}$$


$$\Delta v_O \cong \frac{T}{\tau} \cdot V_{Omax}$$

Output voltage ripple (variation)

$$\Delta v_O \cong \frac{T}{R \cdot C} \cdot (V_{Imax} - 0.7)$$

$$\Delta v_O \cong \frac{V_{Imax} - 0.7}{R \cdot C \cdot f}$$
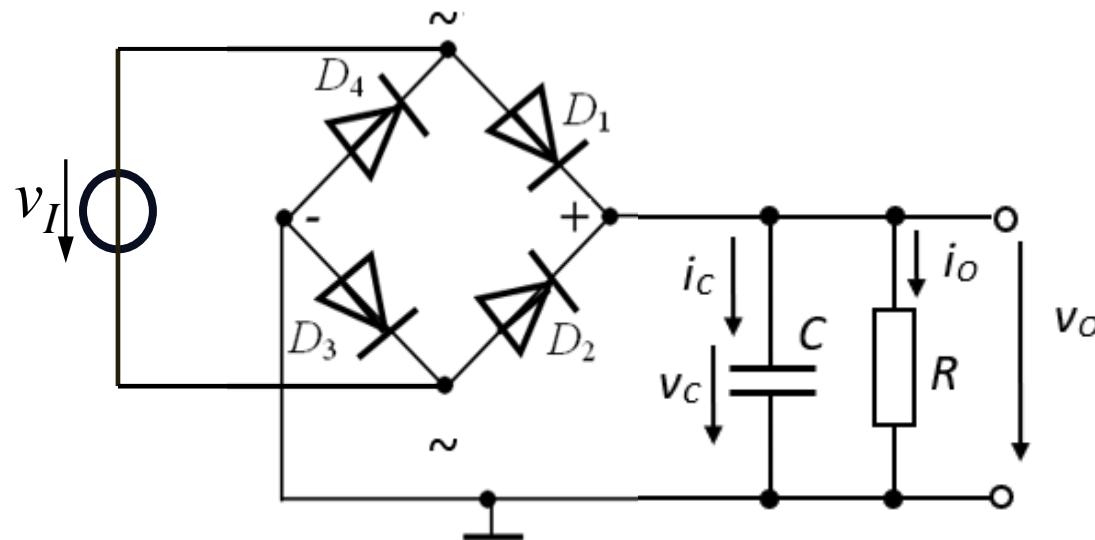
## ➤ Full-wave DRC rectifier w/ capacitive filter



Output voltage ripple (variation)


$$t_d \cong \frac{T}{2}$$

$$\Delta v_O \cong \frac{T}{2 \cdot R \cdot C} \cdot (V_{I\max} - 1.4)$$

$$\Delta v_O \cong \frac{V_{I\max} - 1.4}{2 \cdot R \cdot C \cdot f}$$
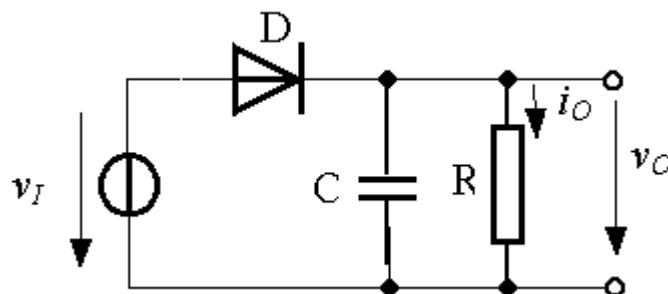
## Example

$$\hat{V}_I = 10.7\text{V} \quad f=50\text{Hz} \quad R_L = 100\Omega \quad \Delta v < 1.5\text{V} \quad C = ?$$



$$\hat{V}_o = \hat{V}_I - 0.7\text{V} = 10\text{V}$$




$$\Delta v = \frac{\hat{V}_o}{fRC} < 1.5\text{V}$$

$$C > \frac{\hat{V}_o}{1.5VfR} = \frac{10}{1.5 \cdot 50 \cdot 100} = 1333\mu\text{F} \quad C > 1333\mu\text{F}$$

Solution: electrolytic capacitor,  $C = 1500 \mu\text{F}/25 \text{ V}$

- What is the actual value of the output ripple?
- What should be a new value of C, to reduce the output ripple to half of the initial value?
- Solve again, assuming full-wave rectification.

## ➤ LED – light emitting diode

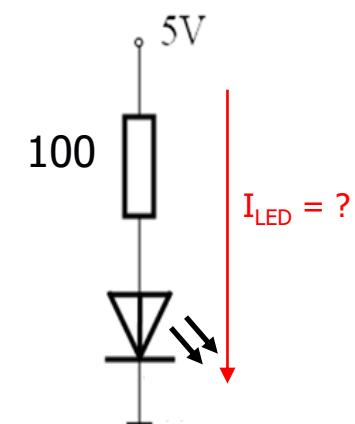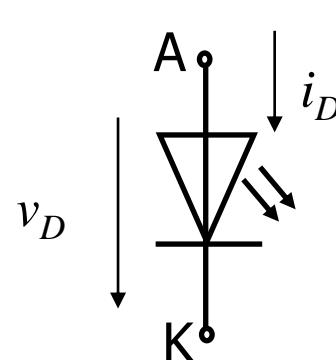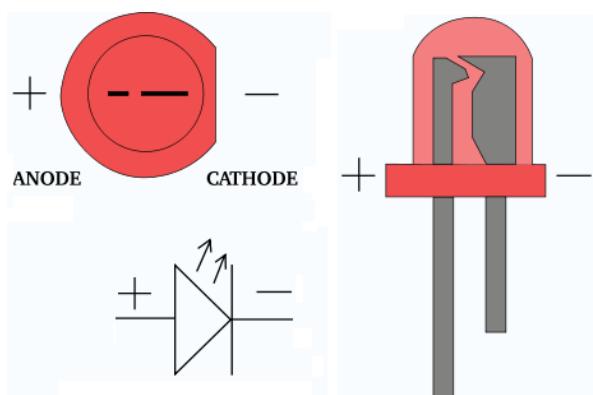


- behavior similar to conventional diodes
- $V_{LED, \text{on}} = 1.5 \text{ V} \dots 3 \text{ V}$  (forward voltage drop)
- in forward bias, the LED lights up:
  - red, yellow, green, blue, white
  - IR – remote control
- emits radiation in the visible, infrared, or laser range
- typical current: 5 mA to 20 mA
- power LED: 3.5 V @ 500 mA




➤ LED – excerpt from datasheet

ABSOLUTE MAXIMUM RATINGS ( $T_{amb} = 25 \text{ }^{\circ}\text{C}$ , unless otherwise specified)				
TLHR440., TLHO440., TLHY440., TLHG440., TLHP440.				
PARAMETER	TEST CONDITION	SYMBOL	VALUE	UNIT
Reverse voltage		$V_R$	6	V
DC forward current		$I_F$	30	mA
Surge forward current	$t_p \leq 10 \mu\text{s}$	$I_{FSM}$	1	A
Power dissipation	$T_{amb} \leq 60 \text{ }^{\circ}\text{C}$	$P_V$	100	mW

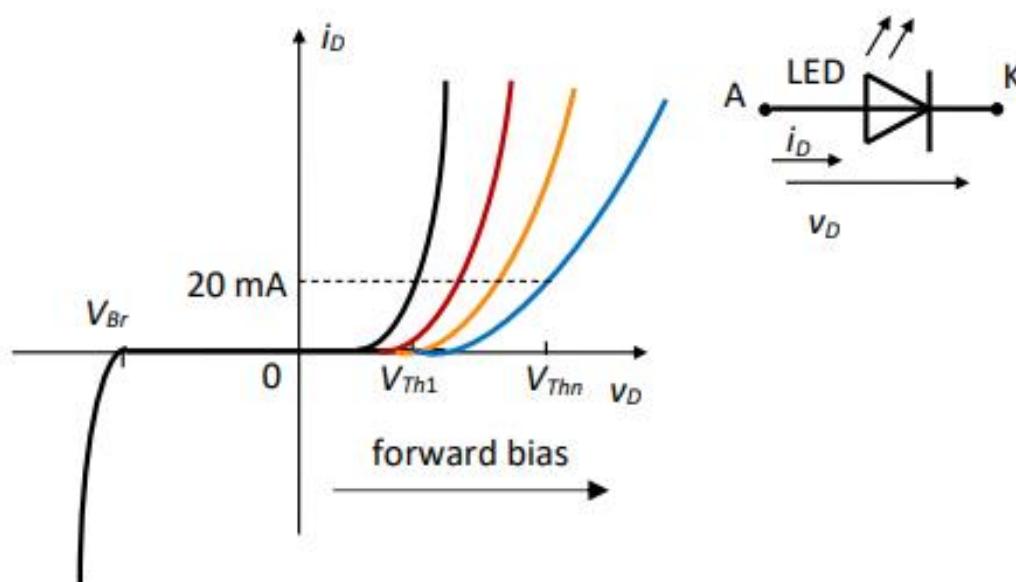


## ➤ LED strips



Single Color LED Strip

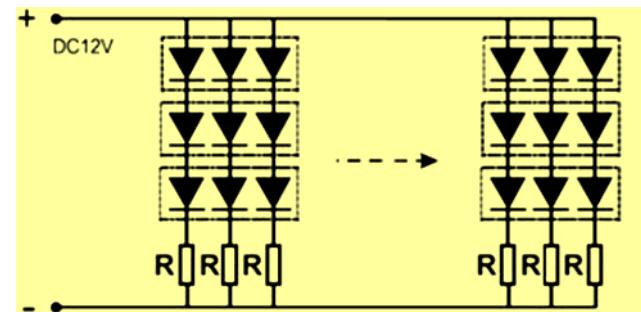

RGB LED Strip

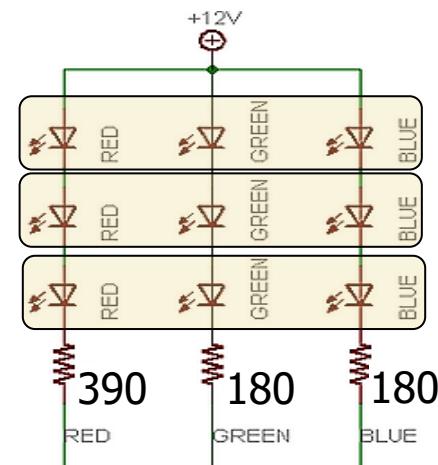

## ➤ Photodiodes

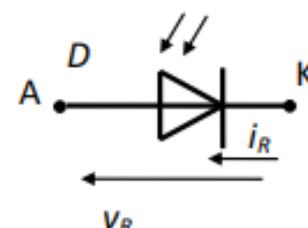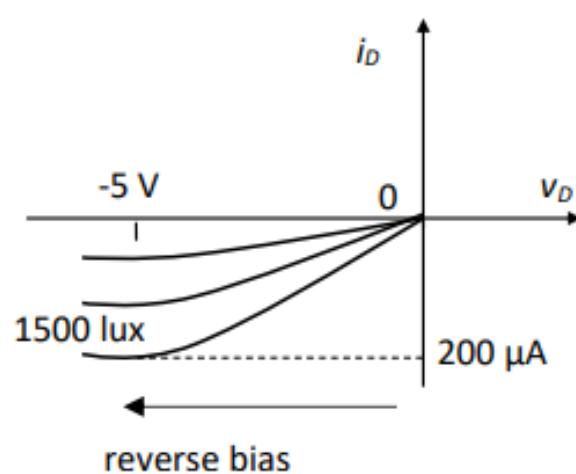

- photosensitive pn-junction
- transforms light into electrical signal (current)
- used in reverse bias

## ➤ Photodiodes - excerpt from datasheet



EVERLIGHT ELECTRONICS CO., LTD.

DEVICE NUMBER : DPD-033-071 REV : 1.0  
ECN : \_\_\_\_\_ PAGE : 1/7

### 5mm Silicon PIN Photodiode, T-1 3/4

MODEL NO : PD333-3C/H0/L2

#### ■ Features :

- Fast response time
- High photo sensitivity
- Small junction capacitance

#### ■ Description :

PD333-3C/H0/L1 is a high speed and high sensitive PIN photodiode in a standard 5  $\phi$  plastic package. The device is spectrally matched to infrared emitting diode.

#### ■ Applications :

- High speed photo detector
- Camera
- Infrared remote controller for TVs VCR, audio equipment, air conditioner, etc.

#### ■ Absolute Maximum Ratings at Ta = 25°C

Parameter	Symbol	Rating	Unit	Notice
Reverse Voltage	V <sub>R</sub>	32	V	
Power Dissipation	Pd	150	mW	
Lead Soldering Temperature	Tsol	260	°C	4mm from mold body less than 5 seconds
Operating Temperature	Topr	-25 ~ +85	°C	
Storage Temperature	Tstg	-40 ~ +85	°C	

# Summary

Only now we can safely say diodes are not a secret anymore, after studying:

- DR rectifiers – half-wave and full-wave
- DRC rectifiers (power supply filtering)
- LEDs and photodiodes

Next week: Zener diodes. Operational amplifiers.