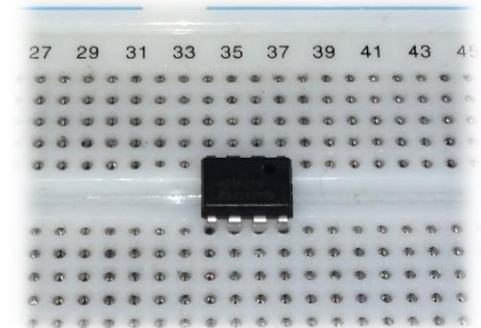




# ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

**C5 – Zener diodes.  
Operational amplifiers.**



# Contents


## ➤ Zener diodes

## ➤ The Operational Amplifier (OpAmp)

- OpAmp terminals
- OpAmp operation
- OpAmp model
- Ideal OpAmp
- Relation between output and input voltages

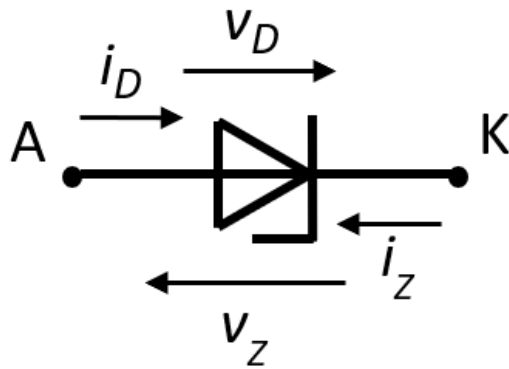
# Zener diodes (ZD)

- named after CM Zener (American physicist)
- ZDs are used in the breakdown region (regulation region) – 3<sup>rd</sup> quadrant
- working w/ positive values is usually preferred -> inverted **I** and **V**




$$i_Z = -i_D$$

$$v_Z = -v_D$$

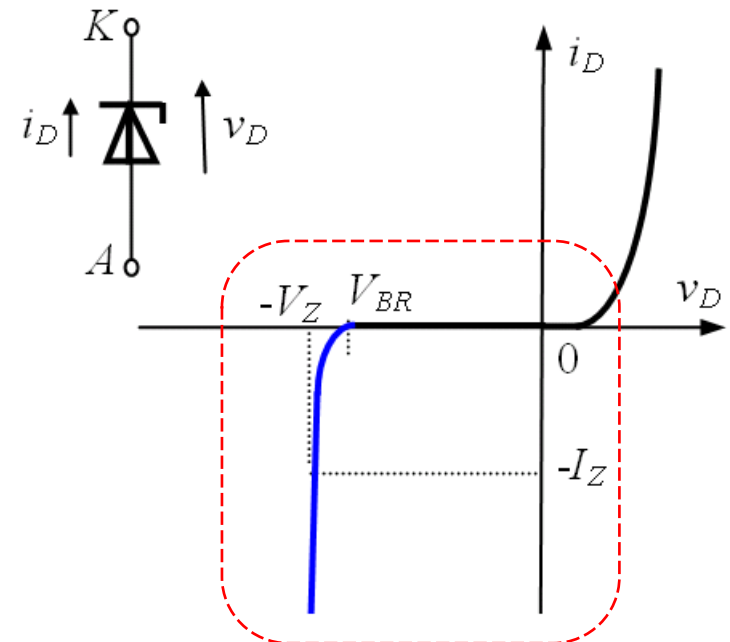

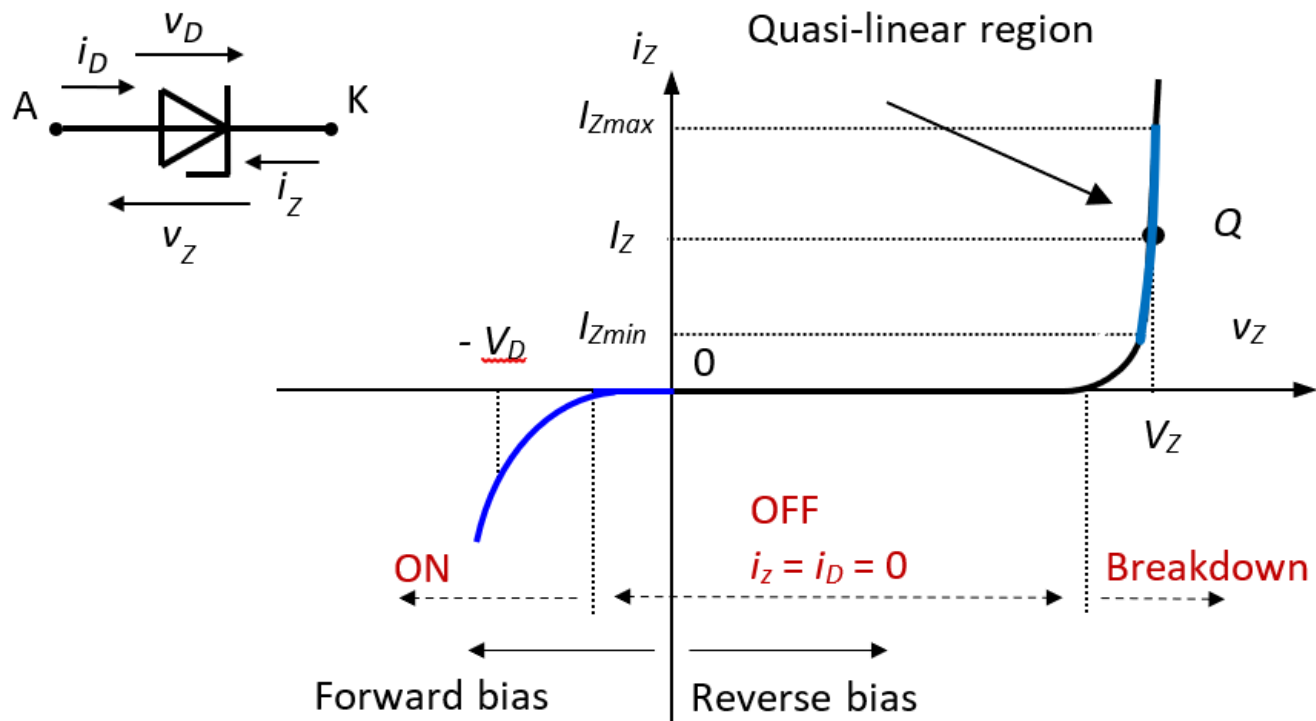
# Zener diodes (ZD)

- typically used for regulation purposes – ZD provides a constant  $V_Z$ , if  $I_Z$  stays between certain boundaries


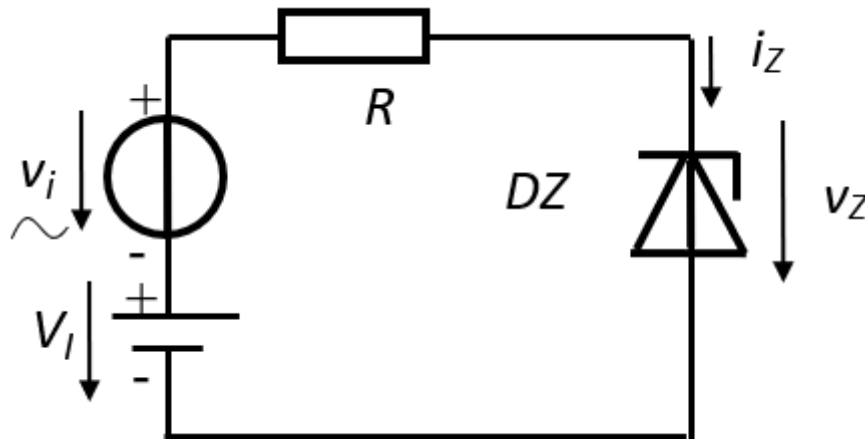
## Zener diodes (ZD)

- typically used for regulation purposes – ZD provides a constant  $V_Z$ , if  $I_Z$  stays between certain boundaries



Relative regulation factor of ZD – ratio between dynamic and static equivalent resistances

$$F_Z = \frac{r_z}{r_Z}$$

$$F_Z = \frac{\frac{\Delta v_Z}{V_Z}}{\frac{\Delta i_Z}{I_Z}}$$

## Example

$$I_Z = 5 \text{ mA:}$$

$$1) \text{ ZD 3V6} \quad V_Z = 3.6 \text{ V}; \quad r_{z\max} = 95 \text{ } \Omega; \quad r_Z = 0.72 \text{ K}\Omega$$

$$2) \text{ ZD 5V1} \quad V_Z = 5.1 \text{ V}; \quad r_{z\max} = 60 \text{ } \Omega; \quad r_Z = 1.02 \text{ K}\Omega$$

$$3) \text{ ZD 10} \quad V_Z = 10 \text{ V}; \quad r_{z\max} = 15 \text{ } \Omega; \quad r_Z = 2 \text{ K}\Omega$$

$$F_{Z1} = \frac{95}{720} = 0.132$$

$$F_{Z2} = \frac{60}{1020} = 0.059$$

$$F_{Z3} = \frac{15}{2000} = 0.0075$$

# Excerpt from the datasheet



## 1N4728A - 1N4758A Zener Diodes

Tolerance = 5%



DO-41 Glass case  
COLOR BAND DENOTES CATHODE

$$I_{Z\max} = \frac{P_{d\max}}{V_Z}$$

### Electrical Characteristics T<sub>a</sub> = 25°C unless other

Device	V <sub>Z</sub> (V) @ I <sub>Z</sub> (Note 1)			Test Current I <sub>Z</sub> (mA)
	Min.	Typ.	Max.	
1N4728A	3.135	3.3	3.465	76
1N4729A	3.42	3.6	3.78	69
1N4730A	3.705	3.9	4.095	64
1N4731A	4.085	4.3	4.515	58
1N4732A	4.465	4.7	4.935	53
1N4733A	4.845	5.1	5.355	49
1N4734A	5.32	5.6	5.88	45
1N4735A	5.89	6.2	6.51	41
1N4736A	6.46	6.8	7.14	37
1N4737A	7.125	7.5	7.875	34
1N4738A	7.79	8.2	8.61	31
1N4739A	8.645	9.1	9.555	28
1N4740A	9.5	10	10.5	25
1N4741A	10.45	11	11.55	23
1N4742A	11.4	12	12.6	21


© 2009 Fairchild Semiconductor Corporation  
1N4728A - 1N4758A Rev. H3

**OPTIONAL**

## Temperature dependence



- The thermal coefficients TC of ZDs depend on the operating current and voltage.
- ZDs w/ **Zener effect** ( $V_Z = 2...5$  V): negative TC
- ZDs w/ **avalanche multiplication** ( $V_Z > 5$  V): positive TC
- ZD5V1  $V_Z = 5.1$  V, TC  $\sim 0$  mV/°C, for small currents.
- ZD6V8  $V_Z = 6.8$  V, TC  $\sim 2$  mV/°C.

Cancelling the temperature dependence

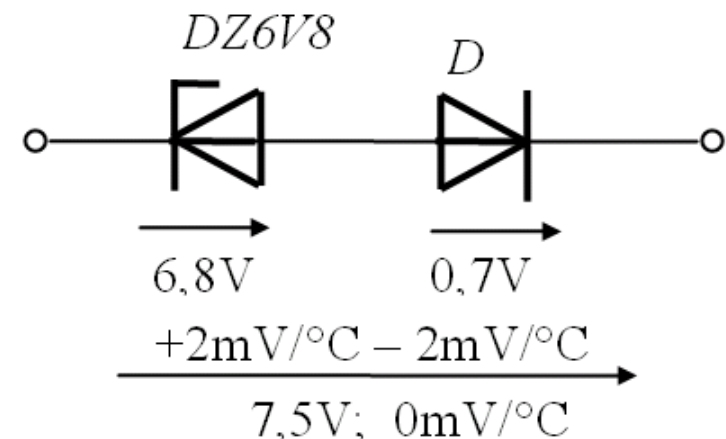




➤ Double voltage clamp (limiter) – 1 ZD

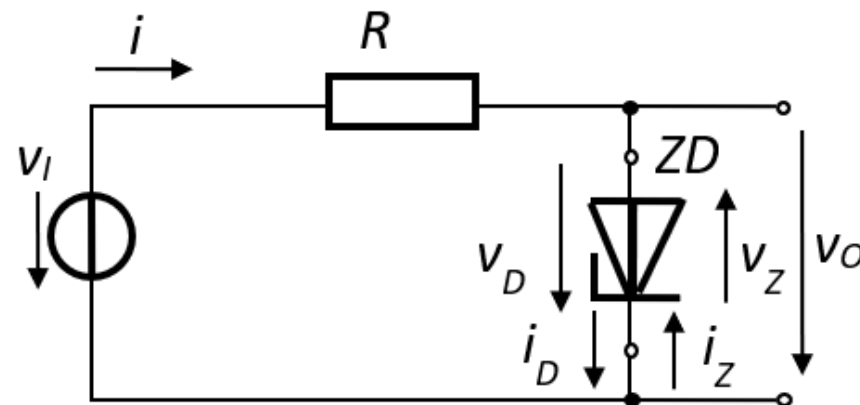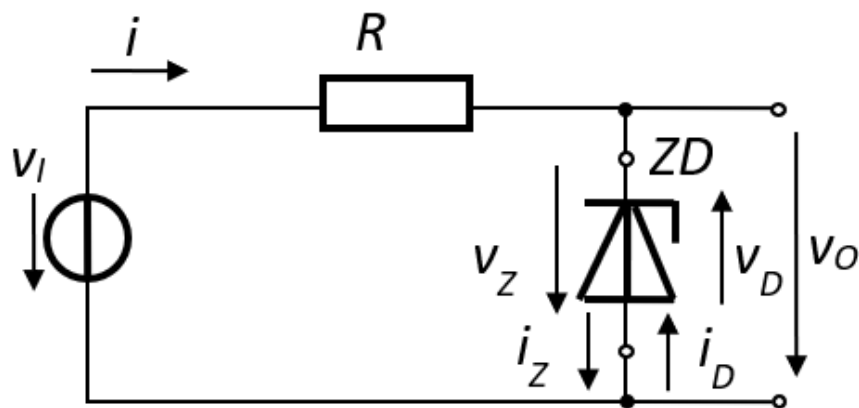

➤ Double voltage clamp (limiter) – 1 ZD

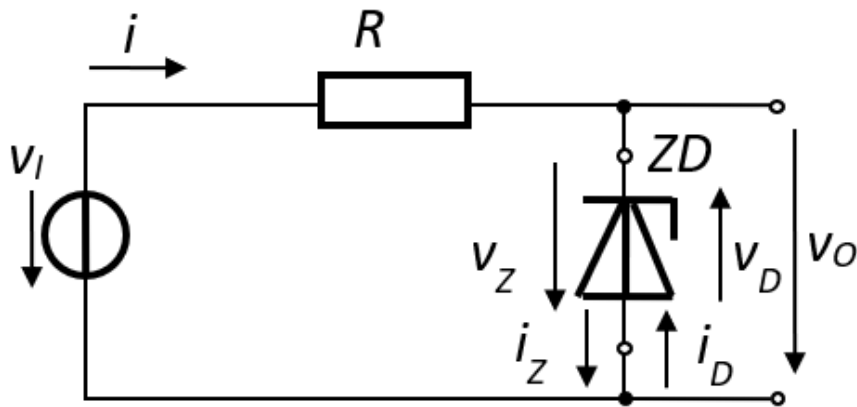


$$v_i = i_z \cdot R + v_o$$

$$v_o = v_Z$$

$$v_i = -i_D \cdot R + v_o$$



$$v_o = -v_D$$

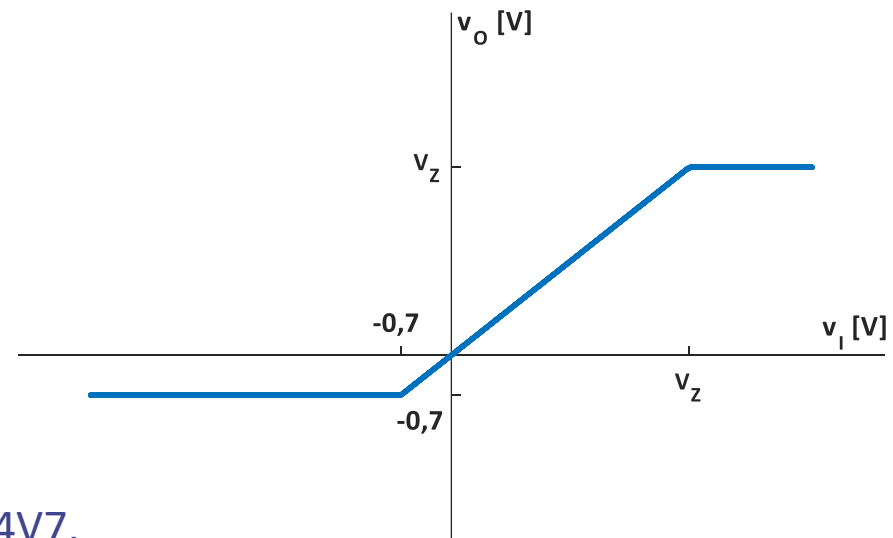- ZD - breakdown for  $v_i > V_Z$ ,  $V_{Omax} = V_Z$
- ZD - on for  $v_i < -0.7 \text{ V}$ ,  $V_{Omin} = -0.7 \text{ V}$
- ZD - off for  $-0.7 \text{ V} < v_i < V_Z$ ,  $v_o = v_i$



Plot  $v_o$  for  $v_i$  – sinewave, 8 V amplitude, and ZD4V7.

➤ Double voltage clamp (limiter) – 2 ZDs

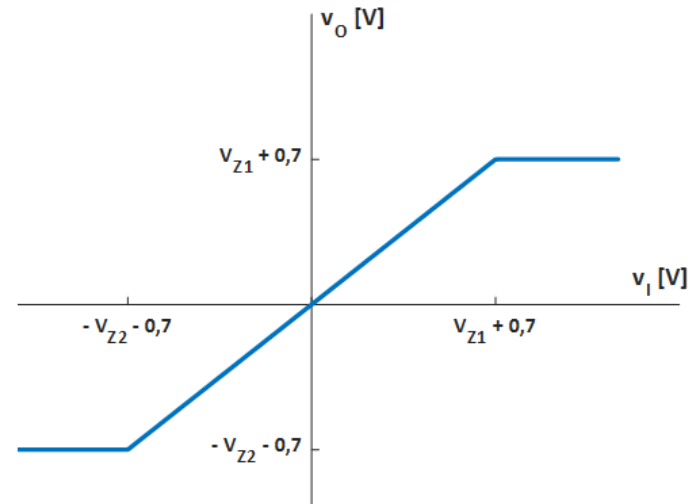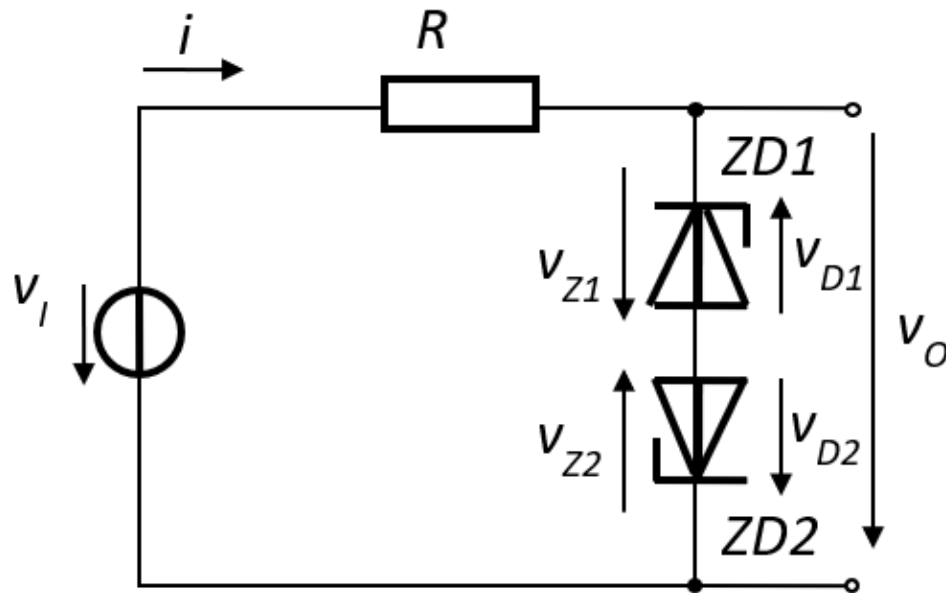

Expression  $v_o(v_I)$ ?



States of ZD1, ZD2?

What does  $v_o$  look like, for  $v_I$  – sinewave, 15 V amplitude and  $ZD1 = ZD2 = ZD5V1$ ?

## ➤ Voltage reference

= electronic device that ideally produces a **constant voltage (denoted  $V_{REF}$ )**, regardless of the loading on the device, power supply variations, temperature changes, and the passage of time.

$$I_0 \ll I_Z$$

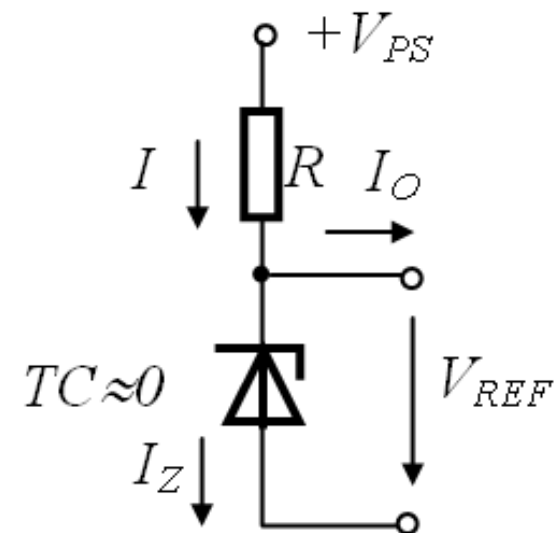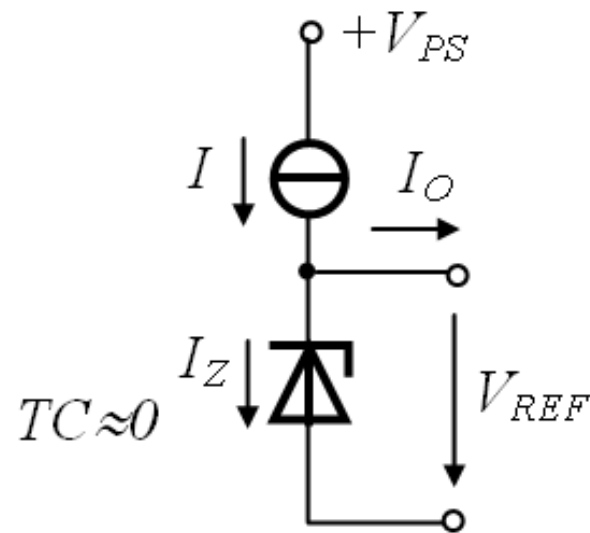



Typical uses: power supplies, AD/DA converters, measurement and control systems.

## ➤ In a nutshell:
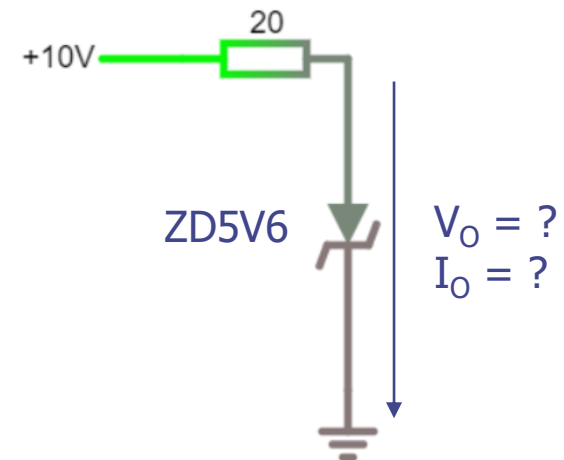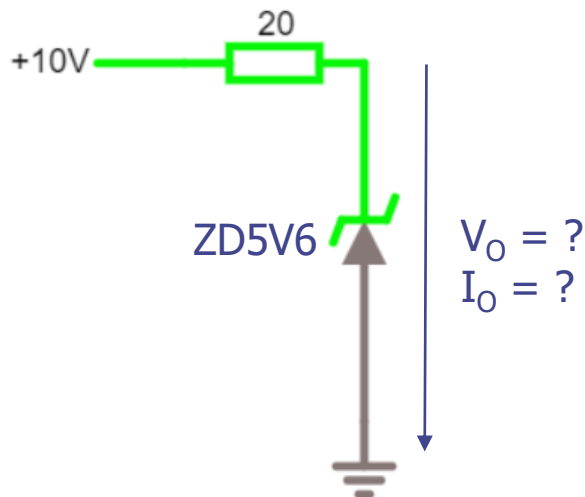
### Zener diodes

in forward bias: ZD  $\equiv$  D (equiv. to a conventional diode)


in breakdown: ZD  $\equiv$  dc voltage source (constant voltage =  $V_Z$ )


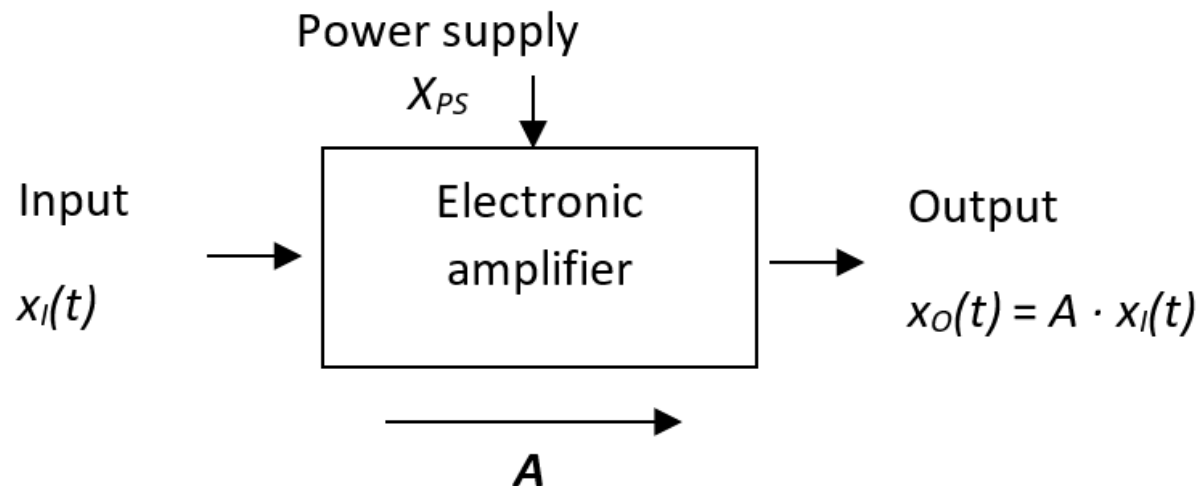
## Electronic amplifiers

Electronic amplifier – circuit with two inputs (input signal and power supply) and one output



The output signal is an amplified (magnified) version of the input signal.




$$A = \frac{x_o(t)}{x_i(t)}$$

$A$  – gain (amplification)

# Electronic amplifiers

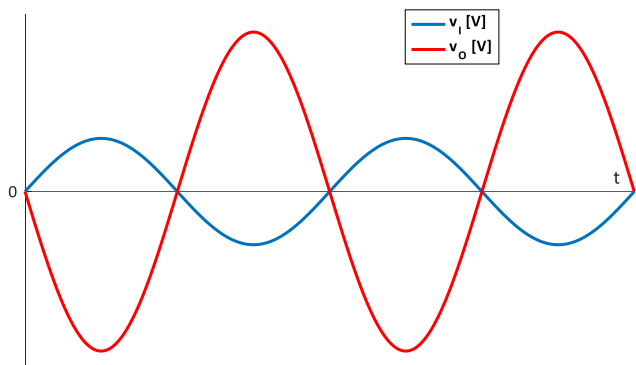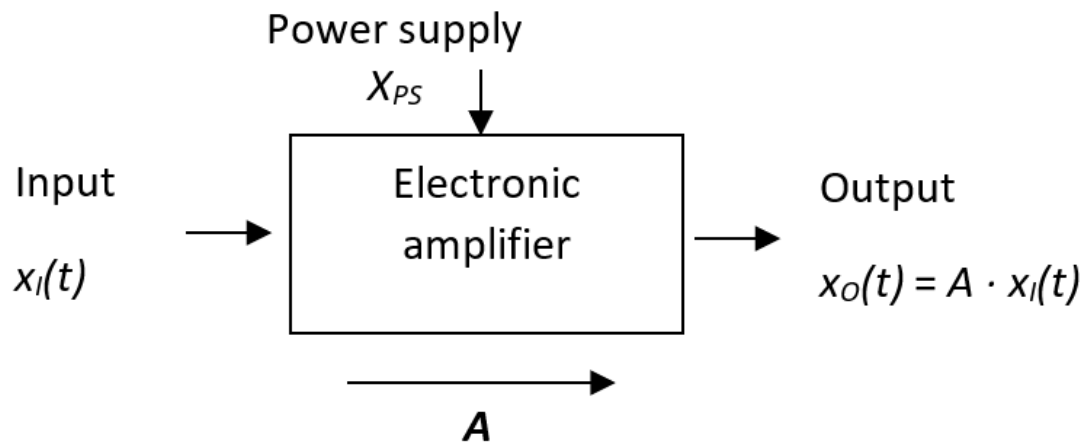

Inverting amplifier ( $A < 0$ )

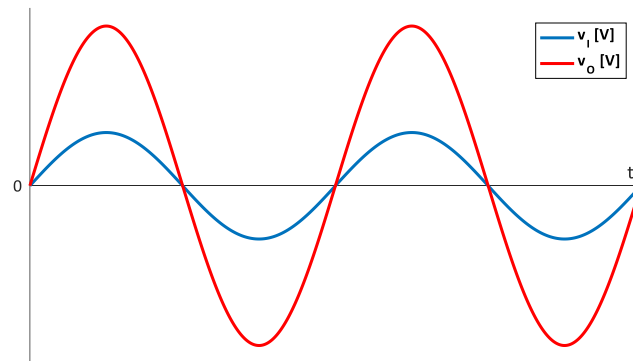

Non-inverting amplifier ( $A > 0$ )


## OpAmp

- invented by Karl D. Swartzel Jr., Bell Labs, 1941
- IC containing a relatively large number of transistors and passive components (R) on the same chip (e.g. OpAmp 741 contains 24 T, 12 R and 1 C).

OpAmps are packed in plastic or metal cases, with 8, 14 or 16 terminals.



Through-hole technology

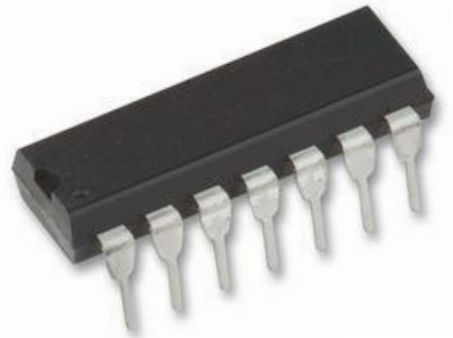

Surface-mount technology (SMT)



## OpAmp


- very popular ICs, due to versatility and ease of use
- terminal characteristics that closely approach the ideal amplifier
- wide variety, optimized for: speed, low noise, low power consumption, high gain, maximum output swing (rail-to-rail), etc

OpAmps will be discussed as **electronic devices**, focusing on the **terminal characteristics** and **main applications**.

The internal structure is of no interest, at this point.


## OpAmp terminals

OpAmp – plastic case, 8 terminals (pins)

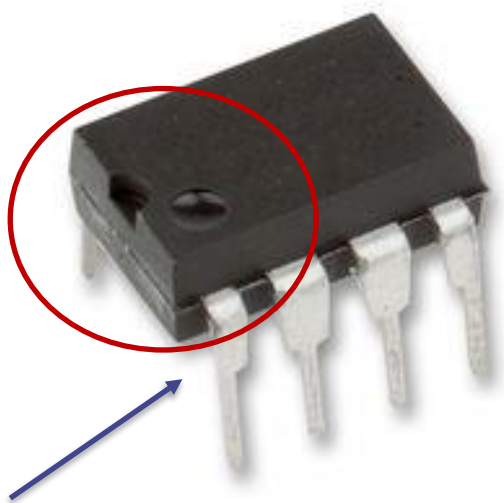


#1

LM741 Pinout Diagram

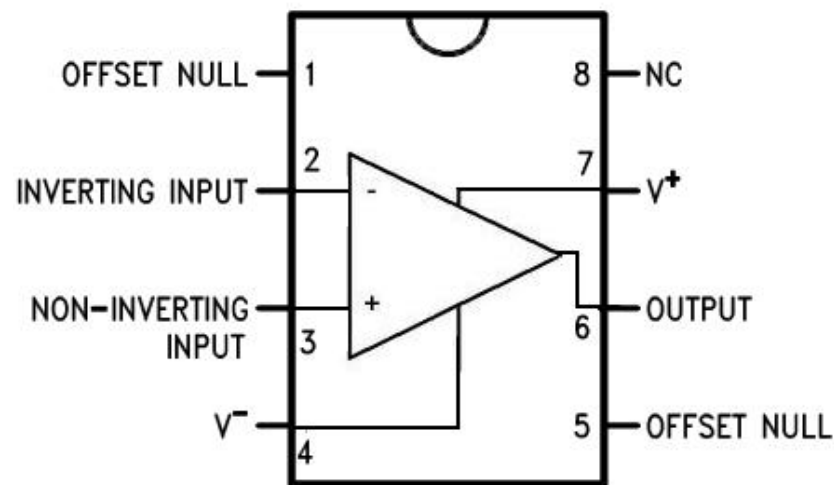


# OpAmp terminals

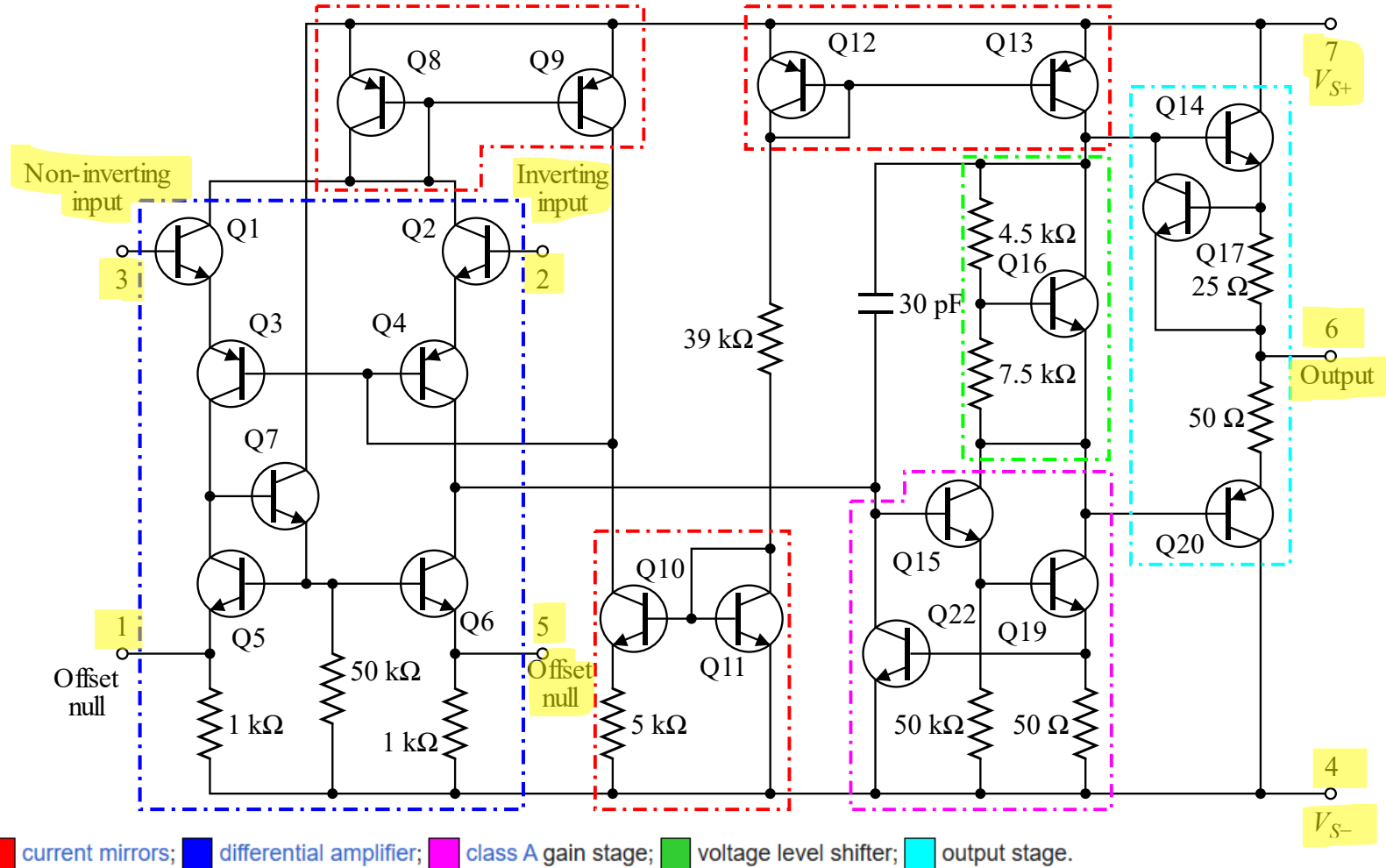


## OpAmp terminals

- 5 terminals - 2 for input voltages (#2 & #3)
- 2 for power supplies (#4 & #7)
- 1 for output voltage (#6)


LM741 Pinout Diagram

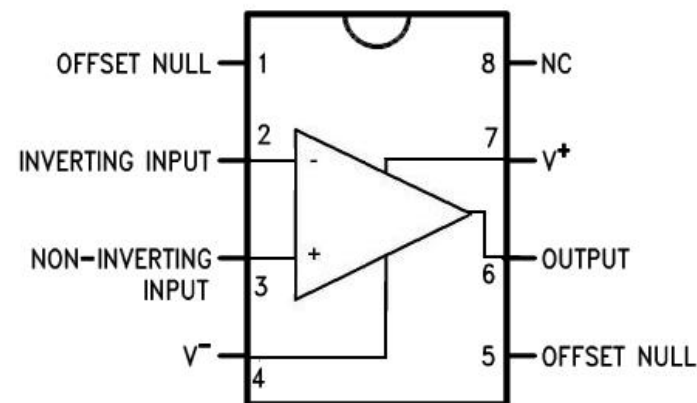

signal terminals

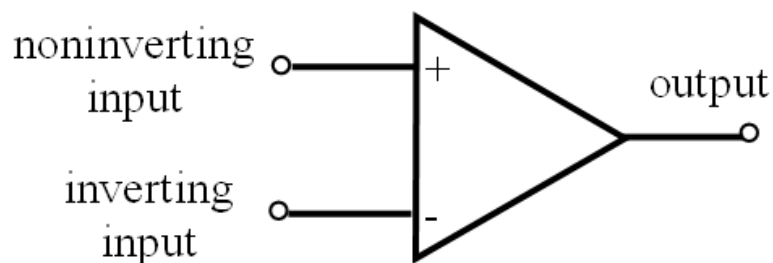



signal and supply terminals

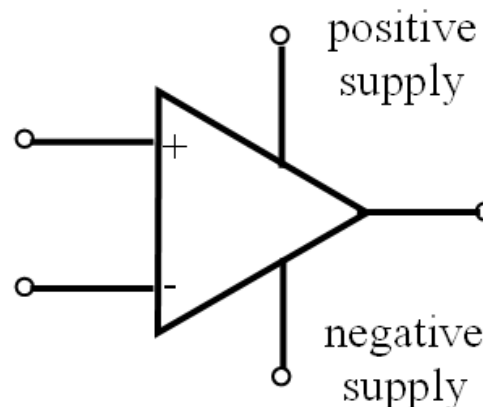


## OpAmp terminals

The supply terminals are frequently omitted from circuit schematics, assuming a correct supply.

**!Find the difference!**

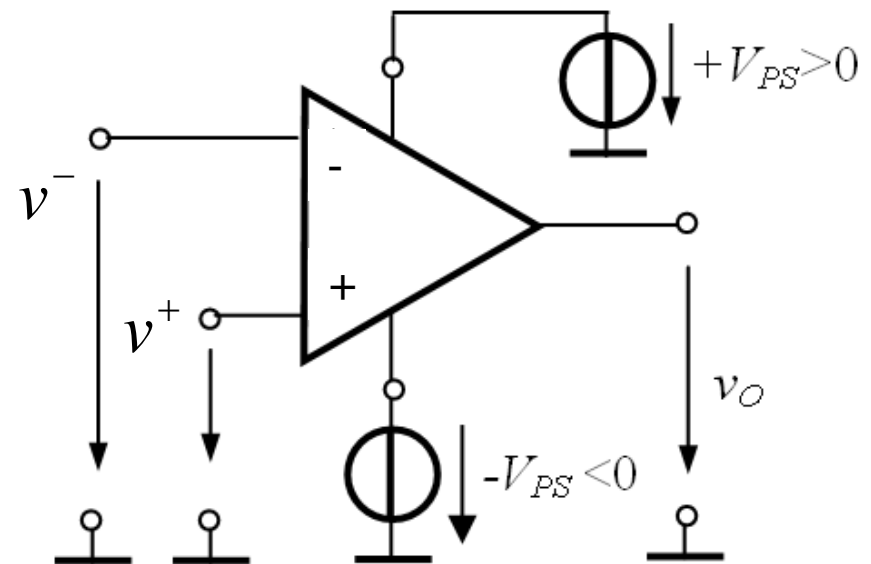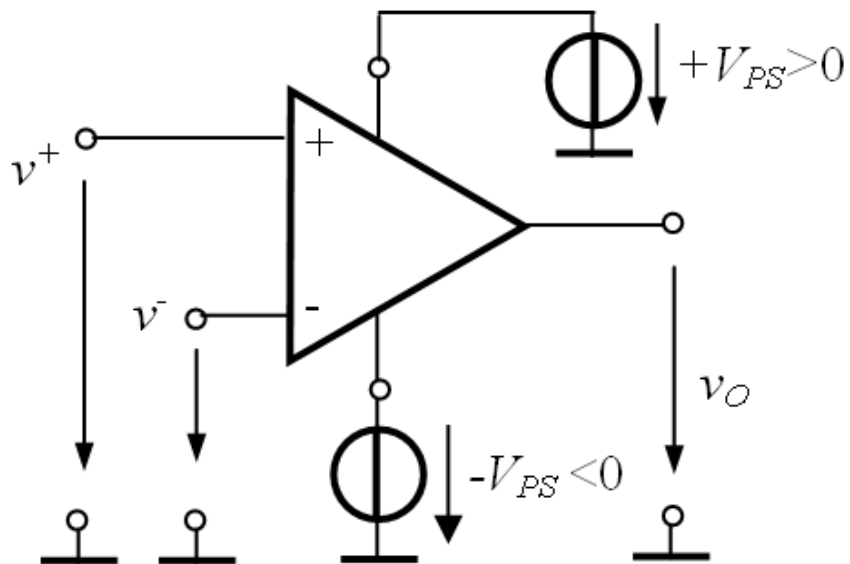

## OpAmp operation

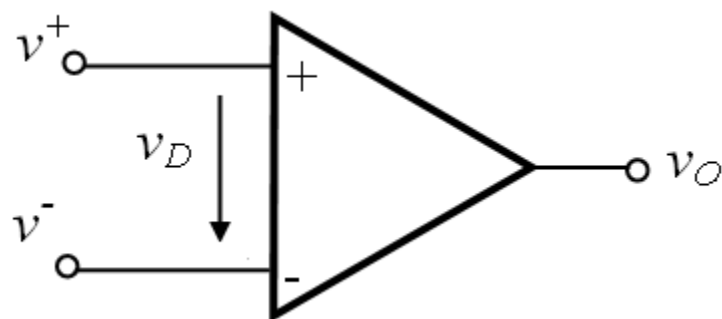

$$v_D = v^+ - v^-$$

a – OpAmp gain (very large, i.e.  $2 \cdot 10^5$ )

$$v_O = a v_D$$

$$v_{O \max} = +V_{PS}$$

$$v_{O \min} = -V_{PS}$$

**!Do not confuse:**


- differential voltage of OpAmp

$$v_D$$

- diode voltage drop



$$v_D = 0.7V$$

## OpAmp model

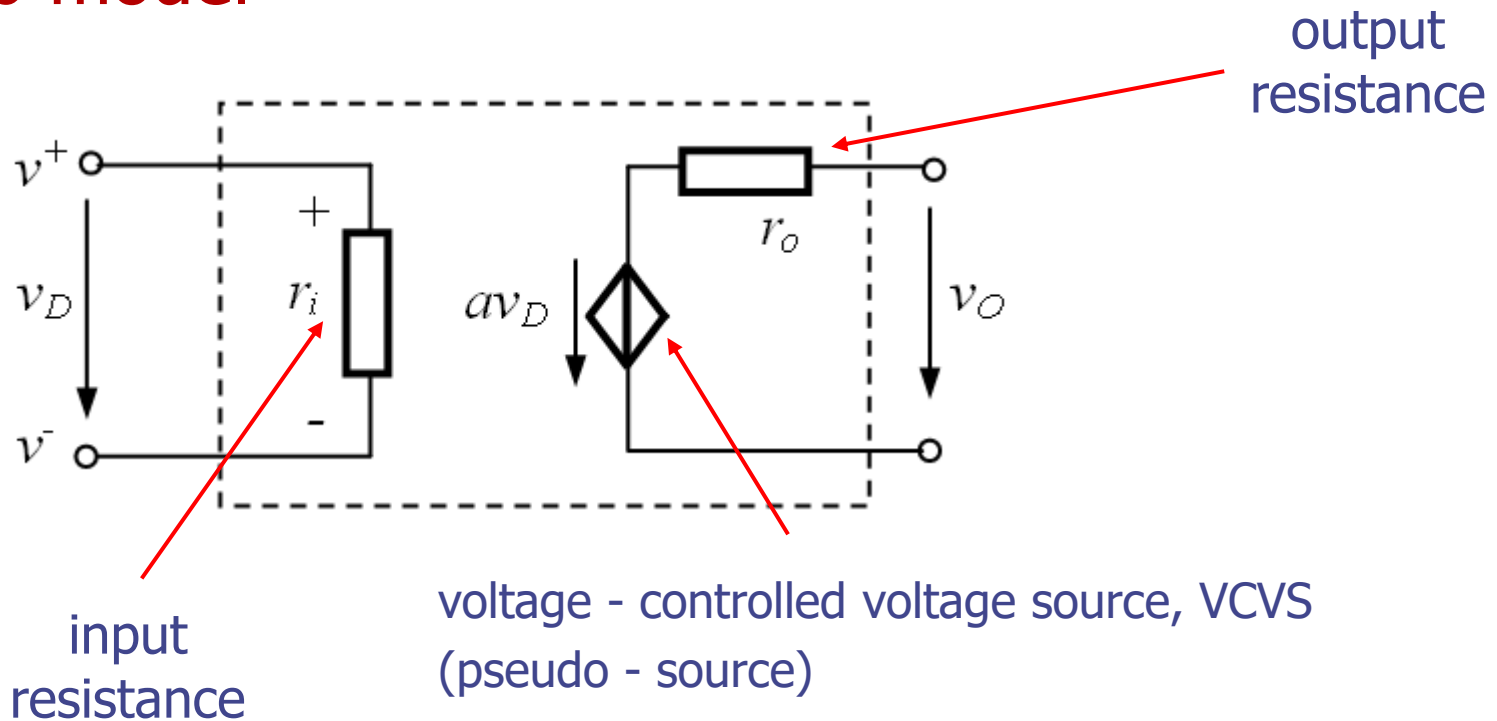

- input voltage is  $v_D = v^+ - v^-$
- if none of the inputs are connected to ground, there is no common terminal between input and output

# Ideal OpAmp

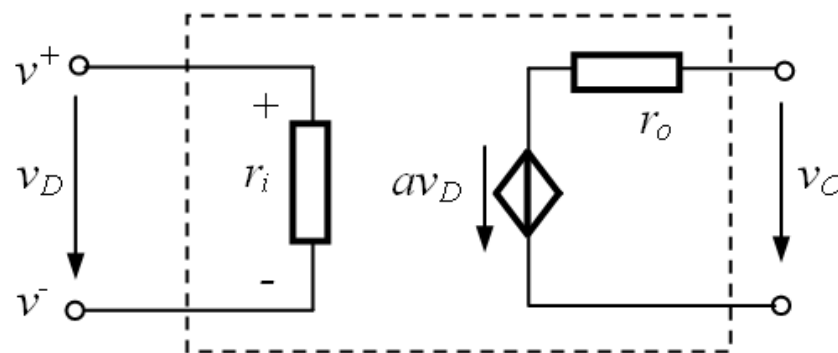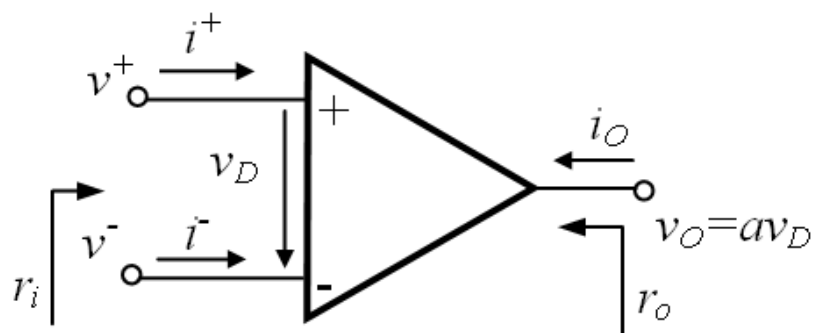

Parameter	Ideal value	Effect
Input resistance	$r_i = \infty$	OpAmp does not draw any input currents $i_+ = i_- = 0$
Output resistance	$r_o = 0$	The output voltage is independent of the current into the load.
Bandwidth	$BW = \infty$	The gain is constant over all the frequency range, from zero frequency (dc) and to infinite frequency.
Gain	$a = \infty$	



## Relation between output and input voltages

Assuming an ideal OpAmp, what is the value of the output voltage?

$$v_O = av_D = \infty \cdot v_D$$

But

$$\left\{ \begin{array}{l} v_{O \max} = +V_{PS} \\ v_{O \min} = -V_{PS} \end{array} \right.$$

Solution?

# Summary

## ➤ Zener diodes

The first encounter with the *little black bug* (OpAmp) revealed details about:

## ➤ The Operational Amplifier (OpAmp)

- OpAmp terminals
- OpAmp operation
- OpAmp model
- Ideal OpAmp
- Relation between output and input voltages

**Next week:** Simple comparators with OpAmp.