

FUNDAMENTAL ELECTRONIC CIRCUITS

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C12-13 – 555 Timer. Class D amplifier.

Contents

- Intro
- 555 Timer
- Class D amplifier

➤ Signal generators/oscillators - revisited

- circuits which produce/generate a variable output signal, of a certain shape (sinusoidal, rectangular, triangular, sawtooth) and frequency, **in the absence** of a variable input signal (power supplies only)
- convert **DC** signals (power supplies) into **AC** signals
- must contain **reactive** components (capacitor, inductor)

➤ Types of signal generators - revisited

Based on the shape of the output signal:

- **sinusoidal** oscillators (aka *linear* or *harmonic* oscillators)

C10, Lab 11, Seminar 6




- **nonsinusoidal** oscillators (aka *relaxation* oscillators)

C11, Seminar 7



rectangular

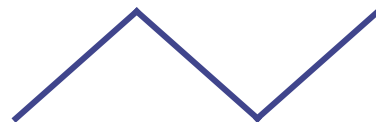

triangular



sawtooth



pulse

➤ Relaxation oscillators – principle and usage

- aka **multivibrators**

= circuits made of a **feedback loop** containing a **switching device** (transistor, comparator, relay, OpAmp) that repetitively **charges** a **capacitor** or **inductor** through a resistance until it reaches a **threshold** level, then **discharges** it again.

The period/frequency of the oscillations depends on the **time constant** of the C or L circuit.

- produce low frequency signals
- easier to design than linear oscillators
- easier to integrate (no inductors)

Applications: blinking lights, electronic beepers, horizontal deflection circuits in CRT oscilloscopes, voltage controller oscillators (VCOs).

Drawbacks: more phase noise, poor frequency stability

➤ Relaxation oscillators – types

What is a stable state?

What does it take for the circuit to switch between states?

Based on the number of stable states:

- **no** stable states – **astable** multivibrator
 - the circuit permanently switches between the two unstable states
- **one** stable state – **monostable** multivibrator
 - a trigger/pulse causes the circuit to enter the unstable state. The circuit returns to the stable state by itself, after a certain period.
- **two** stable states – **bistable** multivibrator (flip-flop or latch)
 - the circuit is stable in either state. An external trigger/pulse is used to switch between states.

➤ LM555 - features

Designed in **1971** by Hans Camezind

- highly stable IC
- used to generate **time delays** or **oscillation**
- timing from **microseconds** through hours
- **adjustable** duty cycle
- output can source or sink **200 mA**
- output and supply TTL **compatible**
- **temperature stability** better than 0.005% per °C

Versions:



- LM555 - in bipolar technology
- LMC555 - in CMOS technology

Used as:


- astable/monostable/bistable circuit
- rectangular and triangular signal generator



➤ LM555 – structure and operation

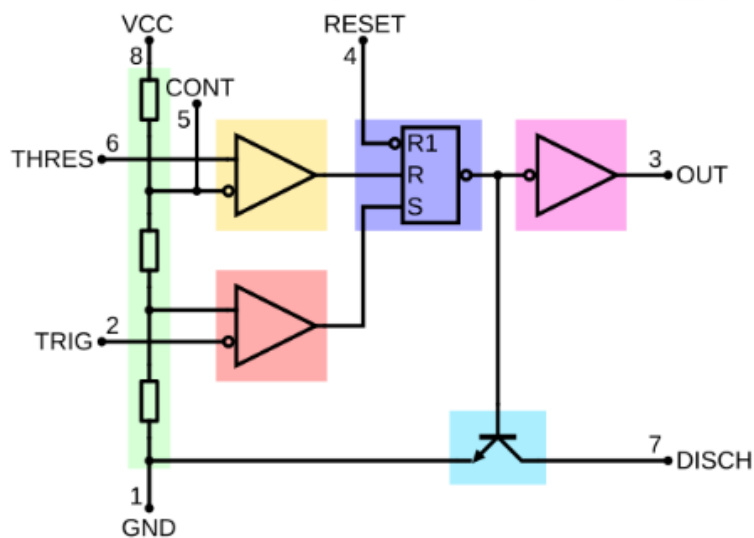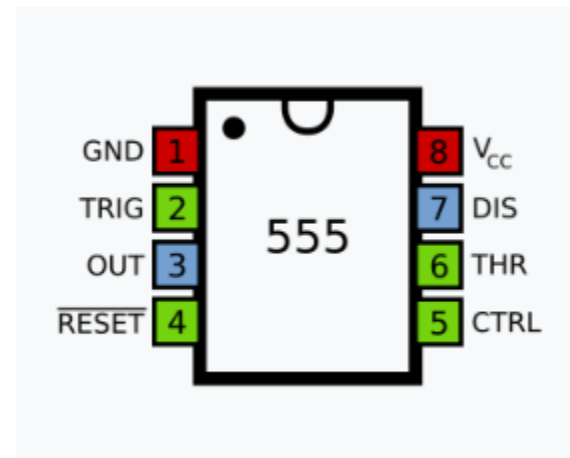

555 internal block diagram^[1]

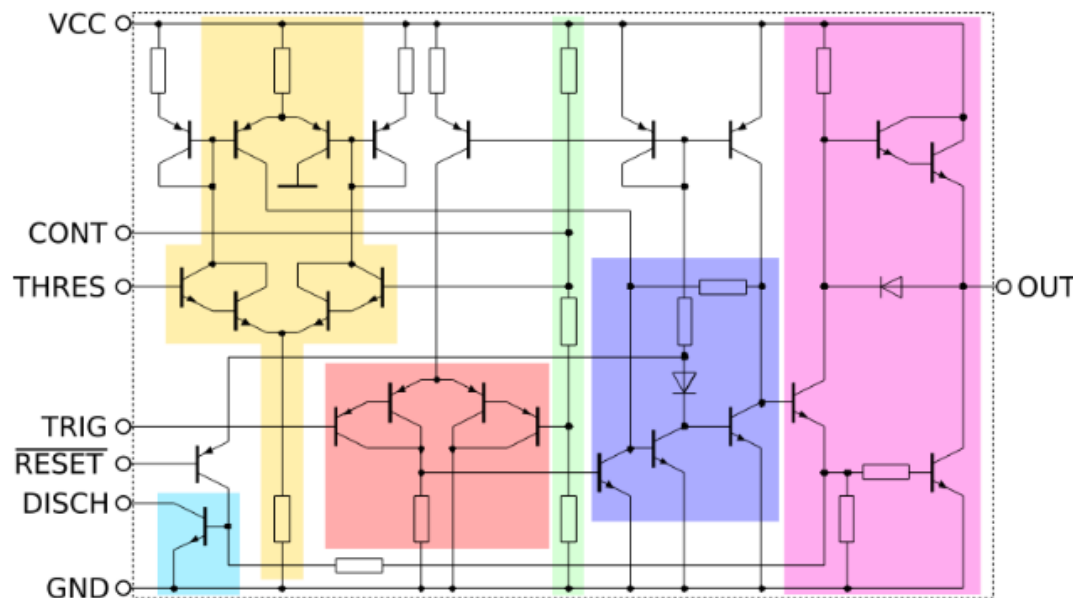

555 internal schematic of bipolar version

➤ LM555 – structure and operation

$$V_{CC} = 5 \dots 15 \text{ V}$$

$$R_1 = 5 \text{ k}\Omega \text{ (hence the name of the IC)}$$

C1 – **non-inverting** simple comparator


- compares *Threshold* to $\frac{2}{3}V_{CC}$

$$v_{O,C1} = \begin{cases} 0, & \text{Threshold} < \frac{2}{3}V_{CC} \\ V_{CC}, & \text{Threshold} > \frac{2}{3}V_{CC} \end{cases}$$

C2 – **inverting** simple comparator

- compares *Trigger* to $\frac{1}{3}V_{CC}$

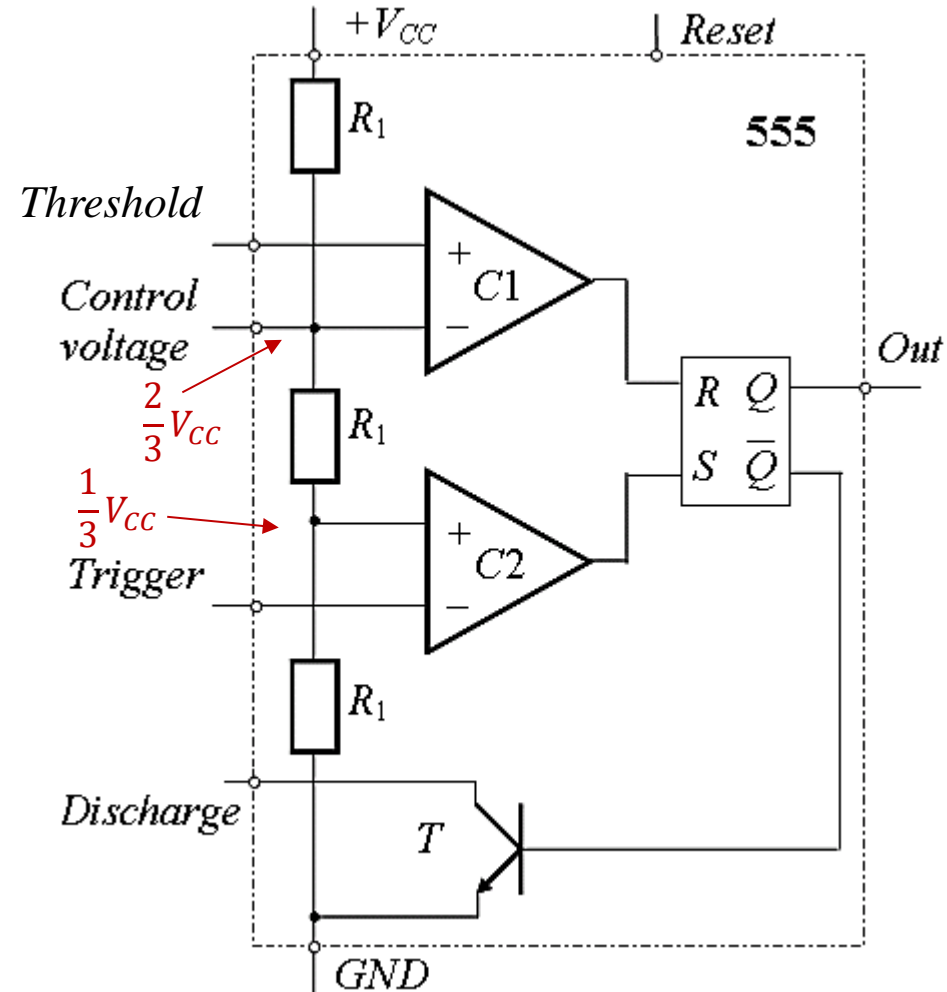
$$v_{O,C2} = \begin{cases} 0, & \text{Trigger} > \frac{1}{3}V_{CC} \\ V_{CC}, & \text{Trigger} < \frac{1}{3}V_{CC} \end{cases}$$



➤ LM555 – structure and operation

$$v_{o,c1} = \begin{cases} 0, & \text{Threshold} < \frac{2}{3}V_{cc} \\ V_{cc}, & \text{Threshold} > \frac{2}{3}V_{cc} \end{cases}$$
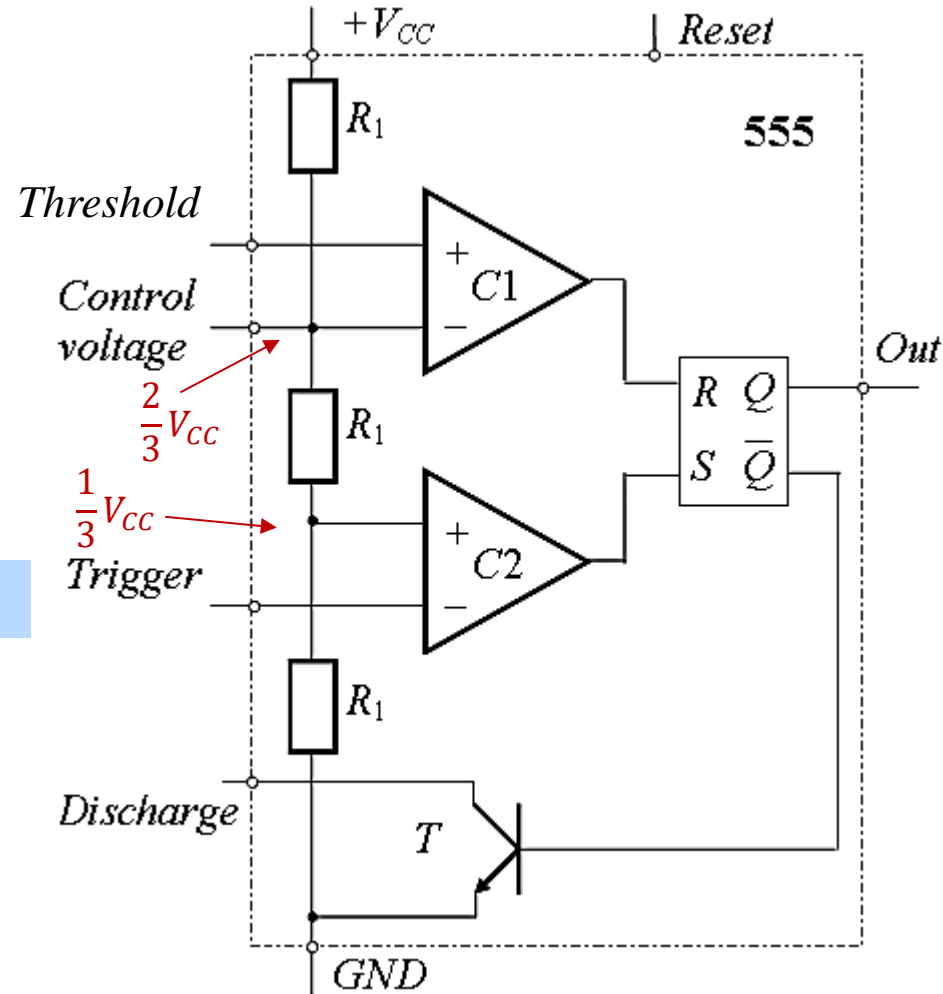
$$v_{o,c2} = \begin{cases} 0, & \text{Trigger} > \frac{1}{3}V_{cc} \\ V_{cc}, & \text{Trigger} < \frac{1}{3}V_{cc} \end{cases}$$



<i>R</i>	<i>S</i>	<i>Q</i>	\bar{Q}
L	L	no change	no change
H	L	L	H
L	H	H	L
H	H	forbidden	forbidden

➤ LM555 – structure and operation

$$v_{o,c1} = \begin{cases} 0, & \text{Threshold} < \frac{2}{3}V_{CC} \\ V_{CC}, & \text{Threshold} > \frac{2}{3}V_{CC} \end{cases}$$

$$v_{o,c2} = \begin{cases} 0, & \text{Trigger} > \frac{1}{3}V_{CC} \\ V_{CC}, & \text{Trigger} < \frac{1}{3}V_{CC} \end{cases}$$

<i>R</i>	<i>S</i>	<i>Q</i>	\bar{Q}
L	L	no change	no change
H	L	L	H
L	H	H	L
H	H	forbidden	forbidden

<i>Thresh</i>	<i>Trig</i>	$v_{o,c1}$	$v_{o,c2}$	<i>R</i>	<i>S</i>	<i>Q</i>	\bar{Q}	<i>T</i>	<i>Out</i>
$< \frac{2}{3}V_{CC}$	$< \frac{1}{3}V_{CC}$	0	V_{CC}	L	H	H	L	off	V_{CC}
$> \frac{2}{3}V_{CC}$	$> \frac{1}{3}V_{CC}$	V_{CC}	0	H	L	L	H	on	0
$< \frac{2}{3}V_{CC}$	$> \frac{1}{3}V_{CC}$	0	0	L	L	no change	no change	no change	no change

➤ Astable multivibrator w/ LM555


Thresh & Trigger receive the same voltage

- charging C

$$\tau_c = (R_A + R_B)C$$

- discharging C



$$\tau_d = R_B C$$

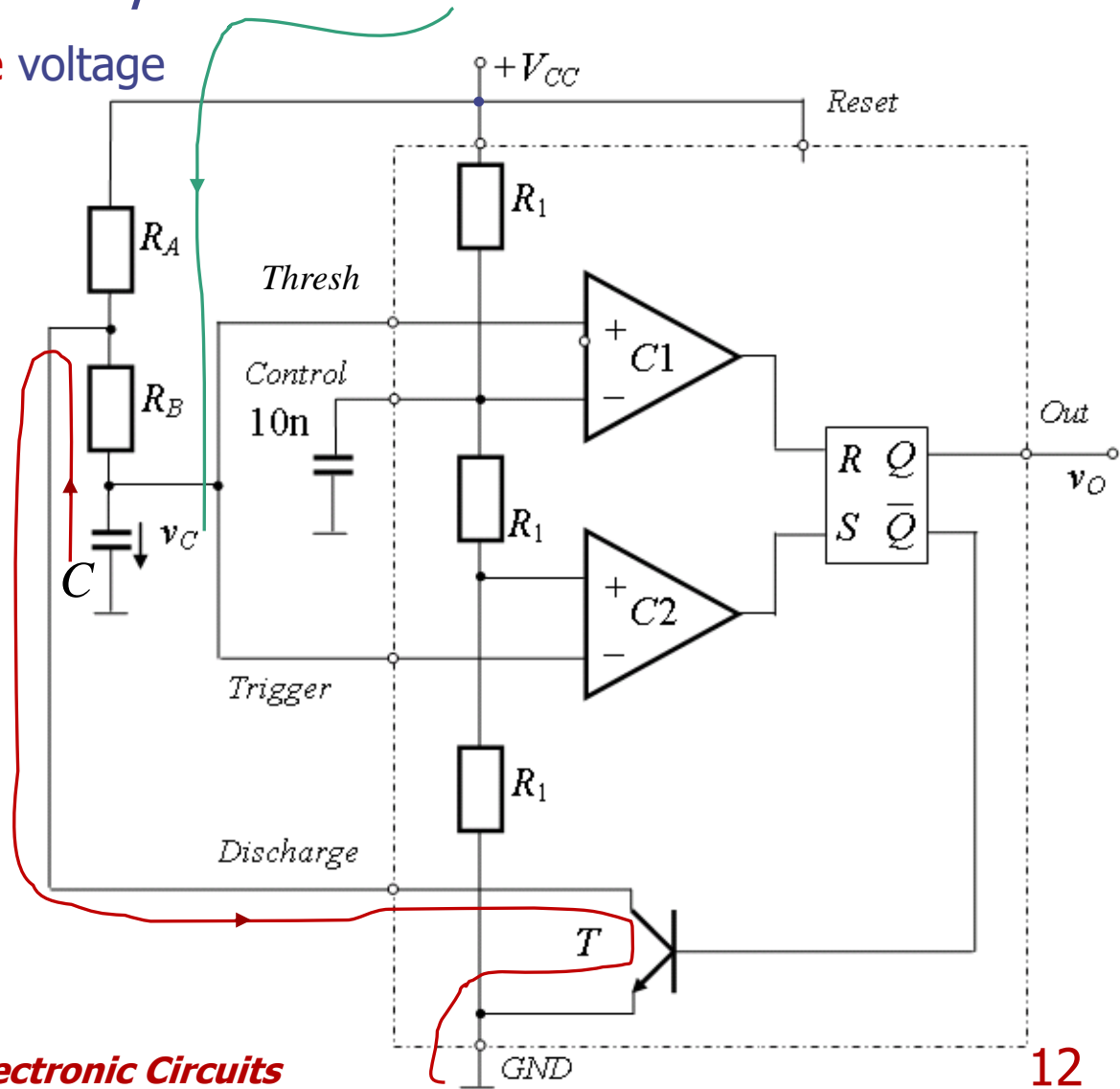


➤ Astable multivibrator w/ LM555

$$\tau_c = (R_A + R_B)C$$

$$\tau_d = R_B C$$

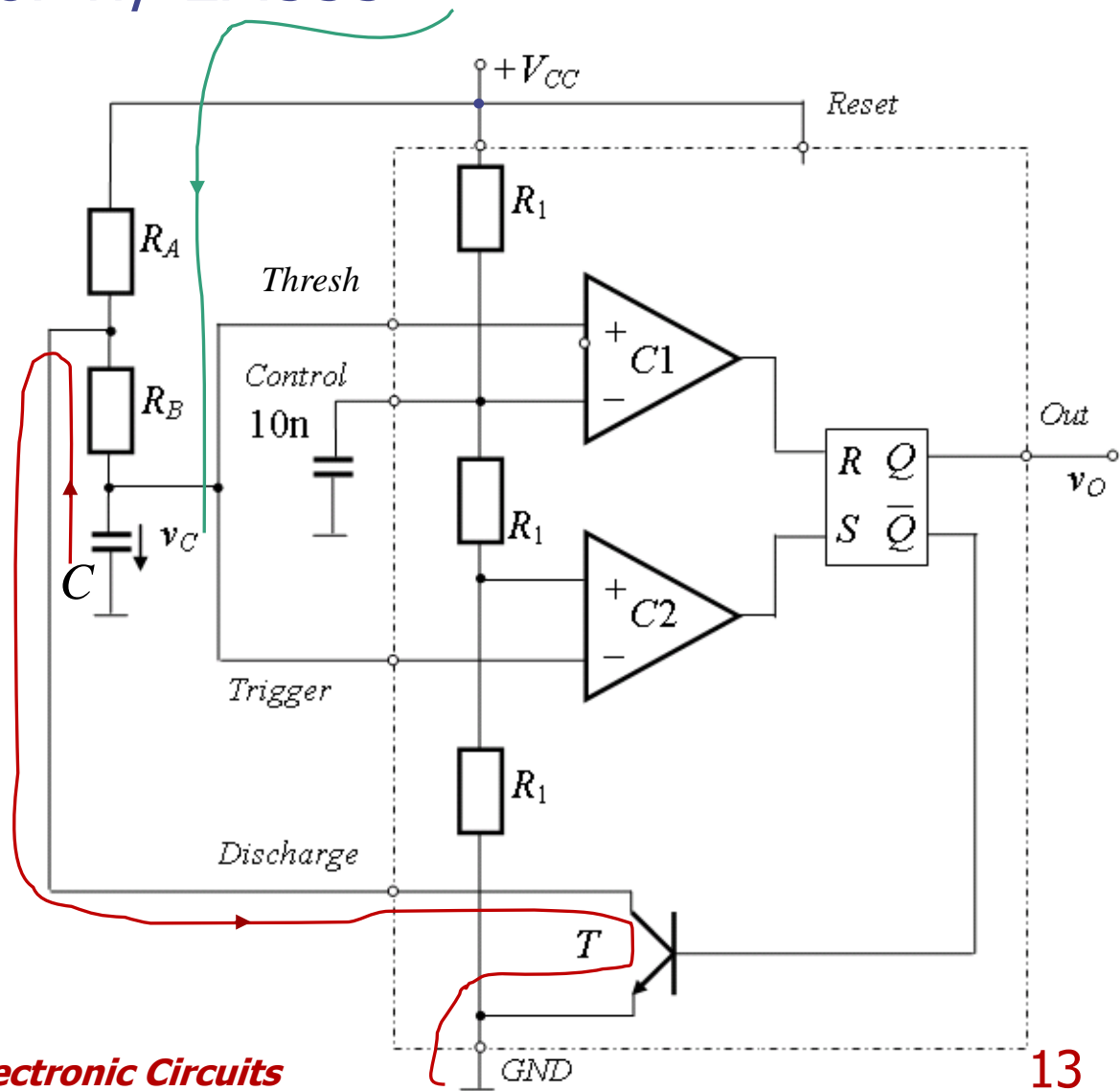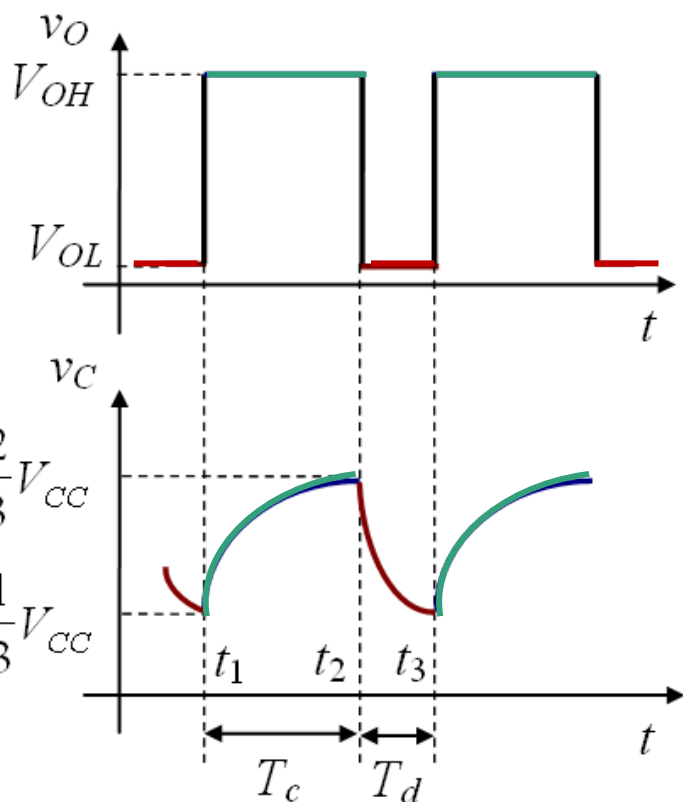

➤ Astable multivibrator w/ LM555

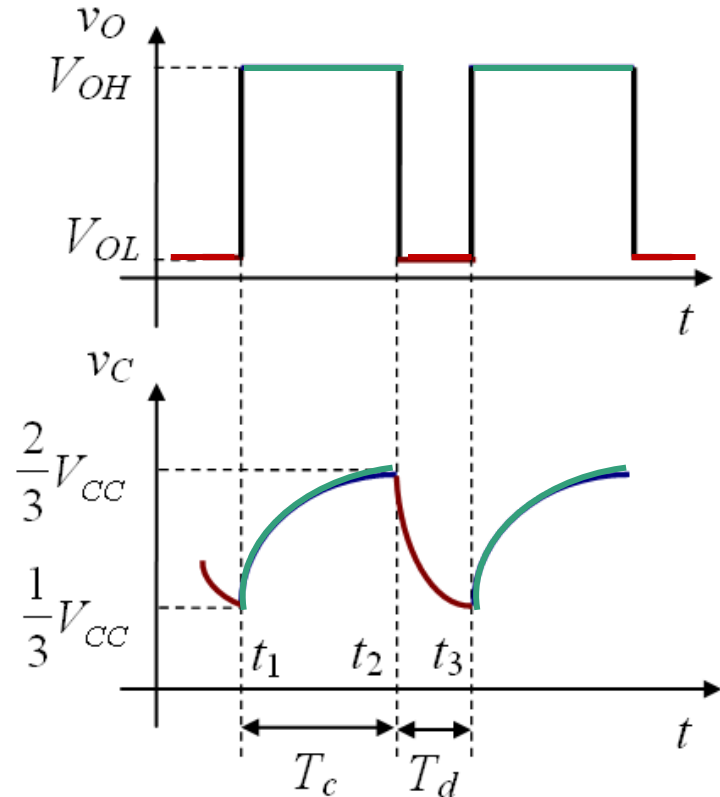

$$v_C(t) = v_C(0)e^{-\frac{t}{\tau}} + (1 - e^{-\frac{t}{\tau}})v_C(\infty)$$

$$t \in (t_1, t_2)$$

$$\frac{2}{3}V_{CC} = \frac{1}{3}V_{CC}e^{-\frac{T_c}{\tau_c}} + (1 - e^{-\frac{T_c}{\tau_c}})V_{CC}$$

$$T_c = (R_A + R_B)C \ln 2 \approx 0.69(R_A + R_B)C$$

$$t \in (t_2, t_3)$$

$$\frac{1}{3}V_{CC} = \frac{2}{3}V_{CC}e^{-\frac{T_d}{\tau_d}} + (1 - e^{-\frac{T_d}{\tau_d}}) \cdot 0$$

$$T_d = R_B C \ln 2 \approx 0.69R_B C$$



$$T = T_c + T_d = (R_A + 2R_B)C \ln 2 \approx 0.69(R_A + 2R_B)C$$

Duty cycle

$$\delta = \frac{T_c}{T_c + T_d} = \frac{R_A + R_B}{R_A + 2R_B}$$


➤ Monostable multivibrator w/ LM555

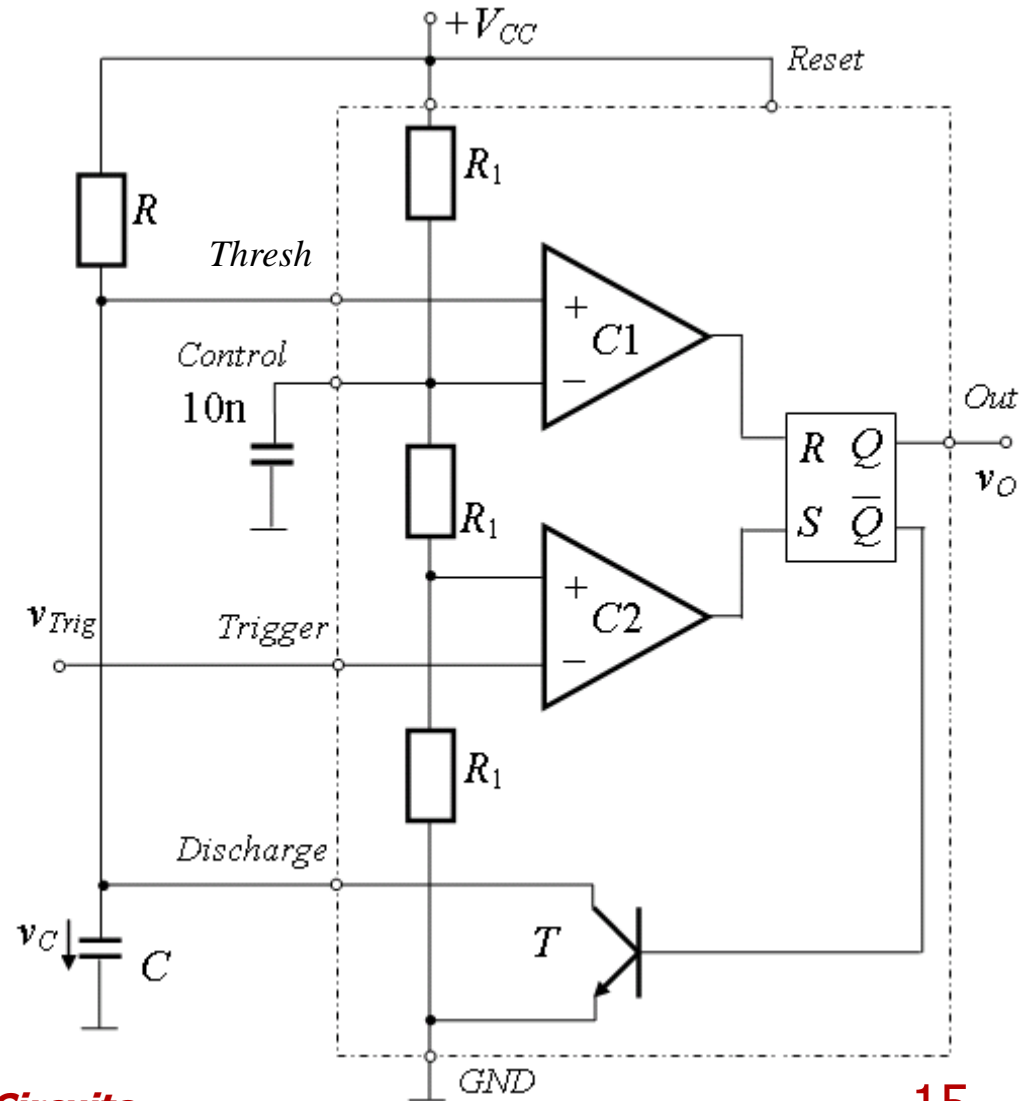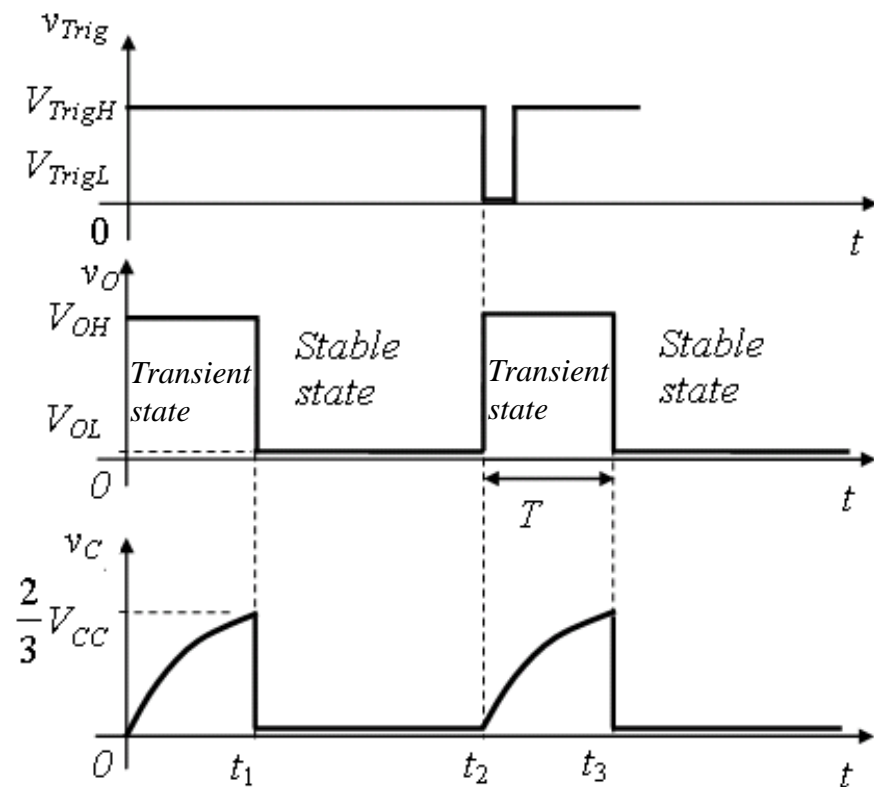V_{Trig} can come from a sensor/pushbutton



➤ Monostable multivibrator w/ LM555

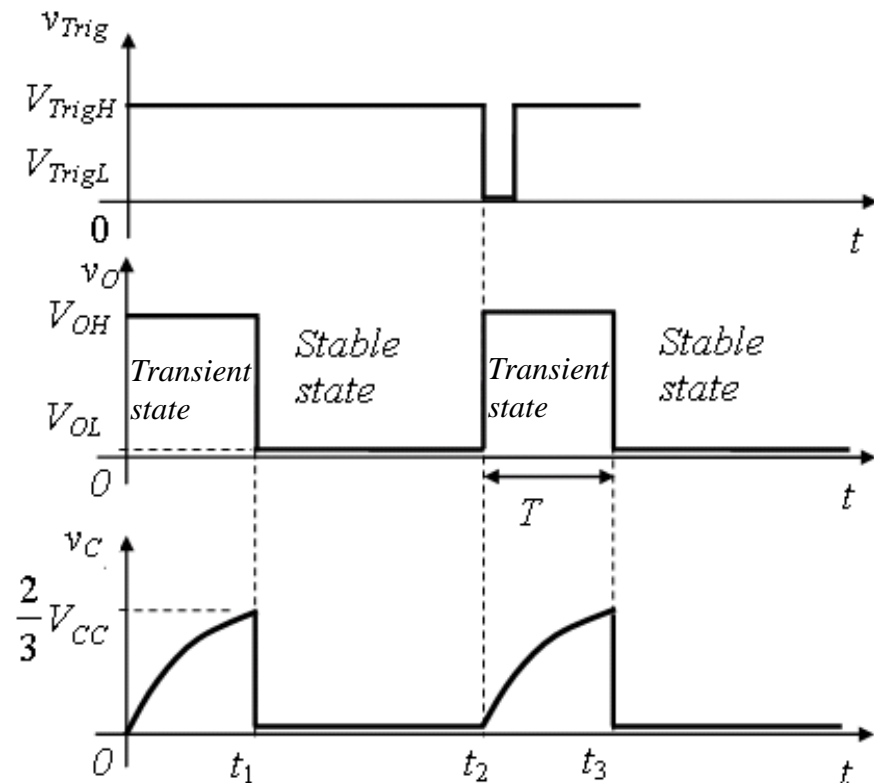V_{Trig} can come from a sensor/pushbutton



$$V_{TrigH} > \frac{1}{3}V_{CC}$$

$$V_{TrigL} < \frac{1}{3}V_{CC}$$

$$t \in (t_2, t_3) \quad \tau = RC$$

$$\frac{2}{3}V_{CC} = 0 \cdot e^{-\frac{T}{\tau}} + (1 - e^{-\frac{T}{\tau}})V_{CC}$$

$$T = RC \ln 3 = 1.1RC$$

T – timing period

➤ Rectangular and triangular signal generator w/ LM555

Thresh & Trigger receive the **same** voltage


Current I_2 **charges** C

Current I_1 **discharges** C

OpAmp – total NF, $V_+ = V_- = V_{OA}$

v_O – rectangular, 0...15 V

v_{O2} – triangular, 5...10 V

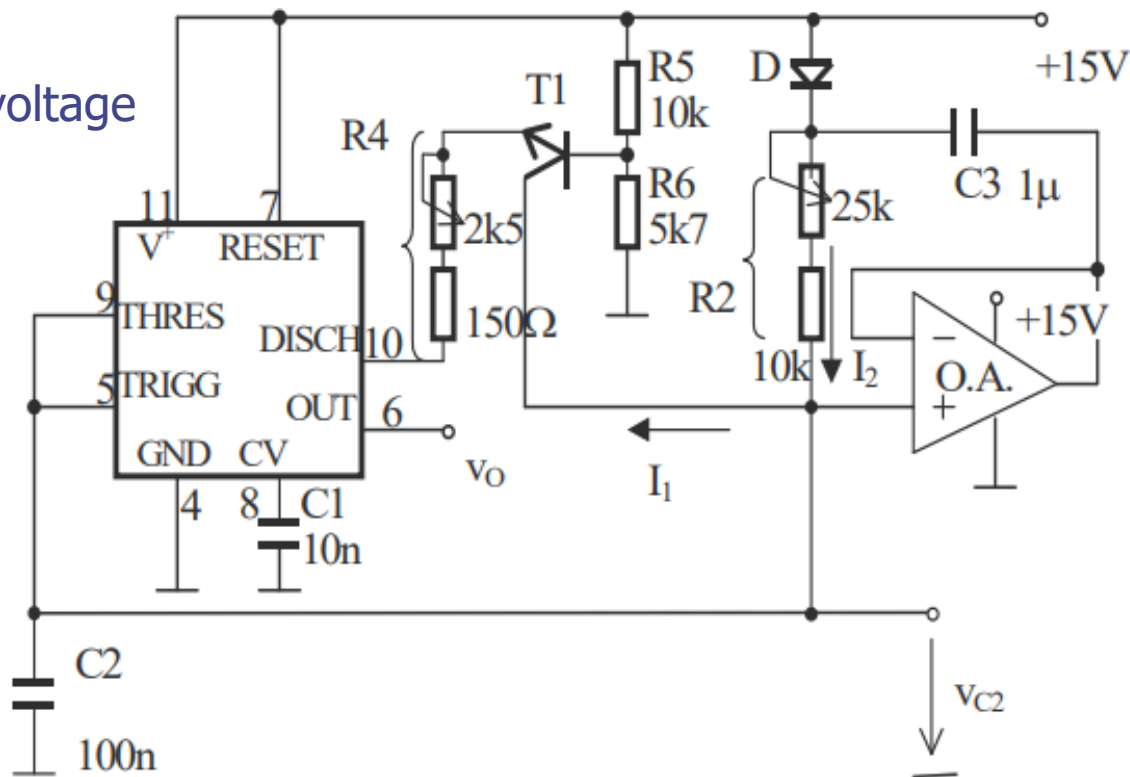

Prove that I_1 and I_2 are constant!

➤ Rectangular and triangular signal generator w/ LM555

$V_{C2} = 5\text{ V}$

D – on

C_3 – charges

$V_{C3} = (14.3 - 5)\text{ V} = 9.3\text{ V}$

V_{C2} – increases up to 10 V


C_3 – stays charged

D – turns off

$V_{C3} = 9.3\text{ V}$

$V_{R2} = V_{C3} = 9.3\text{ V}$

$I_2 = 9.3/R_2 = \text{constant}$

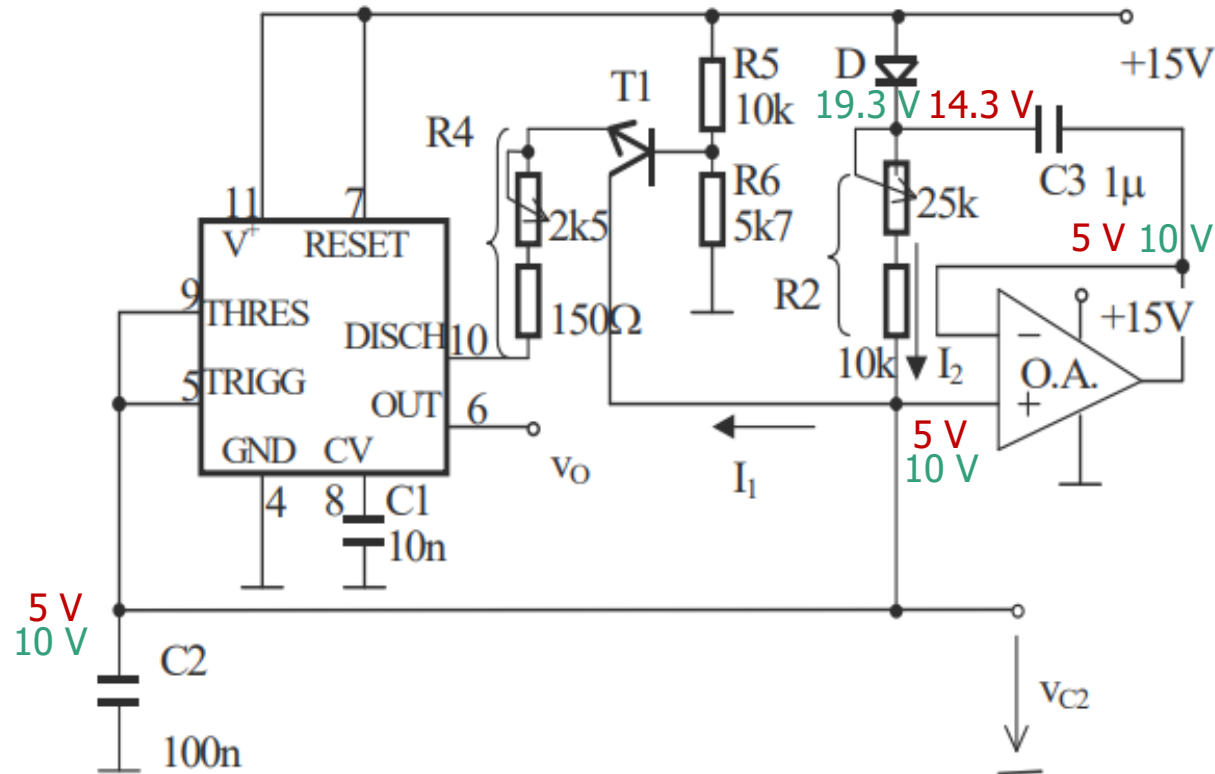


➤ Rectangular and triangular signal generator w/ LM555



$$V_{R6} = \frac{R_6}{R_5 + R_6} \cdot 15$$

$$I_1 = \frac{V_{R6} - V_{BE,on}}{R_4} = \frac{V_{R6} - 0.7}{R_4}$$

$$I_1 = \text{constant}$$

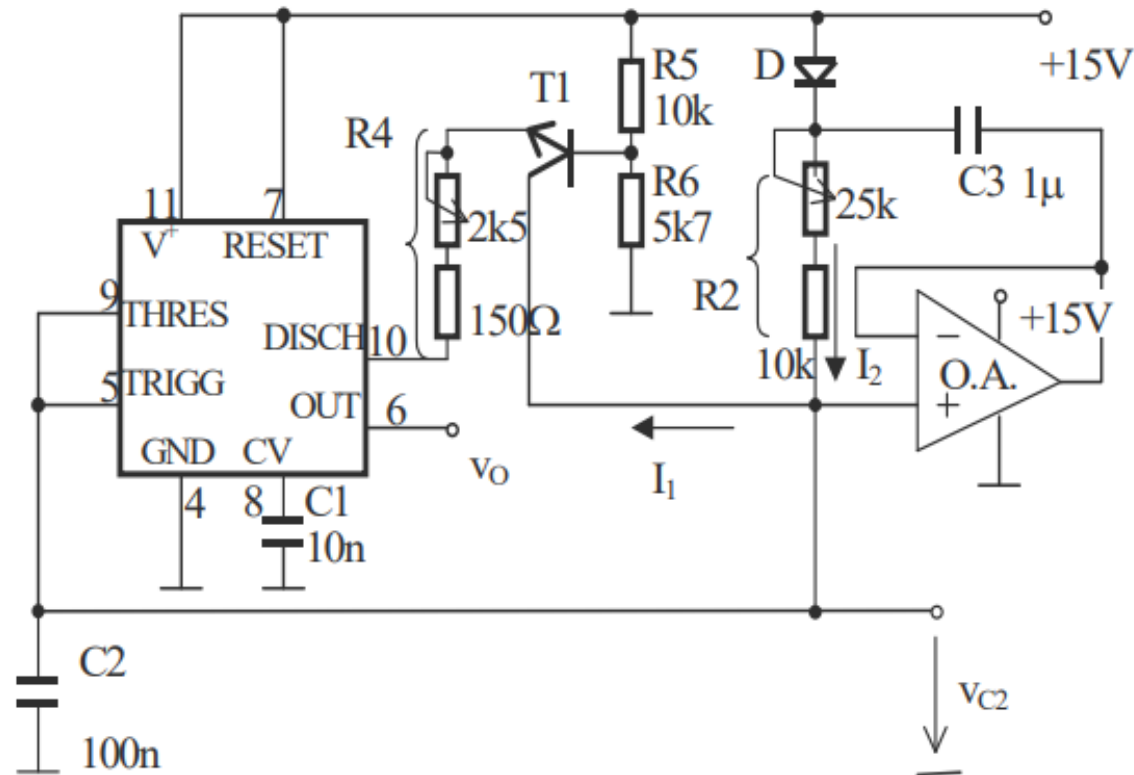

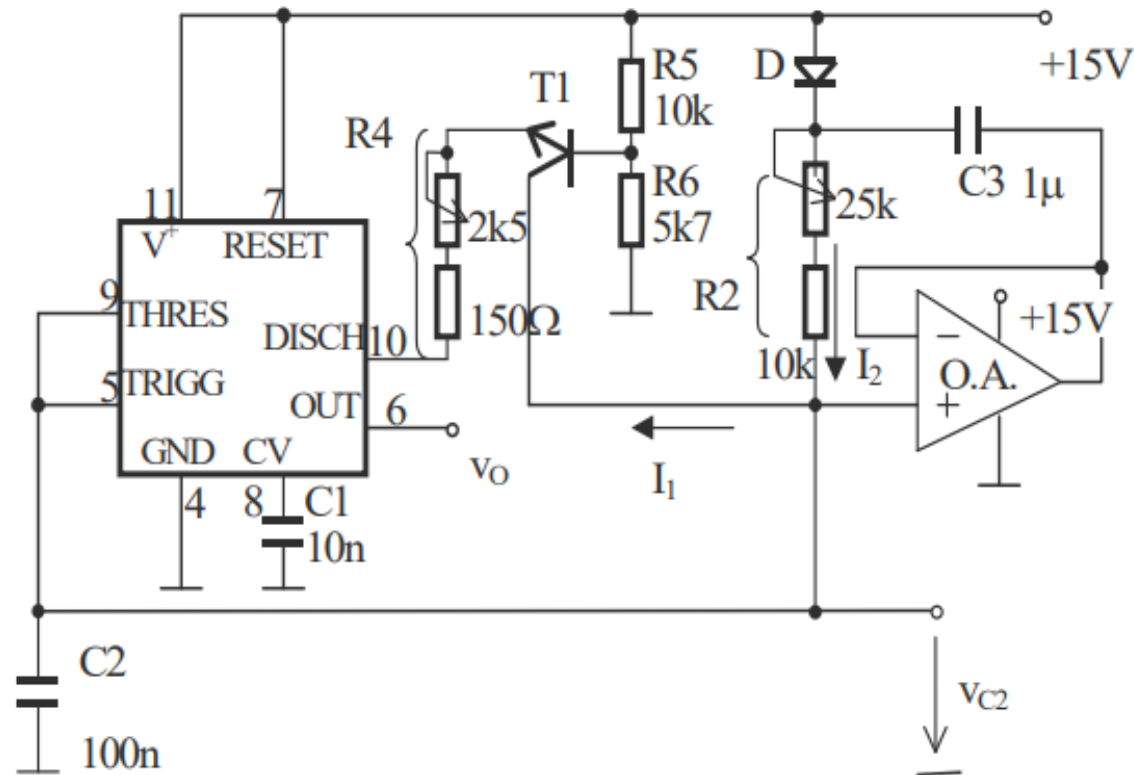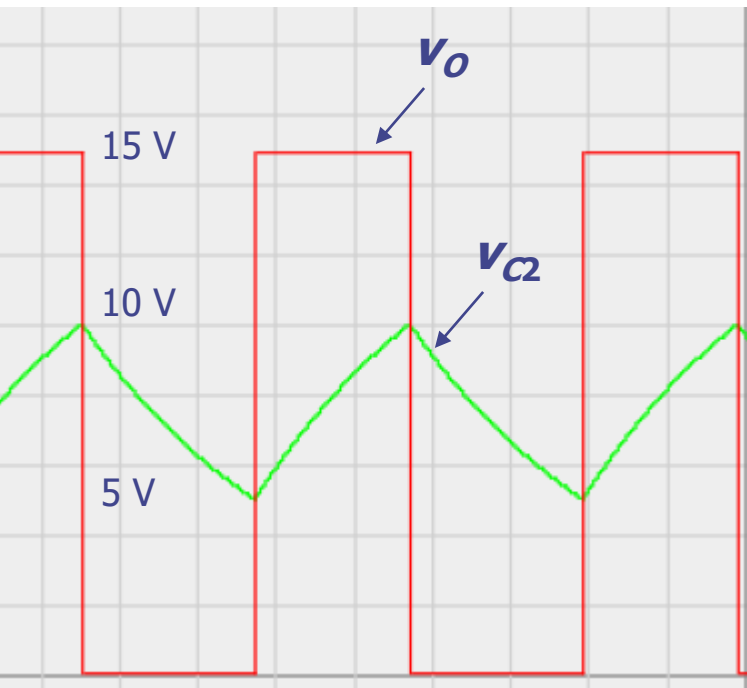➤ Rectangular and triangular signal generator w/ LM555



$$I_2 = 9.3/R_2 \text{ - charging}$$


$$I_1 = \frac{V_{R6}-0.7}{R_4} \text{ - discharging}$$

R_2 and R_4 - adjustable duty cycle

➤ Power amplifiers - revisited

Power amplifier = a circuit which provides little or no voltage gain, but **significant** current gain

= large signal or output amplifier

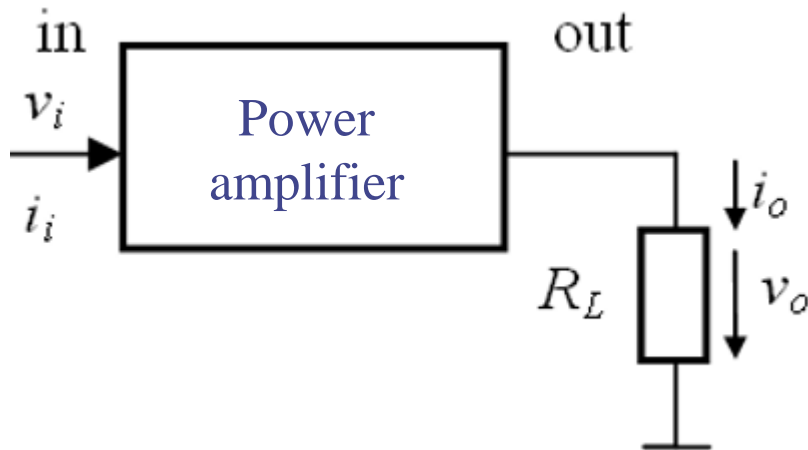

$$v_o \approx v_i \quad A_v \approx 1$$


$$i_o > i_i \quad A_i > 1$$

$$p_o = v_o \cdot i_o$$

$$p_i = v_i \cdot i_i$$

$$p_o > p_i$$

➤ Power amplifiers - revisited

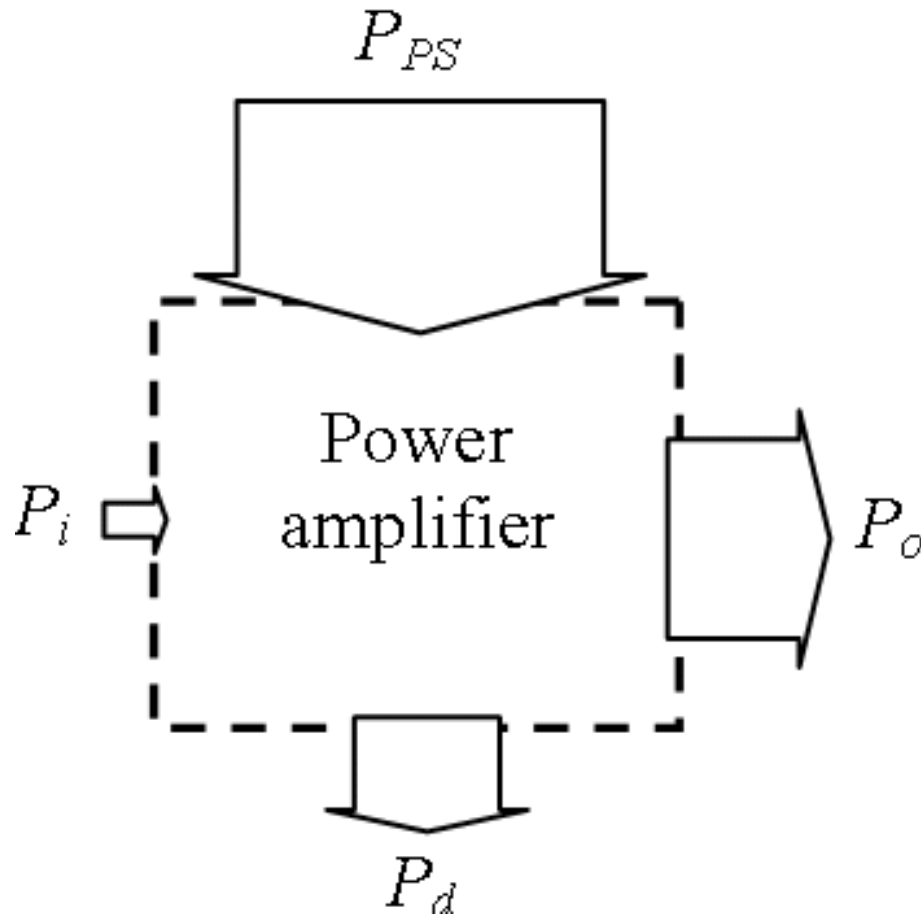

$$P_i + P_{PS} = P_d + P_o$$

P_i - power from the input source

P_{PS} - power drawn from the power supplies

P_d - dissipated power (heat)

P_o - power delivered at the output (on R_L)

$$P_i \ll P_{PS}$$

$$\eta = \frac{P_o}{P_{PS}}$$

efficiency of the stage

η [%] or $\eta \in (0, 1)$


➤ Power amplifiers - revisited

The classes are defined in relation to the interval of time in which the amplifier device (transistor) is **active**, expressed as a **fraction of the period** of the input signal.

Classes: A, B, AB, C, D, E, F, G, I, S, T, etc

efficiency of the stage

$$\eta = \frac{P_o}{P_{PS}}$$

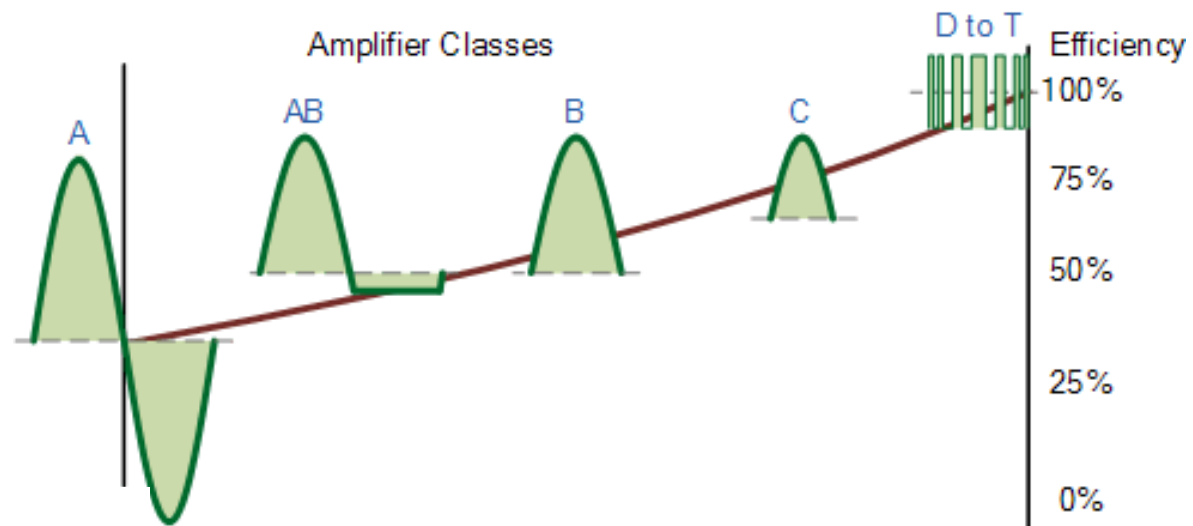

The less time T is active during a period, the higher the efficiency

➤ Power amplifiers - revisited

Class	Conduction interval	Max. efficiency	Notes
A	$t_c = T$	25%	Small-signal amplifiers
B	$t_c = T/2$	78.5%	Audio amplifiers; crossover distortions
AB	$T/2 < t_c < T$	78.5%	Audio amplifiers; no crossover distortions
C	$t_c < T/2$	90%	RF transmitters
D	switching mode	80%-95%	PWM and passive filtering
E	switching mode	90%	RF transmitters
G	more efficient version of class AB		
H	similar to class G	100%	Power supply modulated by the signal
I	similar to class B, switching mode		Interleaved PWM amplifier
S, T	similar to class D, switching mode		

➤ Class D power amplifier - intro

- **switching amplifier** based on pulse-width modulation (**PWM**) techniques


Purpose: high efficiency 80% - 95%

The reduction of the power dissipated by the amplifying transistors is due to the **switching** operation mode.

- **increase** in efficiency and **reduction** of the physical dimensions of the heatsink

Usage: portable equipment, battery operated equipment, equipment with space constraints, etc.

➤ Block diagram & operating principle

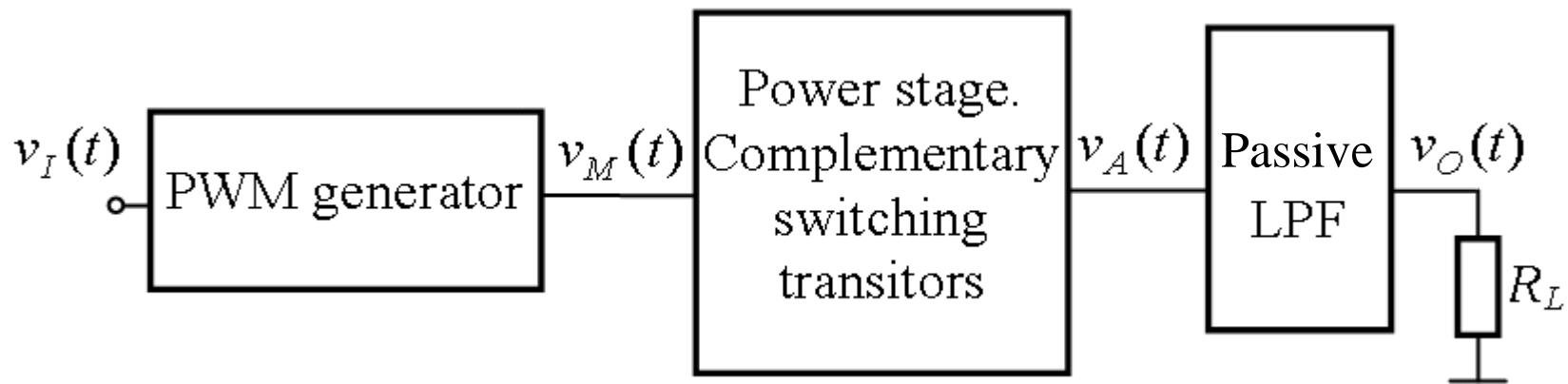

The input signal v_I is converted into a pulse-width-modulated (PWM) signal v_M with a much higher frequency (switching frequency).




v_M has a **constant period** but **variable duty-cycle**, modulated by the instantaneous value of the input signal.

Reconstruction of the useful signal

LP filtering: the **fundamental frequency** is extracted from the amplified PWM signal v_A while the **switching frequency** and **superior harmonics** and components are **removed**.

➤ PWM generator


frequency of $v_T \gg$ frequency of v_I

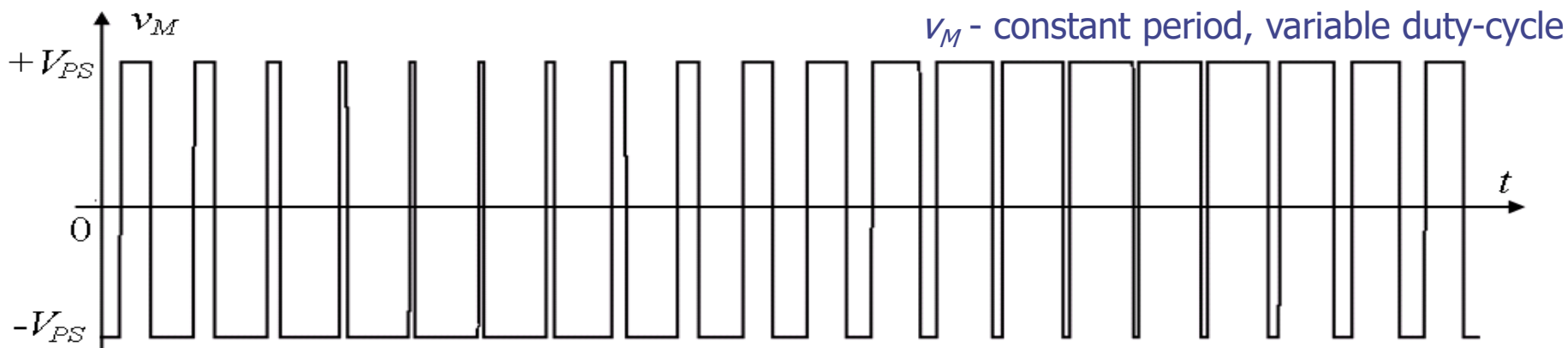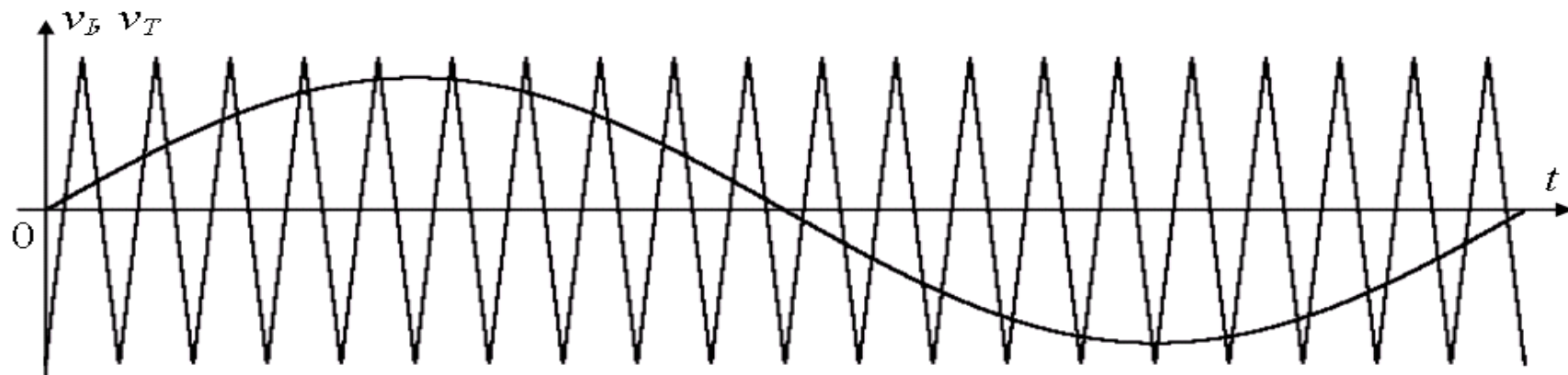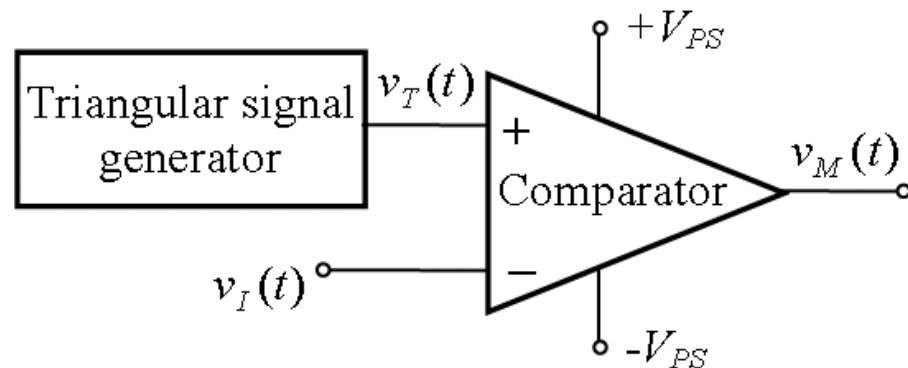

➤ Power stage + LPF

Each transistor commutation happens in a finite time.

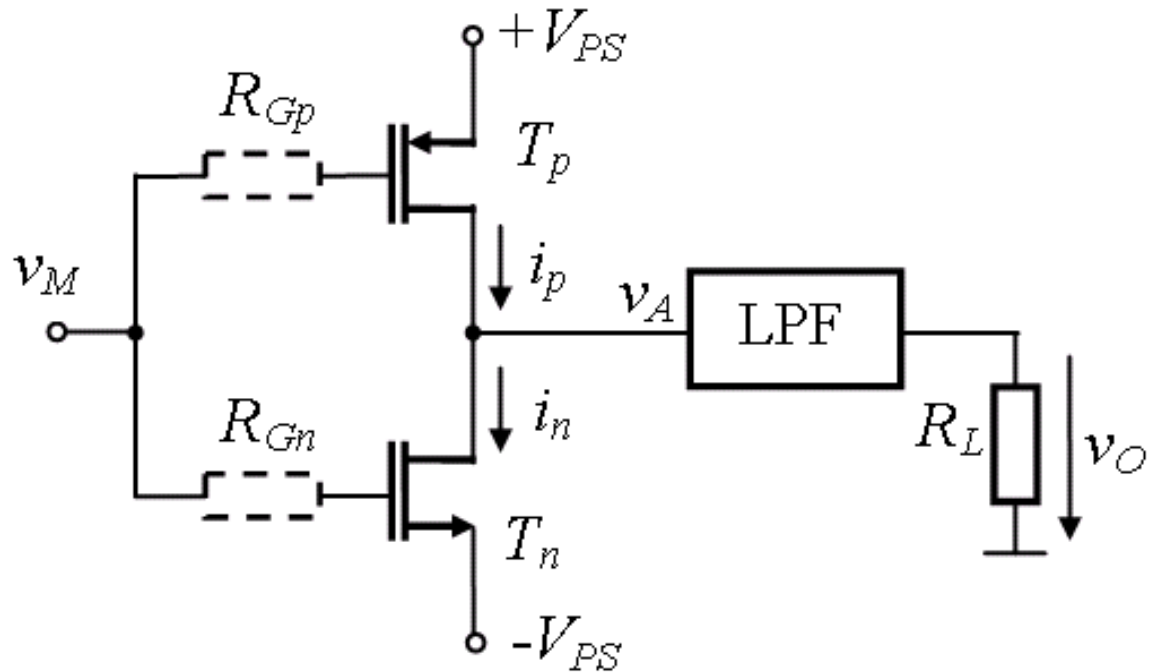During the commutation, there is a (small) power dissipation across the transistors.





$$v_{M_L} = -V_{PS} \quad T_p(\text{on}), T_n(\text{off}) \quad v_A = +V_{PS}$$

$$v_{M_H} = +V_{PS} \quad T_p(\text{off}), T_n(\text{on}) \quad v_A = -V_{PS}$$

At the frequencies of the input signal, the equivalent LPF impedance should be sufficiently low (zero).

Inverting current amplifier (MOSFET logic inverter)

➤ Power stage + LPF - problem

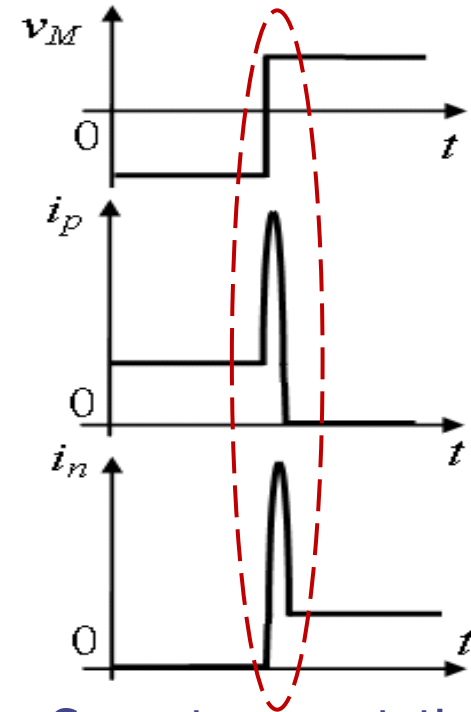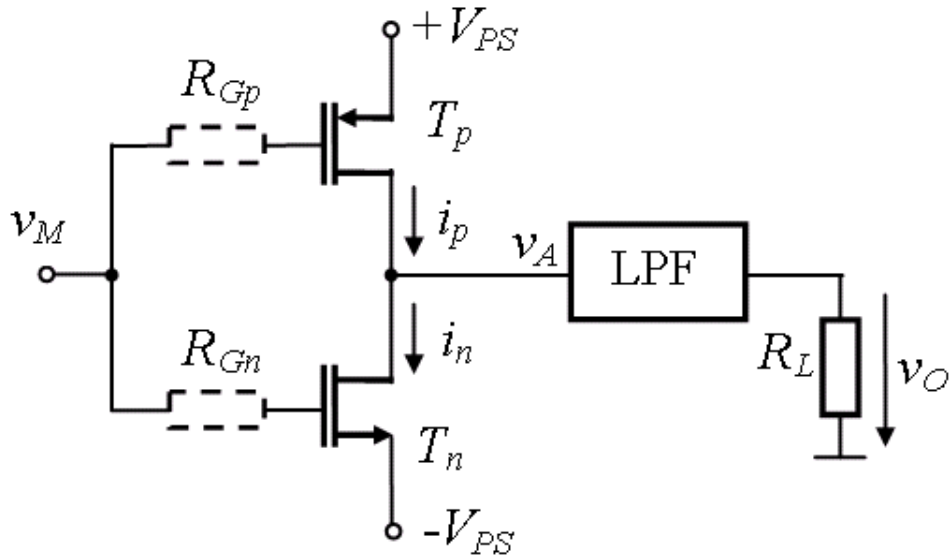

Current commutation for


T_p : (on) \rightarrow (off)

T_n : (off) \rightarrow (on)


- the conducting transistor can not be turned off instantly
- there is a time interval when **both transistors** are **on**, resulting in a **high current pulse** between supplies, through the transistors
- can lead to transistor failure

Solution?

➤ Power stage + LPF - solution

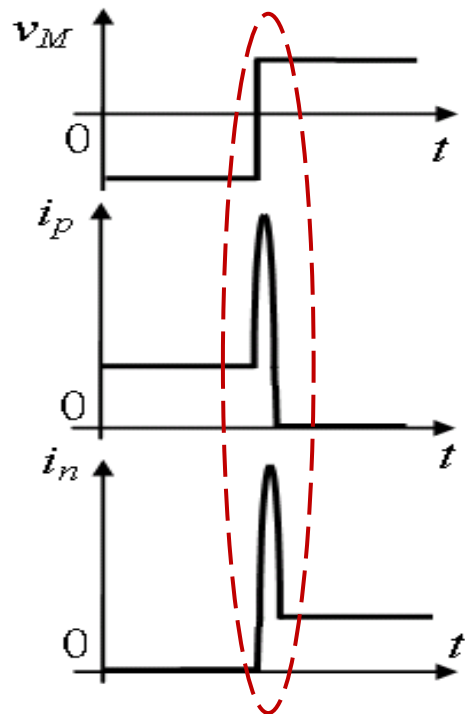

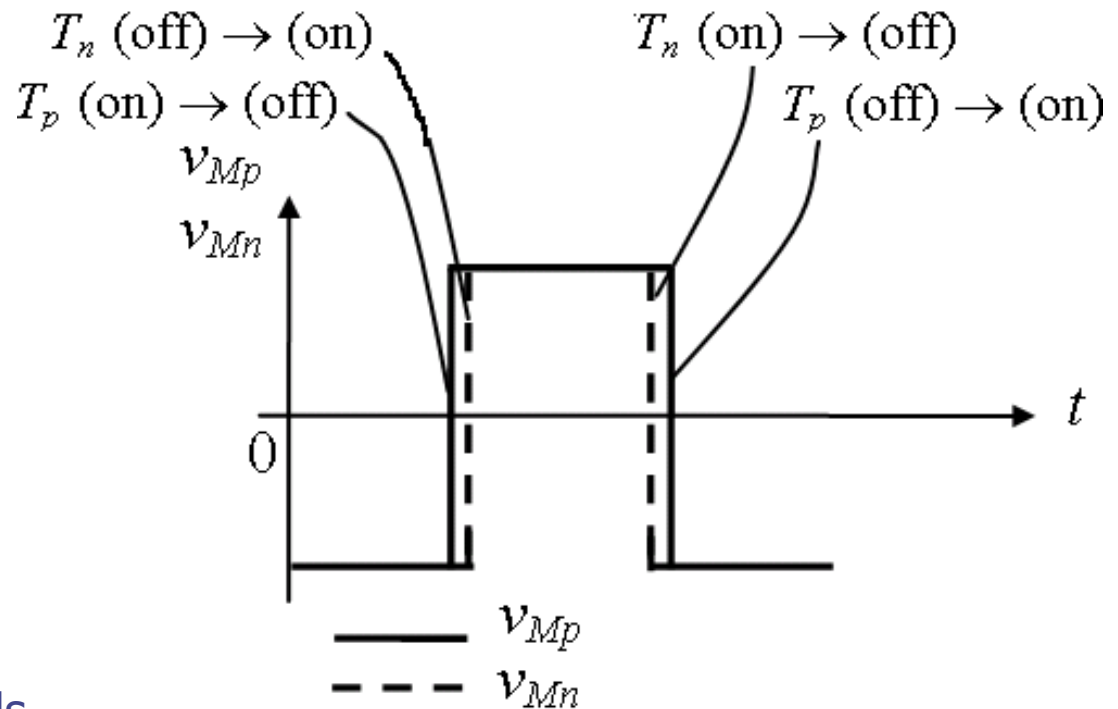The control signal for (off)->(on) must be delayed in comparison with the control signal for (on)->(off)




Control of the transistors using different (delayed) control signals

➤ Passive LPF - necessity

The frequency spectrum of the pulse-width-modulated signal contains input signal frequency (f_i), switching frequency (f_T), and harmonics:
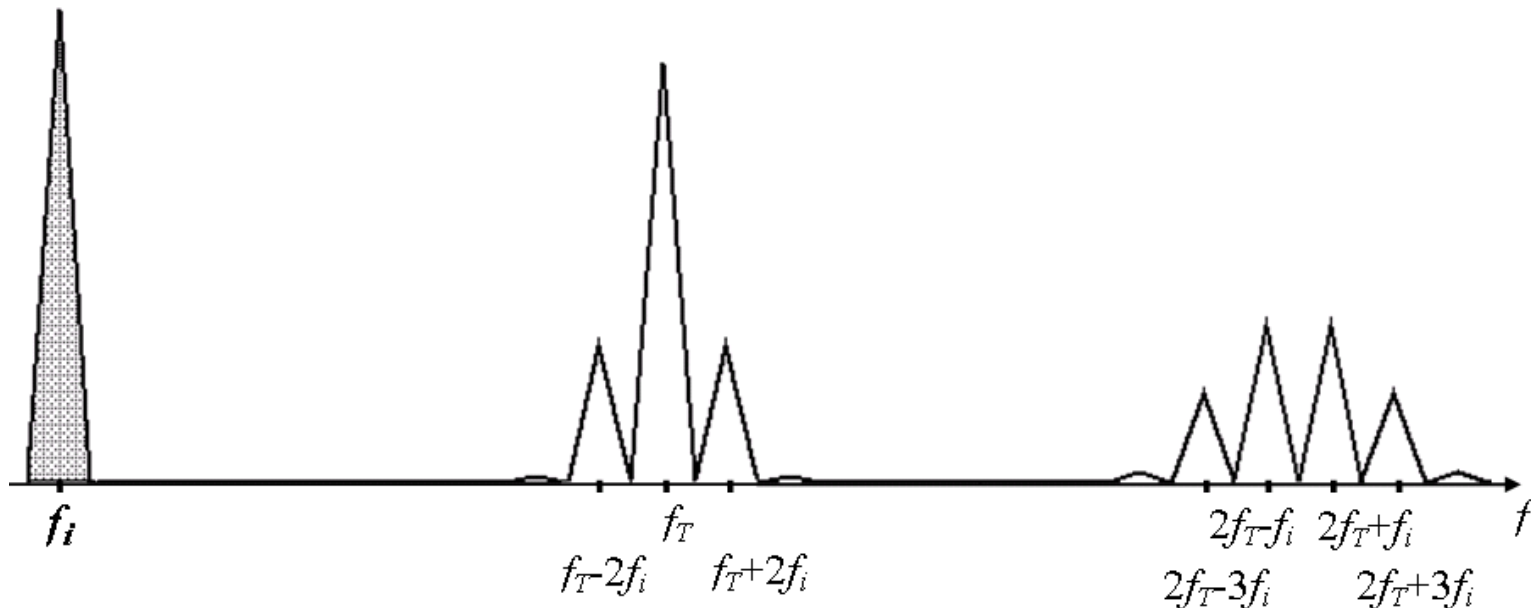
$$f_i, f_T, f_T \pm 2f_i, 2f_T \pm f_i, 2f_T \pm 3f_i$$



The LPF gets rid of any frequency above f_i allowing the **reconstruction** (demodulation) of the input signal.

➤ Passive LPF - circuit


$$F(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = \frac{1}{1 + j\omega LC \frac{1}{R_L C} + (j\omega)^2 LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 R_L C$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
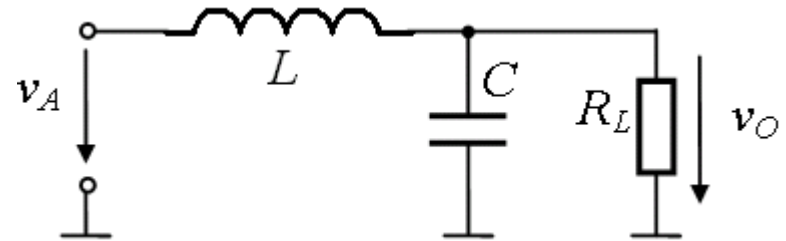
$$F(j\omega) = \frac{1}{1 + j \frac{\omega}{\omega_0} \frac{1}{Q} + \left(j \frac{\omega}{\omega_0}\right)^2}$$



single stage, second order LC filter


The filter should highly attenuate f_T

$$f_0 < (1/10)f_T \text{ - for at least 40dB attenuation at } f_T$$


Switching frequency should be **at least 10 times greater** than the maximum signal frequency.

$Q=0.707$ provides a frequency response that introduces -3dB at corner frequency.

➤ Class D amplifier – complete circuit

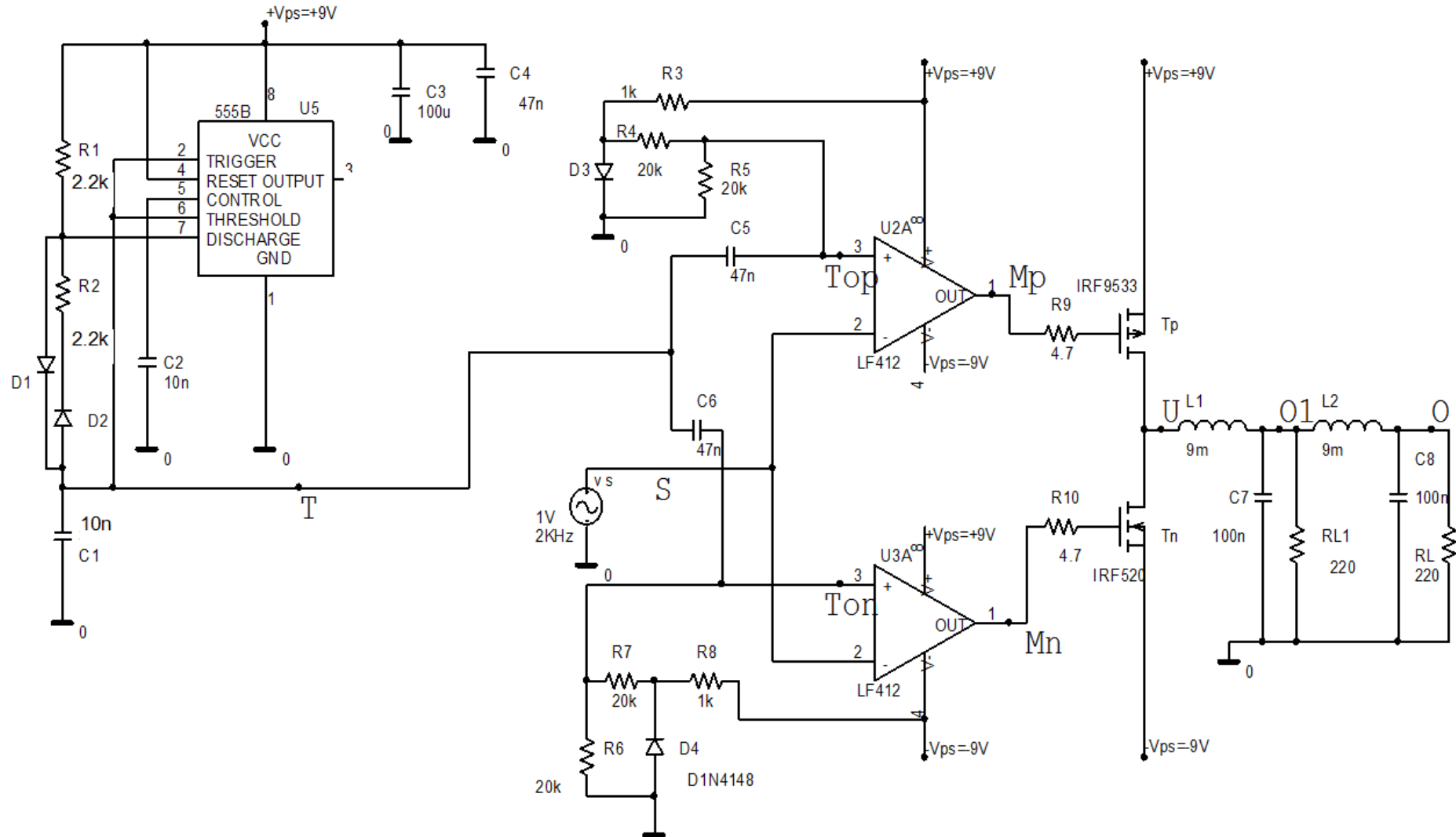


➤ Class D amplifier – complete circuit

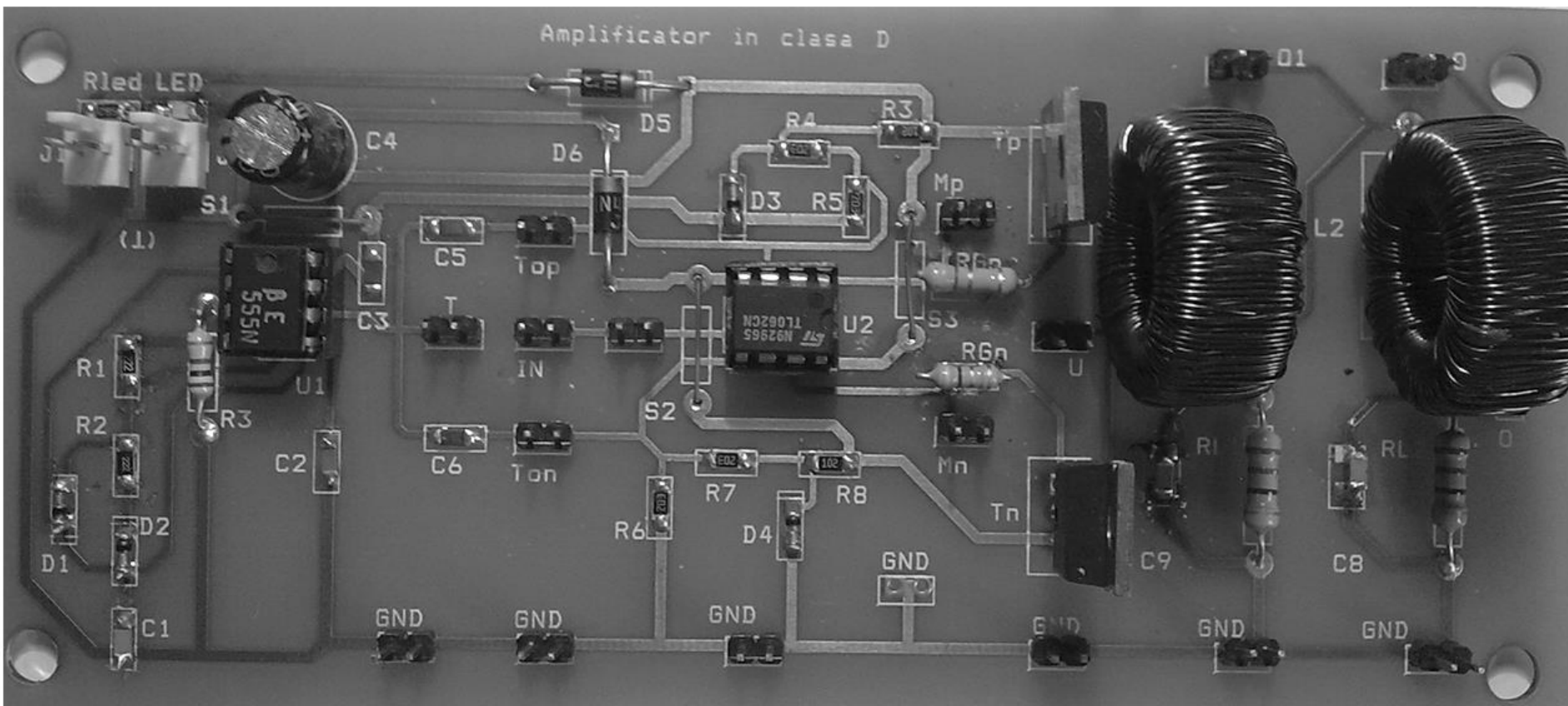

➤ Class D amplifier – specialized integrated circuits

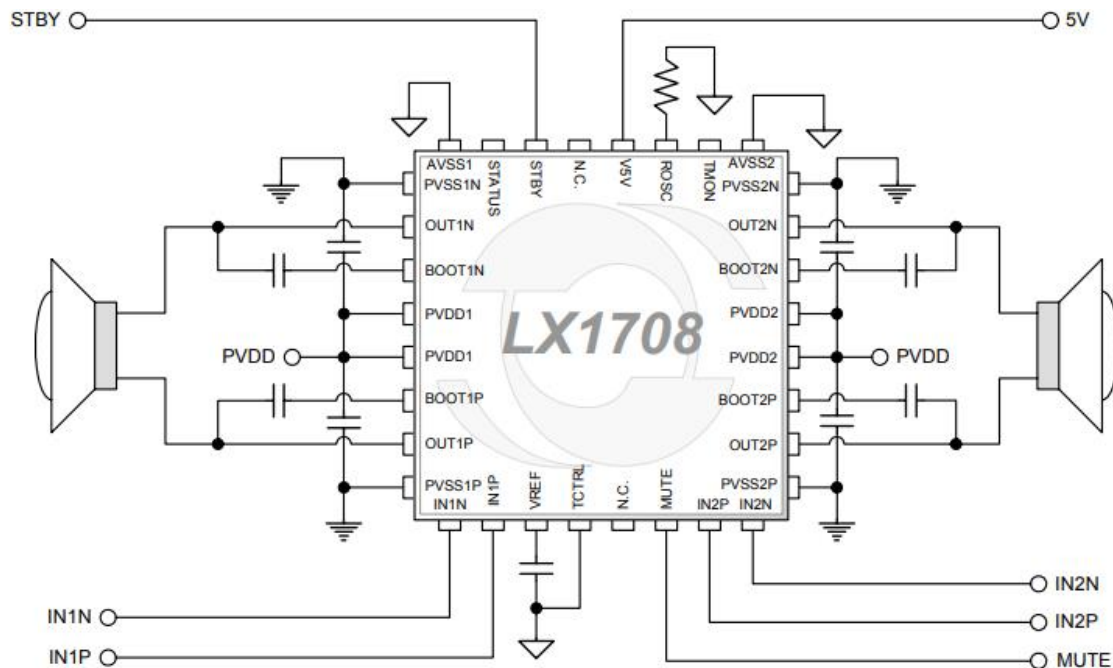- LX1721/1722: Class-D Stereo Power Amplifier Controller
- LX1725 : 15W X 2 30W BTL CLASS-D AUDIO AMPLIFIER
- LX1708: 15W+15W Stereo Filterless Class D Amplifier



Summary

- Intro
- 555 Timer
- Class D amplifier

Next week: Recap. Preparation for the exam.