

FUNDAMENTAL ELECTRONIC CIRCUITS


Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C4 – BJT basic amplifiers

Contents

- BJT small-signal model
- BJT basic amplifiers
- Comparison and analysis

➤ Small-signal motivation - revisited

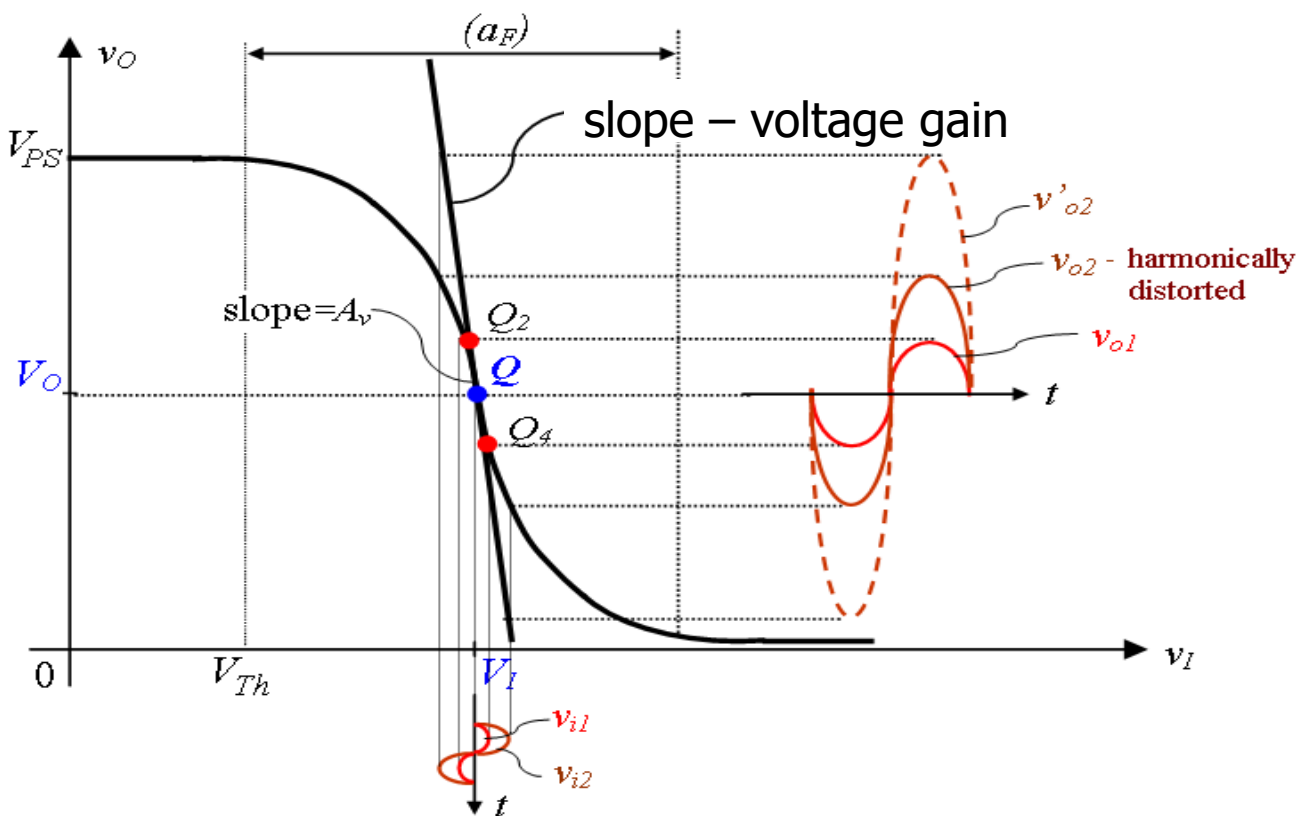


**Small-signal model
(linear model)**
needed to compute

Voltage gain: $A_v = \frac{v_o}{v_i}$

Small-signal model is valid in the **narrow linear region around Q** .

➤ Small-signal operation - intro

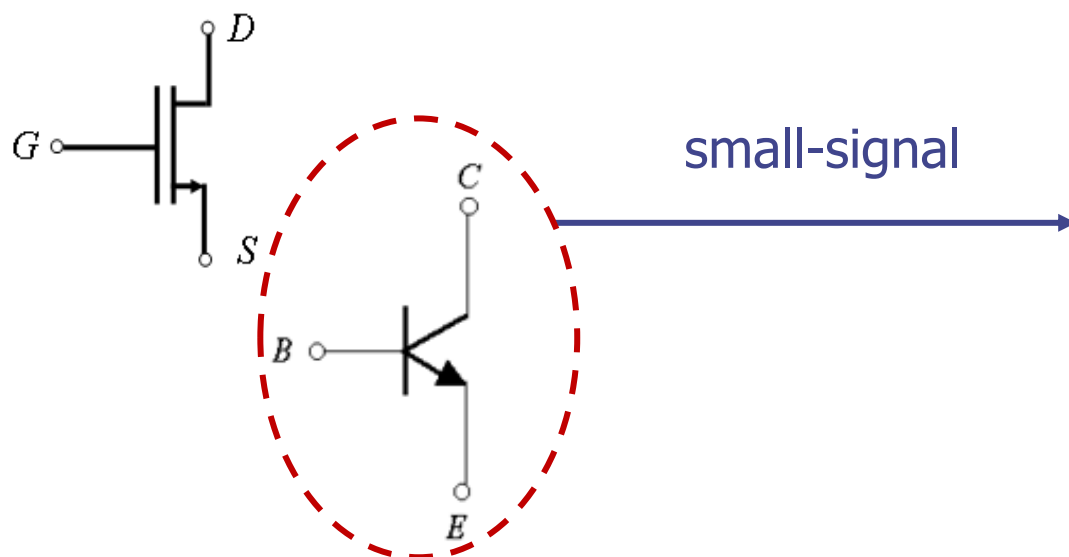

Some components

Some connections


Some parameters

small-signal model of T

Hints:

- keep names of terminals
- use voltage-controlled current source
- values of parameters are computed in $Q(V_{DS}; I_D)$ or $Q(V_{CE}; I_C)$

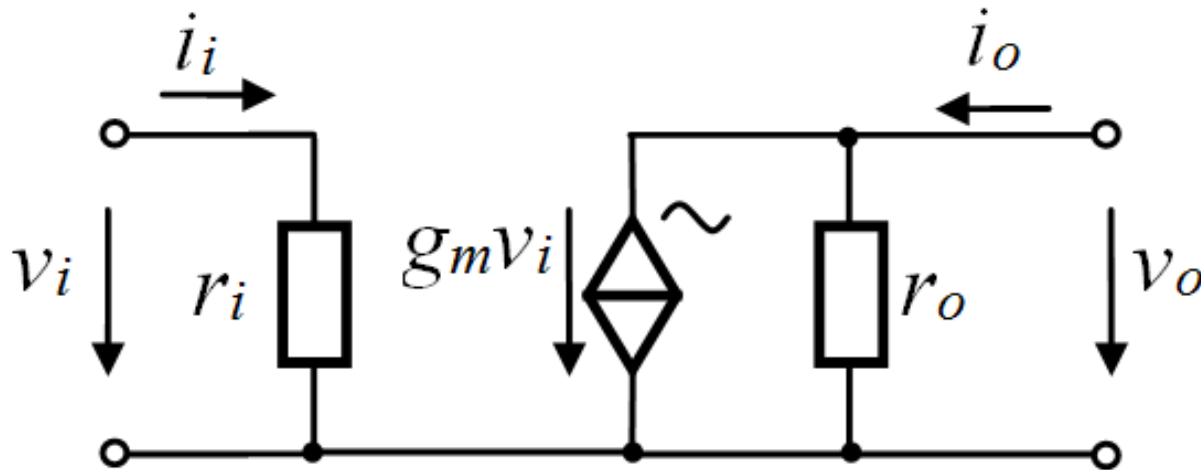
➤ Small-signal model – low & medium frequency



• two-port network

- ✓ input resistance: r_i
- ✓ transfer: voltage-controlled current source: $g_m v_i$
- ✓ output resistance: r_o

- Small-signal model – high frequency

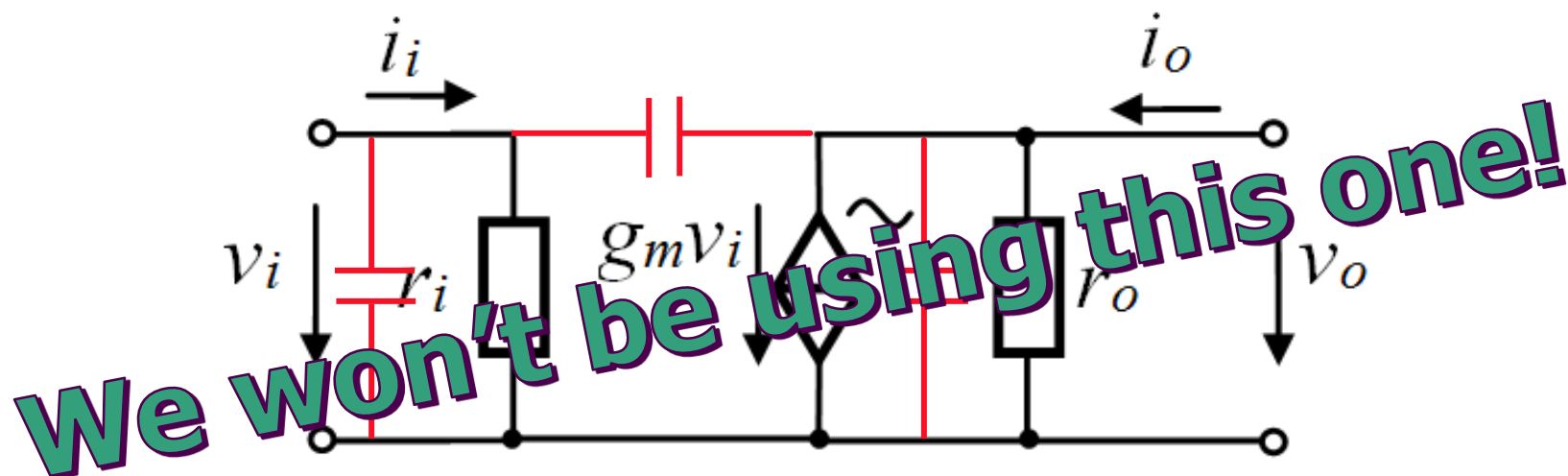


- two-port network

- ✓ r_i
- ✓ $g_m v_i$
- ✓ r_o


+ parasitic capacitances between terminals

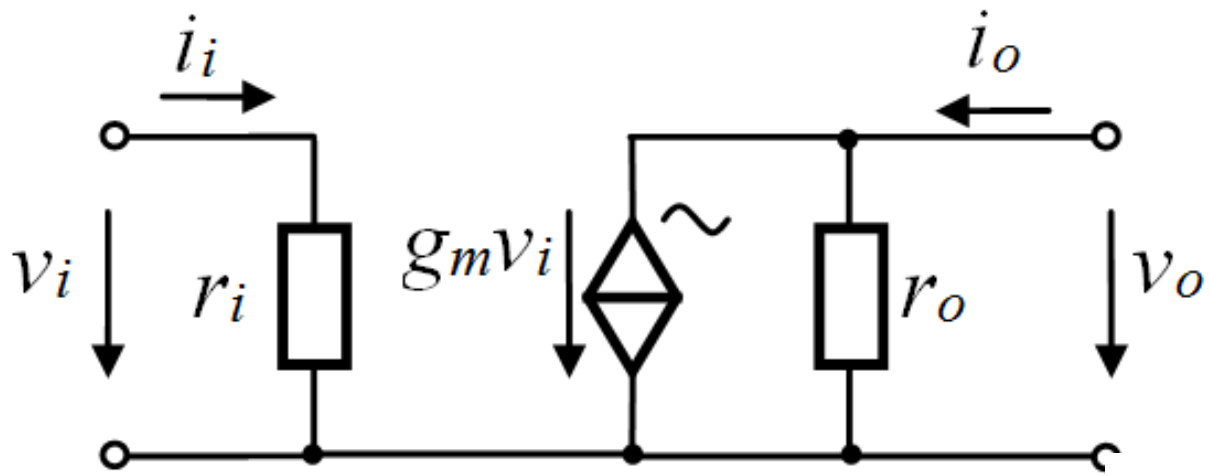➤ Small-signal model – low & medium frequency



Custom model for BJT?

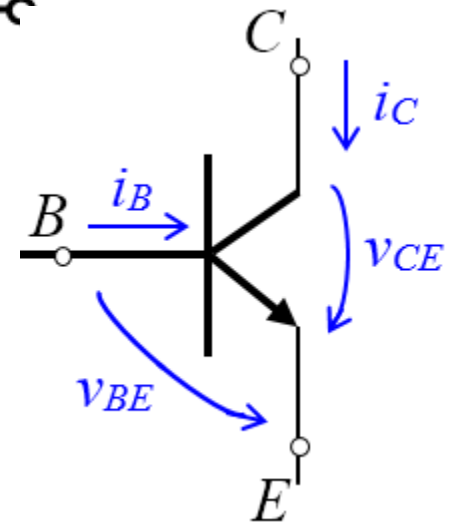- ✓ $r_i = ?$
- ✓ $g_m = ?, v_i = ?$
- ✓ $r_o = ?$



➤ Small-signal parameters

Input resistance r_i


$$r_i = r_{be} = \left. \frac{\partial v_{BE}}{\partial i_B} \right|_{v_{CE} = cst} = \left. \frac{v_{be}}{i_b} \right|_{v_{CE} = cst}$$

$\frac{\partial v_{BE}}{\partial i_B}$ - derivative of v_{BE} with respect to i_B

Major difference from MOSFET: $i_B \neq 0$

$$r_{be} = \frac{\beta}{g_m}$$

Who are β and g_m ?

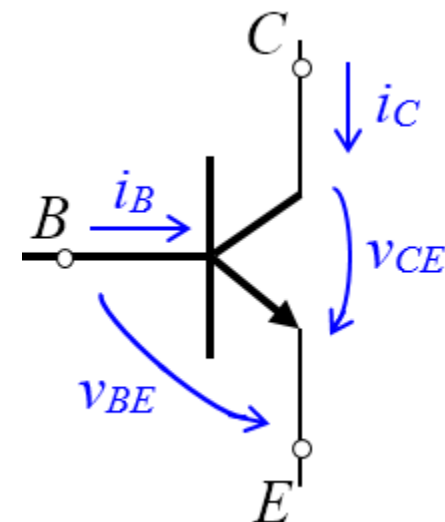

➤ Small-signal parameters

Transconductance g_m

- shows the transfer from variable input voltage v_{BE} to variable output current i_c

$$g_m = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_{v_{CE} = cst} = \left. \frac{i_c}{v_{be}} \right|_{v_{CE} = cst}$$

$$i_c \approx I_S e^{\frac{v_{BE}}{V_T}}$$

I_S - saturation current \sim nA – pA

V_T - thermal voltage, \approx 25 mV@20°C

$$g_m = \frac{I_C}{V_T} \approx 40 I_C \quad @20^\circ\text{C}$$

g_m – [mS] for I_C – [mA]


$$V_T = \frac{KT}{q}$$

K - Boltzmann's constant

q - elementary charge (electric charge carried by a single electron)

T - absolute temperature measured in K

Temperature ↗ g_m ↘

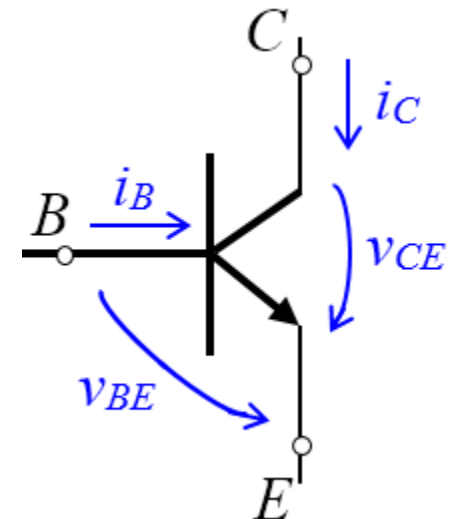

➤ Small-signal parameters

Current gain β


- shows the transfer from variable input current i_B to variable output current i_C

$$\beta = \left. \frac{\partial i_C}{\partial i_B} \right|_{v_{CE} = cst} = \left. \frac{i_C}{i_b} \right|_{v_{CE} = cst}$$

$\beta = 100$ - common value for BJTs

Note: there are **some differences** between the dc current gain and the small-signal current gain

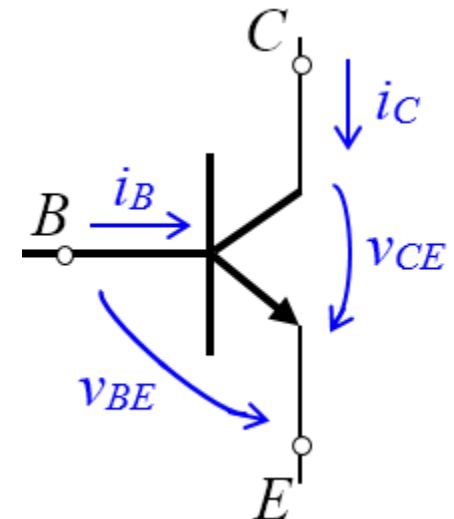For simplicity, we're assuming $\beta = 100$ for both dc and small-signal analysis.



➤ Small-signal parameters

Output resistance r_o

$$r_o = r_{ce} = \frac{1}{g_o} = \frac{\partial v_{CE}}{\partial i_C} \Big|_{v_{BE} = cst} = \frac{v_{ce}}{i_c} \Big|_{v_{BE} = cst}$$

$$r_{ce} = \frac{V_A}{I_C}$$

$$i_C = I_S e^{\frac{v_{BE}}{V_T}} \left(1 + \frac{v_{CE}}{V_A} \right)$$


V_A – Early voltage

$V_A = 100$ V for npn BJT

$V_A = 50$ V for pnp BJT

I_S - saturation current \sim nA – pA
 V_T - thermal voltage, ≈ 25 mV@20°C

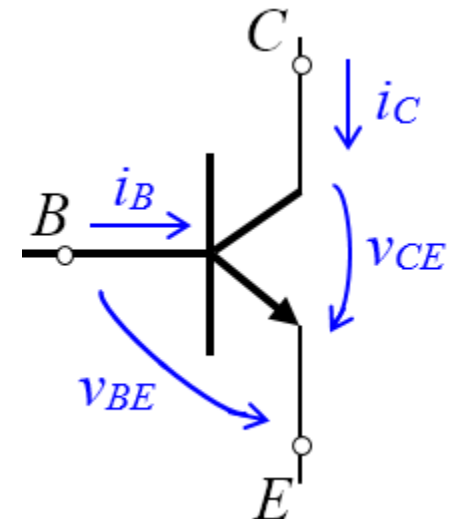$\frac{\partial v_{CE}}{\partial i_C}$ - derivative of v_{CE} with respect to i_C





➤ Small-signal model & parameters - summary

$$r_i = r_{be} = \frac{\beta}{g_m} \quad g_m = 40I_C \quad r_o = r_{ce} = \frac{V_A}{I_C} \quad i_c = g_m v_{be} = 40I_C v_{be}$$

hybrid- π models

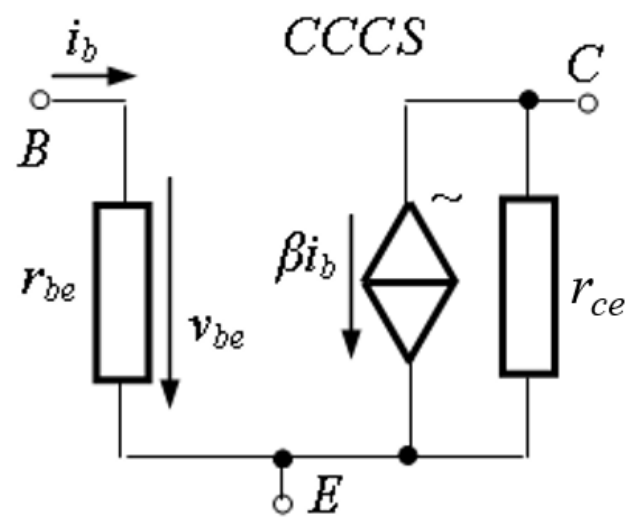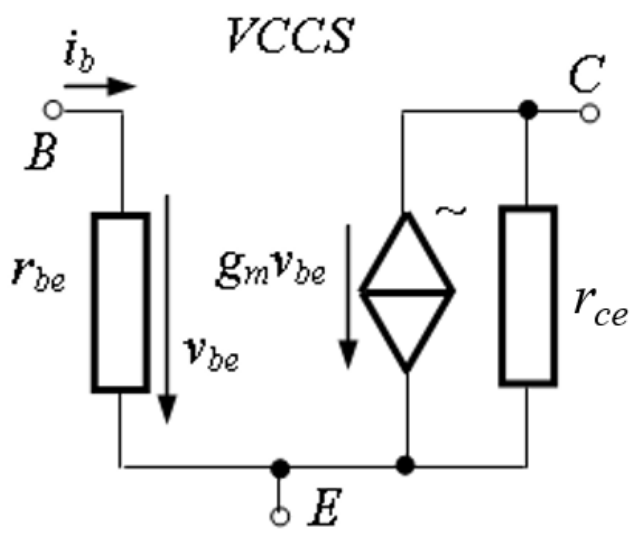VCCS – voltage-controlled current source
 CCCS – current-controlled current source





Valid for low & medium frequency

➤ Small-signal model & parameters - **summary**

$$r_i = r_{be} = \frac{\beta}{g_m} \quad g_m = 40I_C \quad r_o = r_{ce} = \frac{V_A}{I_C} \quad i_c = g_m v_{be} = 40I_C v_{be}$$

simplified *hybrid-π* models - $r_{ce} = \infty$

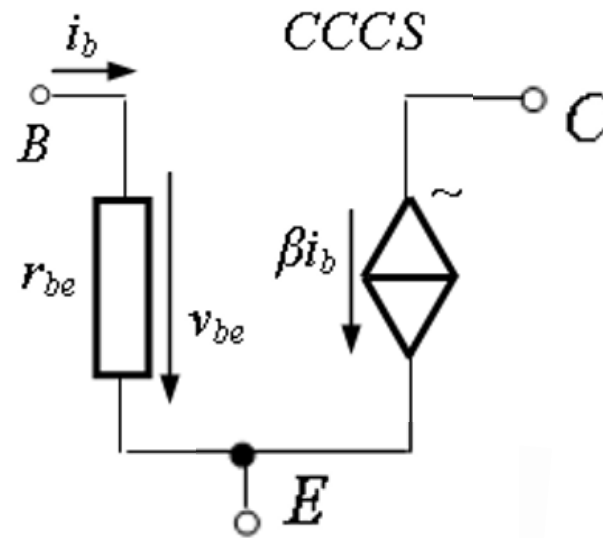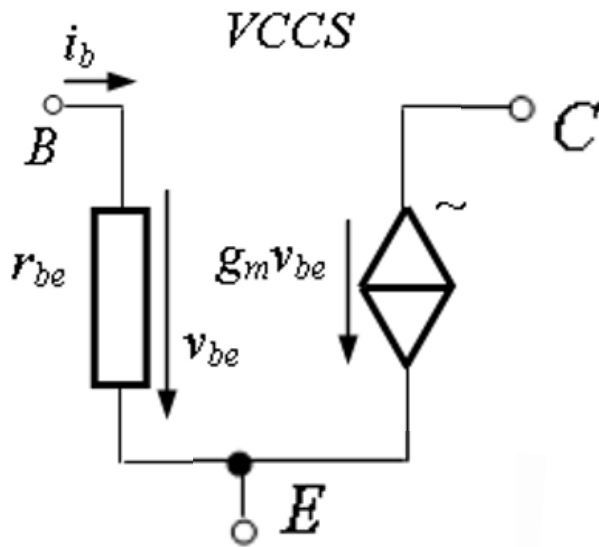VCCS – voltage-controlled current source
 CCCS – current-controlled current source




Valid for low & medium frequency

➤ Small-signal model & parameters - summary

$$r_i = r_{be} = \frac{\beta}{g_m} \quad g_m = 40I_C \quad r_o = r_{ce} = \frac{V_A}{I_C} \quad i_c = g_m v_{be} = 40I_C v_{be}$$

hybrid- π model - high frequency

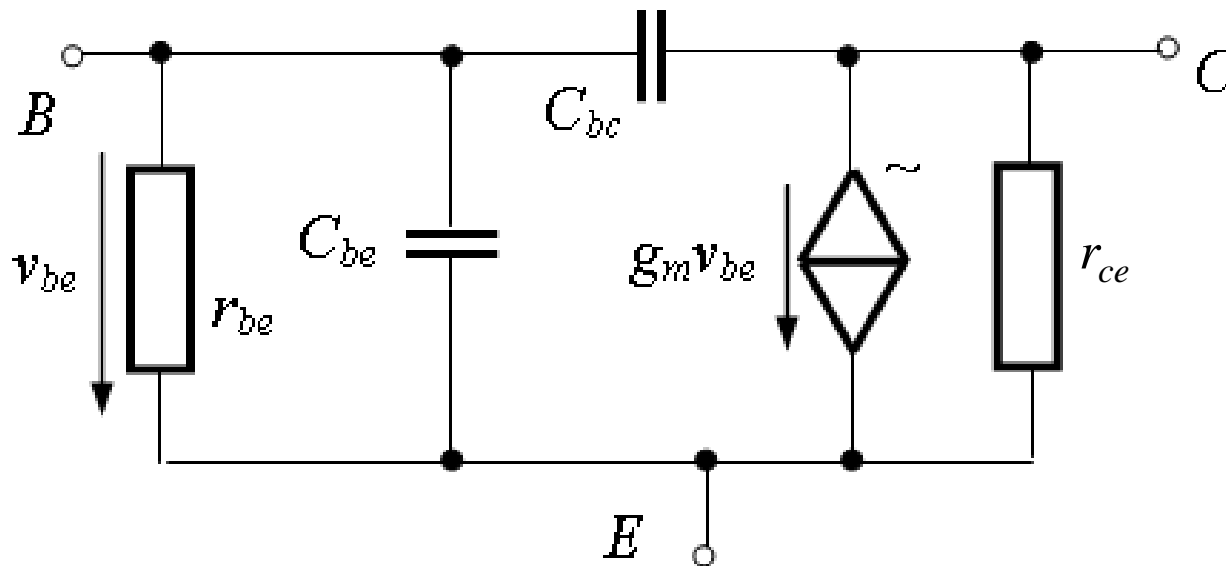

Parasitic capacitances (pF or less) between terminals **decrease** the gain at high frequencies. How/why? We'll see next week!

➤ Small-signal model & parameters - examples

Assume low & medium frequency operation




Ex. 1 $\beta = 100, V_A = 100 \text{ V}; I_C = 100 \mu\text{A}$

$$g_m = 40I_C = 4 \text{ mS} \quad r_{be} = \frac{\beta}{g_m} = 25 \text{ K}\Omega \quad r_{ce} = \frac{V_A}{I_C} = 1 \text{ M}\Omega$$

Ex. 2 $\beta = 100, V_A = 100 \text{ V}; I_C = 1 \text{ mA}$

$$g_m = 40I_C = 40 \text{ mS} \quad r_{be} = \frac{\beta}{g_m} = 2.5 \text{ K}\Omega \quad r_{ce} = \frac{V_A}{I_C} = 100 \text{ K}\Omega$$

➤ Configurations

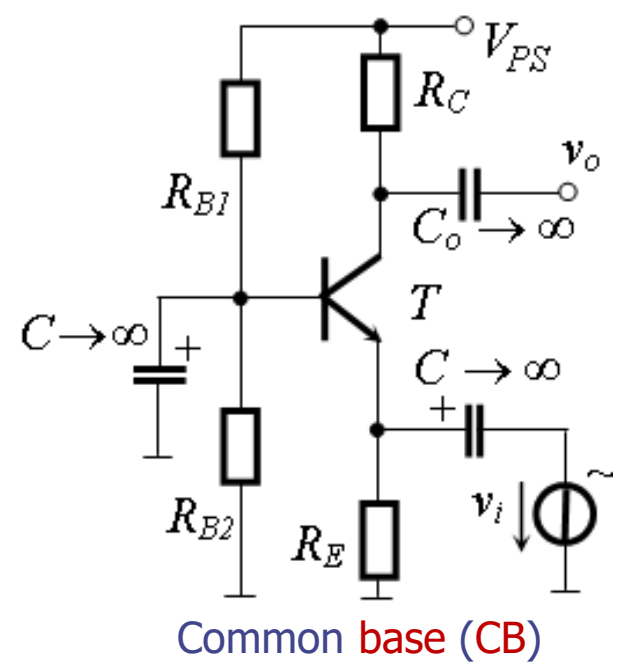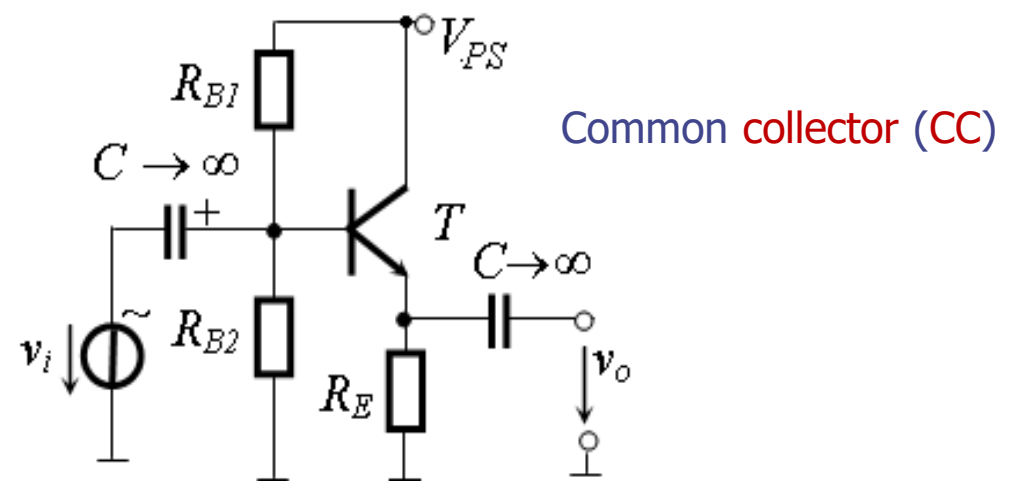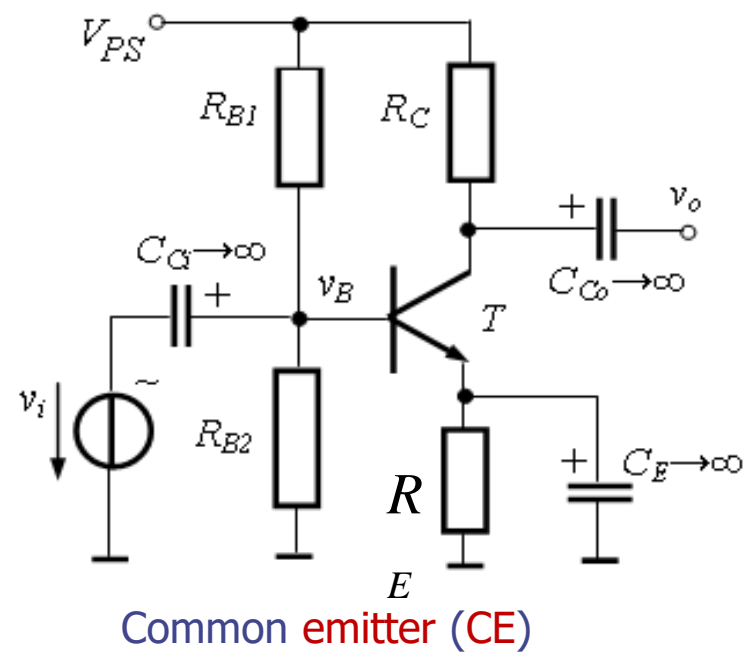

- How many possible configurations? What will they be called?
- Why are the capacitors necessary?
- How are the circuits analyzed?

➤ Configurations

- Common emitter/collector/base

The terminal that is connected to **ground** in the **small-signal equivalent schematic** gives the name of the configuration.

- Why are the capacitors necessary?

Capacitors separate the variable signals from the dc ones (at the input, output, or in other points of the circuit).

The capacitances need to be **high enough** so that they can be considered **short circuits** at the operating frequency (their equivalent impedance \ll the series/parallel resistances connected with them).

On the **dc equivalent schematic** (the one used to determine the operating point Q), the capacitors are considered **open circuits**.

- How are the circuits analyzed?

See next slide(s)

➤ Transistor amplifier analysis - steps

Start with full amplifier circuit (transistor, resistors, capacitors, dc sources, ac sources)

1. Draw dc equivalent circuit

- compute the operating point $Q(V_{CE}; I_C)$
- determine dc potentials in the three terminals of the transistor
- compute small-signal parameters of the transistor: g_m r_{be} r_{ce}

C – open-circuit

2. Draw small-signal equivalent circuit


- compute amplifier performance:
gain A_v input resistance R_i output resistance R_o

C – short-circuit
dc sources - passive

3. Plot waveforms in various points of the amplifier

- small-signal waveforms
- full waveforms (dc + small-signal)

➤ Common emitter (CE) basic amplifier

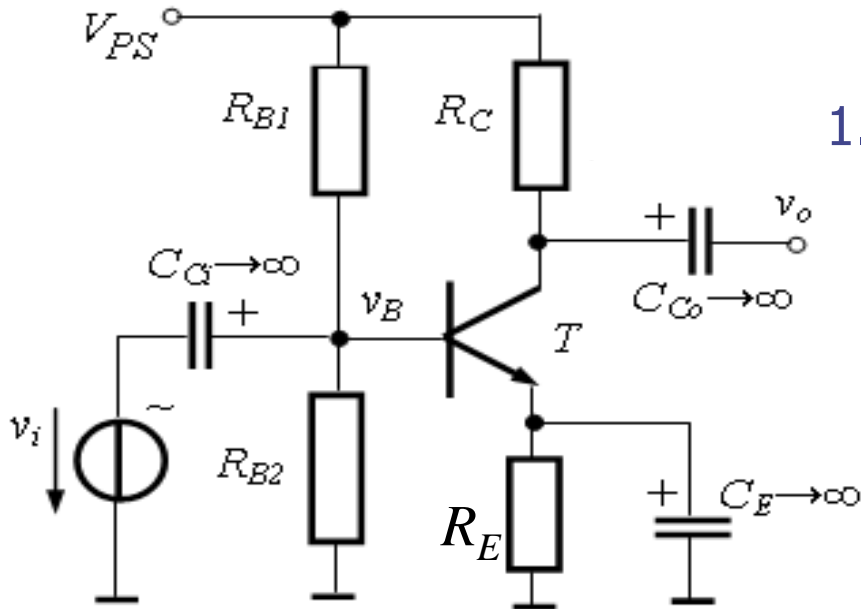

1. Draw dc equivalent circuit


- compute the operating point $Q(V_{CE}; I_C)$
- determine dc potentials in the three terminals of the transistor

- compute small-signal parameters of the transistor: g_m r_{be} r_{ce}

See Seminar 1 and C2

$$g_m = 40I_C \quad r_{be} = \frac{\beta}{g_m} \quad r_{ce} = \frac{V_A}{I_C}$$

➤ Common emitter (CE) basic amplifier

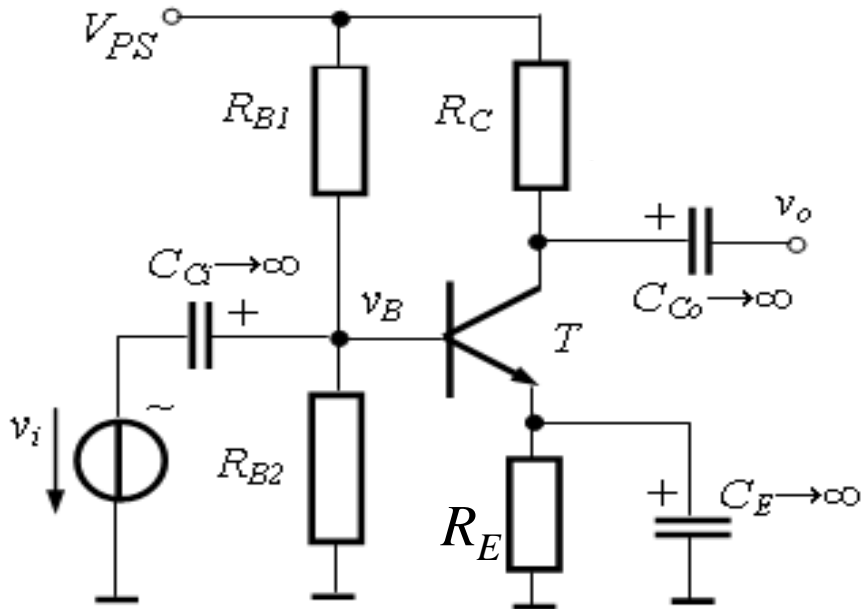


2. Draw small-signal equivalent circuit

- compute amplifier performance:


gain A_v

input resistance R_i

output resistance R_o

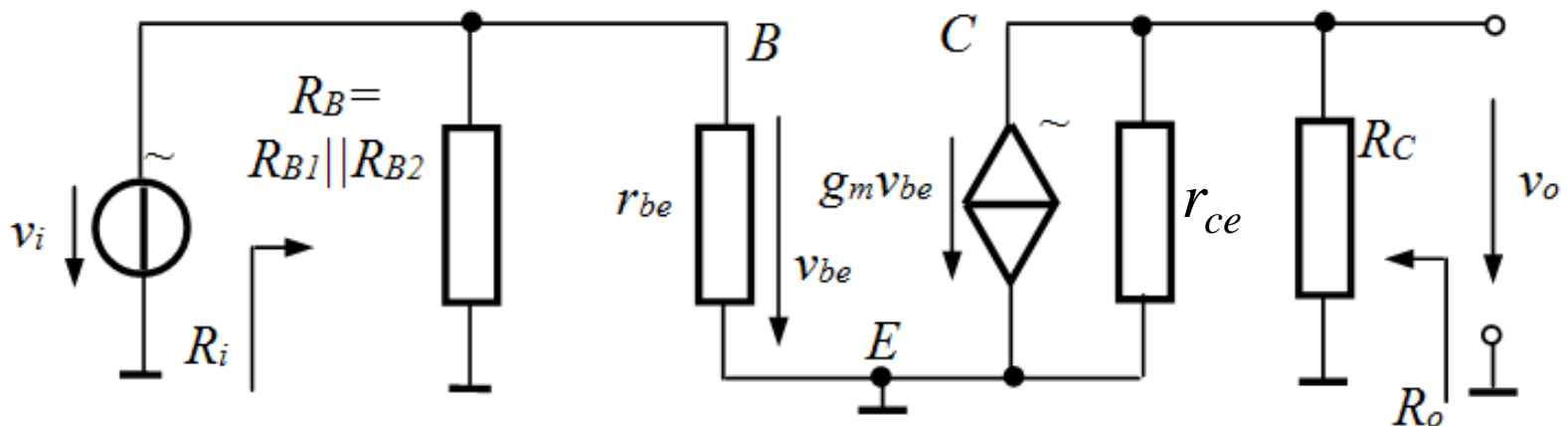

➤ Common emitter (CE) basic amplifier

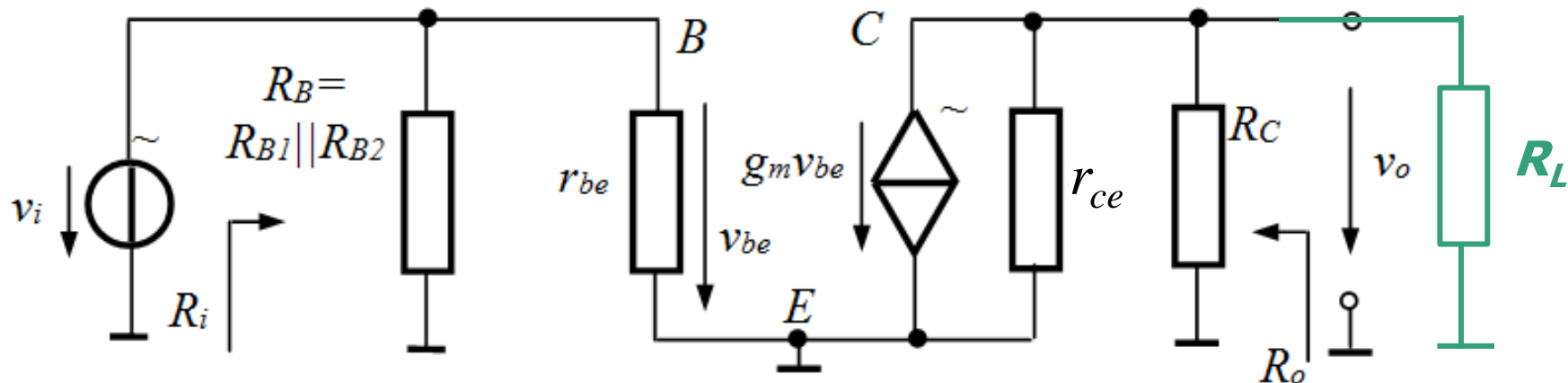

$$R_i = R_{B1} || R_{B2} || r_{be}$$

Usually, $R_C \ll r_{ce}$, so $A_v \approx -g_m R_C$

$$A_v = \frac{v_o}{v_i}$$

$$R_o = R_C || r_{ce} \approx R_C$$

$$v_i = v_{be}$$

$A_v < 0$ – inverting amplifier

$$v_o = -g_m v_{be} (R_C || r_{ce})$$


If R_L is present:

$$A_v = -g_m (R_C || r_{ce} || R_L)$$

$$A_v \approx -g_m (R_C || R_L)$$

$$A_v = -g_m (R_C || r_{ce})$$

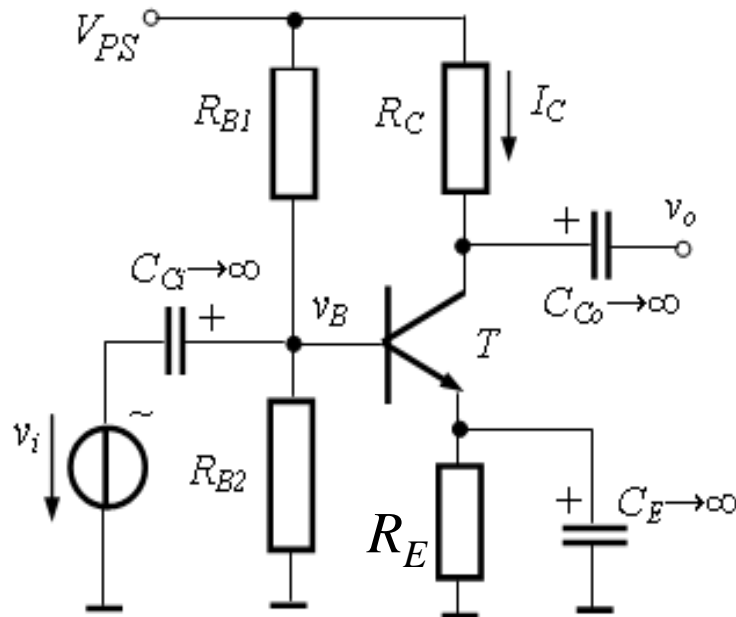➤ Common emitter (CE) basic amplifier - example



$$V_{PS} = 12 \text{ V}$$

$$R_{B1} = 49 \text{ K}\Omega \quad R_{B2} = 22 \text{ K}\Omega$$

$$R_C = 2 \text{ K}\Omega, \quad R_E = 2.5 \text{ K}\Omega$$


$$\beta = 100 \quad V_A = 100 \text{ V}$$

$$V_{BE, on} = 0.7 \text{ V}$$

- Draw the dc equivalent circuit. Determine $Q(V_{CE}, I_C)$.
- Compute the small-signal parameters of the transistor, g_m, r_{be}, r_{ce} .
- Draw the small-signal equivalent circuit. What is the configuration of the stage? Justify.
- Compute the gain, input and output resistances.
- For $v_i(t)$ - triangular wave, 10 mV amplitude, plot $v_B(t), v_o(t), v_{ce}(t), v_E(t)$.
- What changes when $R_L = 10 \text{ K}\Omega$ is connected at the output of the circuit? Recompute any of the previously determined values that are subject to change.

➤ Common emitter (CE) basic amplifier - example

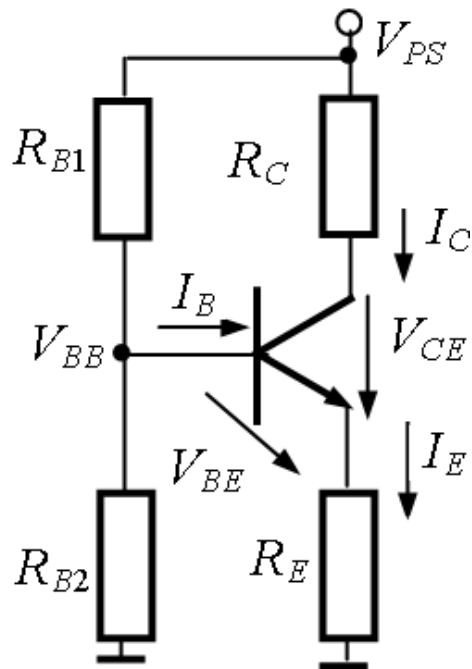- Draw the dc equivalent circuit. Determine $Q(V_{CE}, I_C)$.
- Compute the small-signal parameters of the transistor, g_m, r_{be}, r_{ce} .



$$Q(6.6 \text{ V}; 1.2 \text{ mA})$$


$$g_m = 40I_C = 48 \text{ mS}$$

$$r_{be} = \frac{\beta}{g_m} = 2.08 \text{ k}\Omega$$

$$r_{ce} = \frac{V_A}{I_C} = 83.33 \text{ k}\Omega$$

➤ Common emitter (CE) basic amplifier - **example**

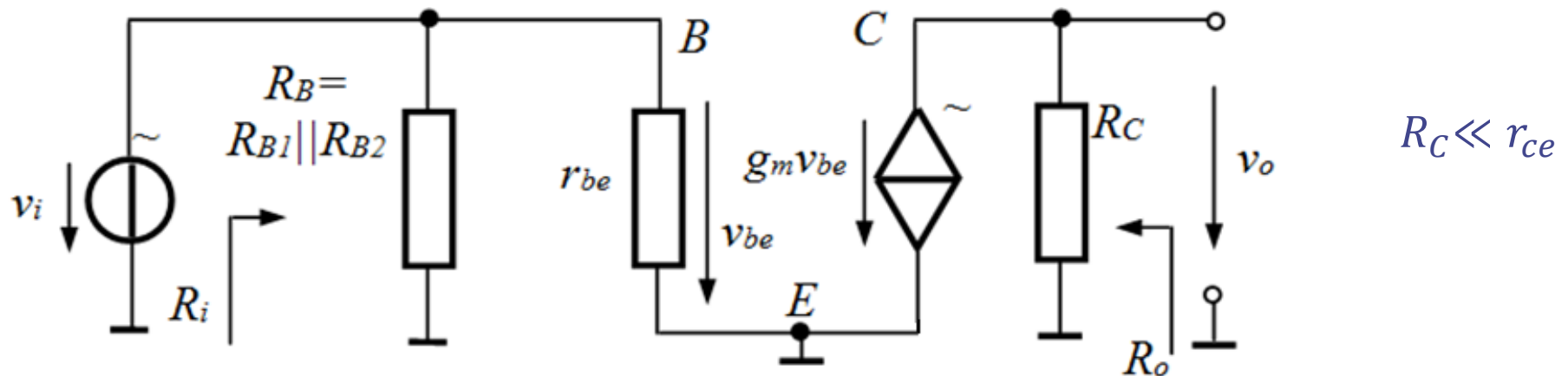- d) Draw the small-signal equivalent circuit. What is the configuration of the stage? Justify.
- e) Compute the gain, input and output resistances.




$$A_v \approx -g_m R_C = -48 \cdot 2 = -96$$

$$R_i = R_B = R_{B1} || R_{B2} || r_{be} = 1.83 \text{ K}\Omega$$

$$R_o = R_C || r_{ce} \approx R_C = 2 \text{ K}\Omega$$


common emitter, terminal E is connected to ground

➤ Common base (CB) basic amplifier

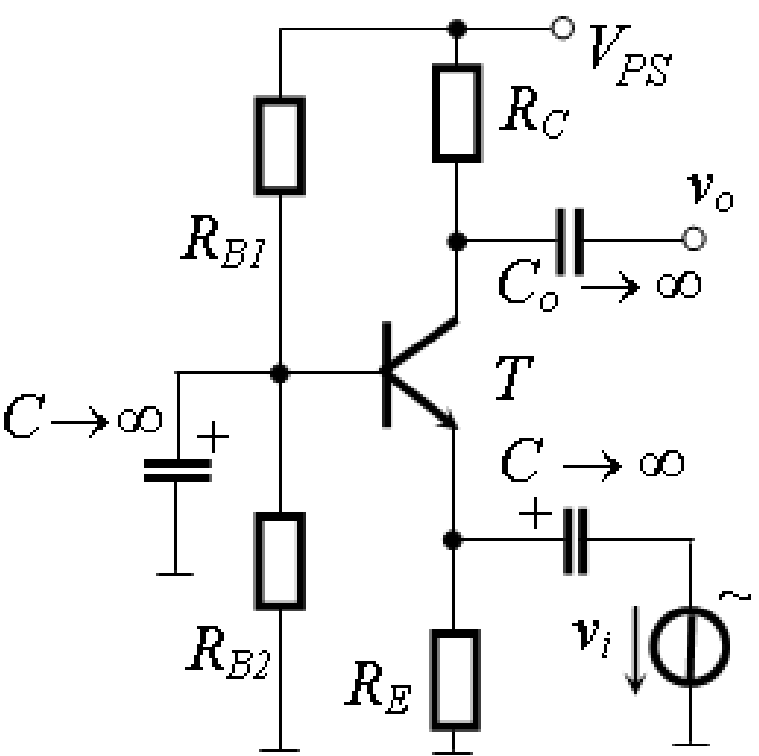

$$R_o = R_C$$

$$A_v = g_m R_C$$

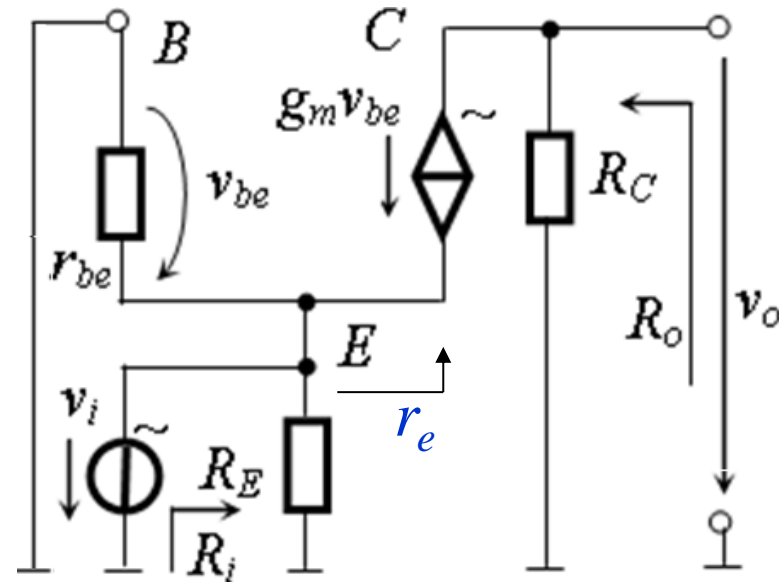

T for small-signal – simplified hybrid- π model

r_e - resistance seen into E when $v_i = 0$

$$v_o = -R_C g_m v_{be}$$



$$v_i = -v_{be}$$

$$A_v = \frac{-R_C g_m v_{be}}{-v_{be}} = g_m R_C$$

$$r_e = \frac{-v_{be}}{-v_{be}/r_{be} - g_m v_{be}} = \frac{1}{\frac{1}{r_{be}} + g_m} = \frac{1}{\frac{g_m}{\beta} + g_m} \approx \frac{1}{g_m}$$

$$R_i = R_E || r_e = R_E || \frac{1}{g_m} \approx \frac{1}{g_m}$$

➤ Common collector (CC) basic amplifier

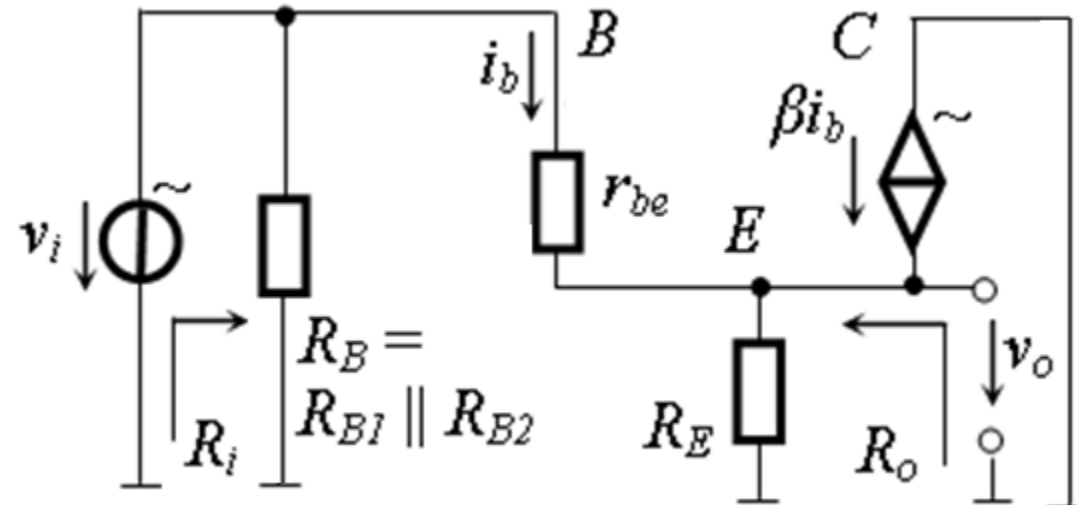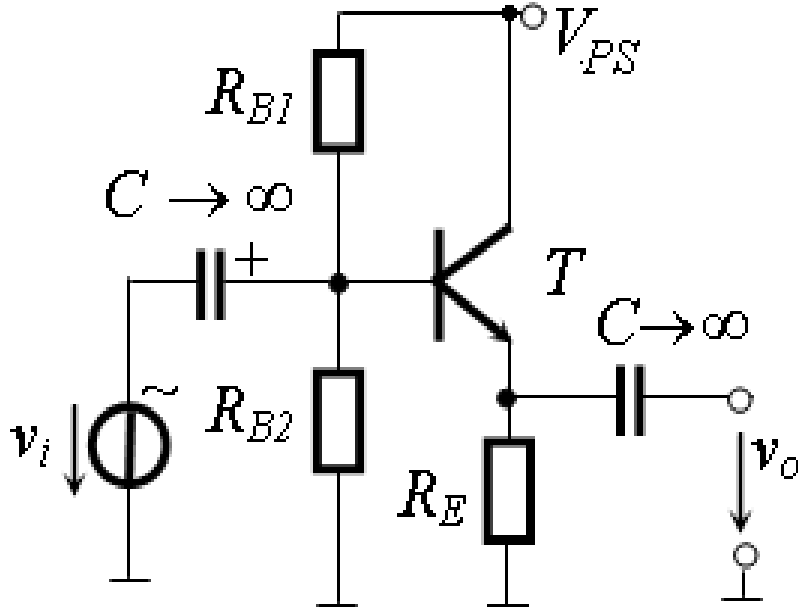

T for small-signal – simplified hybrid- π model

$$A_v = \frac{v_o}{v_i} = \frac{g_m R_E}{1 + g_m R_E} \approx 1$$

$$A_v \approx 1$$

Voltage follower (emitter follower)

$$R_i = R_B \parallel (r_{be} + (\beta + 1)R_E)$$

$$R_o = R_E \parallel \frac{1}{g_m} \approx \frac{1}{g_m}$$

➤ BJT basic amplifiers - summary

Common emitter CE

$$A_v = -g_m(R_C || r_{ce}) \approx -g_m R_C$$

$$R_i = R_{B1} || R_{B2} || r_{be}$$

$$R_o = R_C$$

Common base CB

$$A_v \approx g_m R_C$$

$$R_i \approx \frac{1}{g_m}$$

$$R_o = R_C$$

Common collector CC

$$A_v \approx 1$$

$$R_i = R_B || (r_{be} + (\beta + 1)R_E)$$

$$R_o \approx \frac{1}{g_m}$$

Which one is best? What does best mean for gain, input/output resistance?

➤ Transistor amplifiers - requirements

- high gain
- high input resistance
- low output resistance

Common emitter CE

$$A_v = -g_m(R_C || r_{ce}) \approx -g_m R_C$$

high gain (absolute value)

$$R_i = R_{B1} || R_{B2} || r_{be}$$

rather **low** input resistance

Common collector CC


$$A_v \approx 1$$

low (unitary) gain

$$R_i = R_i = R_B || (r_{be} + (\beta + 1)R_E)$$

high input resistance

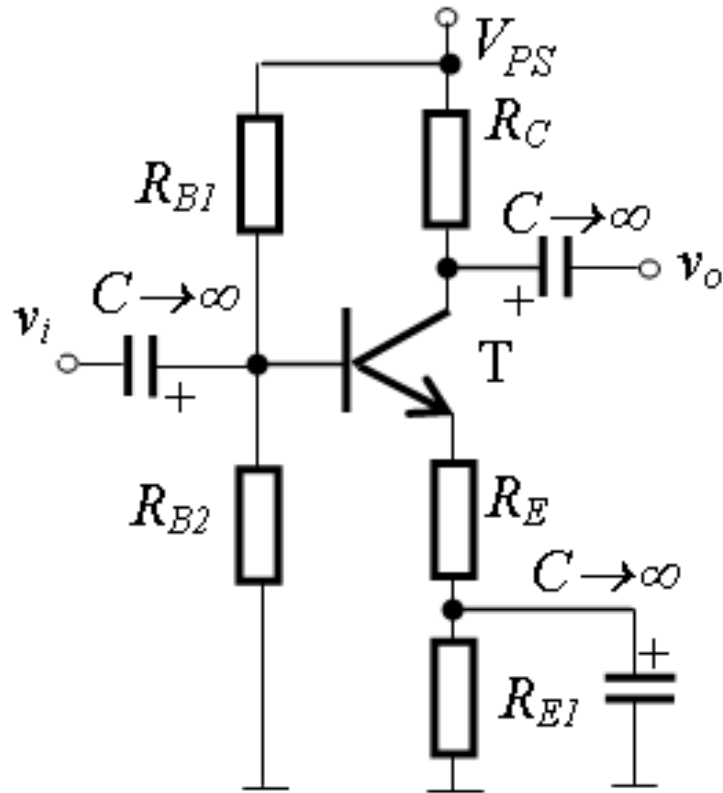➤ Modified CE (emitter degeneration) amplifier



$R_E + R_{E1}$ appear in dc – sets I_C

R_E appears in ac – sets the gain

$$A_v \approx -\frac{g_m R_C}{1 + g_m R_E}$$

If $g_m R_E \gg 1$

$$A_v \approx -\frac{R_C}{R_E}$$

➤ stable gain, independent of transistor parameters

$$R_i = R_B \parallel [r_{be} + (\beta + 1)R_E]$$

$$R_o = R_C$$

➤ Summary of single-stage transistor amplifiers

Config	Gain	Input resistance	Output resistance
CS	$-g_m(R_D r_{ds}) \approx -g_m R_D$	R_G	$R_D r_{ds} \approx R_D$
CE	$-g_m(R_C r_{ce}) \approx -g_m R_C$	$R_{B1} R_{B2} r_{be}$	R_C
CG	$g_m(R_D r_{ds}) \approx g_m R_D$	$\approx 1/g_m$	$R_D r_{ds} \approx R_D$
CB	$g_m(R_C r_{ce}) \approx g_m R_C$	$\approx 1/g_m$	R_C
CD	≈ 1	R_G	$\approx R_S 1/g_m$
CC	≈ 1	$R_B [r_{be} + (\beta + 1)R_E]$	$\approx 1/g_m$
Emitter degeneration	$\approx -R_C/R_E$	$R_B [r_{be} + (\beta + 1)R_E]$	R_C

Summary

- BJT small-signal model
- BJT basic amplifiers
- Comparison and analysis

Next week: Frequency response. Current sources and current mirrors.