

FUNDAMENTAL ELECTRONIC CIRCUITS

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C5 – Frequency response. Current sources and current mirrors.


Contents

- Frequency response of transistor amplifiers
 - qualitative analysis for CS amplifier
 - quantitative analysis for CS and CE amplifiers
 - cascode amplifiers
- Current sources
- Current mirrors

➤ CS amplifier - revisited

Mid-frequency complete circuit

Coupling capacitors: C_{ci} C_{co} C_s

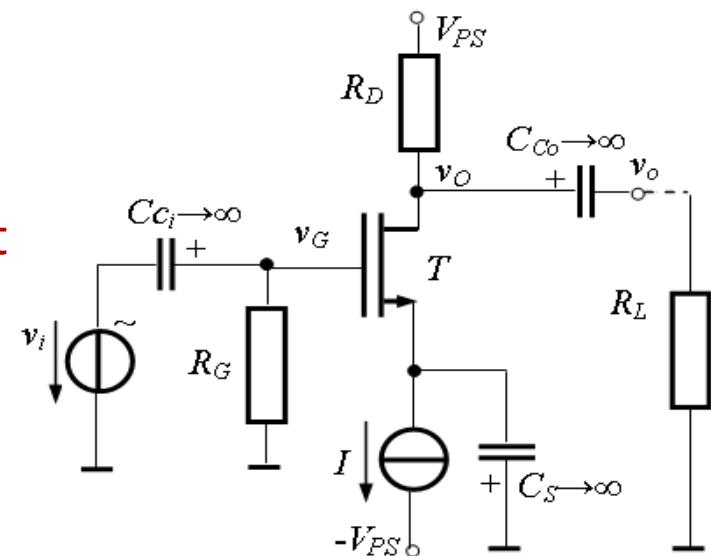


➤ Premises

- mid-frequency:
 - coupling capacitors → short-circuits
 - internal parasitic capacitances → open-circuits
- low-frequency:
 - coupling capacitors → equivalent impedances
 - internal parasitic capacitances → open-circuits
- high-frequency:
 - coupling capacitors → short-circuits
 - internal parasitic capacitances → equivalent impedances



The effect of the output resistance of the input signal source and load
resistance must be taken into account.

➤ Gain – frequency plot of CS amplifier

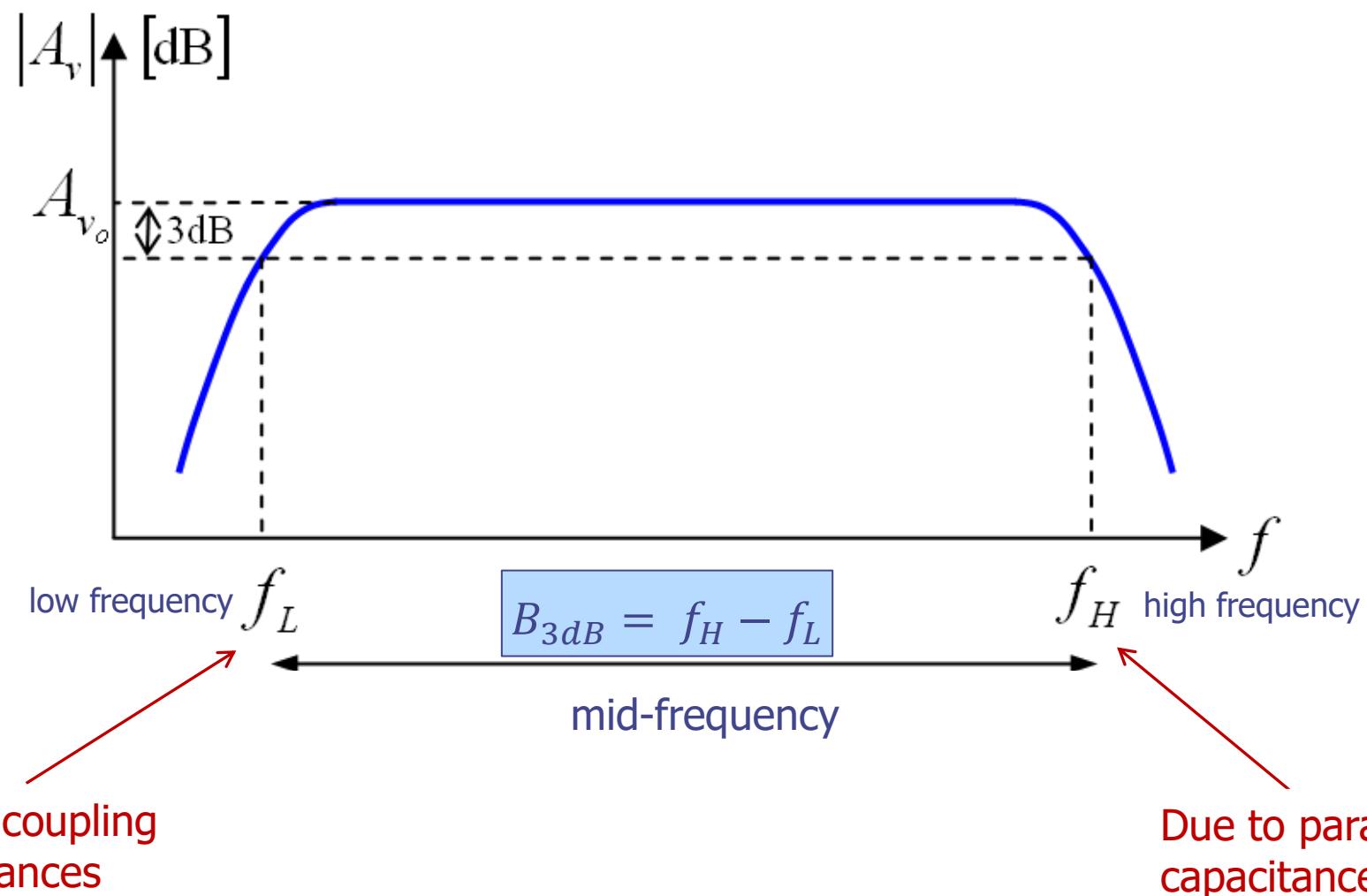

➤ Gain – frequency plot of CS amplifier

- mid-frequency:

$$|A_v(j\omega)| = \text{const}$$


- low-frequency:
 - coupling capacitors determine f_L

$$f \downarrow, |A_v(j\omega)| \downarrow$$

- high-frequency:
 - internal parasitic capacitances determine f_H


$$f \uparrow, |A_v(j\omega)| \downarrow$$

➤ CS amplifier – mid-frequency

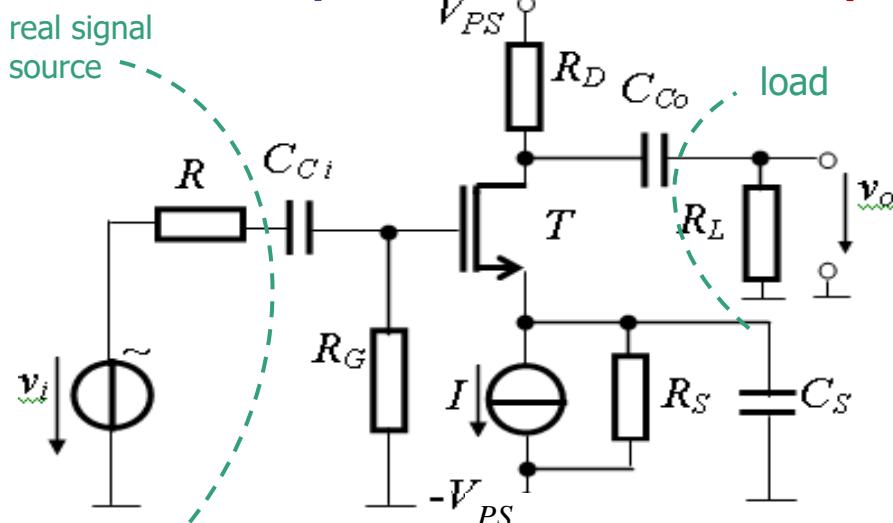


- **No capacitors** in the small-signal equivalent circuit
- **Frequency independent** behavior

$$|A_v(j\omega)| = \text{const}$$

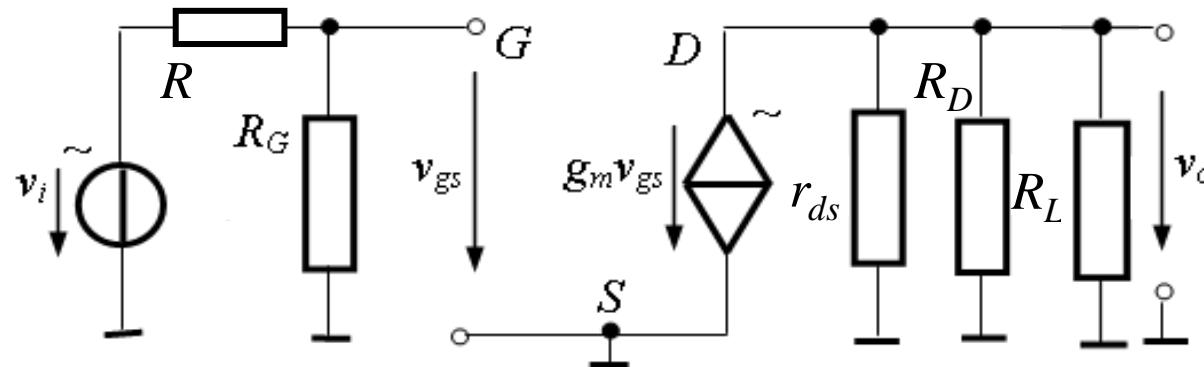


➤ CS amplifier – low frequency

OPTIONAL

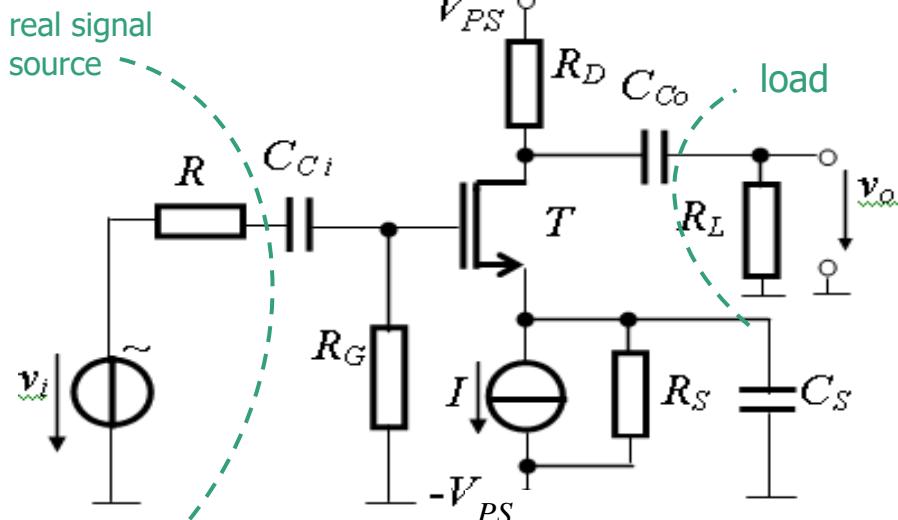

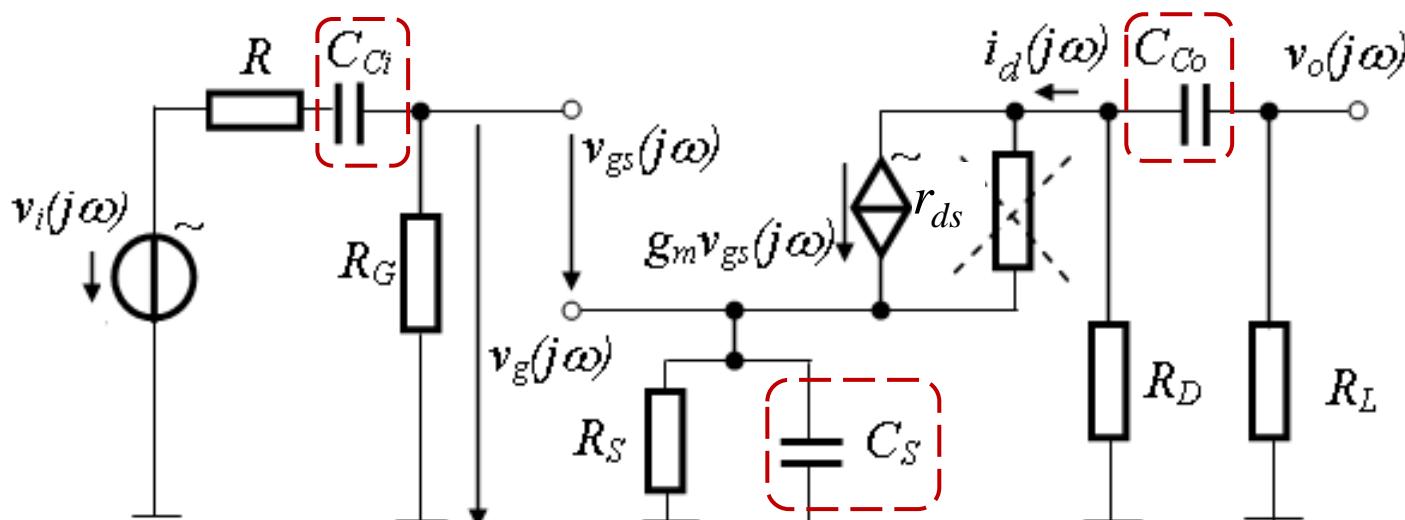- **Coupling capacitors** in the small-signal equivalent circuit
- **Frequency dependent** behavior (high-pass type)




$$f \downarrow, |A_v(j\omega)| \downarrow$$

Sets f_L – low cutoff frequency


➤ CS amplifier – high frequency

OPTIONAL

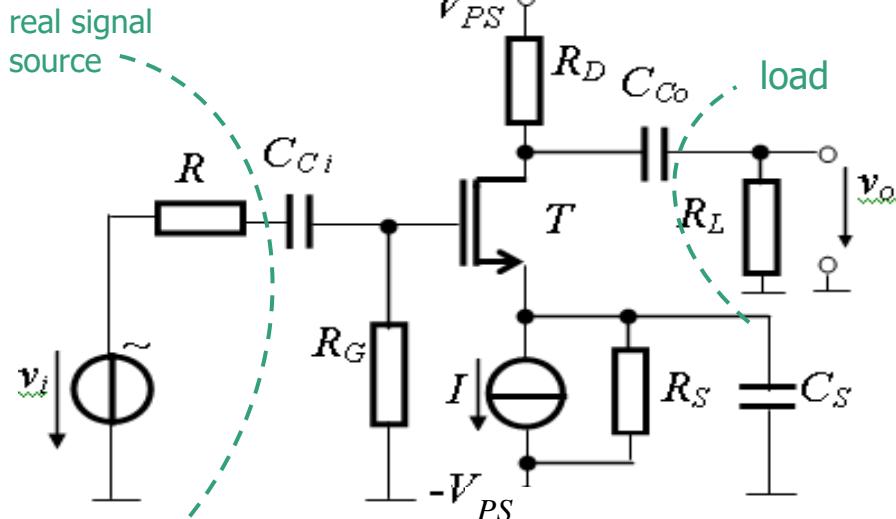


- **Parasitic capacitors** in the small-signal equivalent circuit
- **Frequency dependent** behavior (low-pass type)

$$f \uparrow, |A_v(j\omega)| \downarrow$$

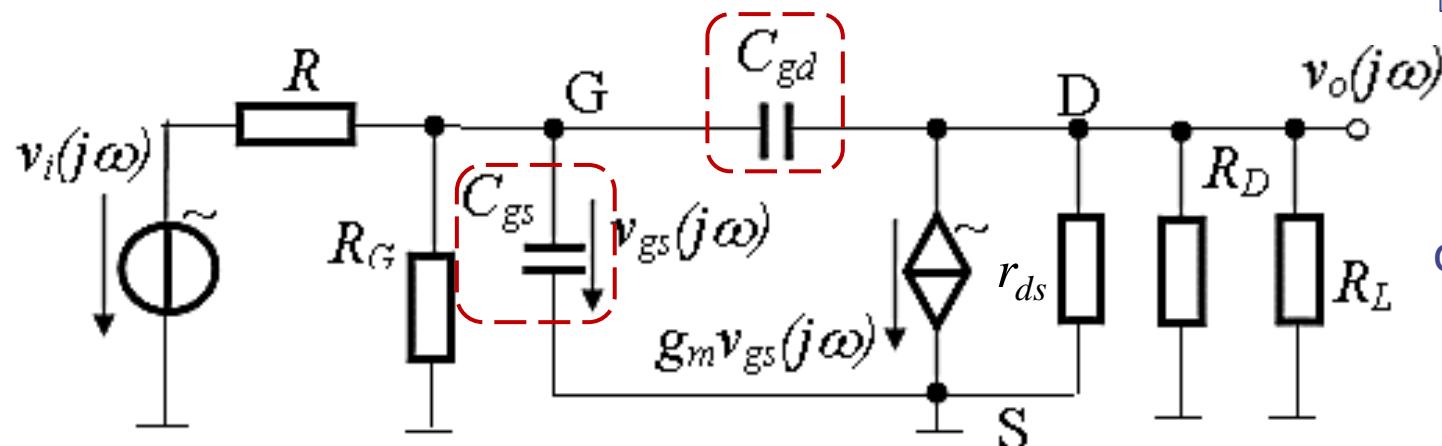

➤ CS amplifier – low frequency analysis

OPTIONAL

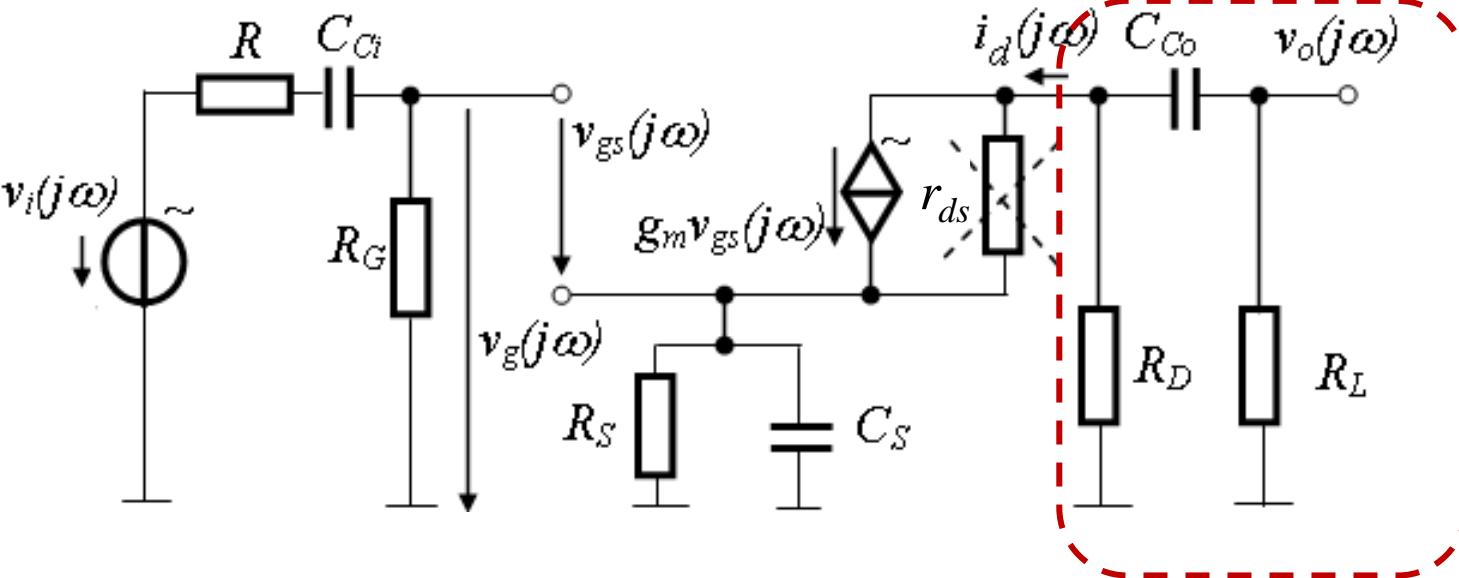

$$A_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$$

$$v_g(j\omega) = F_i(j\omega) \cdot v_i(j\omega)$$

$$i_d(j\omega) = F_S(j\omega) \cdot v_g(j\omega)$$

$$v_o(j\omega) = F_o(j\omega) \cdot i_d(j\omega)$$

$$A_v(j\omega) = F_o(j\omega) \cdot F_S(j\omega) \cdot F_i(j\omega)$$

➤ CS amplifier – low frequency analysis

$$A_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = F_o(j\omega) \cdot F_S(j\omega) \cdot F_i(j\omega)$$

- each coupling capacitor determines a low cutoff frequency

$$F_i(j\omega) = \frac{v_g(j\omega)}{v_i(j\omega)} = \frac{j\omega R_G C_{Ci}}{1 + j\omega(R + R_G)C_{Ci}}$$

$$f_{Li} = \frac{1}{2\pi(R + R_G)C_{Ci}}$$

$$F_S(j\omega) = \frac{i_d(j\omega)}{v_g(j\omega)} = \frac{g_m v_{gs}(j\omega)}{v_{gs}(j\omega) + g_m v_{gs}(j\omega) \left(R_S \parallel \frac{1}{j\omega C_S} \right)}$$

$$f_{LS} = \frac{1}{2\pi \left(\frac{1}{g_m} \parallel R_S \right) C_S}$$

$$F_o(j\omega) = \frac{v_o(j\omega)}{i_d(j\omega)}$$


$$f_{Lo} = \frac{1}{2\pi(R_D + R_L)C_{Co}}$$

Dominant pole: $\max(f_{Li}, f_{LS}, f_{Lo})$, if the nearest pole or zero is at least a decade away.
Usually given by f_{LS} for equal coupling capacitances



➤ CS amplifier – high frequency analysis

OPTIONAL

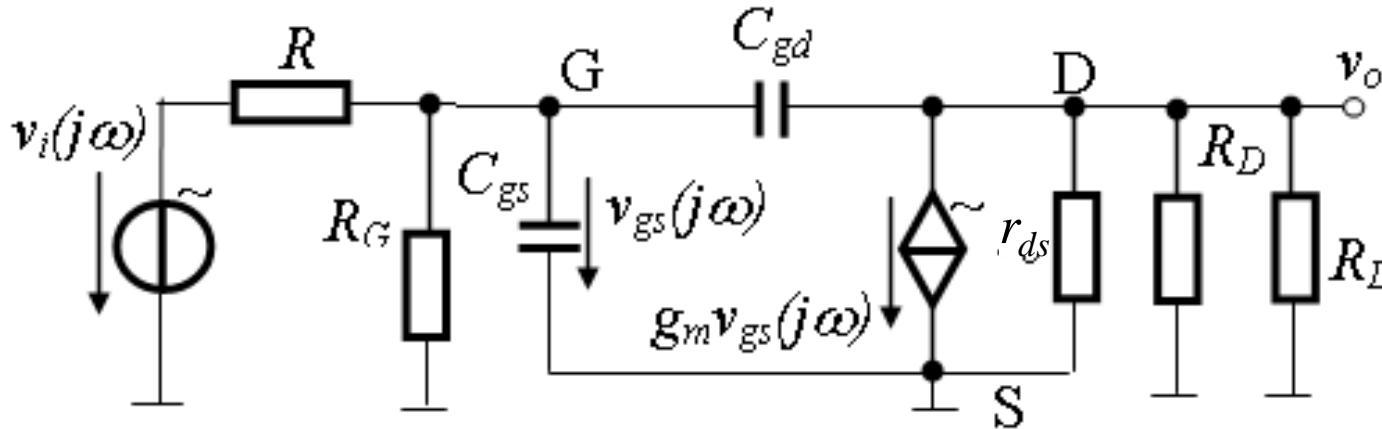

$$A_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$$


C_{ds} - not shown, since it generates a pole at a much higher frequency than the one generated by C_{gs} and C_{gd}

$$C_{gd,eq} = (1 - a_v)C_{gd}$$

$$a_v = -g_m R'_L = -g_m (R_L || R_D || r_{ds})$$


$$C_{gd,eq} = (1 + g_m R'_L)C_{gd}$$

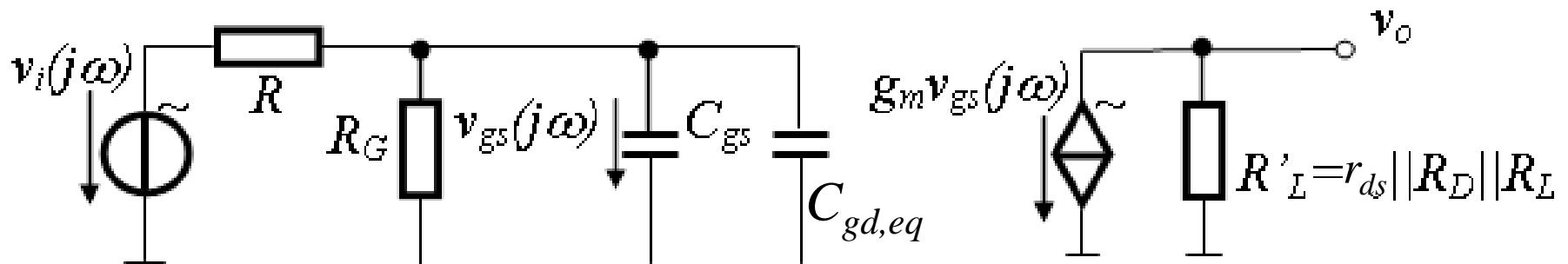C_{gd} is reflected at the input according to Miller's theorem



➤ CS amplifier – high frequency analysis

OPTIONAL

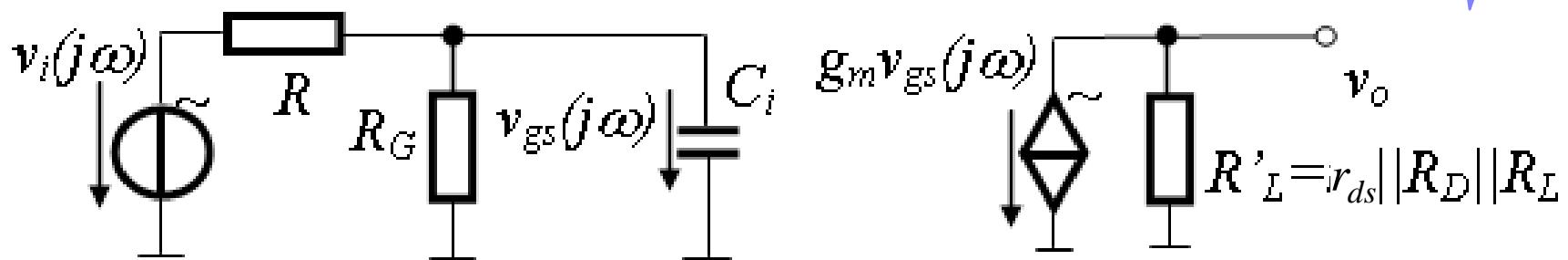

$$C_i = C_{gs} + C_{gd,eq} = C_{gs} + (1 + g_m R'_L) C_{gd}$$

$$A_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = -\frac{R_G}{R + R_G} g_m R'_L \frac{1}{1 + j\omega(R||R_G)C_i}$$

$$A_{vo} = -\frac{R_G}{R + R_G} g_m R'_L$$

$$f_H = \frac{1}{2\pi(R||R_G)C_i}$$

➤ CS amplifier – frequency analysis summary




$$f_{Li} = \frac{1}{2\pi(R + R_G)C_{Ci}}$$

$$f_H = \frac{1}{2\pi(R || R_G)C_i}$$

$$f_{Ls} = \frac{1}{2\pi\left(\frac{1}{g_m} || R_S\right)C_s}$$

$$f_{Lo} = \frac{1}{2\pi(R_D + R_L)C_{Co}}$$

$$f_L = \max(f_{Li}, f_{Ls}, f_{Lo})$$

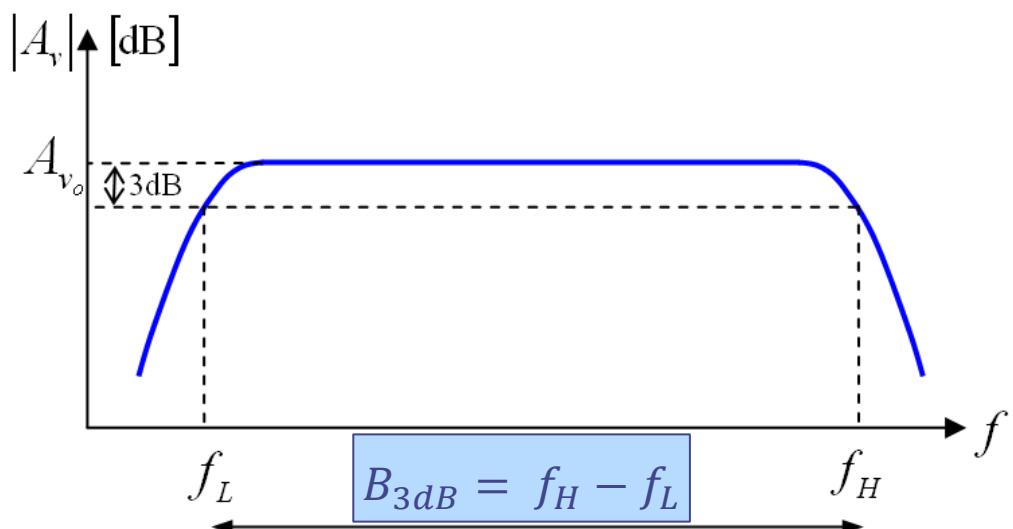

➤ CS amplifier – frequency analysis example



$C_{ci} = C_{Co} = C_s = 10 \mu\text{F}$, $R = 20 \text{ k}\Omega$, $R_G = 2 \text{ M}\Omega$, $R_D = 10 \text{ k}\Omega$, $R_L = 20 \text{ k}\Omega$, $R_s = 10 \text{ k}\Omega$, $I = 400 \mu\text{A}$
 $K = 100 \mu\text{A/V}^2$, $(W/L) = 18$, $V_A = 100 \text{ V}$
 $C_{gs} = C_{gd} = 1 \text{ pF}$ @ $I = 400 \mu\text{A}$

Compute f_L , f_H , A_{vo} . Draw the gain-frequency plot.

$$g_m = 1.2 \text{ mS} \quad r_o = 250 \text{ k}\Omega$$

$$f_{Li} = \frac{1}{2\pi(R + R_G)C_{ci}} = \frac{1}{2\pi(20 + 2000)10^3 \cdot 10 \cdot 10^{-6}} \cong 8 \text{ mHz}$$

$$\mathbf{f_L = 21 \text{ Hz}}$$

$$f_{Ls} = \frac{1}{2\pi\left(\frac{1}{g_m} || R_s\right)C_s} = \frac{1}{2\pi\left(\frac{1}{1.2} || 10\right)10^3 \cdot 10 \cdot 10^{-6}} \cong 21 \text{ Hz}$$

$$f_{Lo} = \frac{1}{2\pi(R_D + R_D)} = \frac{1}{2\pi(10 + 20)10^3 \cdot 10 \cdot 10^{-6}} \cong 0.5 \text{ Hz}$$

➤ CS amplifier – frequency analysis example



$C_{ci} = C_{Co} = C_s = 10 \mu\text{F}$, $R = 20 \text{ k}\Omega$, $R_G = 2 \text{ M}\Omega$, $R_D = 10 \text{ k}\Omega$, $R_L = 20 \text{ k}\Omega$, $R_s = 10 \text{ k}\Omega$, $I = 400 \mu\text{A}$
 $K = 100 \mu\text{A/V}^2$, $(W/L) = 18$, $V_A = 100 \text{ V}$

$C_{gs} = C_{gd} = 1 \text{ pF}$ @ $I = 400 \mu\text{A}$

Compute f_L , f_H , A_{vo} . Draw the gain-frequency plot.

$$A_{vo} = -\frac{R_G}{R + R_G} g_m R'_L = -\frac{2}{0.02 + 2} \cdot 1.2 \cdot 6.5 = -7.7$$

$$|A_{vo}|_{\text{dB}} = 20 \log(7.7) = 17.7$$

$$C_i = C_{gs} + [1 + g_m(r_o || R_D || R_L)] C_{gd} = 1 + [1 + 1.2(250 || 10 || 20)] \cdot 1 \cong 9.8 \text{ pF}$$

$$f_H = \frac{1}{2\pi(R || R_G)C_i} = \frac{1}{2\pi(20 || 2000) \cdot 10^3 \cdot 9.8 \cdot 10^{-12}} = 820 \text{ KHz}$$

➤ CS amplifier – frequency analysis example




$C_{ci} = C_{Co} = C_s = 10 \mu\text{F}$, $R = 20 \text{ k}\Omega$, $R_G = 2 \text{ M}\Omega$, $R_D = 10 \text{ k}\Omega$, $R_L = 20 \text{ k}\Omega$, $R_s = 10 \text{ k}\Omega$, $I = 400 \mu\text{A}$

$K = 100 \mu\text{A/V}^2$, $(W/L) = 18$, $V_A = 100 \text{ V}$


$C_{gs} = C_{gd} = 1 \text{ pF}$ @ $I = 400 \mu\text{A}$

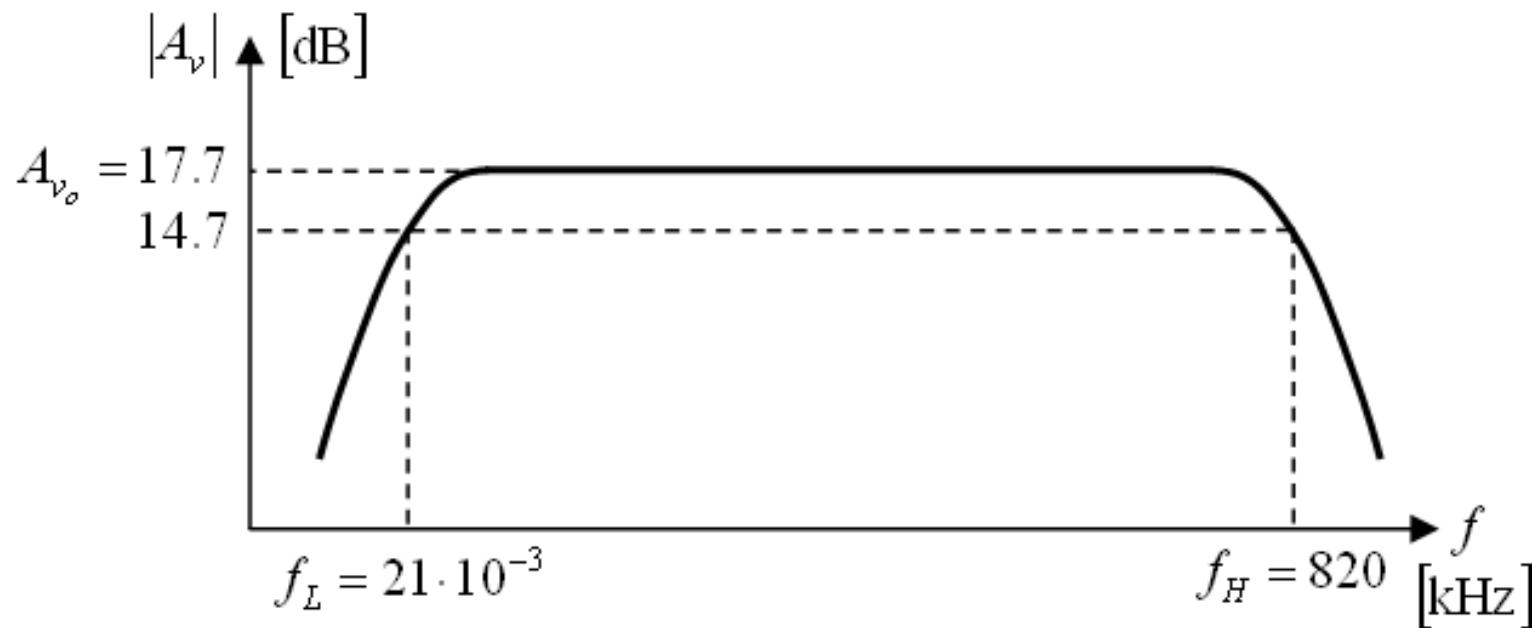Compute f_L , f_H , A_{vo} . Draw the gain-frequency plot.



➤ CE amplifier – low frequency

OPTIONAL

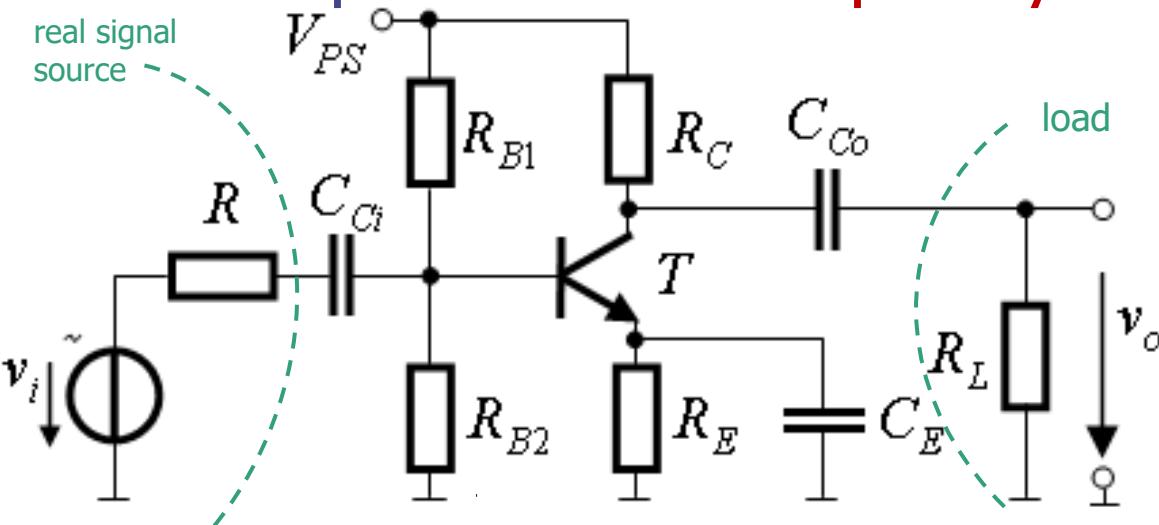

$$f_{Li} = \frac{1}{2\pi(R + R_i)C_{ci}} = \frac{1}{2\pi(R + R_B || r_{be})C_{ci}}$$

$$f_{Le} = \frac{1}{2\pi(R' || R_E)C_E} = \frac{1}{2\pi R'_E C_E}$$

$$f_{Lo} = \frac{1}{2\pi(R_O + R_L)C_{co}} = \frac{1}{2\pi(R_C + R_L)C_{co}}$$



$$R_B = R_{B1} || R_{B2}$$

$$R'_E = R_E || R' = R_E || \frac{r_{be} + R_B || R}{\beta + 1}$$

$$f_L = \max(f_{Li}, f_{Le}, f_{Lo})$$

➤ CE amplifier – high frequency

OPTIONAL

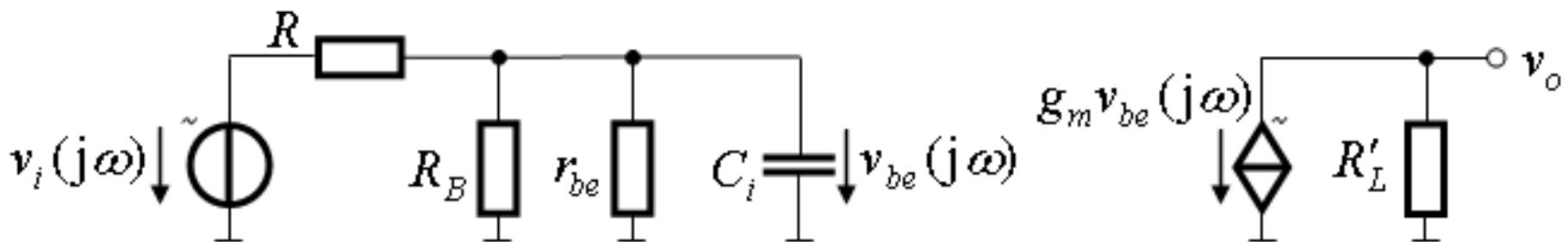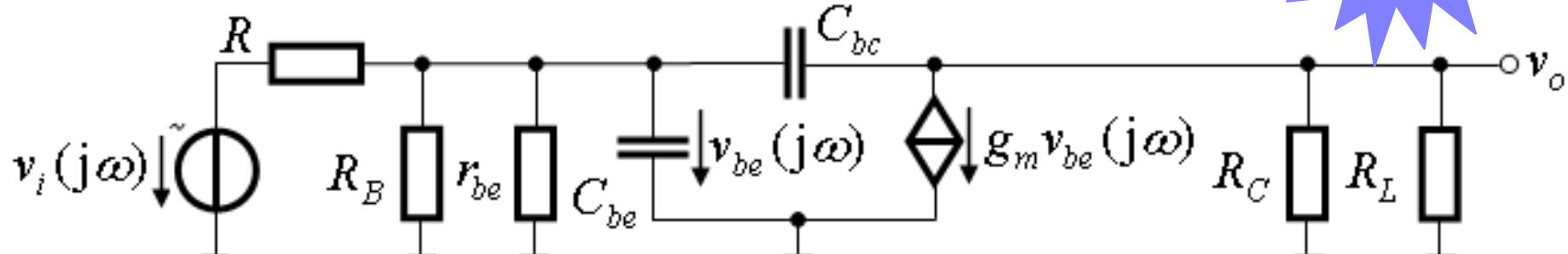

$$A_v(j\omega) = -\frac{R_B || r_{be}}{R + R_B || r_{be}} g_m (R_C || R_L) \frac{1}{1 + j\omega R'_i C_i}$$

$$R'_i = r_{be} || R_B || R$$

$$C_i = C_{be} + (1 + g_m R'_L) C_{bc}$$

$$A_{vo} = -\frac{R_B || r_{be}}{R + R_B || r_{be}} g_m (R_C || R_L)$$

$$f_H = \frac{1}{2\pi(r_{be} || R_B || R) C_i}$$

➤ CS & CE amplifiers - summary

CS

$$A_{vo} = -\frac{R_G}{R + R_G} g_m R'_L$$

$$f_H = \frac{1}{2\pi(R||R_G)C_i}$$

$$C_i = C_{gs} + C_{gd_{eq}} = C_{gs} + (1 + g_m R'_L) C_{gd}$$

CE

$$A_{vo} = -\frac{R_B || r_{be}}{R + R_B || r_{be}} g_m (R_C || R_L)$$

$$f_H = \frac{1}{2\pi(r_{be}||R_B||R)C_i}$$

$$C_i = C_{be} + (1 + g_m R'_L) C_{bc}$$

Problem: when the gain increases, the parasitic capacitance reflected at the input also increases, so the high cutoff frequency decreases


$$A_{vo} \uparrow, C_i \uparrow, f_H \downarrow$$

Solution?


Cascode amplifiers: CS+CG or CE+CB, to obtain a wide bandwidth



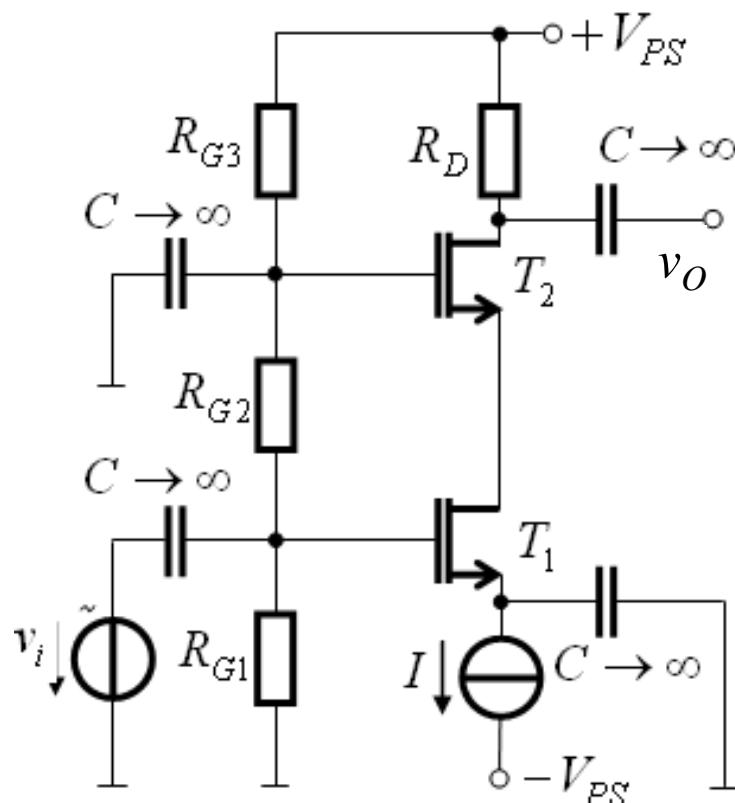➤ Cascode amplifiers – CS + CG – medium frequency



same current through T_1 , T_2

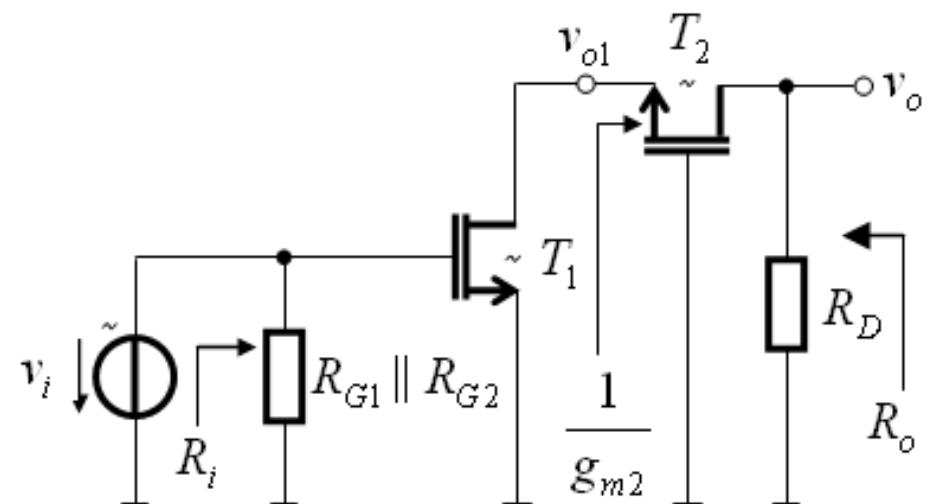

$$R_i = R_{G1} \parallel R_{G2} = R_G$$


$$R_o = R_D \parallel (r_{o1} + r_{o2} + g_{m2}r_{o1}r_{o2}) \approx R_D$$

$$g_m = g_{m1} = g_{m2}$$

$$A_v = -g_m R_D$$



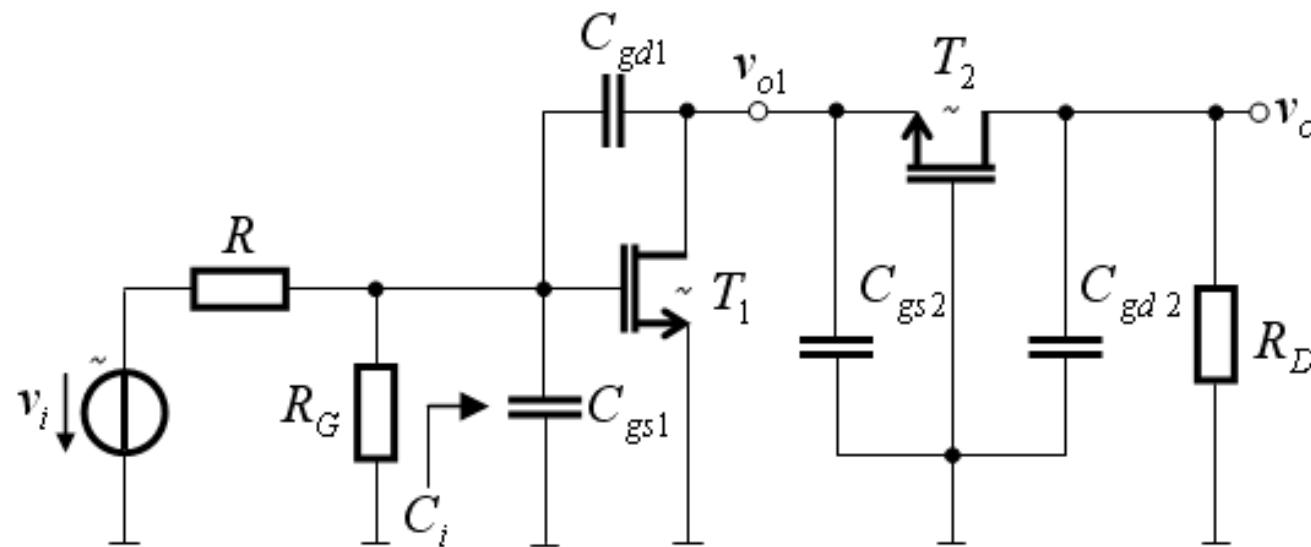➤ Cascode amplifiers – CS + CG – high frequency




$$C_i = C_{gs1} + (1 - A_{v1})C_{gd1} = C_{gs1} + 2C_{gd1}$$

$$f_H = \frac{1}{2\pi(R||R_G)C_i}$$



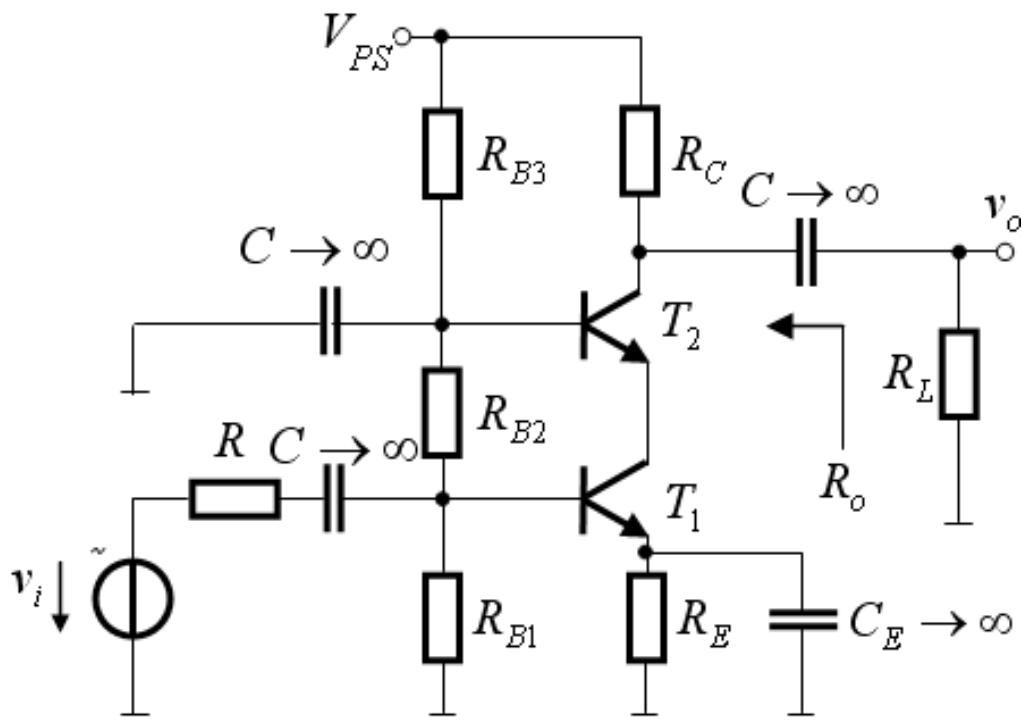➤ Cascode amplifiers – CE + CB (BJT amplifiers)



For identical T_1 and T_2 transistors

$$R_B = R_{B1} \parallel R_{B2}$$

$$r_{be} = r_{be1} = r_{be2}$$

$$g_m = g_{m1} = g_{m2}$$



$$A_v = -\frac{R_B \parallel r_{be}}{R + R_B \parallel r_{be}} g_m (R_C \parallel R_L)$$

$$f_H = \frac{1}{2\pi(r_{be} \parallel R_B \parallel R)(C_{be} + 2C_{bc})}$$

➤ To begin with

- What is a current source?
 - a circuit where the current is independent of the load resistance $I_O \neq f(R_L)$
 - the current is not influenced by the supply voltage, temperature variations or other operating conditions

$$I_O \neq f(V_{PS}), I_O \neq f(T)$$


- What is a current mirror? Where is it used?
 - a circuit that generates dc currents in direct ratio with a reference current
 - The reference current is mirrored. $I_O = \text{ratio} \cdot I_{REF}$
 - used to bias integrated circuits
- Current sources and current mirrors w/ MOSFET or BJT?
Yes!

➤ MOSFET current sources

Current sink

(absorbs current)

$T_n - (a_F)$

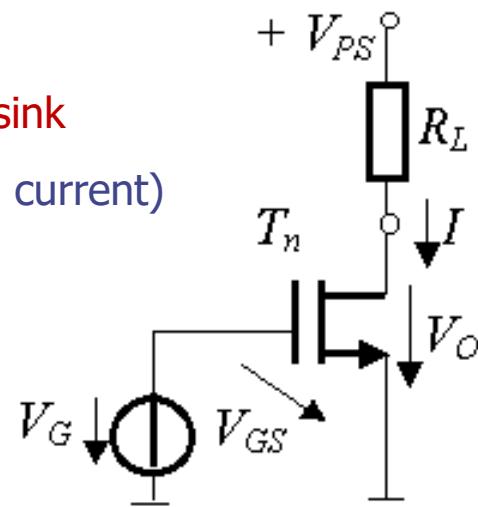

$$I = \beta_n (V_{GS} - V_{Thn})^2$$

$$V_O = V_{PS} - R_L I$$

$$V_O > V_{DSSat}$$


$$V_{PS} - R_L I > V_{DSSat}$$

$$V_{PS} - R_L I > V_{GS} - V_{Thn}$$

Current source

(generates current)


$T_p - (a_F)$

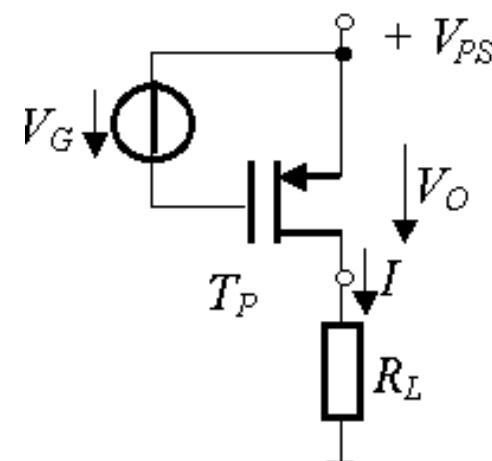

$$I = \beta_p (V_{GS} - V_{Thp})^2$$

pseudo-sources, consume power
voltage sources are necessary

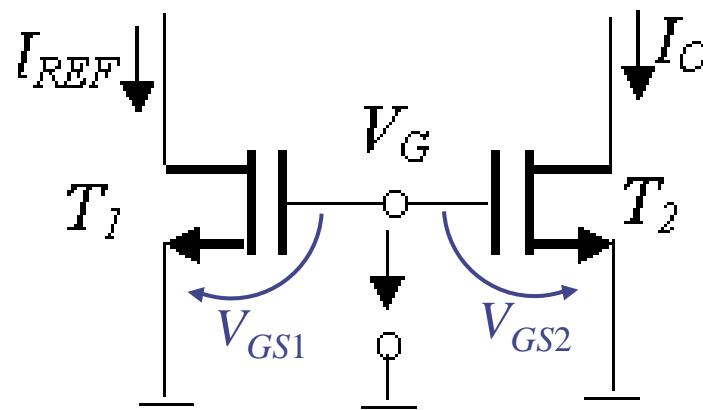➤ MOSFET current mirror (integrated transistors)



$$V_{GS1} = V_G = V_{GS2}$$



$$I = \frac{k}{2} \frac{W}{L} (V_{GS} - V_{Th})^2$$

If $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$ then $I_O = I_{REF}$

For identical transistors, the currents are **equal**.

How can I_{REF} be obtained?

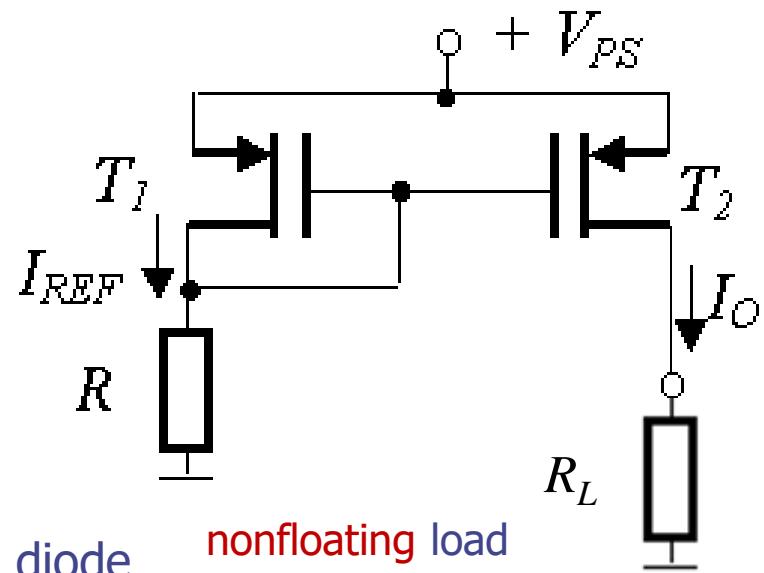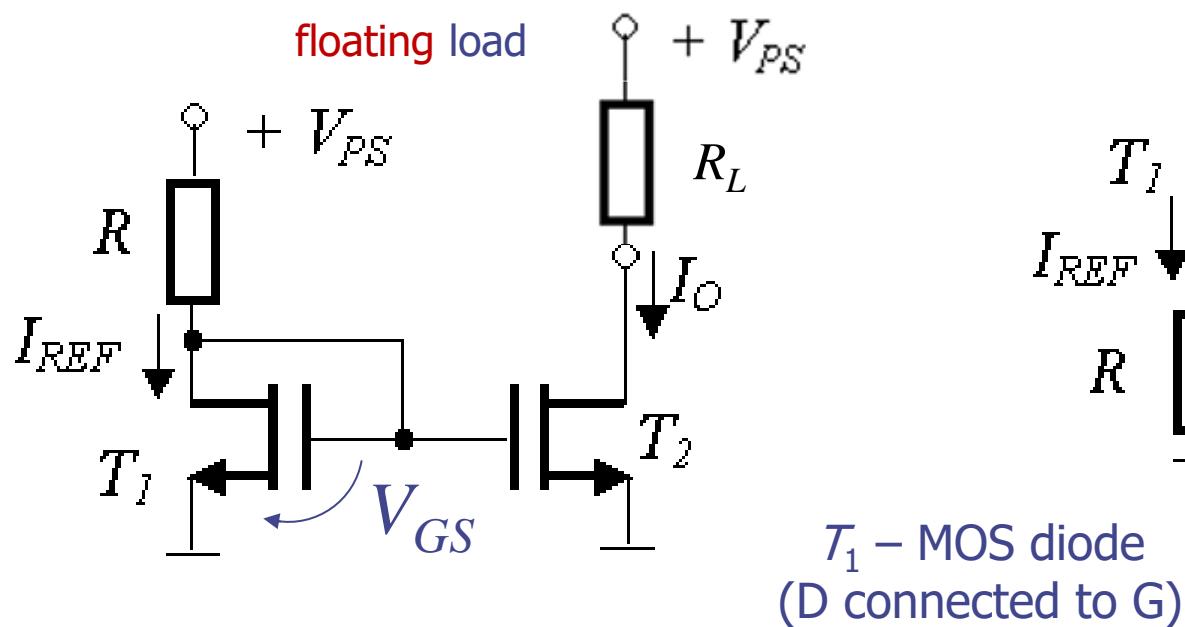➤ MOSFET current mirror (integrated transistors)





To compute I_{REF} :

$$\begin{cases} I_{REF} = \frac{V_{PS} - V_{GS}}{R} \\ I_{REF} = \frac{K_1}{2} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{Th1})^2 \end{cases}$$

To size R for a certain I_{REF} :

$$R = \frac{V_{PS} - V_{GS}}{I_{REF}}$$

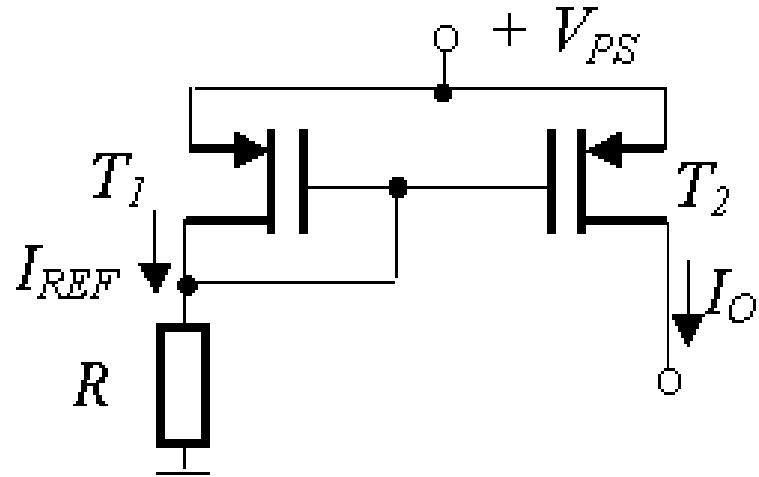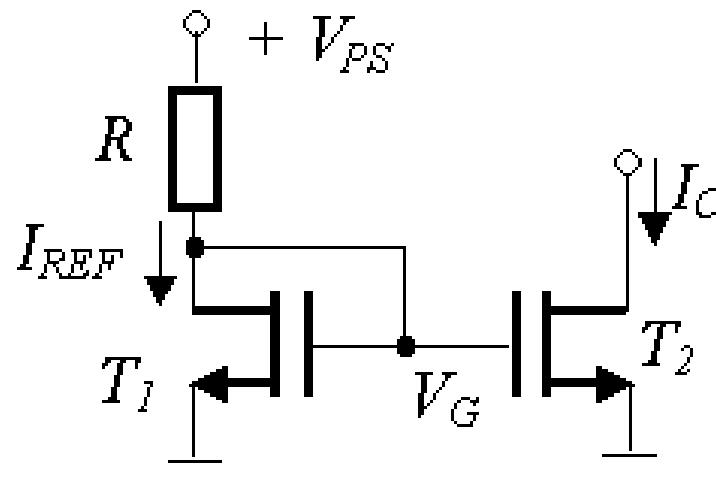➤ MOSFET current multiplier mirrors (different W/L ratios)




$$I_{REF} = \frac{K_1}{2} \left(\frac{W}{L} \right)_1 (V_G - V_{Th1})^2$$

$$I_O = \frac{K_2}{2} \left(\frac{W}{L} \right)_2 (V_G - V_{Th2})^2$$

If $K_1 = K_2$ and $V_{Th1} = V_{Th2}$ then

$$I_O = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$

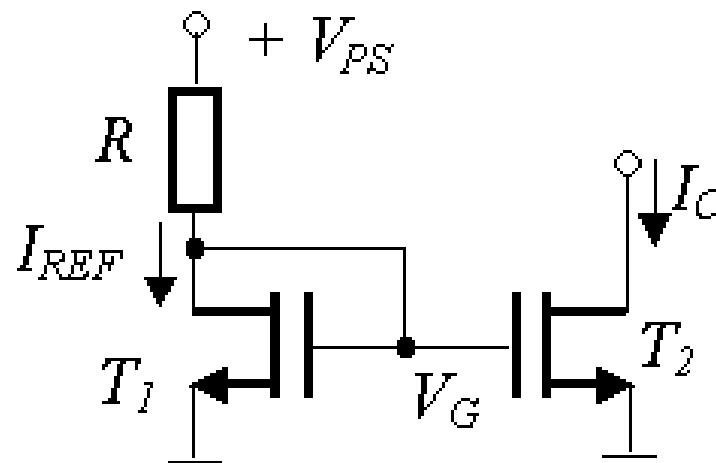➤ MOSFET current multiplier mirrors – example 1



$$V_{PS} = 12 \text{ V}, K = 40 \mu\text{A/V}^2,$$

$$V_{Th} = 1.2 \text{ V}, (W/L)_1 = 2, (W/L)_2 = 8$$


Size R for $I_O = 800 \mu\text{A}$.

$$I_{REF} = \frac{(W/L)_1}{(W/L)_2} I_O = \frac{2}{8} \cdot 800 = 200 \mu\text{A}$$

$$V_{GS1} = V_{Th} + \sqrt{\frac{I}{K} \left(\frac{W}{L}\right)_1} = 1.2 + \sqrt{\frac{200}{40} \cdot 2} = 3.44 \text{ V}$$

$$R = \frac{V_{PS} - V_{GS1}}{I_{REF}} = \frac{12 - 3.44}{0.2} = 42.8 \text{ k}\Omega$$

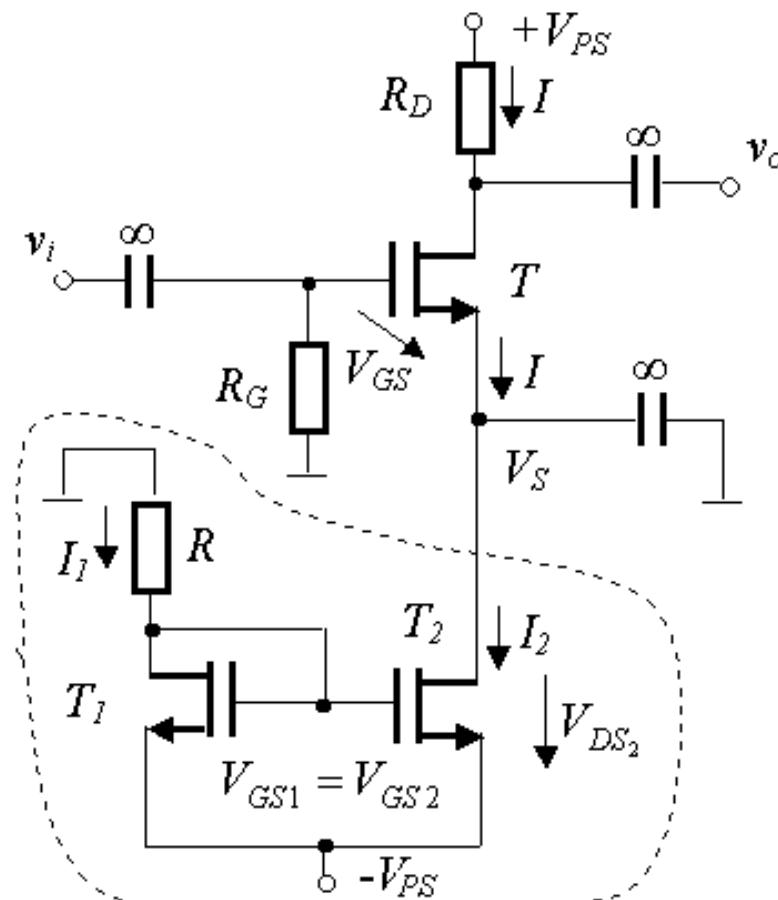➤ MOSFET current multiplier mirrors – example 2



$$V_{PS} = 12 \text{ V}, K = 0.04 \text{ mA/V}^2, R = 42.8 \text{ k}\Omega$$

$$V_{Th} = 1.2 \text{ V}, (W/L)_1 = 2, (W/L)_2 = 10, (W/L) = 4$$


Compute I . What is the operating region for T_1 and T_2 ?

$$\begin{cases} I_1 = \frac{0 - V_{GS1} - (-V_{PS})}{R} = \frac{V_{PS} - V_{GS1}}{R} \\ I_1 = \frac{K}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{Th})^2; \\ I_1 = 0.2 \text{ mA} \end{cases}$$

$$I = I_2 = I_1 \frac{(W/L)_2}{(W/L)_1}$$

$$I = 0.2 \cdot \frac{10}{2} = 1 \text{ mA}$$

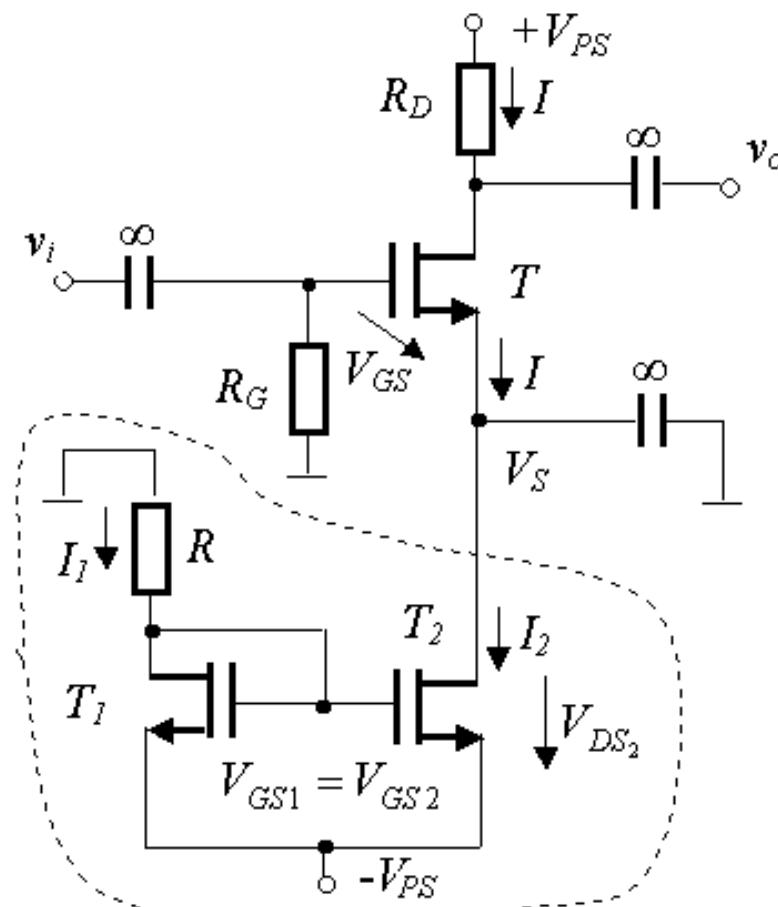➤ MOSFET current multiplier mirrors – example 2



$$V_{PS} = 12 \text{ V}, K = 0.04 \text{ mA/V}^2, R = 42.8 \text{ k}\Omega$$

$$V_{Th} = 1.2 \text{ V}, (W/L)_1 = 2, (W/L)_2 = 10, (W/L) = 4$$

Compute I . What is the operating region for T_1 and T_2 ?

T_1 - MOS diode, always in (a_F)

$$I = \frac{K}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{Th})^2$$


$$V_{GS} = V_{Th} + \sqrt{\frac{I}{\frac{K}{2} \left(\frac{W}{L} \right)}} = 1.2 + \sqrt{\frac{1}{0.04 \cdot 4}} \approx 4.7 \text{ V}$$

$$V_S = -4.7 \text{ V} \quad V_{DS2} = -4.7 - (-12) = 7.3 \text{ V}$$

$$V_{GS2} \approx 3.4 \text{ V} \quad V_{DSsat2} = 2.2 \text{ V}, T_2 - (a_F)$$

➤ Biasing a MOSFET integrated circuit


OPTIONAL

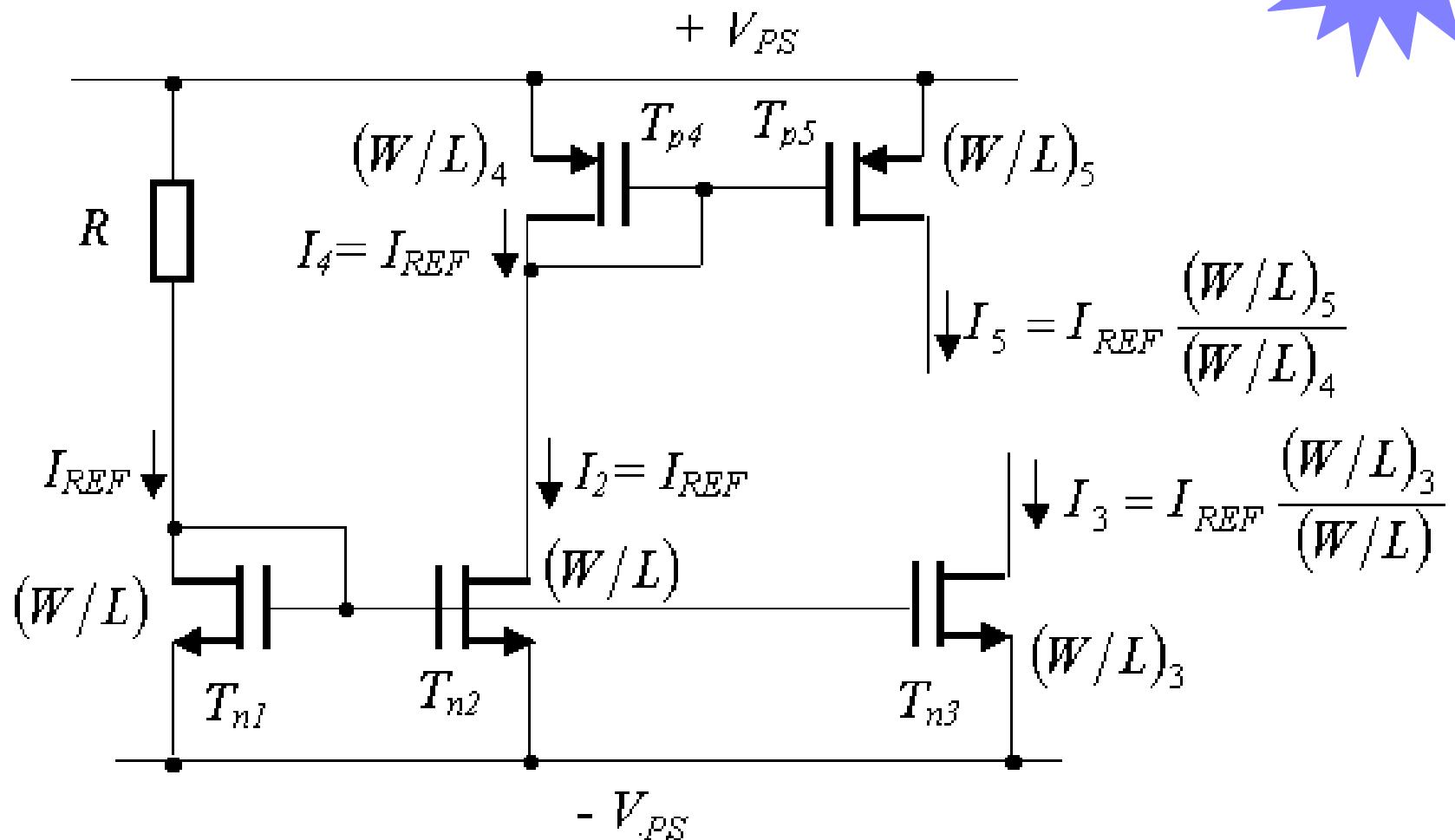

➤ BJT current sources

Current sink

(absorbs current)

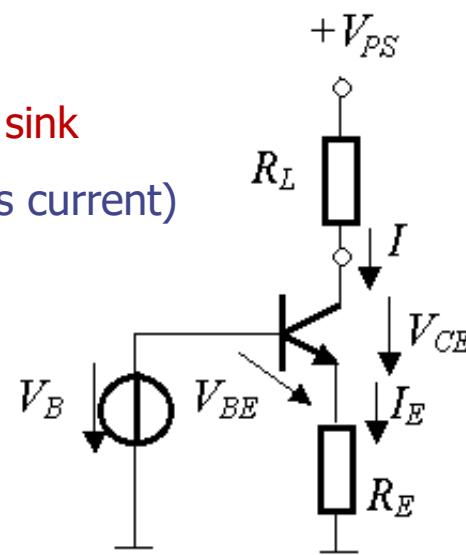

$$R_L I < V_{PS} - V_{CESat} - V_B + V_{BE}$$


$$I = \frac{\beta}{\beta + 1} I_E; \quad I_E = \frac{V_B - V_{BE}}{R_E}$$

$$I = \frac{\beta}{\beta + 1} \frac{V_B - V_{BE}}{R_E} \cong \frac{V_B - V_{BE}}{R_E}$$

T must stay in a_F : $V_{CE} > V_{CESat}$



Current source

(generates current)

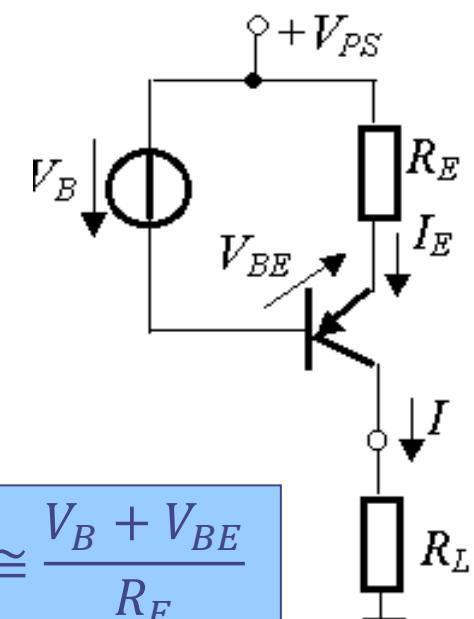

$$I \cong \frac{V_B + V_{BE}}{R_E}$$

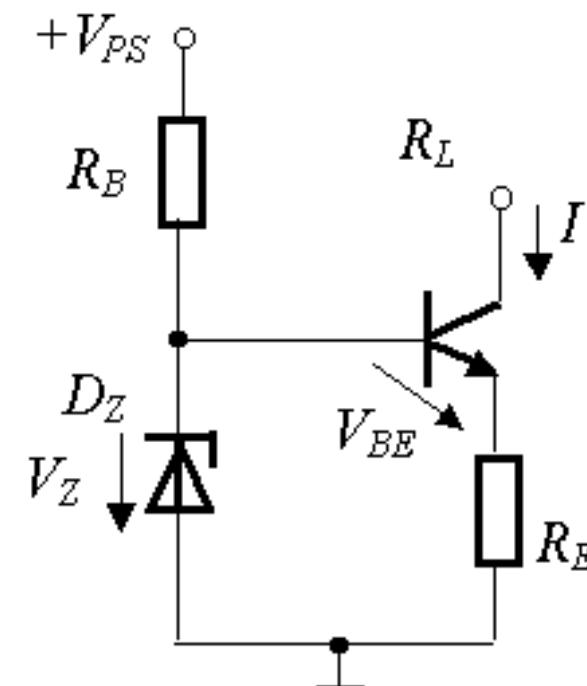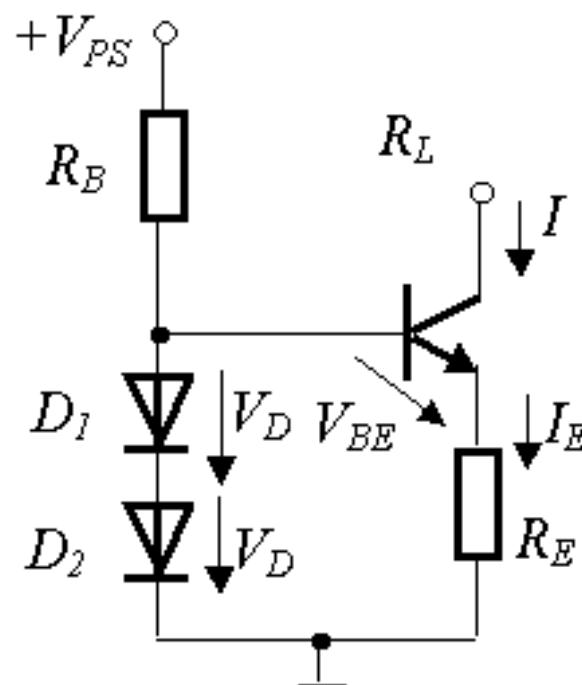➤ BJT current sinks – setting the base potential




$$I = \frac{2V_D - V_{BE}}{R_E} \cong \frac{0.7 \text{ V}}{R_E}$$

$$I = \frac{V_Z - V_{BE}}{R_E}$$

➤ BJT current mirror

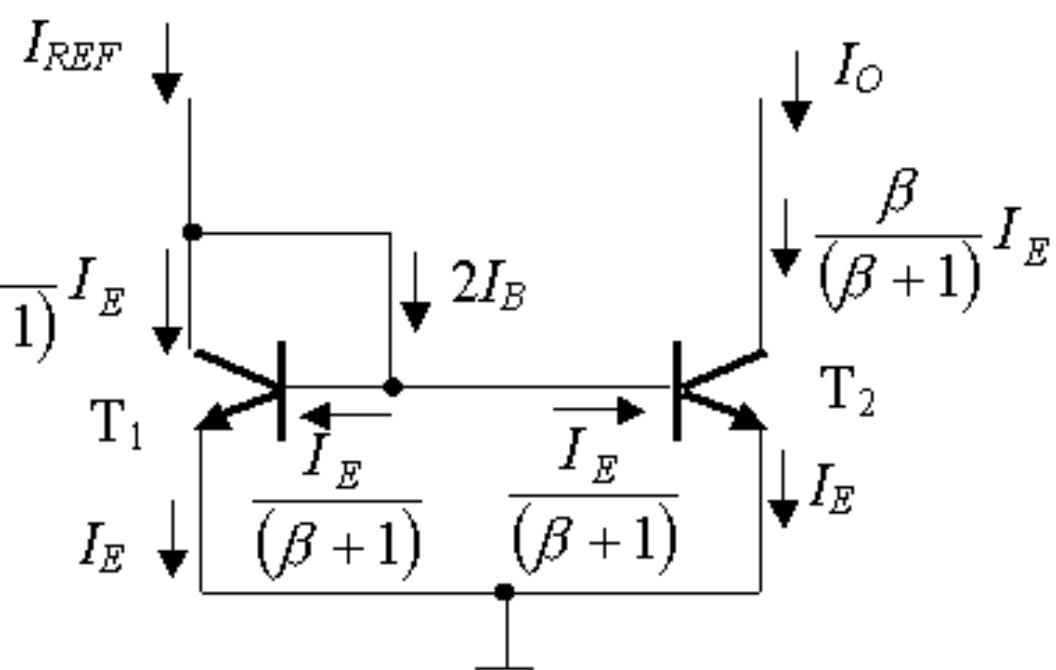
$$I_{REF} = \frac{\beta}{\beta + 1} I_E + 2 \frac{I_E}{\beta + 1} = \frac{\beta + 2}{\beta + 1} I_E$$



$$I_O = \frac{\beta}{\beta + 1} I_E$$

$$I_O = \frac{1}{1 + 2/\beta} I_{REF} \cong I_{REF}$$


➤ BJT current mirror

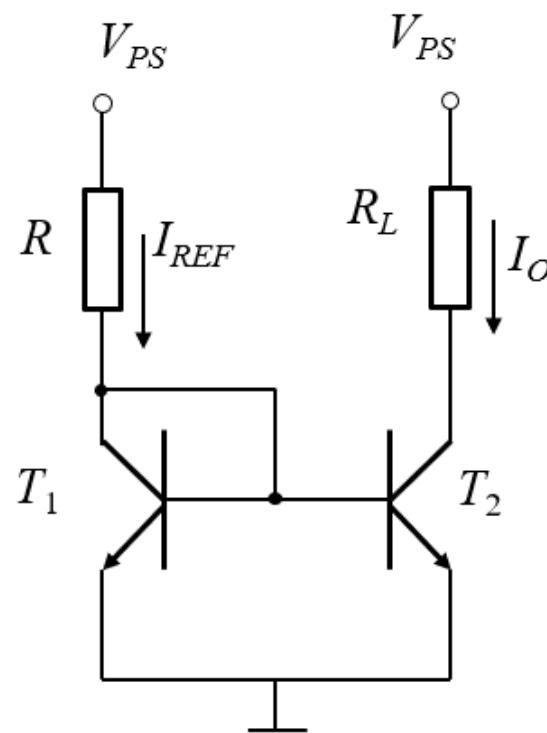

$$I_O = \frac{1}{1 + 2/\beta} I_{REF} \cong I_{REF}$$


$$I_{REF} = \frac{V_{PS} - V_{BE}}{R} = \frac{V_{PS} - 0.7}{R}$$

➤ Biasing a BJT integrated circuit

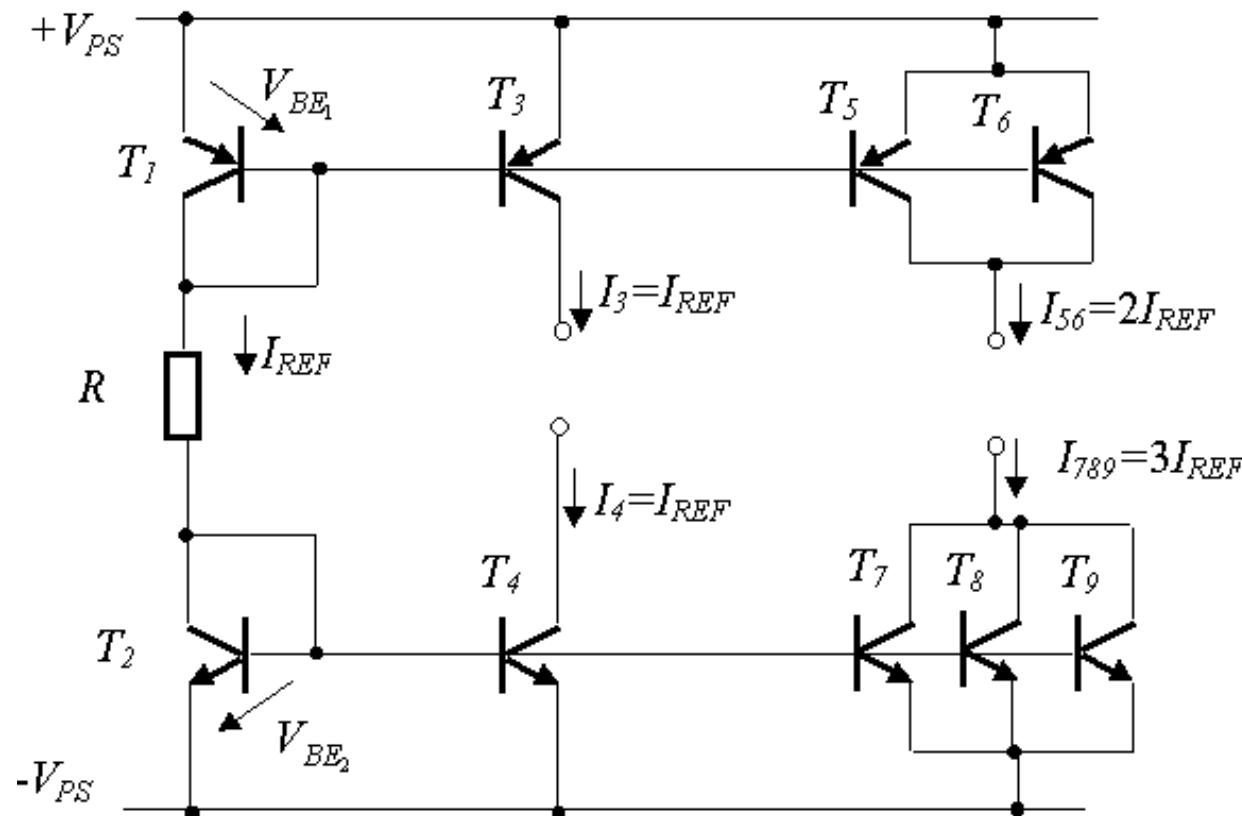OPTIONAL

$$I_{REF} = \frac{2V_{PS} - V_{BE_1} - V_{BE_2}}{R}$$

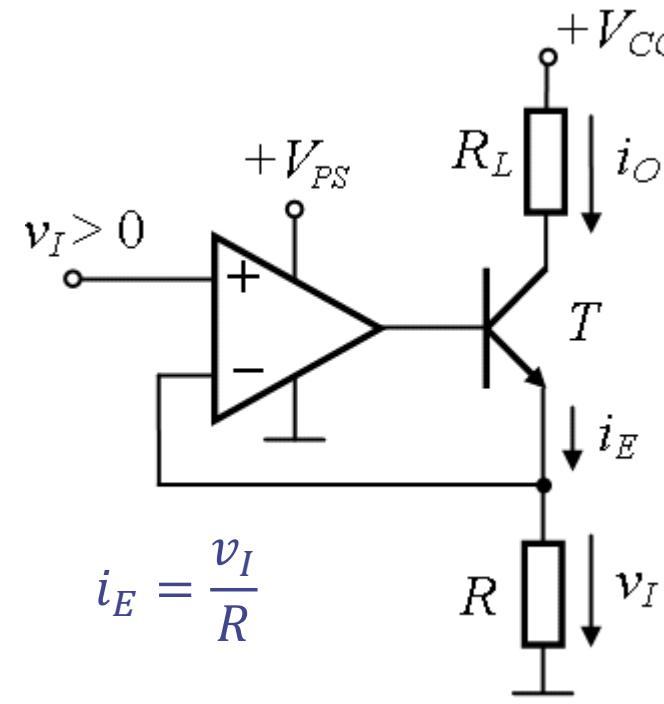
➤ Current sources w/ OpAmp and T, floating load



Negative feedback NF

$$i_O = \frac{\beta}{\beta + 1} \frac{v_I}{R} \approx \frac{v_I}{R}$$

$$R_L i_O < V_{CC} - v_I - V_{CEsat}$$

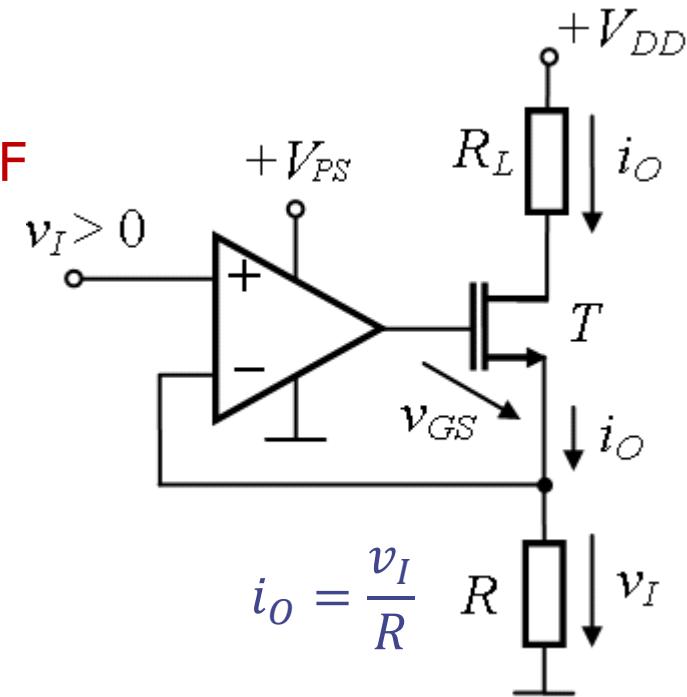


Adjustable current sources:

- modifying v_I - voltage-controlled current source
- a potentiometer in series with R .

See Seminar 3 & Lab 6

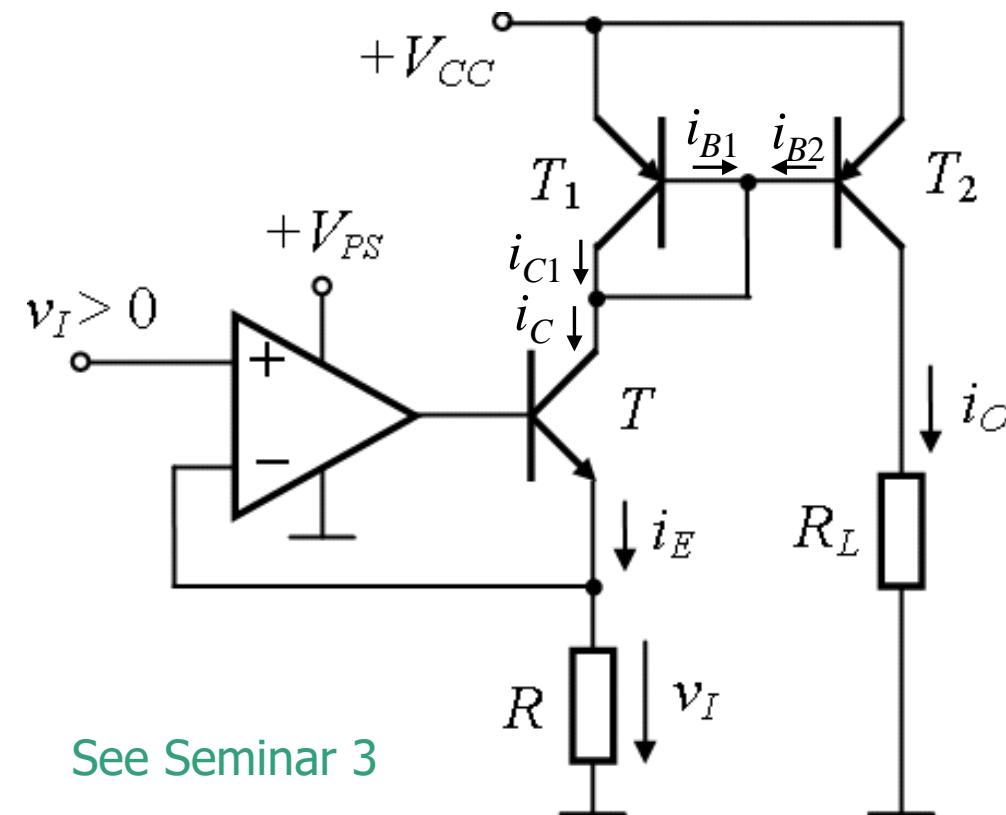➤ Current source w/ OpAmp and T, nonfloating load



See Seminar 3

$$i_O = \frac{\beta}{\beta + 1} \frac{1}{1 + \frac{2}{\beta_1}} \frac{v_I}{R} \approx \frac{v_I}{R}$$

T_1 and T_2 - identical transistors

$$i_{B1} = i_{B2} \quad i_O = \beta_1 i_{B2}$$

$$i_C = i_{C1} + 2i_{B2} = \beta_1 i_{B1} + 2i_{B2}$$

$$i_C = i_{B2}(\beta_1 + 2) \quad i_{B2} = \frac{i_c}{\beta_1 + 2}$$

$$i_O = \beta_1 \frac{i_c}{\beta_1 + 2} = i_c \frac{\beta_1}{\beta_1 + 2}$$

$$i_O = i_c \frac{1}{1 + \frac{2}{\beta_1}} \quad i_c = \frac{\beta}{\beta + 1} i_E$$

$$i_O = \frac{\beta}{\beta + 1} \frac{1}{1 + \frac{2}{\beta_1}} i_E \quad i_E = \frac{v_I}{R}$$

Summary

- Frequency response of transistor amplifiers
- Current sources
- Current mirrors

Next week: Power amplifiers – class A, B, AB