

FUNDAMENTAL ELECTRONIC CIRCUITS

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C6 – Power amplifiers – class A, B, AB

Contents


- Intro
- Class A power amplifier
- Class B power amplifier
- Class AB power amplifier

➤ To begin with

- What is a power amplifier? How is it different from a voltage amplifier?
- Where are power amplifiers used? What requirements do they need to meet?
- How is the performance of a power amplifier measured? Who gives the name/class?
- Power amplifiers w/ BJT or MOSFET?
Both are possible, but we're studying BJT power amplifiers only.

➤ What is a power amplifier?

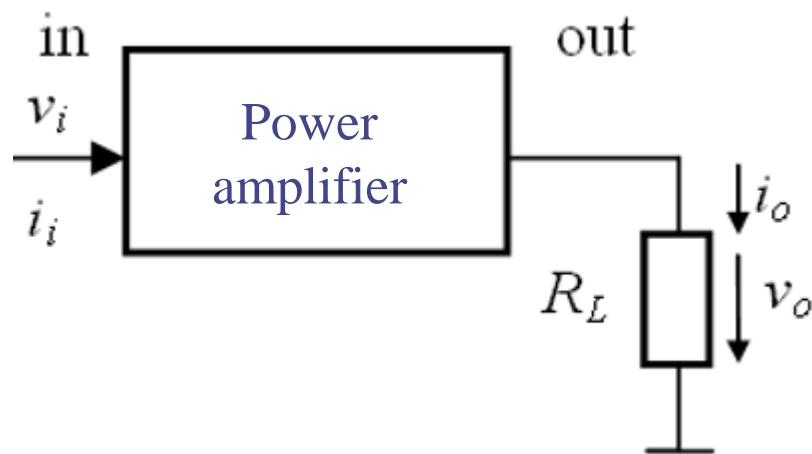- = a circuit which provides little or no voltage gain, but **significant** current gain
- = large signal or output amplifier




$$v_o \approx v_i \quad A_v \approx 1$$



$$i_o > i_i \quad A_i > 1$$

$$\begin{aligned} p_o &= v_o \cdot i_o \\ p_i &= v_i \cdot i_i \\ p_o &> p_i \end{aligned}$$


➤ Placement & usage

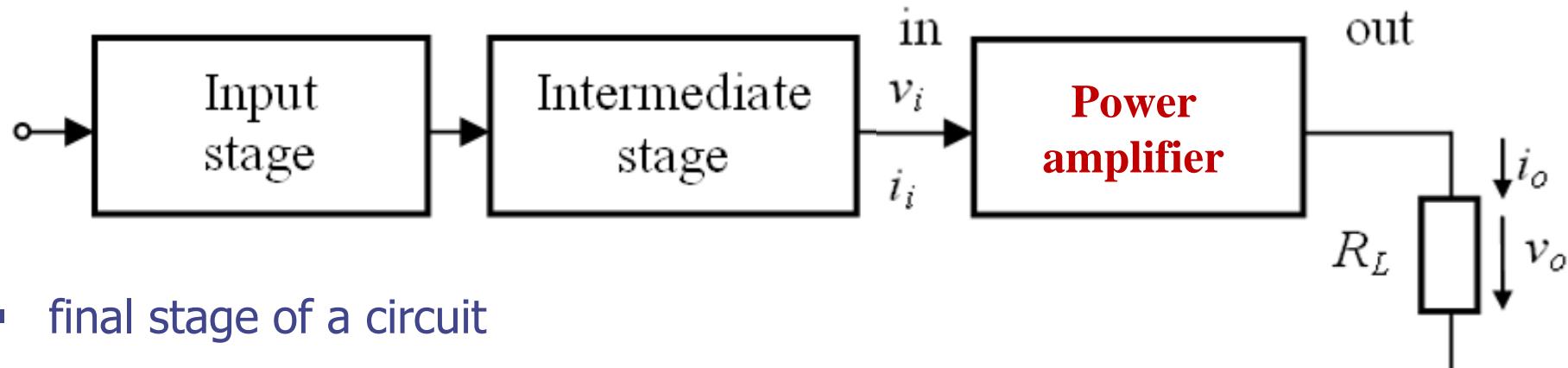

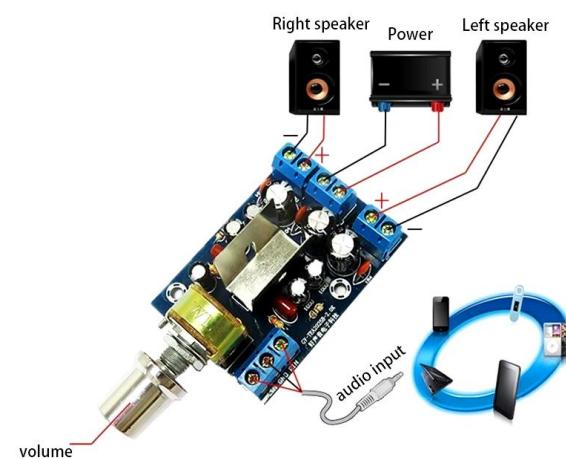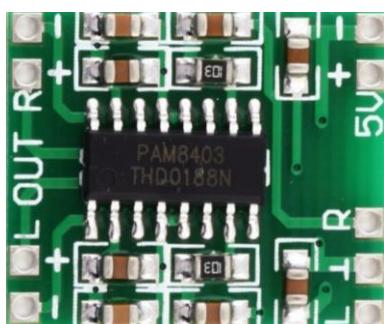- final stage of a circuit
- usage: **audio systems** (loudspeakers, headphones) – to increase sound volume




➤ Placement & usage

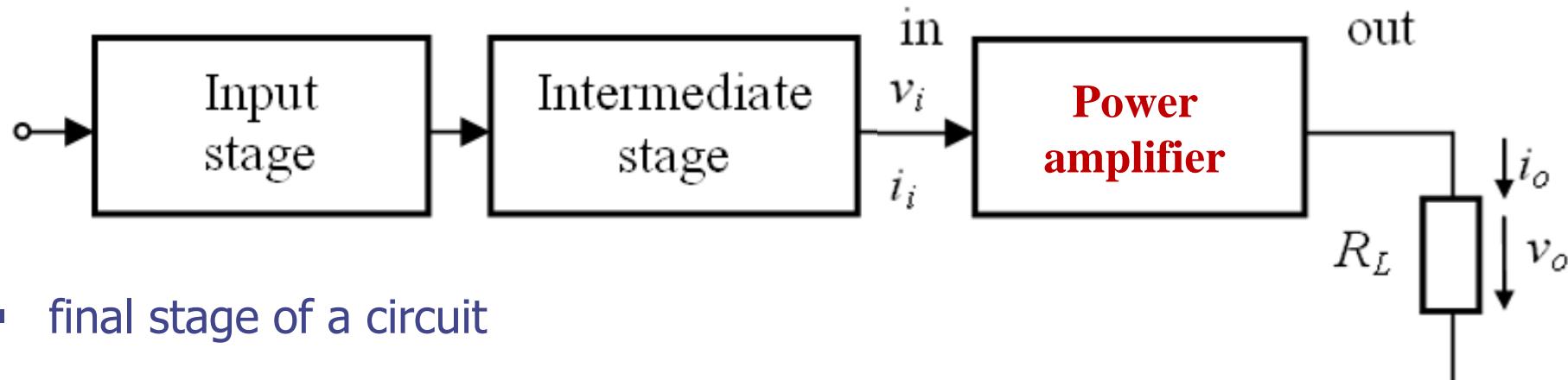

- final stage of a circuit
- usage: **radiofrequency (RF) transmitters** – to increase the power of the transmitted signal (communications systems)



Transmitter

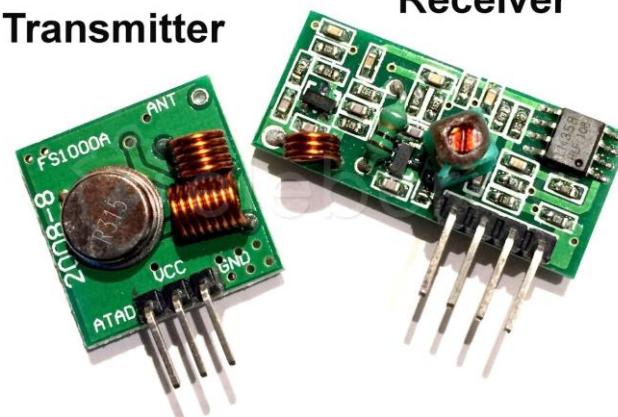

Receiver

➤ Requirements

- low output resistance (can deliver output signal without loss of gain)
- (very) high efficiency (enhances battery life)
- good linearity (non distorted output signal)

$$THD = \frac{\sqrt{V_{RMS2}^2 + V_{RMS3}^2 + V_{RMS4}^2 + \dots}}{V_{RMS1}}$$

THD < 1% for Hi-Fi amplifiers


RMS voltage ≡ effective voltage

THD – total harmonic distortion

RMS – root mean square

V_{RMSi} - RMS value of the ith harmonic of the original signal, i = 2, 3, 4, ...

➤ Power transfer

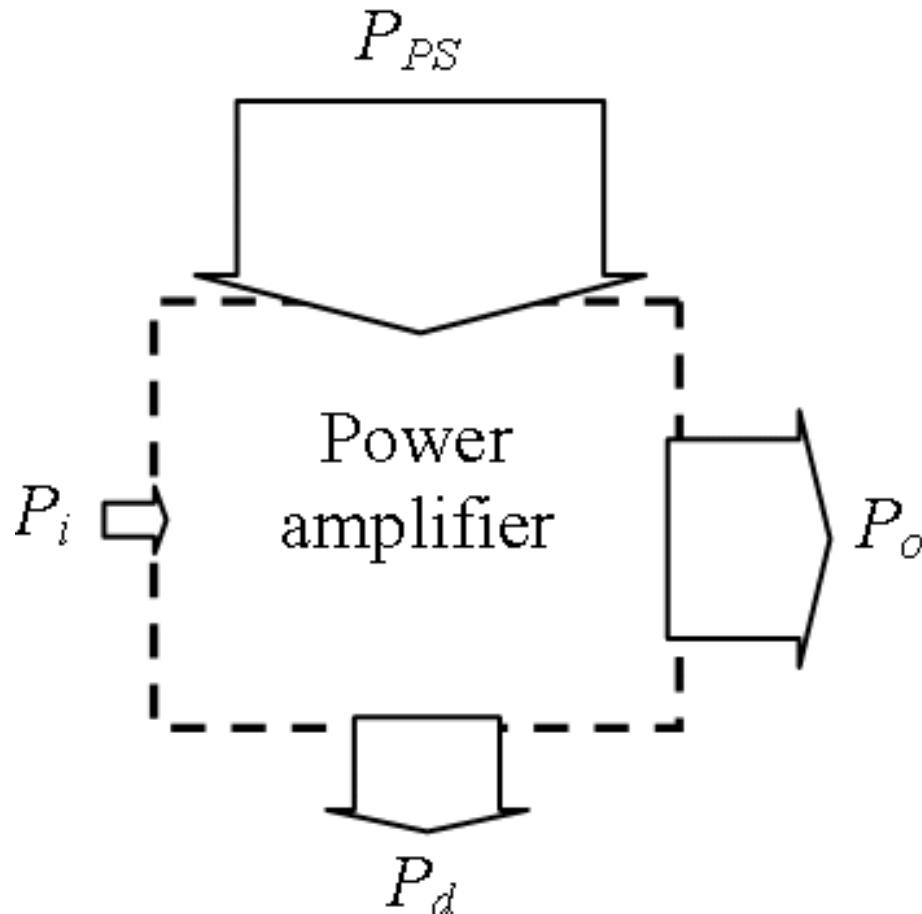

$$P_i + P_{PS} = P_d + P_o$$

P_i - power from the input source

P_{PS} - power drawn from the power supplies

P_d - dissipated power (heat)

P_o - power delivered at the output (on R_L)

$$P_i \ll P_{PS}$$


$$\eta = \frac{P_o}{P_{PS}}$$

efficiency of the stage

$$\eta [\%] \text{ or } \eta \in (0, 1)$$

➤ Power gain

real input voltage source ($R_s \neq 0$)

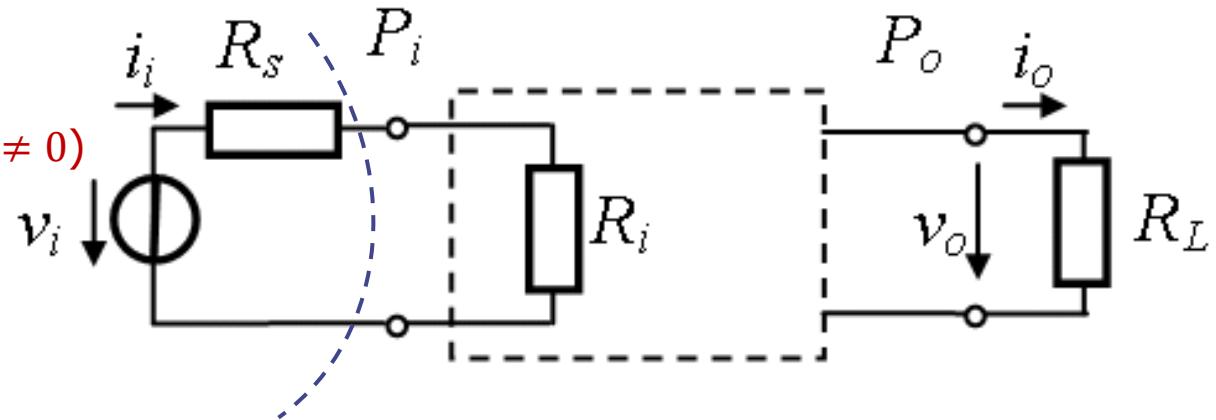

Assume sinusoidal regime, average power:

$$P_o = \left(\frac{\hat{V}_o}{\sqrt{2}} \right)^2 \frac{1}{R_L} = \frac{\hat{V}_o^2}{2R_L}$$

$$P_i = R_i \left(\frac{\hat{I}_i}{\sqrt{2}} \right)^2 = R_i \frac{\hat{V}_i^2}{2(R_i + R_s)^2}$$

$$A_p = \frac{P_o}{P_i} = \left(\frac{\hat{V}_o}{\hat{V}_i} \right)^2 \frac{(R_i + R_s)^2}{R_i R_L}$$

If $R_i \gg R_s$

$$A_p \approx \left(\frac{\hat{V}_o}{\hat{V}_i} \right)^2 \frac{R_i}{R_L}$$


➤ Power amplifier classes

The classes are defined in relation to the interval of time in which the amplifier device (transistor) is **active**, expressed as a **fraction of the period** of the input signal.

Classes: A, B, AB, C, D, E, F, G, I, S, T, etc

efficiency of the stage

$$\eta = \frac{P_o}{P_{PS}}$$

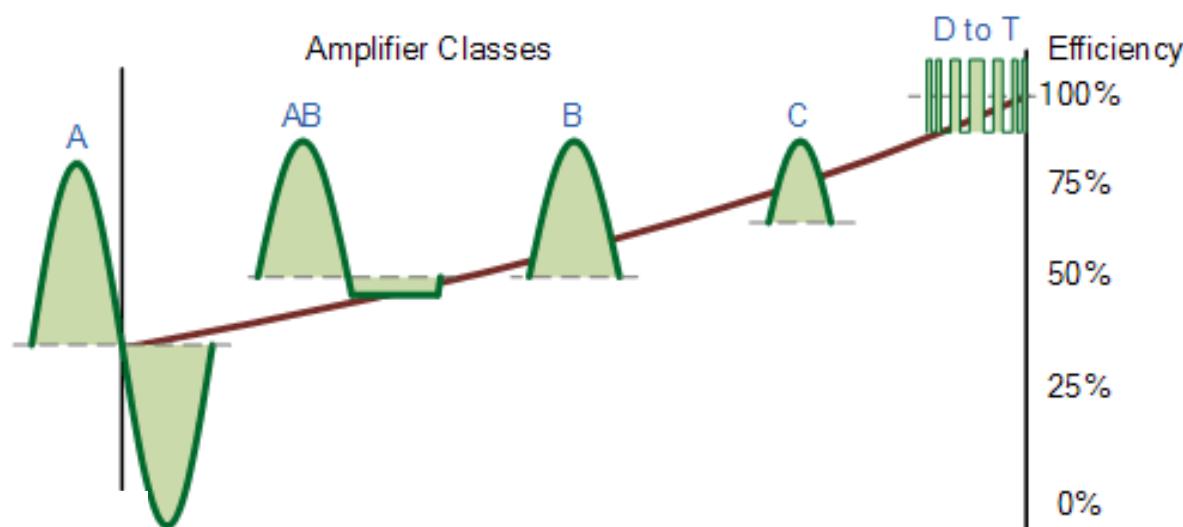


The less time T is active during a period, the higher the efficiency

➤ Power amplifier classes

Class	Conduction interval	Max. efficiency	Notes
A	$t_c = T$	25%	Small-signal amplifiers
B	$t_c = T/2$	78.5%	Audio amplifiers; crossover distortions
AB	$T/2 < t_c < T$	78.5%	Audio amplifiers; no crossover distortions
C	$t_c < T/2$	90%	RF transmitters
D	switching mode	80%-95%	PWM and passive filtering
E	switching mode	90%	RF transmitters
G	more efficient version of class AB		
H	similar to class G	100%	Power supply modulated by the signal
I	similar to class B, switching mode		Interleaved PWM amplifier
S, T	similar to class D, switching mode		

Classes A, B, AB – C6, Lab 7, Seminar 4; Class D – C13 (in 2025 ☺)

➤ Class A - circuit

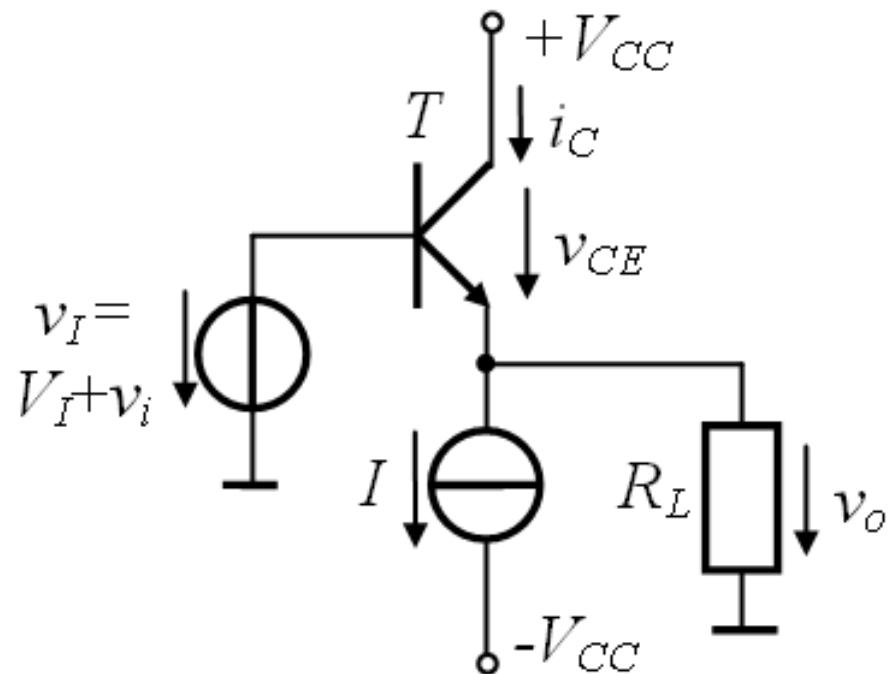

Type of configuration?

emitter **follower** for variable input voltage


common collector (CC) topology

$V_I = 0.7 \text{ V}$ – to bias T

$v_o \approx v_i$

How can we implement the current source?

➤ Class A – operation

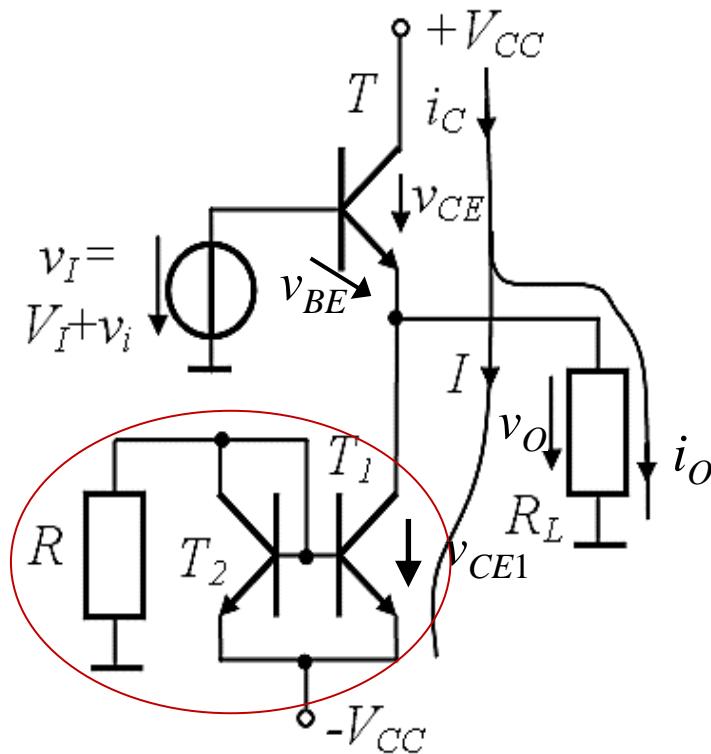

Current source

$$I \downarrow \ominus \quad I = \frac{V_{CC} - V_{BE2}}{R}$$

$$\mathbf{v}_O = v_I - v_{BE} = v_I - 0.7$$

$$v_O = V_{CC} - v_{CE}$$

$$v_O = v_{CE1} - V_{CC}$$

$$v_I \uparrow, \quad v_O \uparrow, \quad v_{CE} \downarrow$$

$$\mathbf{v}_{Omax} = V_{CC} - v_{CEsat} \approx V_{CC}$$

T – reaches saturation

$$v_{Imax} = v_{Omax} + 0.7 \approx V_{CC} + 0.7$$

$$v_I \downarrow, \quad v_O \downarrow, \quad v_{CE1} \downarrow$$


$$\mathbf{v}_{Omin} = -V_{CC} + v_{CE1sat} \approx -V_{CC}$$

T_1 – reaches saturation

$$v_{Imin} = v_{Omin} + 0.7 \approx -V_{CC} + 0.7$$

➤ Class A – VTC


$$v_O = v_I - v_{BE} = v_I - 0.7$$

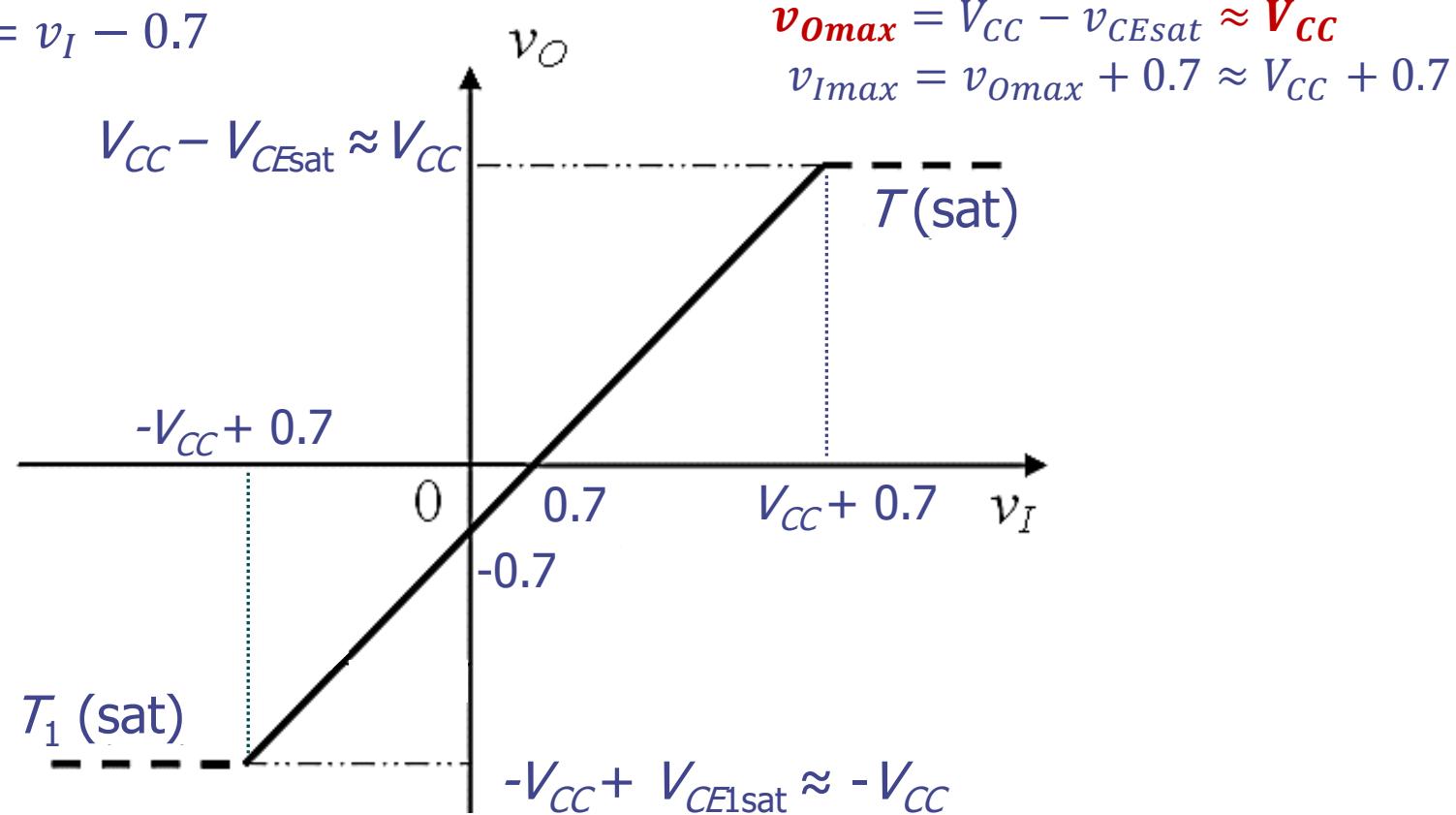

$$v_{Omin} = -V_{CC} + v_{CE1sat} \approx -V_{CC}$$

$$v_{Imin} = v_{Omin} + 0.7 \approx -V_{CC} + 0.7$$

➤ Class A – maximum output voltage swing

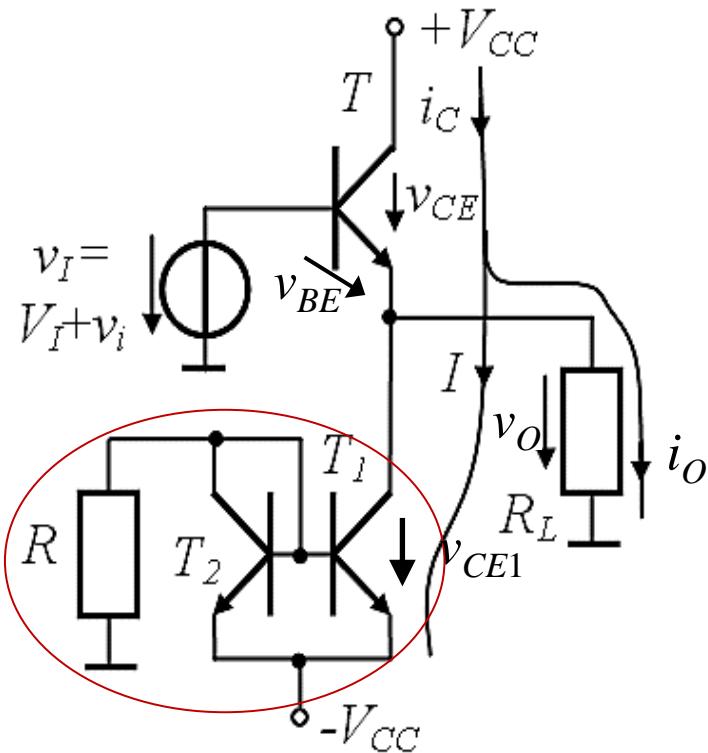

Current source

$$I \downarrow \ominus \quad I = \frac{V_{CC} - V_{BE2}}{R}$$

$$\mathbf{i}_C = I + i_O = I + \frac{v_O}{R_L}$$

$$\mathbf{i}_{Cmax} = I + \frac{v_{Omax}}{R_L} = I + \frac{V_{CC}}{R_L}$$


$$\mathbf{i}_{Cmin} = I + \frac{v_{Omin}}{R_L} = I - \frac{V_{CC}}{R_L}$$

$T - (a_F)$ implies $i_{Cmin} > 0$

$$I - \frac{V_{CC}}{R_L} > 0$$

$$R_L I > V_{CC}$$

➤ Class A – powers

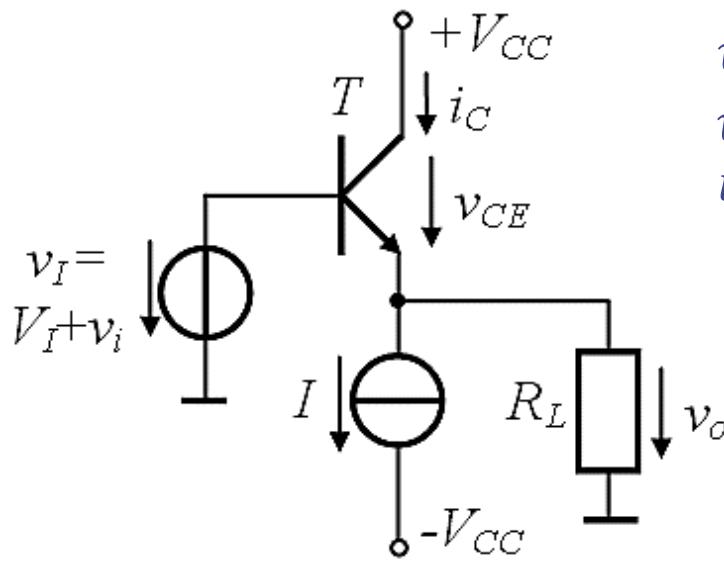

$$\begin{aligned}v_i(t) &= \hat{V}_i \sin \omega t \\v_o(t) &= \hat{V}_o \sin \omega t \\i_o(t) &= \hat{I}_o \sin \omega t\end{aligned}$$

$$\hat{I}_o = \frac{\hat{V}_o}{R_L}$$

Average power from the power supplies

$$P_{PS} = P_{PS+} + P_{PS-} = V_{CC} i_{C, average} + V_{CC} I$$


$$i_C(t) = I + \frac{v_o(t)}{R_L} = I + \frac{\hat{V}_o \sin \omega t}{R_L}$$

$$i_{C, average} = I$$

$$P_{PS} = 2V_{CC}I$$

Same power is consumed regardless the magnitude of the input voltage (even if no input variable voltage is applied) => reduced circuit efficiency.

➤ Class A – powers

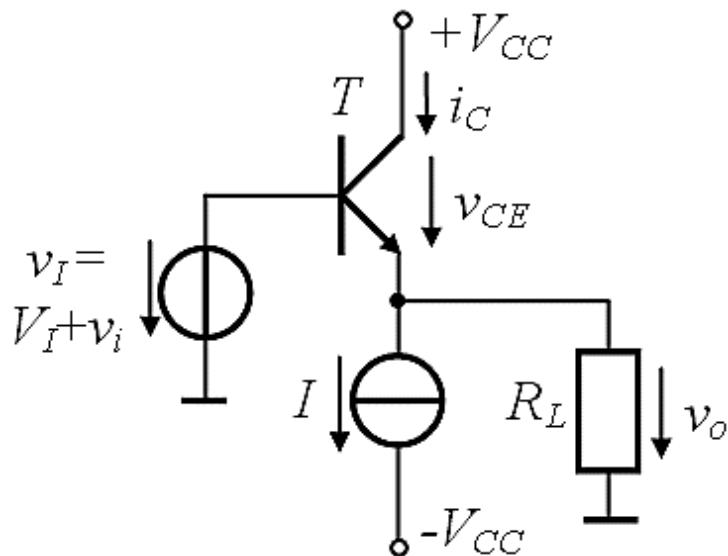

Instantaneous output power

$$p_o(t) = i_o(t)v_o(t) = \frac{v_o^2(t)}{R_L} = \frac{\hat{V}_o^2(\sin \omega t)^2}{R_L}$$

Average output power


$$P_o = \frac{1}{T} \int_0^T \frac{\hat{V}_o^2}{R_L} \left(\sin \frac{2\pi}{T} t \right)^2 dt$$

For sinusoidal output voltage and current:

$$P_o = v_{o_rms} i_{o_rms} = \frac{\hat{V}_o}{\sqrt{2}} \frac{\hat{I}_o}{\sqrt{2}} = \frac{\hat{V}_o \hat{I}_o}{2} = \frac{\hat{V}_o^2}{2R_L}$$

$$P_o = \frac{\hat{V}_o^2}{2R_L}$$

➤ Class A – efficiency

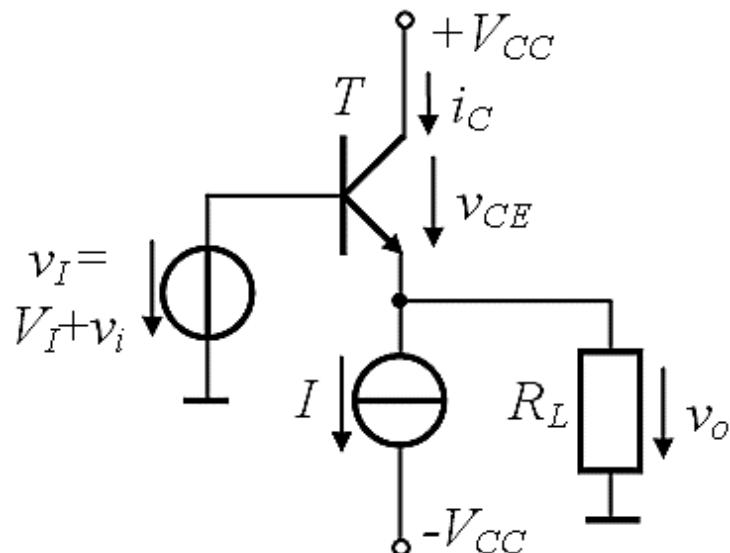

Average efficiency

$$\eta = \frac{P_o}{P_{PS}} = \frac{\frac{\hat{V}_o^2}{2R_L}}{2V_{CC}I} = \frac{\hat{V}_o^2}{4V_{CC}R_L I}$$

Maximum average efficiency

$$\hat{V}_o = V_{CC} \quad \eta_{\max}$$

R_L as small as possible, but keeping the maximum output swing ($R_L I \geq V_{CC}$)


$$R_L I = V_{CC}$$

$$\eta_{\max} = \frac{P_o}{P_{PS}} = \frac{V_{CC}^2}{4V_{CC}V_{CC}} = \frac{1}{4}$$

$$\eta_{\max} = 25\%$$

$$\text{IRL } \eta \leq 20\%$$


➤ Class A – waveforms

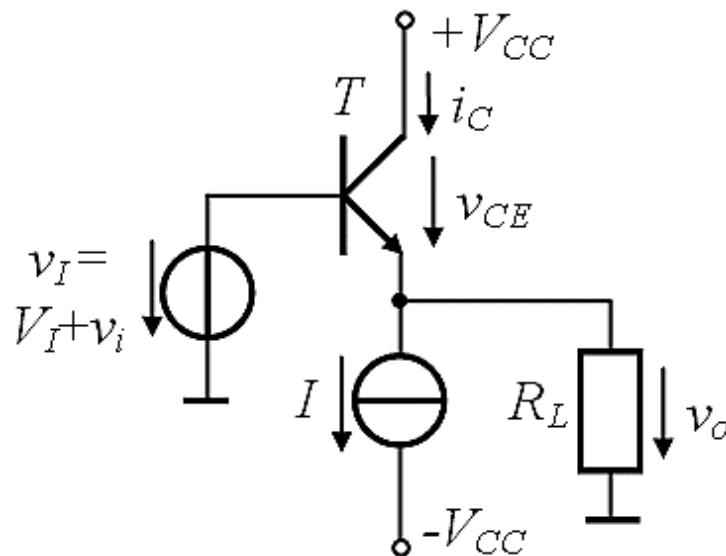


Assume the criteria for maximum efficiency are met:

$$\hat{V}_o = V_{CC}$$

$$R_L I = V_{CC}$$

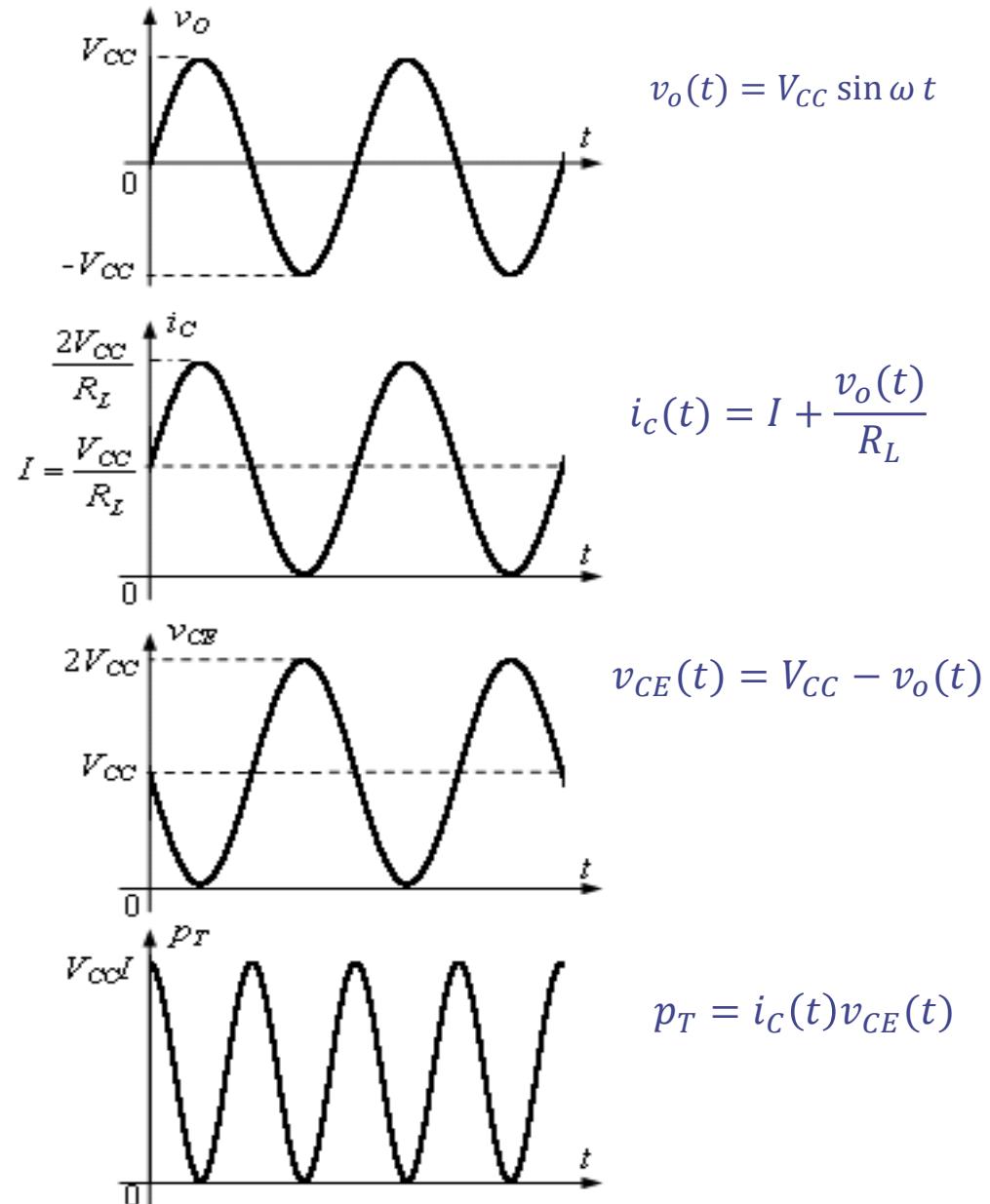

➤ Class A – summary

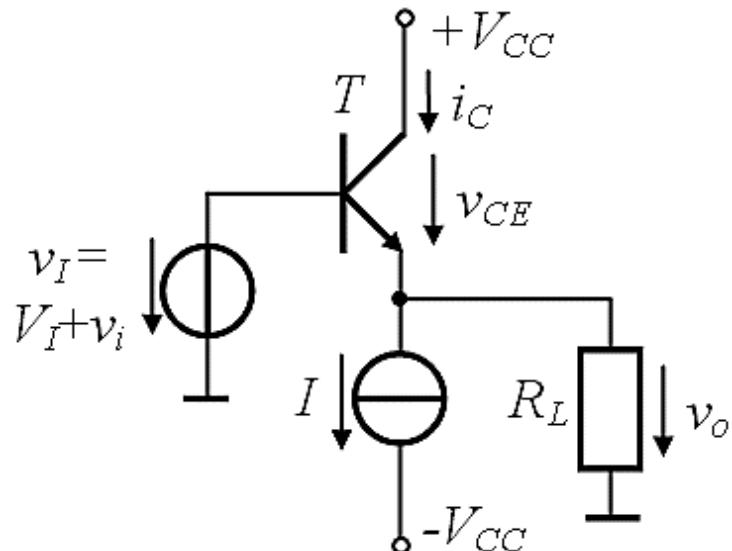

$$P_o = \frac{\hat{V}_o^2}{2R_L}$$


$$P_{PS} = 2V_{CC}I$$

$$\eta_{\max} = \frac{1}{4} = 25\%$$

- emitter **follower** for variable input voltage
- **common collector (CC)** topology
- T – always on

$$v_o \approx v_i$$

➤ Class A – example

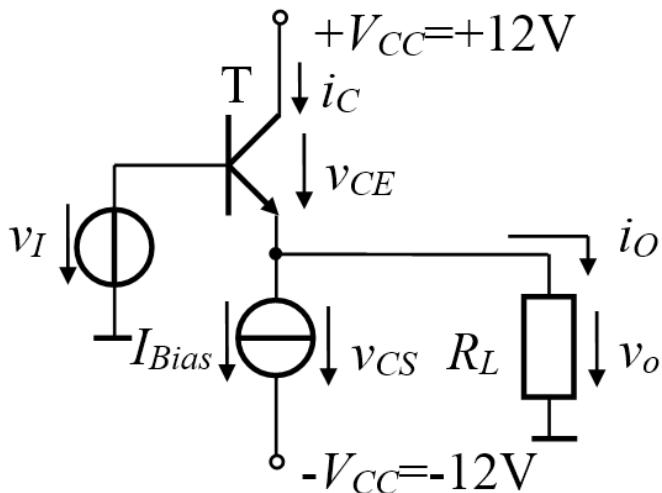


$$v_{BE, \text{on}} = 0.7 \text{ V}, I_{bias} = 0.2 \text{ A}, R_L = 75 \Omega,$$

$$v_I(t) = 0.7 + 6\sin\omega t [\text{V}]$$

- a) Plot the VTC $v_o(v_I)$. The current source is active for $v_{CS} > 0V$. Indicate the transistor state (*off*, *a_F*, *exc*) for every region of the VTC.
- b) Plot $v_I(t)$, $v_o(t)$, $i_o(t)$, $v_{CE}(t)$ and $i_C(t)$.
- c) What is the average value of the power dissipated by the load and average efficiency?
- d) Explain why the average efficiency is less than the maximum average efficiency possible for this stage.

➤ Class B – circuit

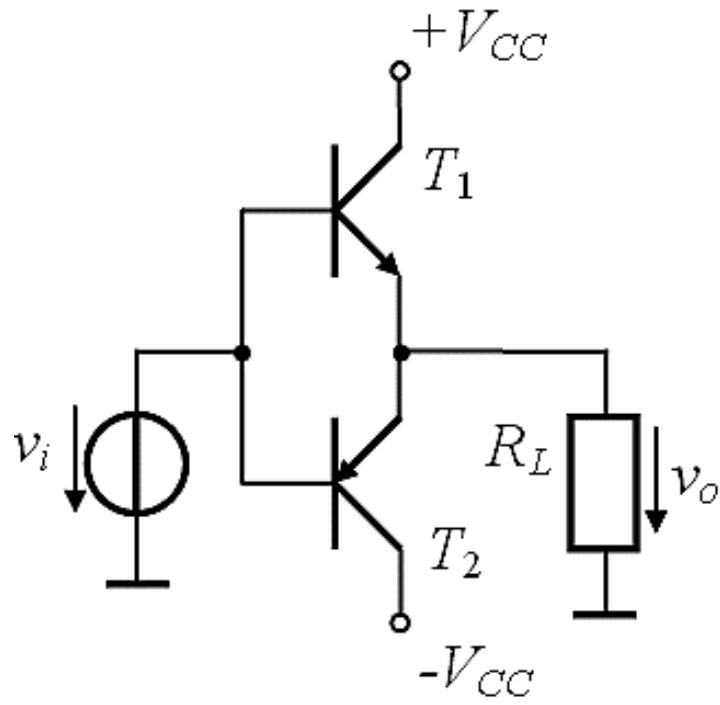

- each transistor conducts for half a period
- complementary pair of transistors
- **push-pull arrangement**

$$v_o = ?$$



$$v_{o\max} = ?$$

$$v_{o\min} = ?$$

Can T_1 , T_2 be (on)/(off) at the same time?

➤ Class B – operation
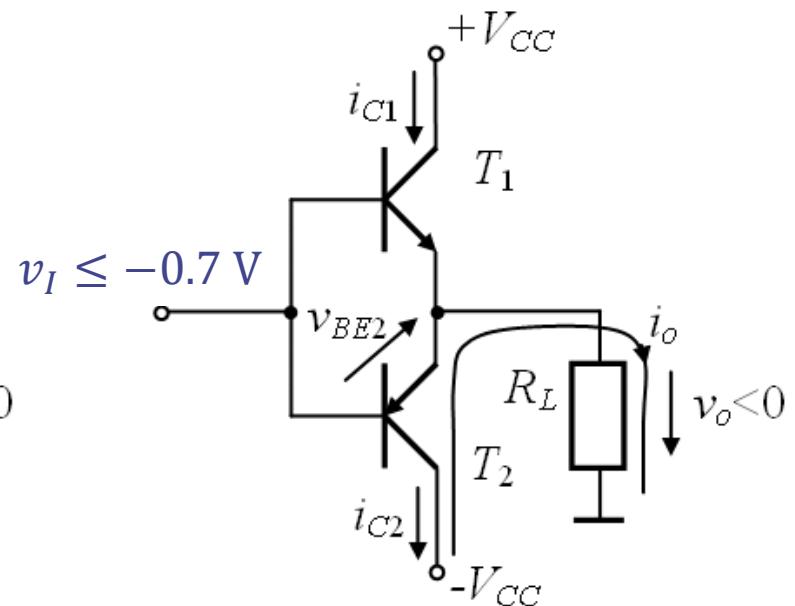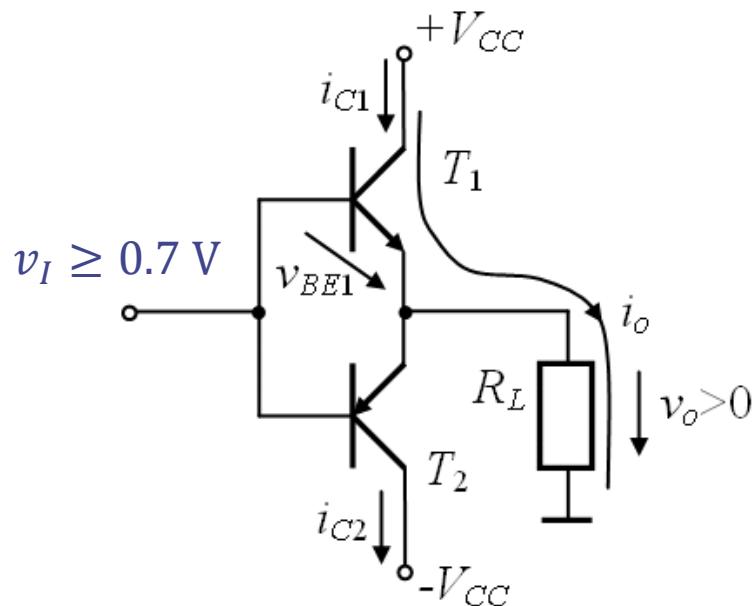
$$v_I \in (-0.7 \text{ V}; +0.7 \text{ V}) \quad T_{1,2} - (\text{off}) \quad v_O = 0 \text{ V} \quad i_O = 0$$



$$v_I \geq 0.7 \text{ V} \quad T_1 - (\text{on}), T_2 - (\text{off})$$

$$v_O = v_I - v_{BE1} = v_I - 0.7 \text{ V}$$

$$\begin{aligned} i_O &> 0 & i_{C1} &= i_O & i_{C2} &= 0 \\ v_{Omax} &= V_{CC} - v_{CE1sat} & \approx V_{CC} \end{aligned}$$


$$v_I \leq -0.7 \text{ V} \quad T_1 - (\text{off}), T_2 - (\text{on})$$

$$v_O = v_I - v_{BE2} = v_I + 0.7 \text{ V}$$


$$\begin{aligned} i_O &< 0 & i_{C2} &= -i_O & i_{C1} &= 0 \\ v_{Omin} &= -V_{CC} + v_{CE2sat} & \approx -V_{CC} \end{aligned}$$

➤ Class B – VTC
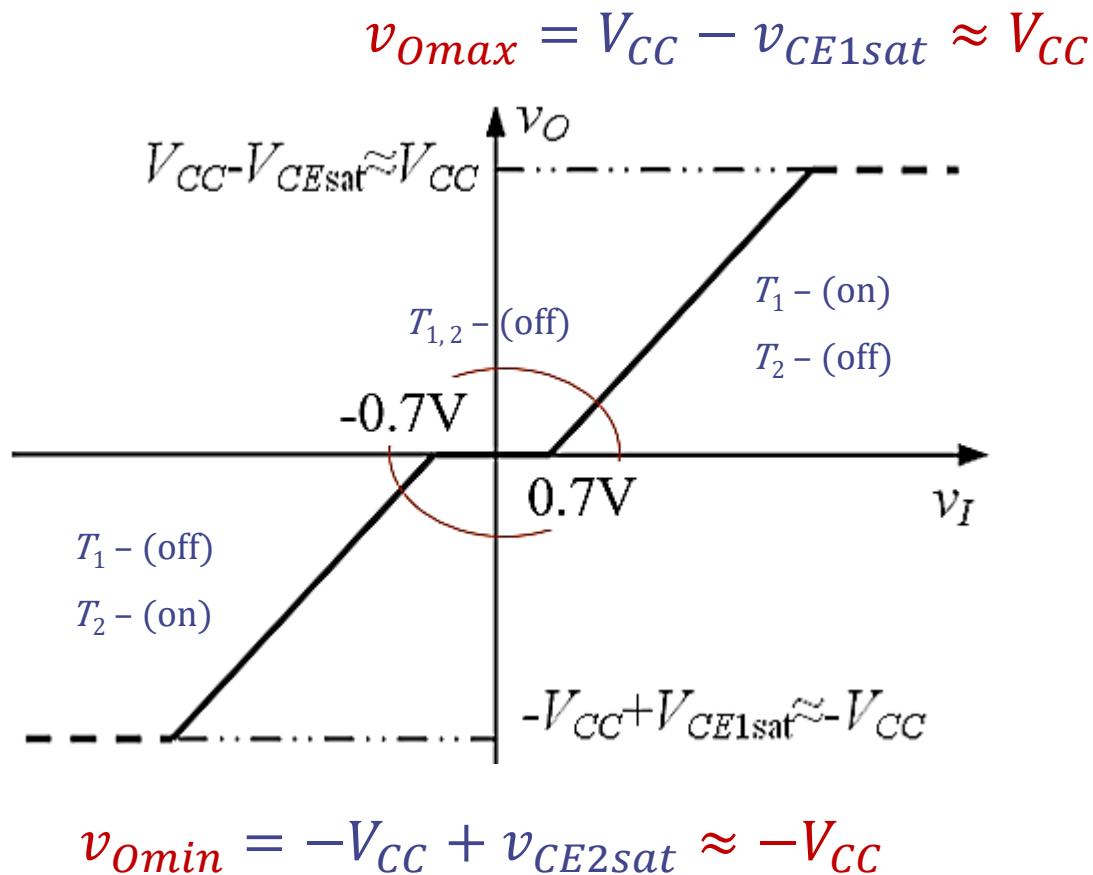
$$v_o = \begin{cases} v_I - 0.7 \text{ V}, & v_I \geq 0.7 \text{ V} \\ 0, & v_I \in (-0.7 \text{ V}; +0.7 \text{ V}) \\ v_I + 0.7 \text{ V}, & v_I \leq -0.7 \text{ V} \end{cases}$$



➤ Class B – waveforms

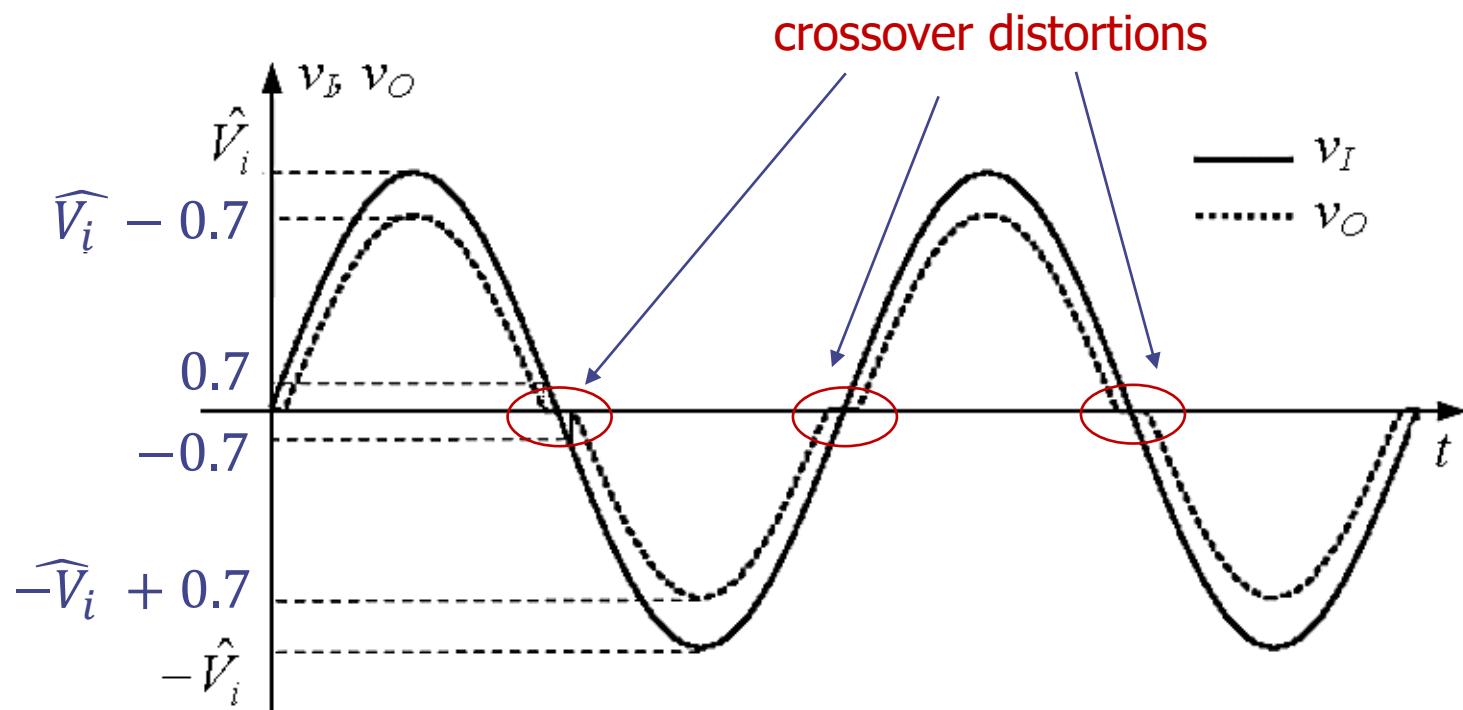

➤ Class B – waveforms


- assume \hat{V}_o – high enough to neglect crossover distortions

$$v_o(t) = \hat{V}_o \sin \omega t$$



$$\hat{V}_o = V_{CC}$$

$$i_{C1}(t) = v_o(t)/R_L$$

T_1 – (on)

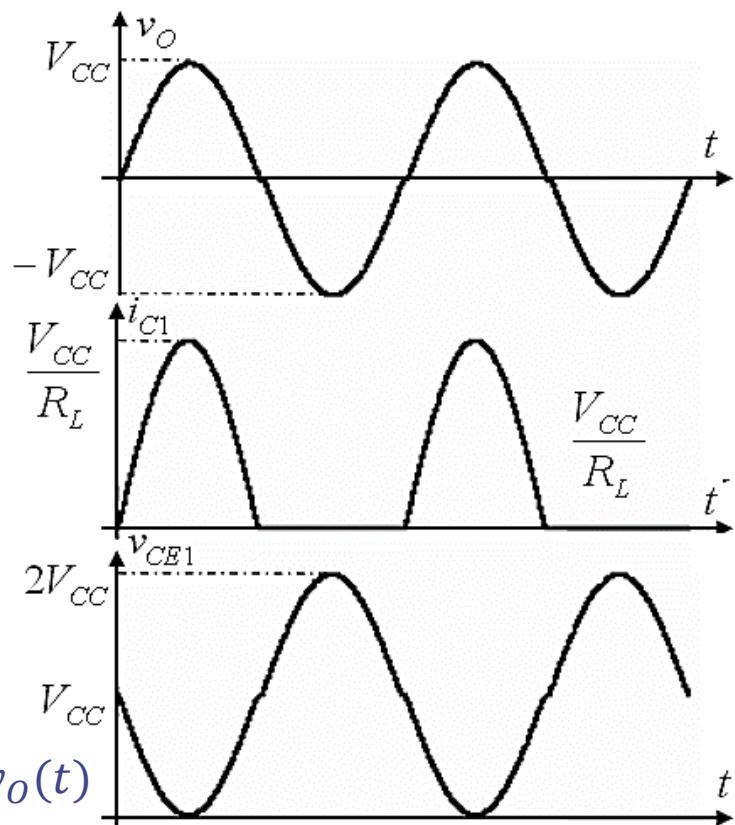

$$v_{CE1}(t) = V_{CC} - v_o(t)$$

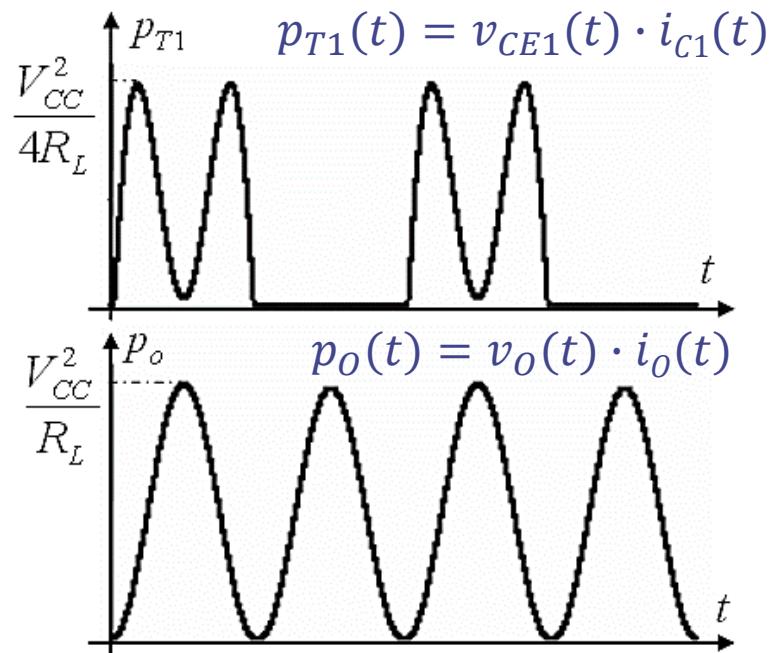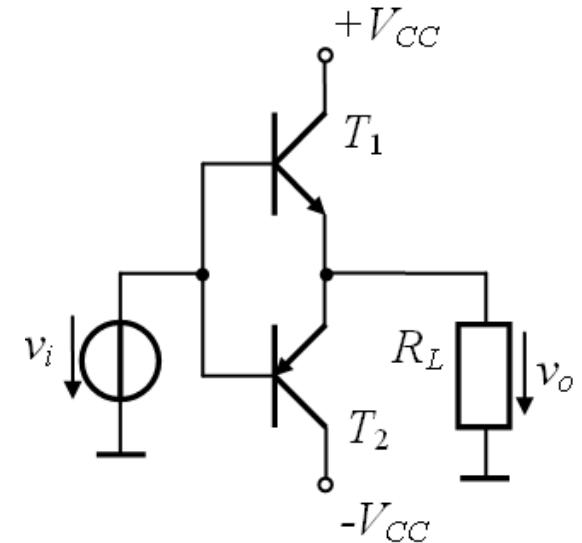

$$p_{T1}(t) = v_{CE1}(t) \cdot i_{C1}(t)$$

$$p_o(t) = v_o(t) \cdot i_o(t)$$

➤ Class B – powers & efficiency

Average power from the power supplies

$$P_{PS}^+ = \frac{1}{T} \int_0^T V_{CC} i_{C1}(t) dt = \frac{1}{T} \int_0^{T/2} V_{CC} \frac{\hat{V}_o \sin \omega t}{R_L} dt = \frac{1}{T} \frac{V_{CC} \hat{V}_o}{R_L} \int_0^{T/2} \sin \frac{2\pi}{T} t dt$$

$$P_{PS}^+ = \frac{1}{\pi} \frac{V_{CC} \hat{V}_o}{R_L}$$

$$P_{PS} = P_{PS}^+ + P_{PS}^- = \frac{2}{\pi} \frac{V_{CC} \hat{V}_o}{R_L}$$

For $\hat{V}_o = V_{CC}$

$$P_{PSmax} = \frac{2}{\pi} \frac{V_{CC}^2}{R_L}$$

Average output power

$$P_o = V_{O rms} I_{O rms} = \frac{\hat{V}_o^2}{2R_L}$$

For $\hat{V}_o = V_{CC}$

$$P_{Omax} = \frac{V_{CC}^2}{2R_L}$$


Average efficiency

$$\eta = \frac{P_o}{P_{PS}} = \frac{\hat{V}_o^2}{2R_L} \frac{\pi}{2} \frac{R_L}{V_{CC} \hat{V}_o} = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}}$$

For $\hat{V}_o = V_{CC}$

$$\eta_{max} = \frac{\pi}{4} = 78.5\%$$

➤ Class B – summary

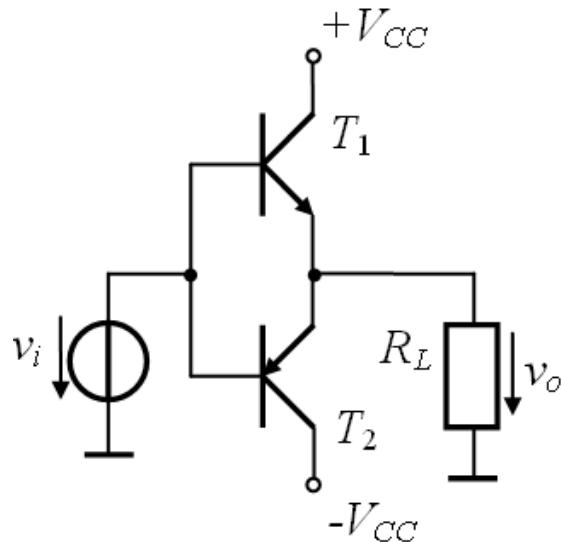

$$P_{O\max} = \frac{V_{CC}^2}{2R_L}$$

$$P_{PS\max} = \frac{2 V_{CC}^2}{\pi R_L}$$

$$\eta_{\max} = \frac{\pi}{4} = 78.5\%$$


- each transistor conducts for half a period
- crossover distortions - how do we get rid of them?

Make them too small to matter – class B w/ additional OpAmp and global NF

OR

Eliminate them by compensating the ± 0.7 V – class AB

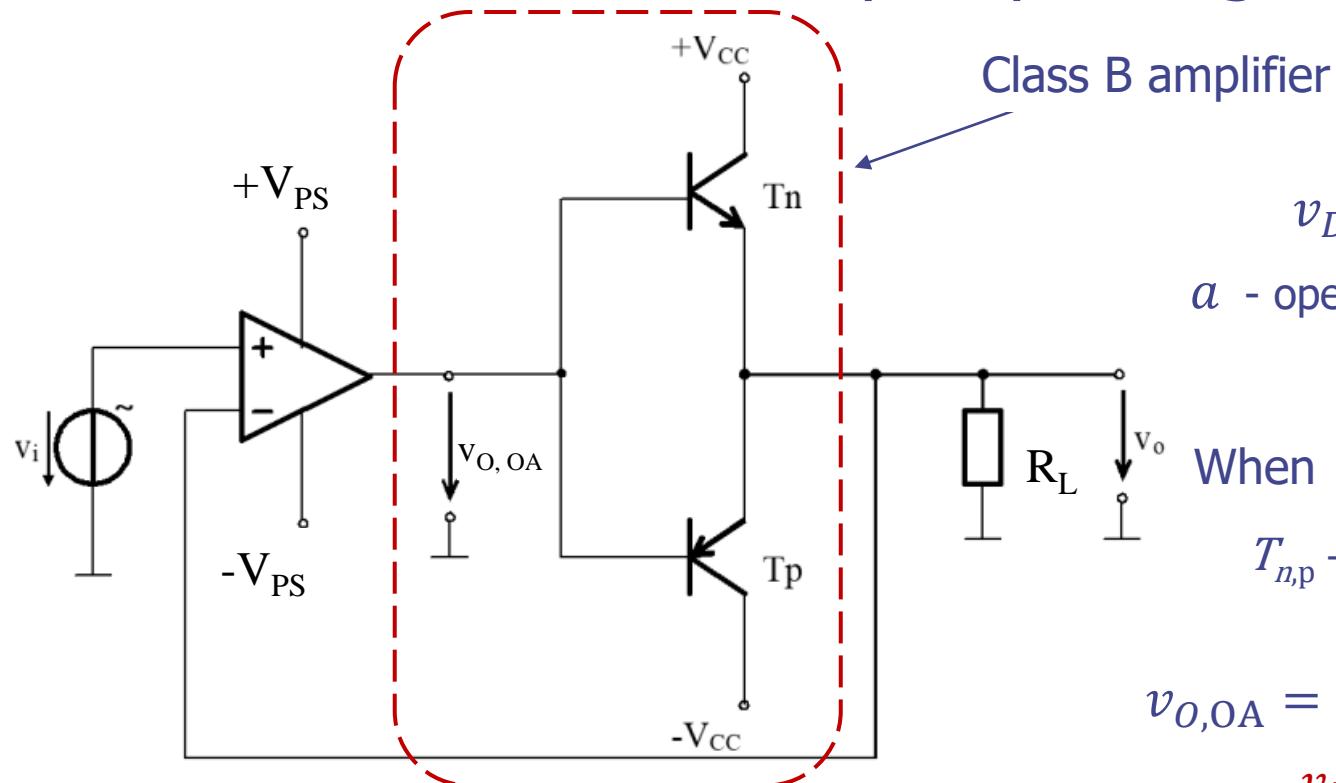➤ Class B w/ additional OpAmp and global NF



Class B amplifier

$$v_{O, OA} = a \cdot v_D$$

$$v_D = V^+ - V^- = v_i - v_o$$

a - open-loop gain of the OpAmp

$$a_{LM741} = 2 \cdot 10^5$$

When $v_{O, OA} \in (-0.7 \text{ V}; +0.7 \text{ V})$

$T_{n,p}$ - (off) $v_o = 0$

no feedback

$$v_{O, OA} = a \cdot v_i$$


$$v_i \in (-0.7 \text{ V}/a; +0.7 \text{ V}/a)$$

When
 $v_i > -0.7 \text{ V}/a$ T_n - (on), T_p - (off),
 $v_i < -0.7 \text{ V}/a$ T_n - (off), T_p - (on),

the NF loop is active and $v_D = 0$ $v_o = v_i$

VTC? Crossover distortions?

➤ Class AB – circuit

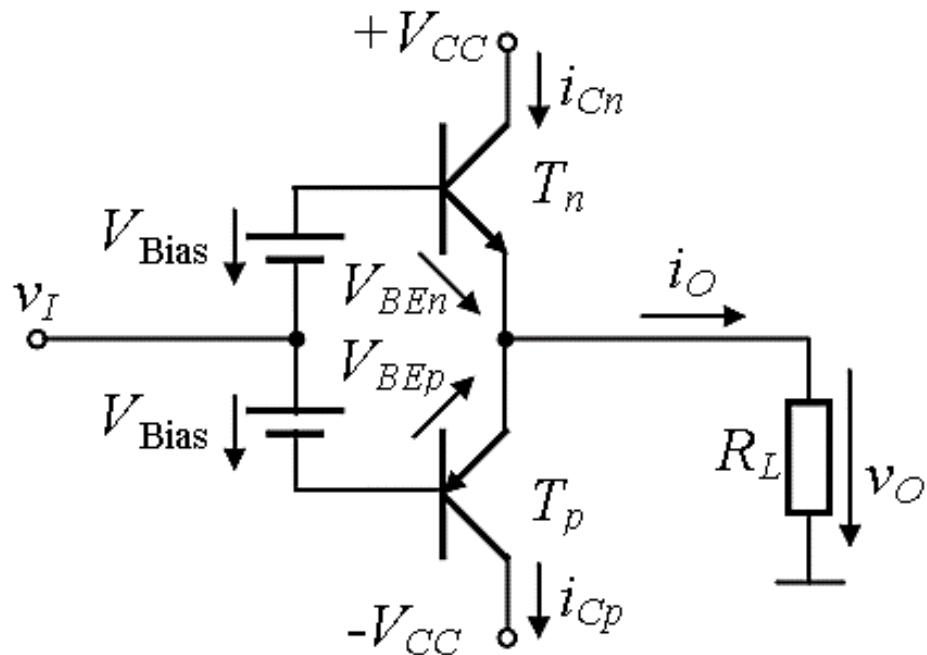

The complementary transistors are biased with a small current.

$$V_{Bias} \approx 0.7 \text{ V}$$

$$I = I_S e^{\frac{V_{Bias}}{V_T}}$$



No more crossover distortions!

$$v_I \text{ - positive} \quad v_O(t) = v_I(t) + V_{Bias} - V_{BEn} \approx v_I(t)$$

$$v_I \text{ - negative} \quad v_O(t) = v_I(t) - V_{Bias} - V_{BEP} \approx v_I(t)$$



➤ Class AB – VTC

$$v_O(t) = v_I(t)$$

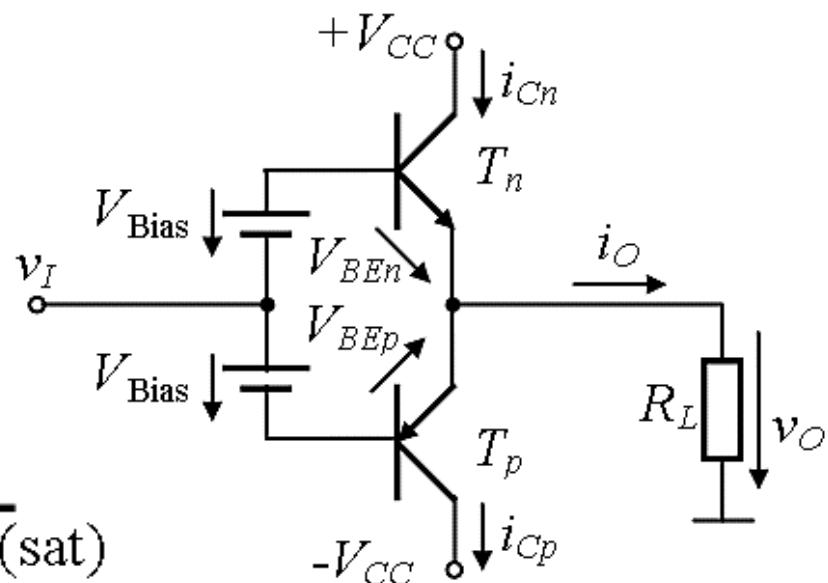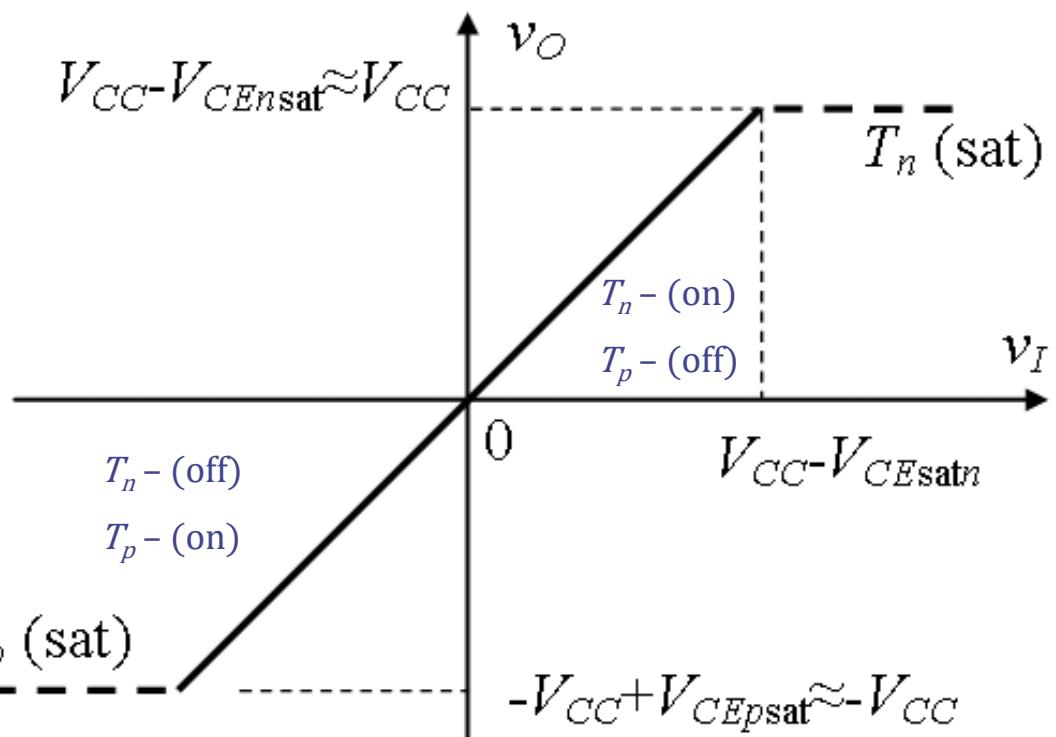

Solutions to generate V_{Bias} ?

➤ Class AB – biasing using diodes

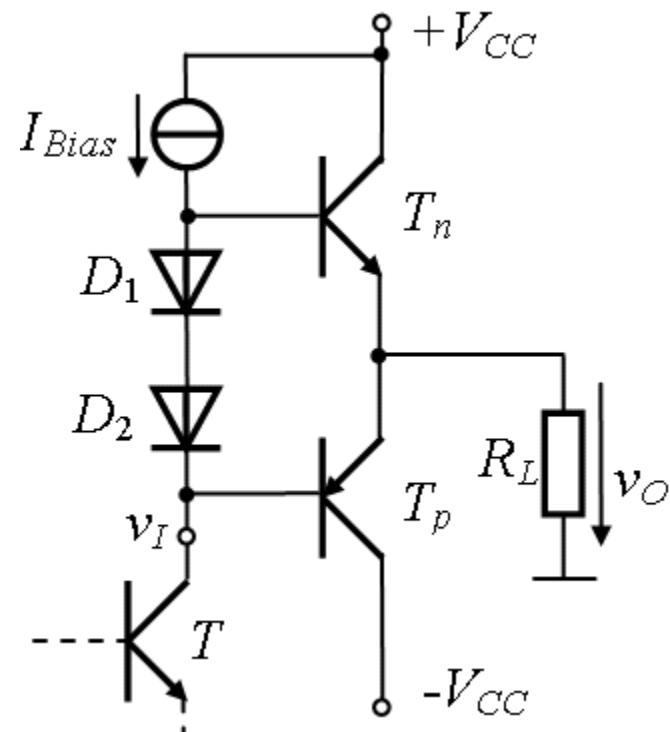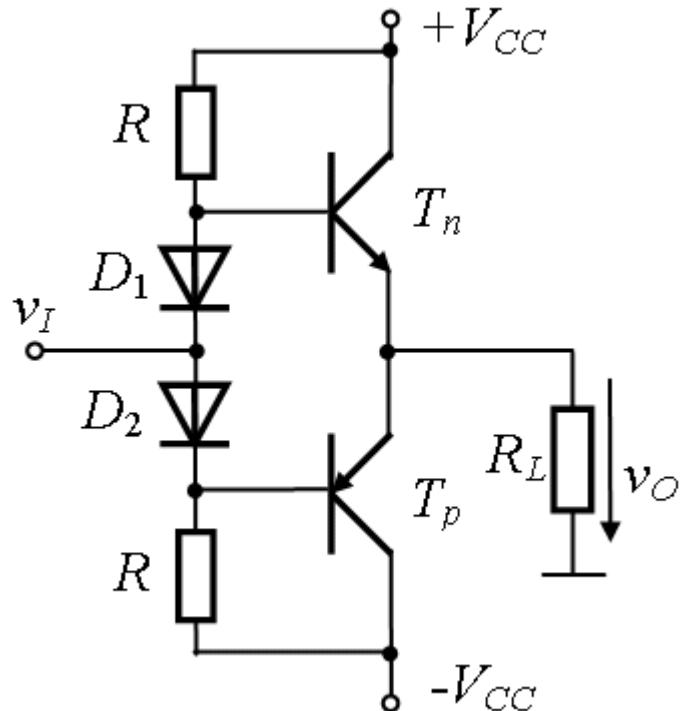


R should allow the currents in the diodes and in the bases of the transistors, even for maximum output current

Sizing R – see Seminar 4


T - driver transistor
from previous amplifier stage




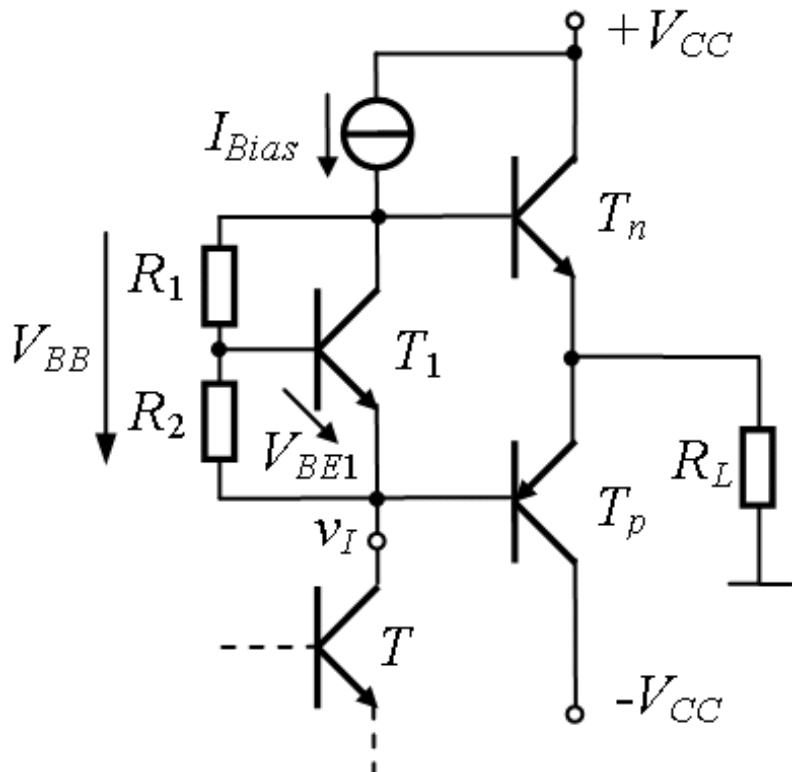
➤ Class AB – biasing using V_{BE} multiplier



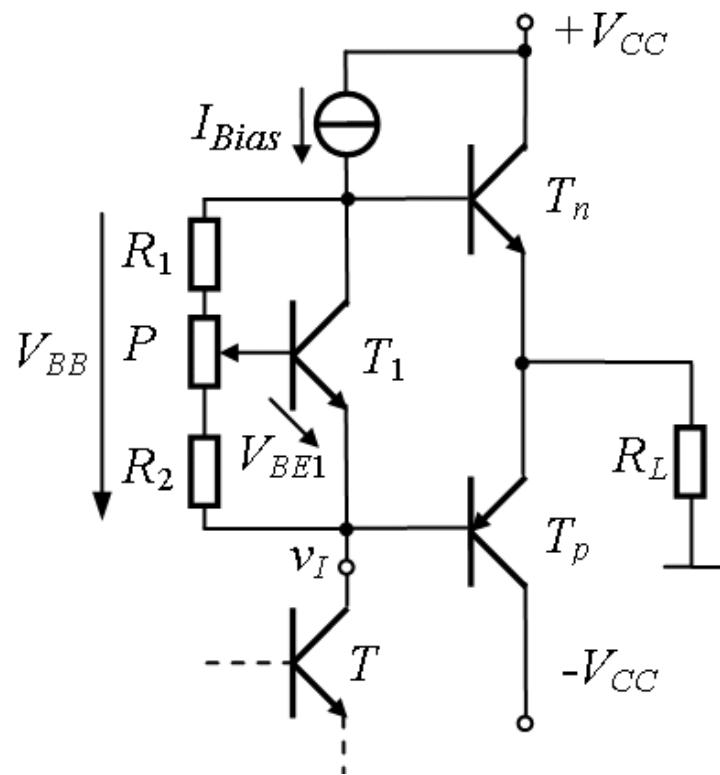
$$V_{BB} = \left(1 + \frac{R_1}{R_2}\right) V_{BE1}$$



➤ Class AB – high output currents

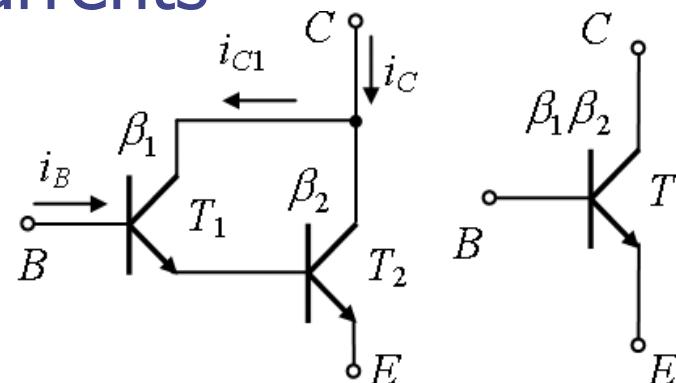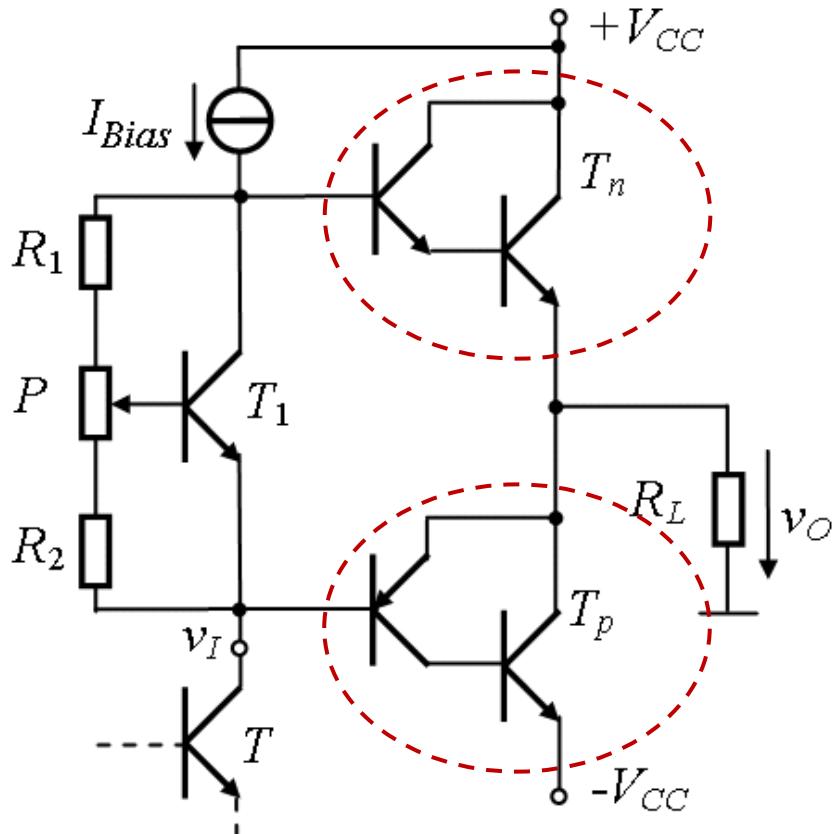

Darlington *npn* configuration

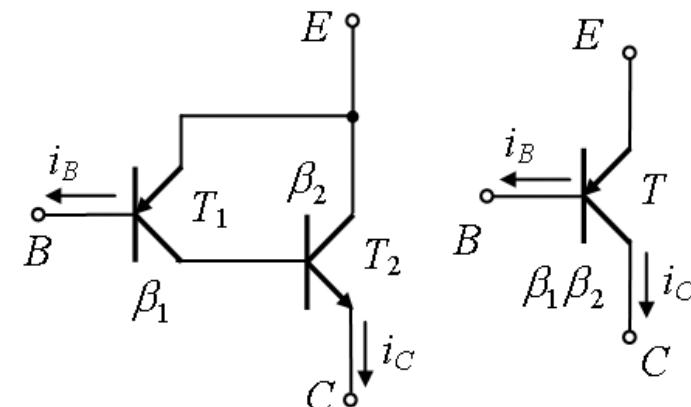


Compound *pnp* configuration
(preferred in IC)





➤ Class AB – short-circuit protection

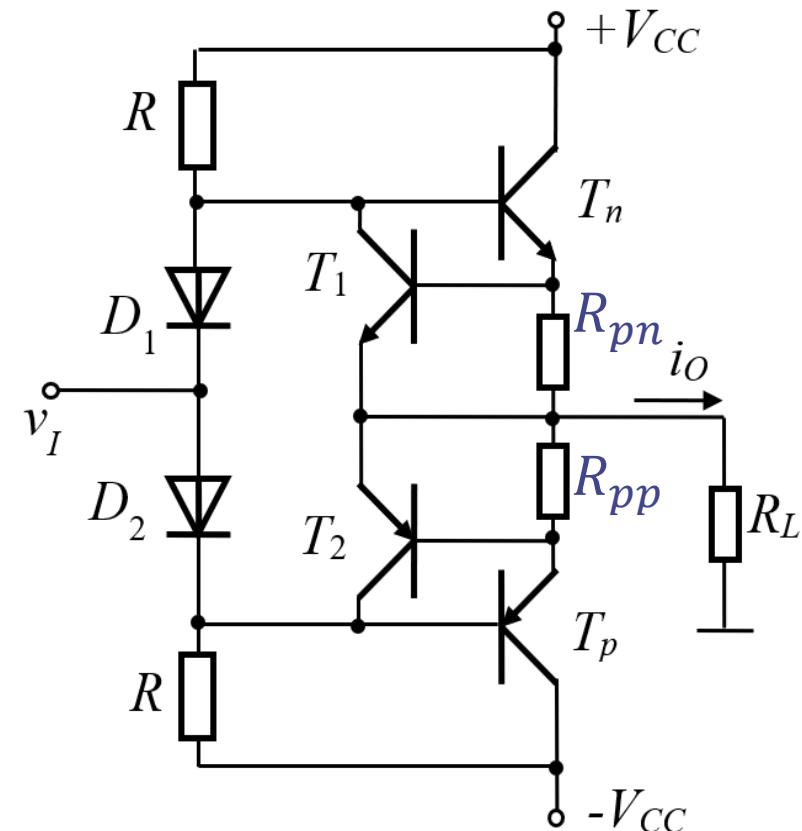

If i_O increases, T_1 turns (on) when $R_{pn}i_O = 0.7 \text{ V}$

Elements for short-circuit protection:

- T_1, R_{pn} when $v_o > 0$
- T_2, R_{pp} when $v_o < 0$


When $v_o > 0$

If $R_{pn}i_O < 0.7 \text{ V}$

$$T_1 - (\text{off}); \quad i_O = \frac{v_o}{R_L}$$

$$i_{Omax} = \frac{V_{BE1,on}}{R_{pn}} = \frac{0.7 \text{ V}}{R_{pn}}$$

➤ Class AB – summary

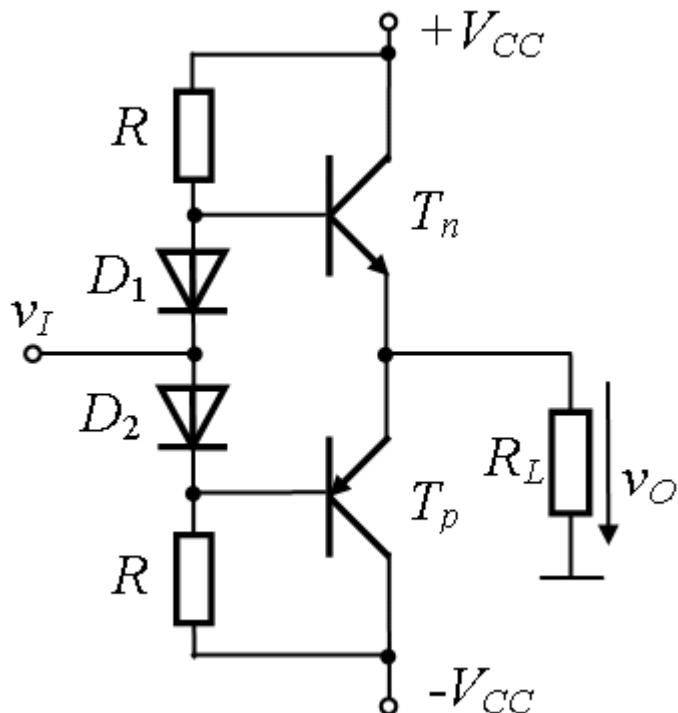

$$v_O(t) = v_I(t)$$

Powers & efficiency – same as for class B

$$P_{O\max} = \frac{V_{CC}^2}{2R_L}$$

$$P_{PS\max} = \frac{2}{\pi} \frac{V_{CC}^2}{R_L}$$

$$\eta_{\max} = \frac{\pi}{4} = 78.5\%$$

- no more crossover distortions – assuming perfect match between $V_{D, on}$ and V_{BE}

Summary

- Intro
- Class A power amplifier
- Class B power amplifier
- Class AB power amplifier

Next week: Feedback circuits