




Diodes

Structure. Symbol

Diode - semiconductor device

Physical structure

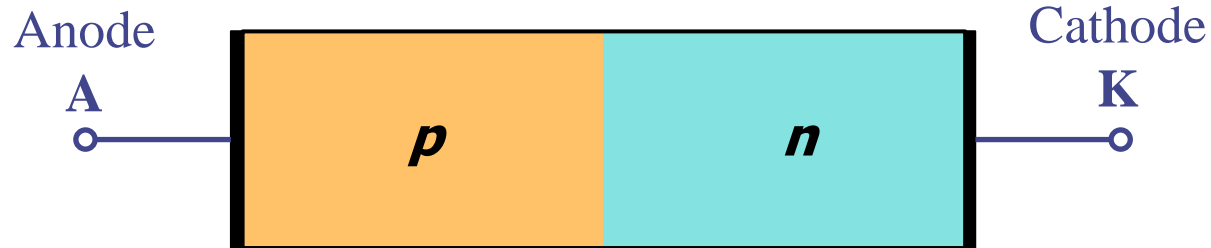

The ***pn* junction** - an interface between two types of semiconductor materials, *p*-type and *n*-type.

In the outer shells of the electrically neutral atoms:


- the *p* (positive) side contains an excess of holes (positive charges)
- the *n* (negative) side contains an excess of electrons (negative charges)

The *pn* junction is created by **doping**:

- ✓ *p*-type doping - an intrinsic semiconductor (e.g. Si) is doped with acceptor impurities (column 3 in the periodic table → excess of holes)
- ✓ *n*-type doping - an intrinsic semiconductor (e.g. Si) is doped with donor impurities (column 5 in the periodic table → excess of electrons)


A pn junction diode allows electric charges to flow **only in one direction**:

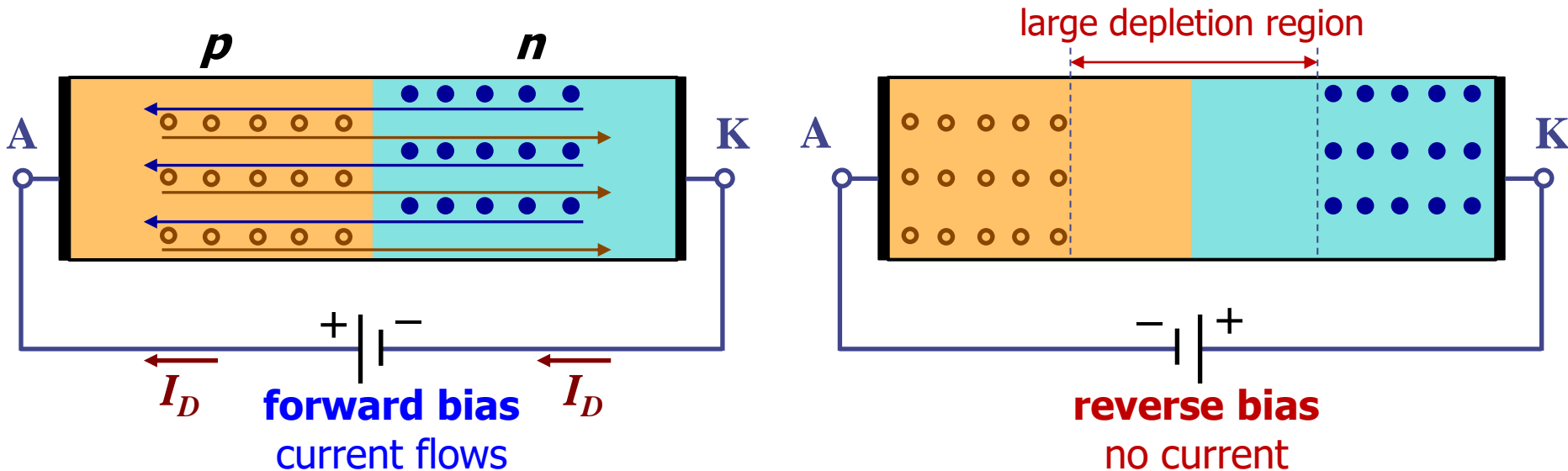- negative charges (electrons) can flow through the junction from n to p but not from p to n ,
- positive charges (holes) can flow through the junction from p to n but not from n to p ,




When the pn junction is forward-biased, electric charge flows freely due to reduced resistance of the pn junction.

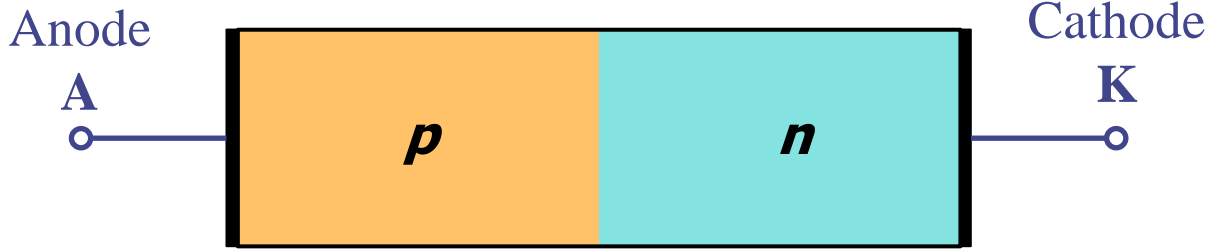
When the p - n junction is reverse-biased, the junction barrier (and therefore resistance) becomes greater and charge flow is minimal (zero).



Circuit symbol

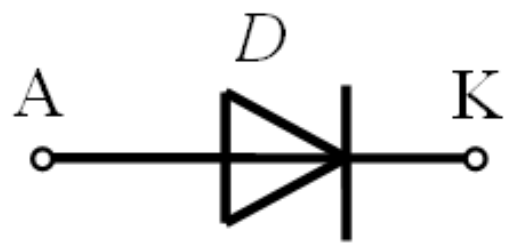

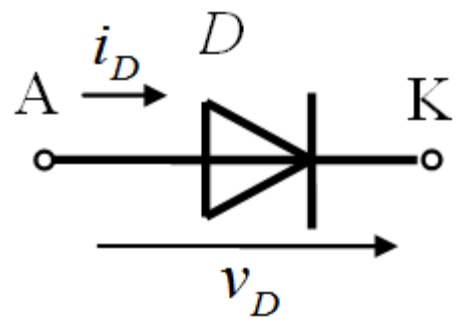Positive directions for current and voltage



The arrow in the diode's symbol points in the direction of forward current flow.

Current – voltage characteristic

The current flowing through the diode is controlled by the voltage drop across the diode itself – **nonlinear semiconductor device**

Shockley diode equation (diffusion equation)

$$i_D = I_S \left(e^{\frac{v_D}{nV_T}} - 1 \right) \approx I_S e^{\frac{v_D}{nV_T}}$$

I_S - saturation current (\sim nA - pA)
depends on temperature

i_D depends exponentially on v_D

$V_T = \frac{KT}{q}$ thermal voltage (*depends on temperature*)

K - Boltzmann's constant

q – elementary charge (electric charge carried by a single electron)

T – absolute temperature measured in K degrees


$$V_T = 25\text{mV @ } 20^\circ\text{C}$$

n – ideality factor (*emission coefficient*)


$n = 2$ discrete diodes

$n = 1$ integrated diodes

Operating regions

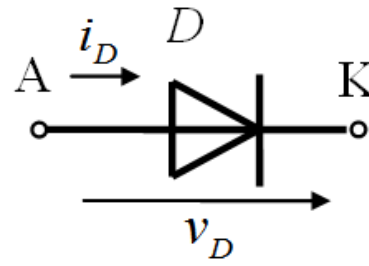
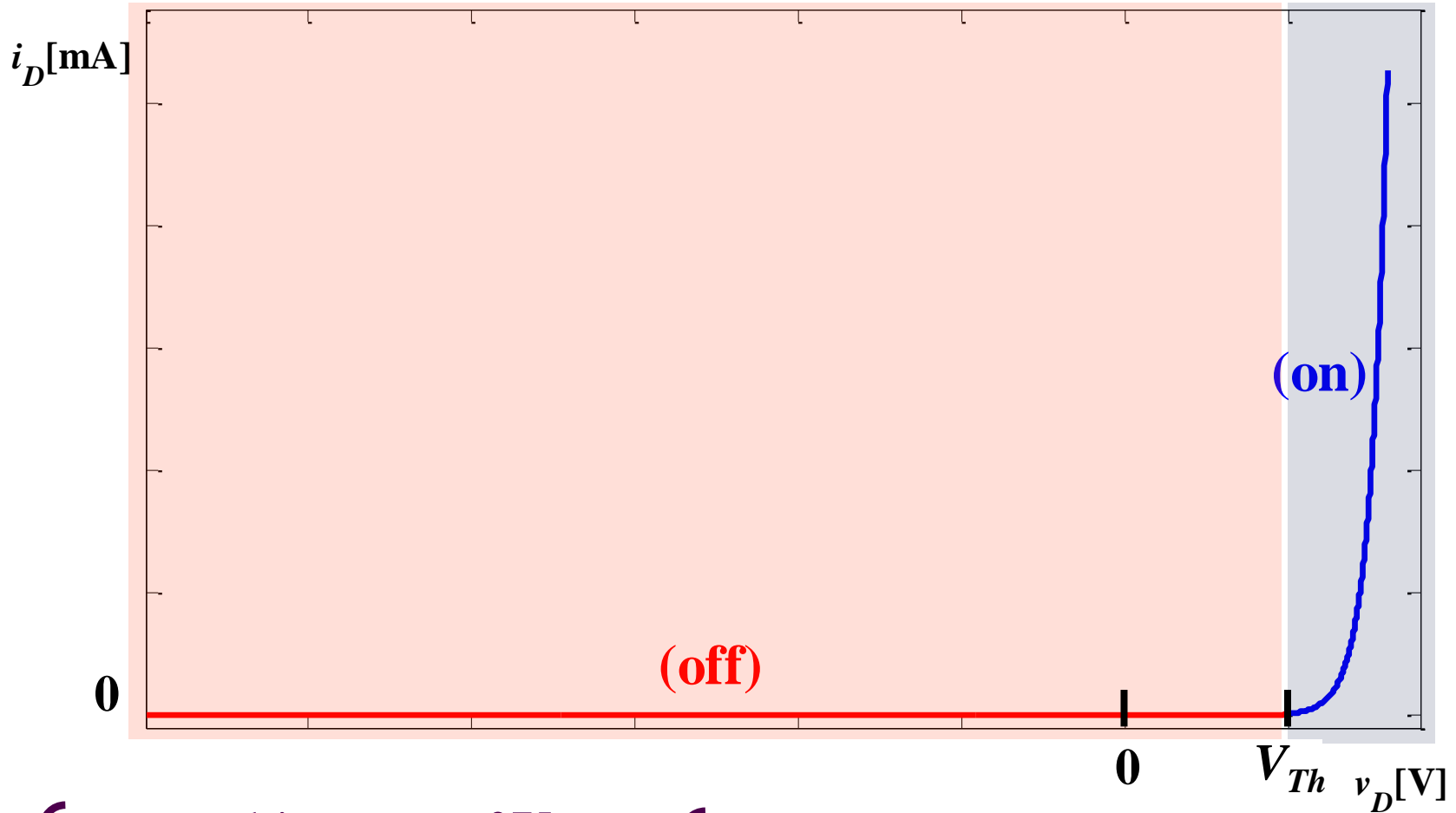
$$i_D \approx I_S \cdot e^{\frac{v_D}{nV_T}}$$




{ reverse bias $v_D < 0V$
 { forward bias $v_D > 0V$

{ (off) $v_D < v_{Th}; i_D = 0$
 { (on) $v_D > v_{Th}; i_D > 0$

$V_{Th} \approx 0.6V$

Illustration

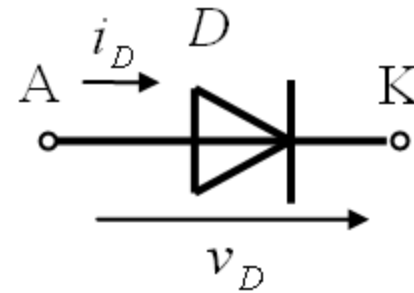

D is a rectifier diode, 1N400x with $I_S=14\text{nA}$, $n = 2$

Assuming a voltage drop across the diode in conduction

$$v_D = 0.7\text{V} = 700 \text{ mV}$$

$$V_T = 25\text{mV} @ 20^\circ\text{C}$$


the current through the diode results as:

$$i_D = 14 \cdot 10^{-9} \cdot e^{\frac{700}{25}} = 16.8\text{mA}$$

Operating (quiescent) point

$$Q(V_D; I_D)$$

Illustration for 1N400x with $I_S=14\text{nA}$, $n=2$

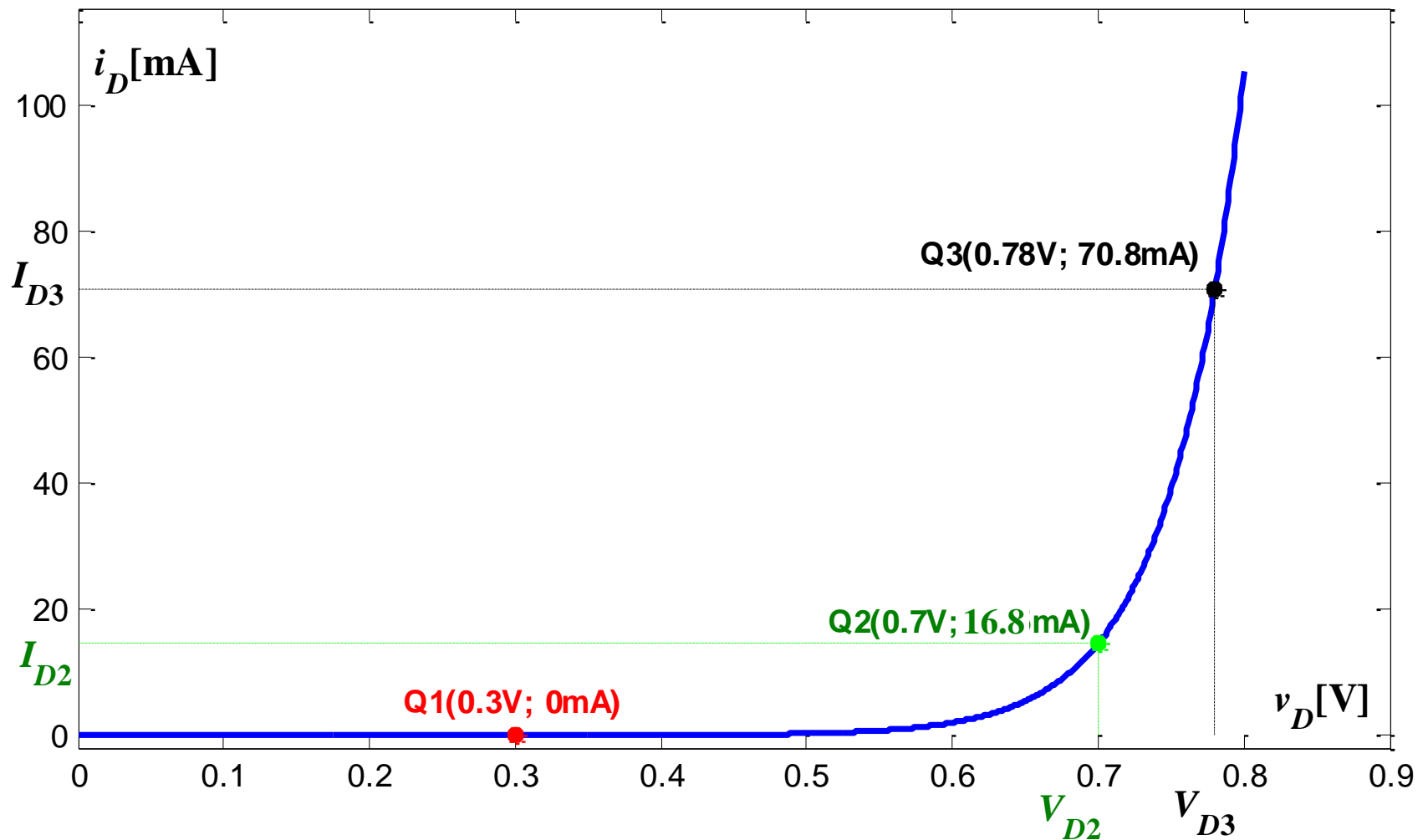


Temperature dependence



$$i_D \cong I_S e^{\frac{v_D}{nV_T}}$$

I_S, V_T - depend directly on the temperature

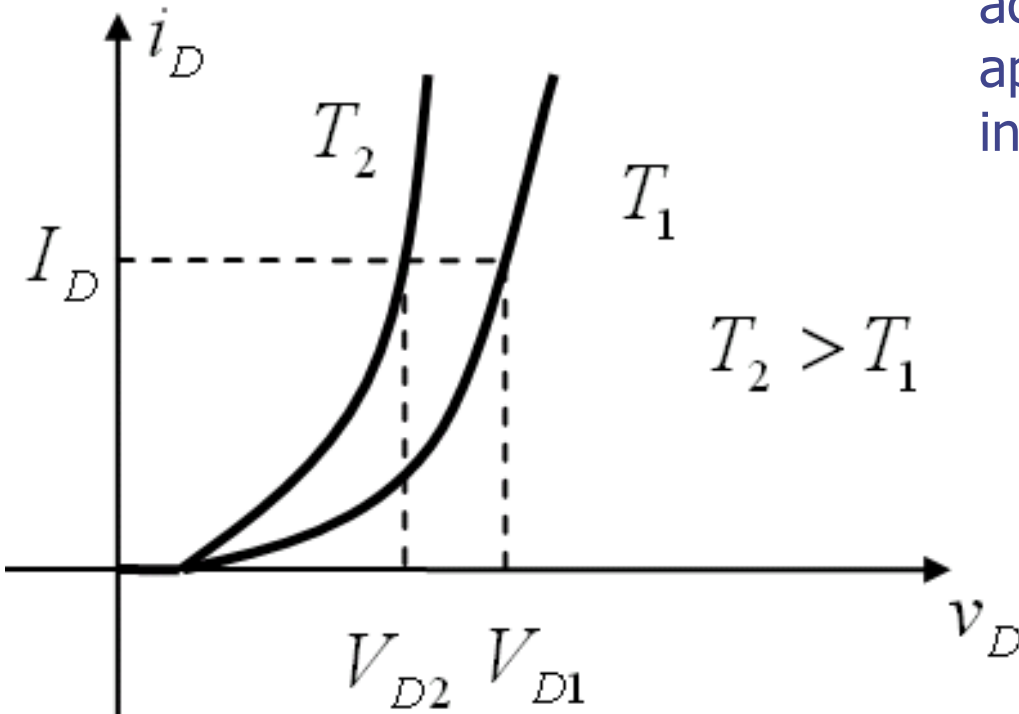At a constant current the voltage across the diode decreases by approximately 2 mV for every 1°C increase in temperature.



Negative tempco

$$TC = -2\text{mV}/^\circ\text{C}$$

$$20^\circ\text{C} \quad v_D = 650\text{mV}$$


$$40^\circ\text{C} \quad v_D = 610\text{mV}$$

$$v_D(T_2) = v_D(T_1) + TC \cdot (T_2 - T_1) \Big|_{I_D\text{-cst}}$$

At a constant voltage across the diode the current increases with the temperature

Determining the operating point

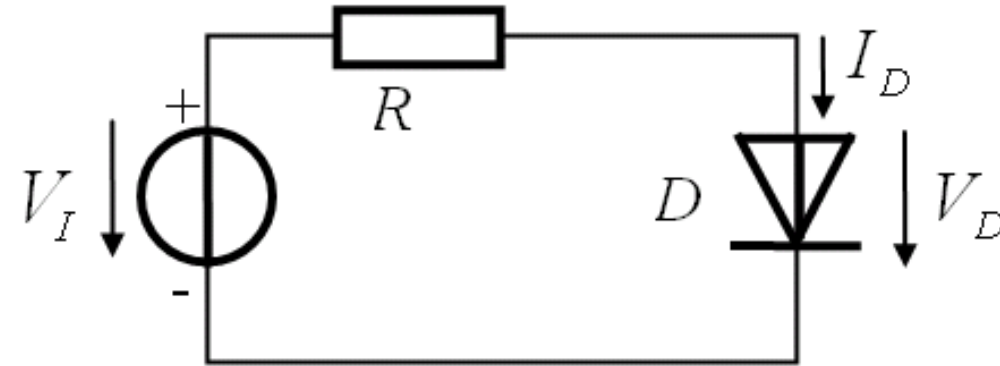- Circuit with a dc voltage source and a resistor



$$I_D = ? \quad V_D = ?$$

$$I_D = I_S e^{\frac{V_D}{nV_T}} \quad \text{Diode equation}$$

$$V_I = RI_D + V_D \quad \text{Circuit equation (load line equation)}$$

$$V_I - \textcircled{V_D} = RI_D = RI_S e^{\frac{\textcircled{V_D}}{nV_T}}$$


⇒ Transcendental equation

Two solving methods:

1. Graphical method


2. Numerical method (successive approximation)

Graphical method

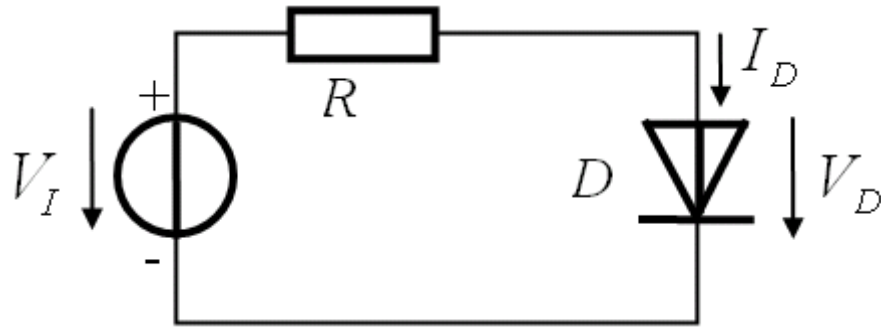

Diode equation: $I_D = I_S e^{\frac{V_D}{nV_T}}$

Load line equation: $V_I = I_D R + V_D$

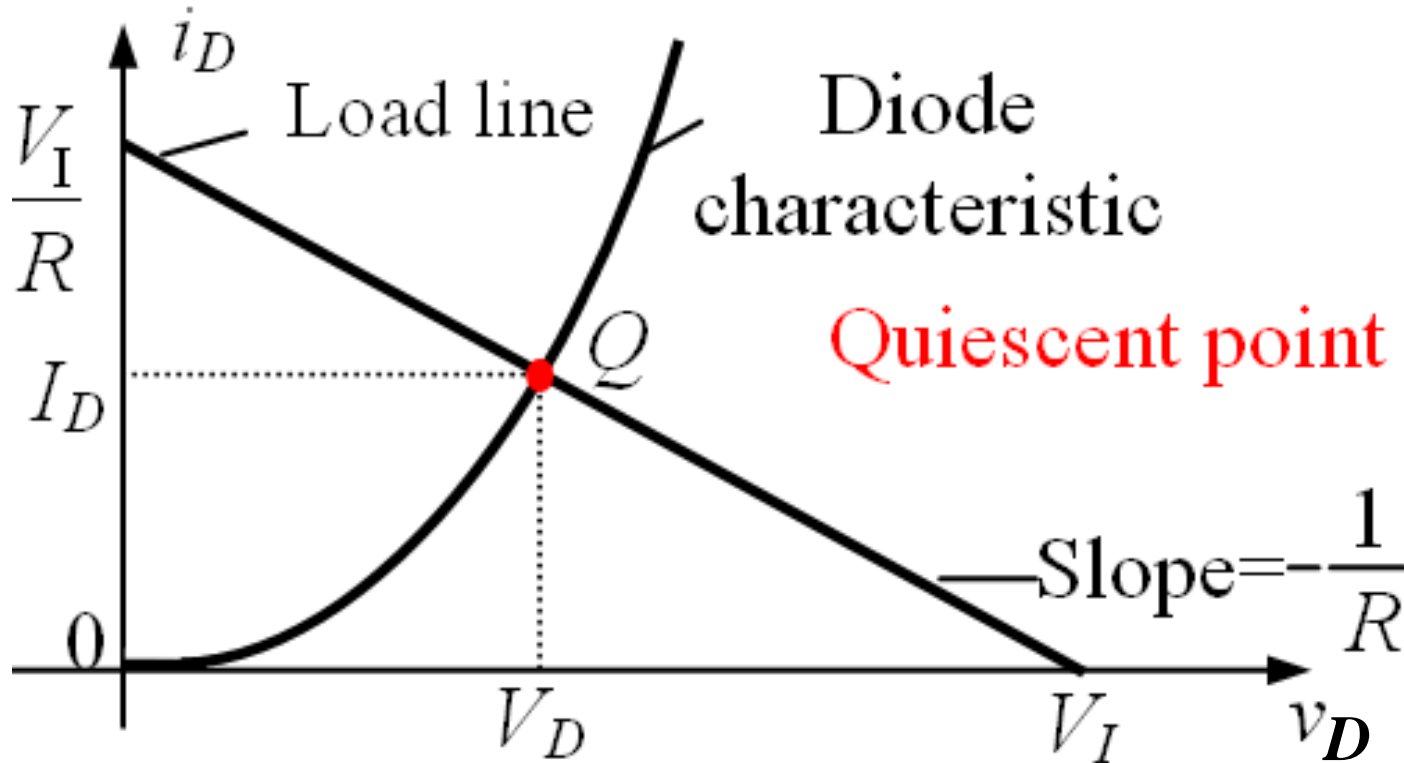


Numerical analysis - simplified

If V_I high enough, the D is on; (else D is off)

Assume the voltage drop across the conducting diode $V_D = 0.7V$ and compute the current I_D using the load line (circuit) equation


Circuit equation: $V_I = I_D R + V_D$

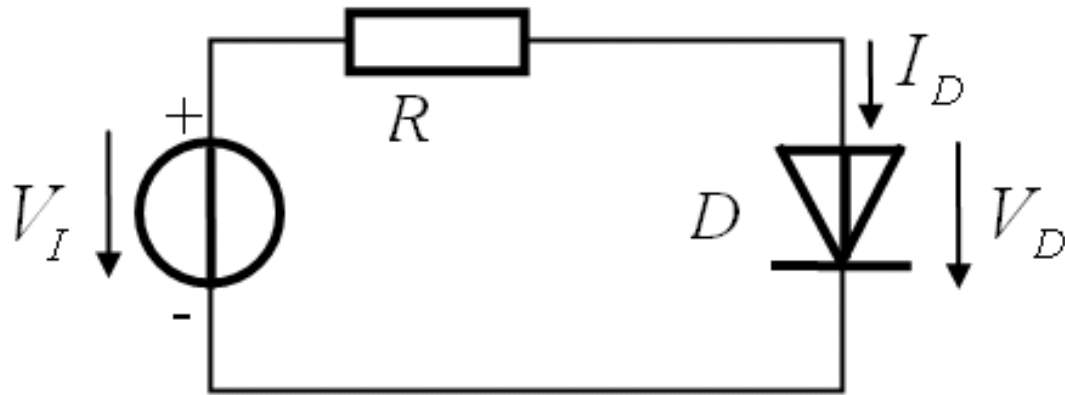

$$V_D = 0.7V$$

$$I_D = \frac{V_I - V_D}{R}$$

Illustration

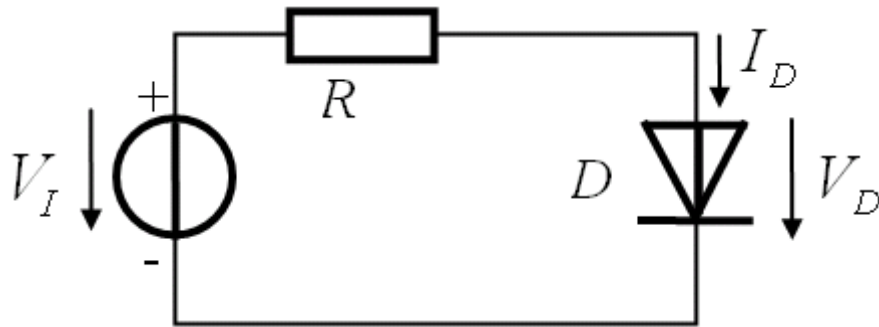

$$V_I = 9\text{V}, R = 0.5\text{K}\Omega$$

a) What is the operating (quiescent) point of the diode D ?

V_D high enough

D – (on)

Assume $V_D = 0.7\text{V}$ across the conducting diode

$$I_D = \frac{V_I - V_D}{R} \quad I_D = \frac{9 - 0.7}{0.5} = 16.6\text{mA}$$

$Q(0.7\text{V}, 16.6\text{mA})$

Numerical analysis - iteratively

1. Consider an initial value of diode voltage, eg. $V_D^{(0)} = 0.7\text{V}$ and compute the current $I_D^{(0)}$ using the load line equation.

$(V_D^{(0)}, I_D^{(0)})$ – initial solution




2. With $I_D^{(0)}$ compute the diode voltage from diode equation, then the current $I_D^{(1)}$ from load line equation

$(V_D^{(1)}, I_D^{(1)})$ – solution after first iteration

We finalize one iteration. If a more accurate solution is necessary, further iteration should be performed.

For quick, first order analysis of the circuit, usually the initial solution is considered!

Illustration

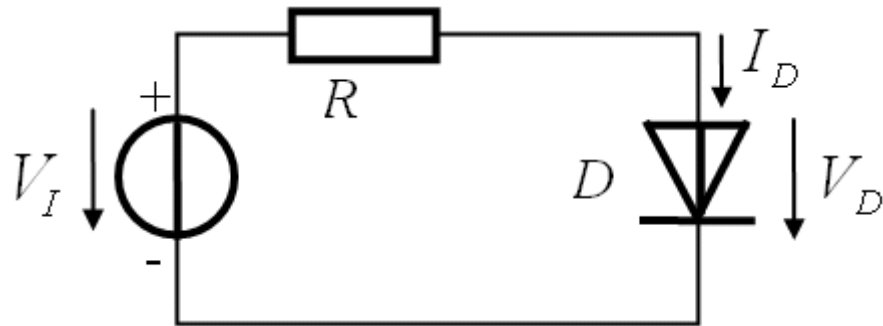

Consider $V_I=3\text{V}$, $R=0.5\text{K}\Omega$, D is 1N400x with $I_S=14\text{nA}$ and $n=2$.

What is the operating (quiescent) point of the diode?

Quick, first order analysis:

$$V_D > 0.6\text{V} \quad D - (\text{on})$$

Assume $V_D = 0.7\text{V}$ in conduction

$$I_D = \frac{V_I - V_D}{R} \quad I_D = \frac{3 - 0.7}{0.5} = 4.6\text{mA} \quad Q(0.7\text{V}, 4.6\text{mA})$$

Detailed analysis:

$$I_D = \frac{V_I - V_D}{R} \quad V_D = nV_T \ln \frac{I_D}{I_S}$$



$$V_D^{(0)} = 0.7\text{V}$$

$$I_D^{(0)} = \frac{3 - 0.7}{0.5} = 4.6\text{ mA}$$

$Q^{(0)}(0.7\text{V}, 4.6\text{mA})$

$$V_D^{(1)} = nV_T \cdot \ln \frac{I_D^{(0)}}{I_S} = 2 \cdot 0.025 \cdot \ln \frac{4.6\text{mA}}{14\text{nA}} = 0.635\text{V}$$

$$I_D^{(1)} = \frac{V_I - V_D^{(1)}}{R} = \frac{3 - 0.635}{0.5} = 4.73\text{mA}$$


$Q^{(1)}(0.635\text{V}, 4.73\text{mA})$

$$V_D^{(2)} = n \cdot V_T \cdot \ln \frac{I_D^{(1)}}{I_S} = 2 \cdot 0.025 \cdot \ln \frac{4.73\text{mA}}{14\text{nA}} = 0.637\text{V}$$

$$I_D^{(2)} = \frac{V_I - V_D^{(2)}}{R} = \frac{3 - 0.637}{0.5} = 4.726\text{mA}$$



$Q^{(2)}(0.637\text{V}, 4.726\text{mA})$

Constant-voltage-drop model

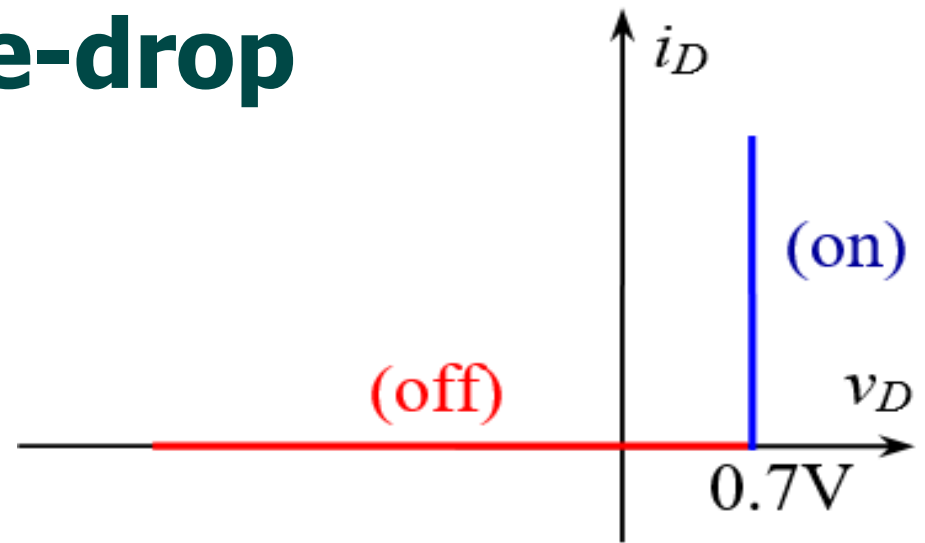

If $v_D < 0.7V$ D – (off)


If v_D tends to be $> 0.7V$ D – (on)

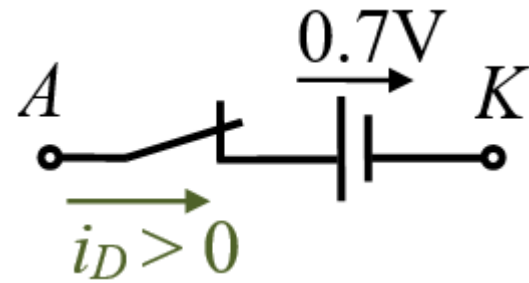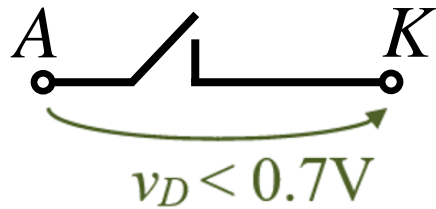

$$\begin{cases} v_D < 0.7V \\ i_D = 0 \end{cases}$$

$$\begin{cases} v_D = 0.7V \\ i_D > 0 \end{cases}$$

DR two-port networks analysis

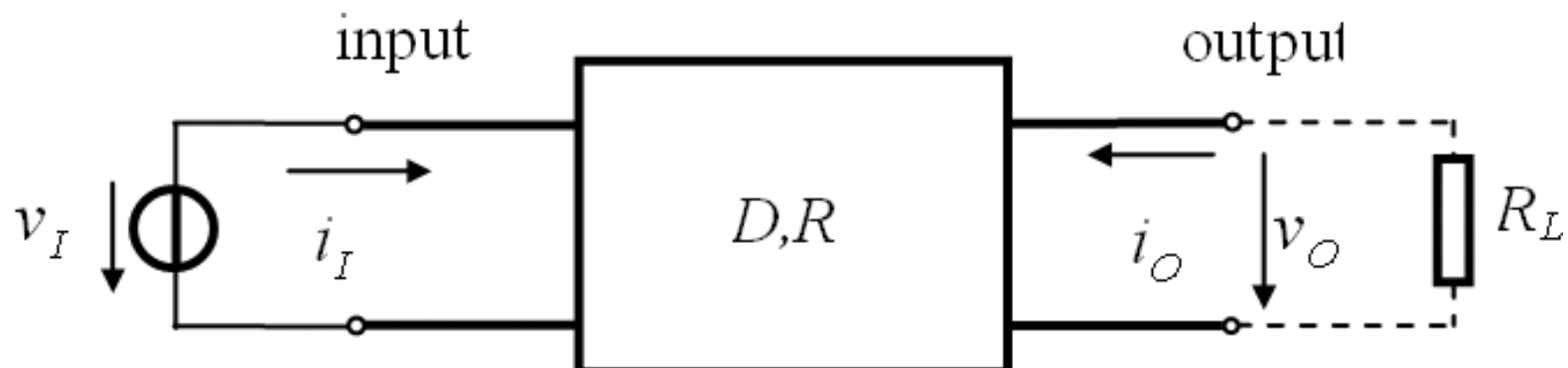


VTC – voltage transfer characteristic

1. Consider **all possible situations** resulting from the combination of the **diode states** (*on, off*)
2. For each situation :
 - i. draw the equivalent circuit
 - ii. find v_O
 - iii. determine the range of v_I for that particular situation
3. Draw **VTC**.


Example

What is the VTC $v_O(v_I)$?

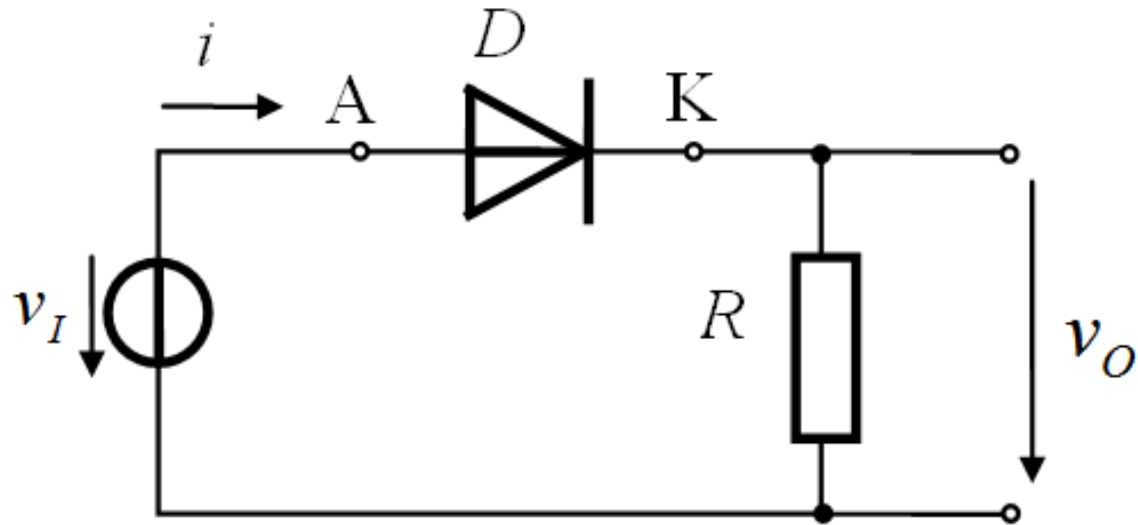


Example - cont

What is the VTC $v_O(v_I)$?

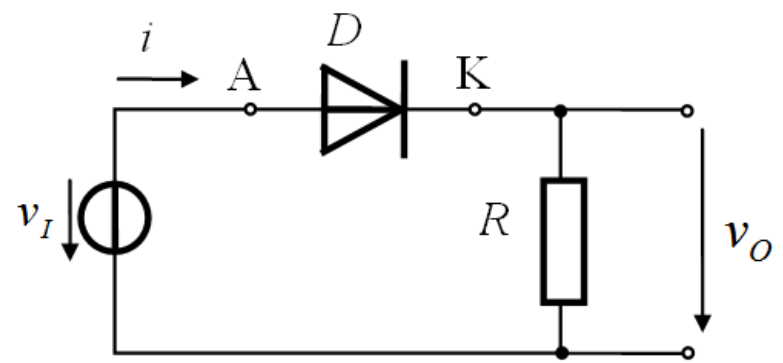

D – (off)

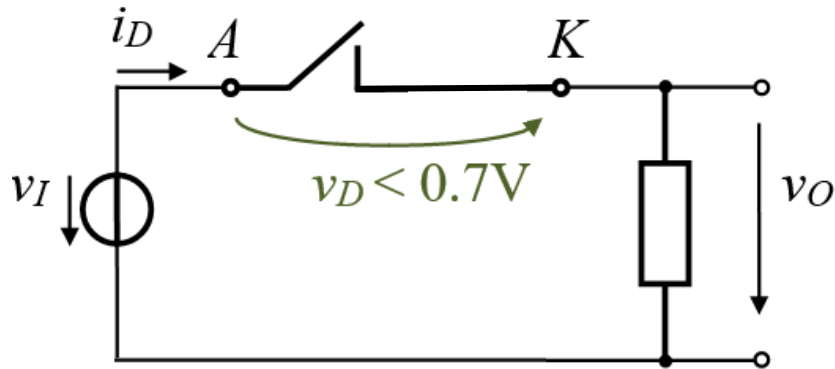


$$v_D < 0.7V \quad i_D = 0$$

$$v_O = 0$$

$$v_D = v_I - v_O$$

$$v_I < 0.7V$$

D – (on)

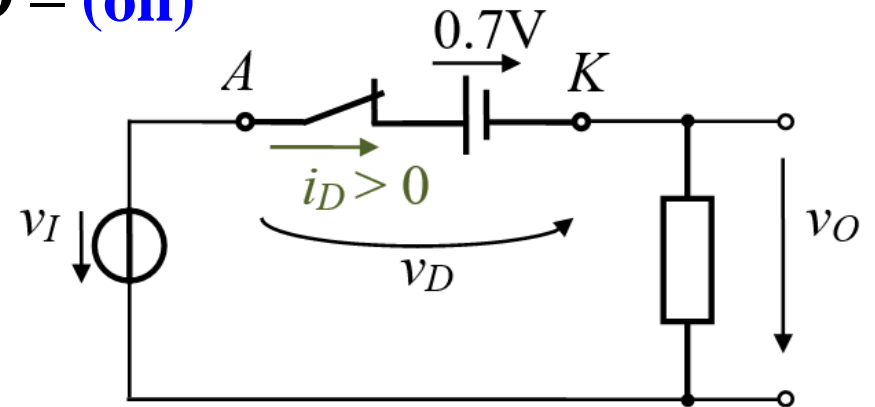


$$i_D > 0 \quad v_D = 0.7V$$

$$v_O = v_I - v_D = v_I - 0.7V$$

$$i_D = \frac{v_O}{R} = \frac{v_I - 0.7V}{R}$$

$$v_I > 0.7V$$

Example - cont

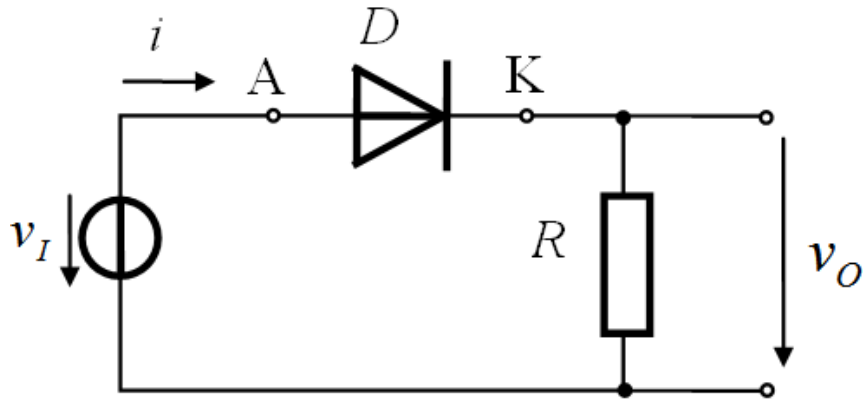


$$v_O = \begin{cases} 0 & v_I < 0.7\text{V} \\ v_I - 0.7\text{V} & v_I > 0.7\text{V} \end{cases}$$


Voltage transfer characteristic

Application:



Voltage rectifier

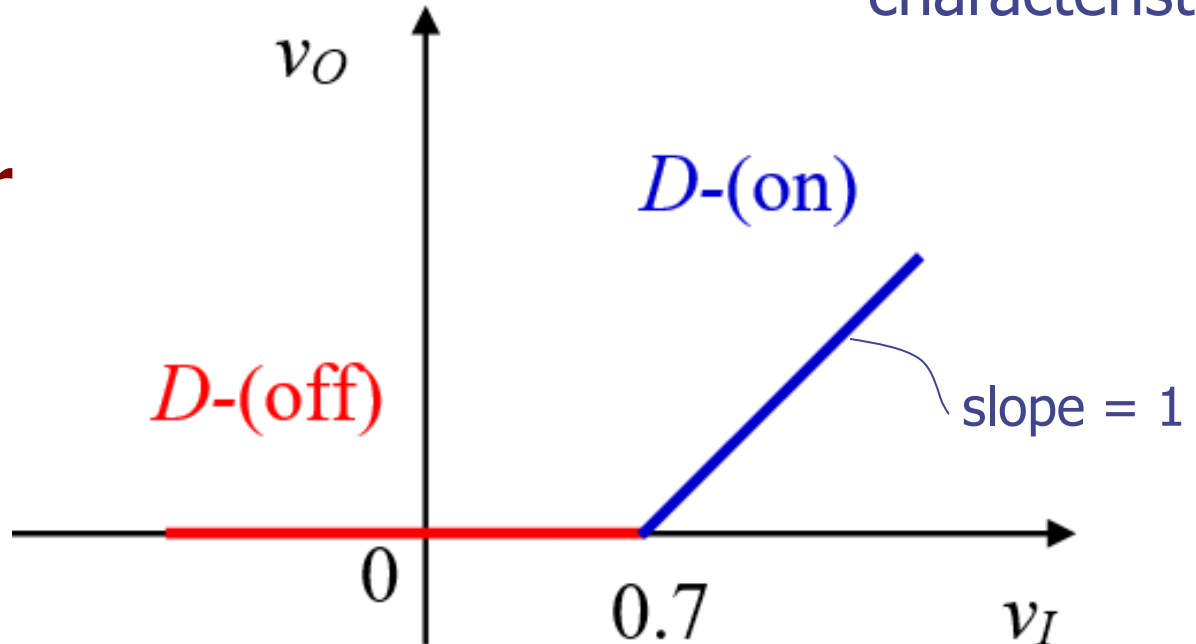

Waveforms for a voltage rectifier

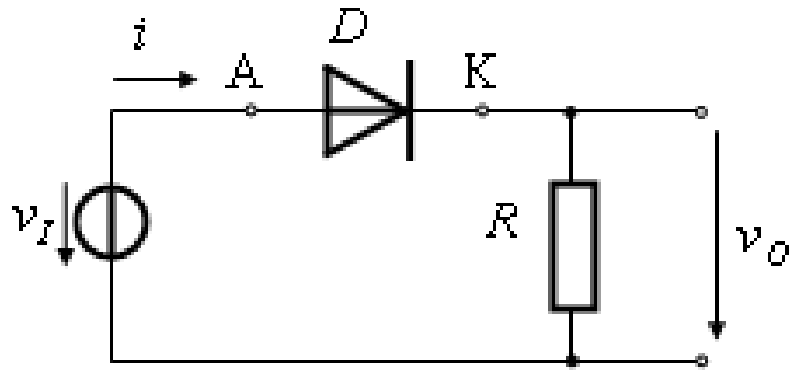

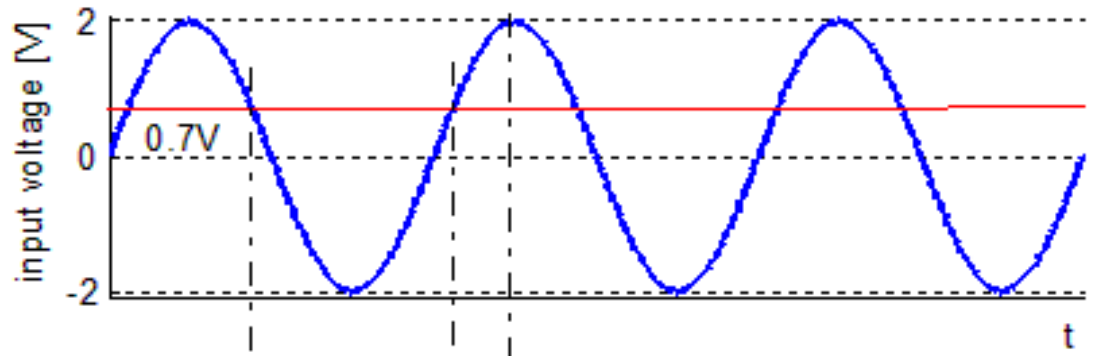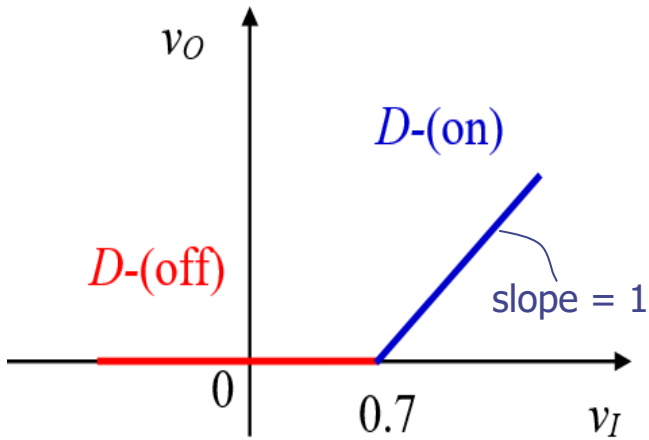
$$v_O = \begin{cases} 0 & v_I < 0.7\text{V} \\ v_I - 0.7\text{V} & v_I > 0.7\text{V} \end{cases}$$






$$v_O(t) = ?$$





Waveforms for a voltage rectifier

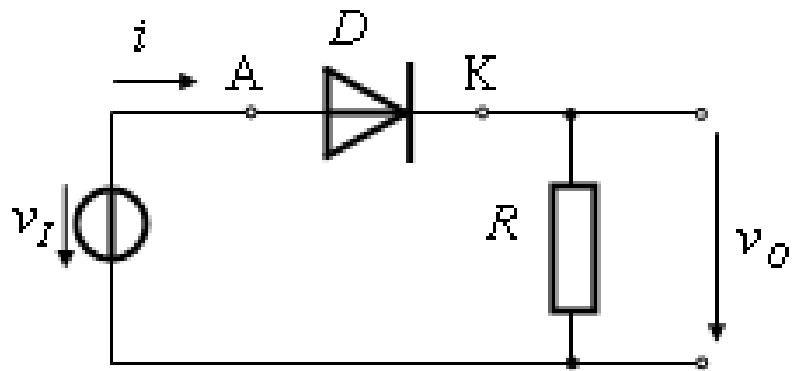
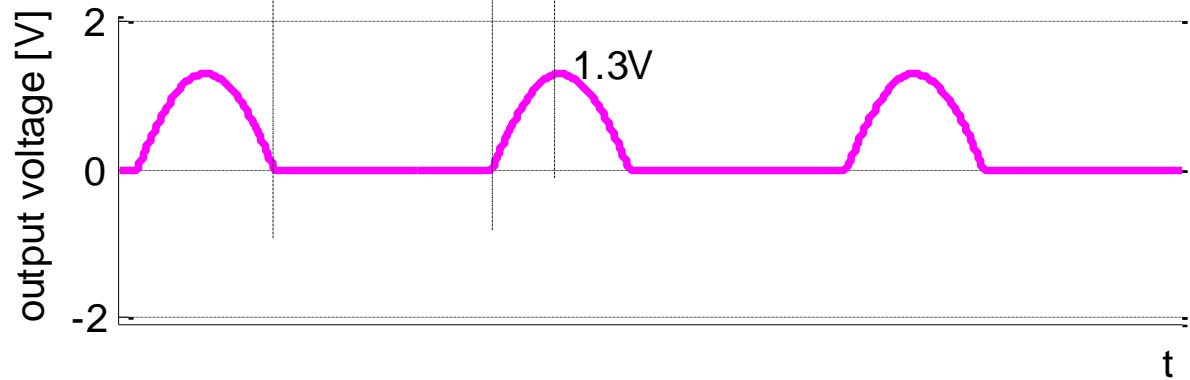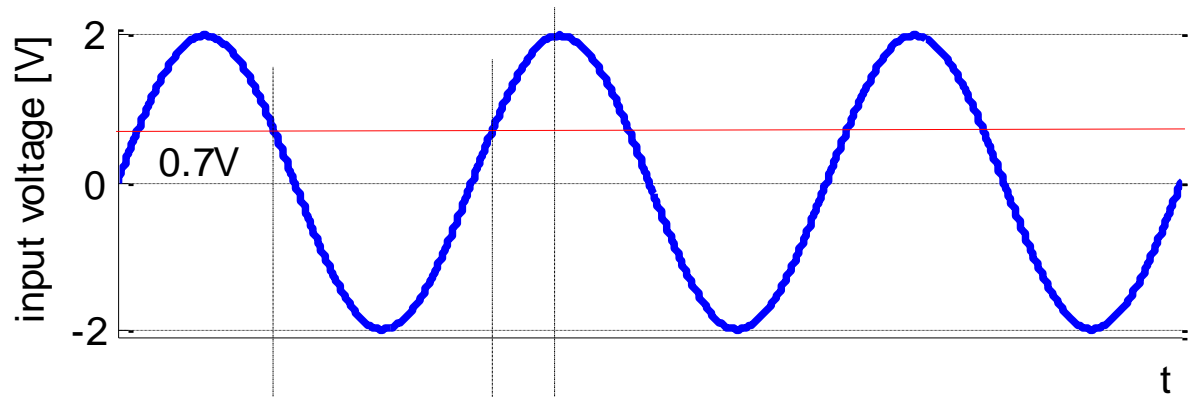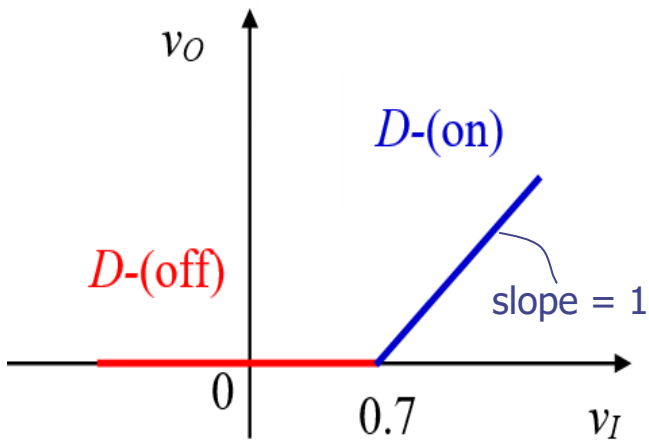
$$v_O = \begin{cases} 0 & v_I < 0.7V \\ v_I - 0.7V & v_I > 0.7V \end{cases}$$



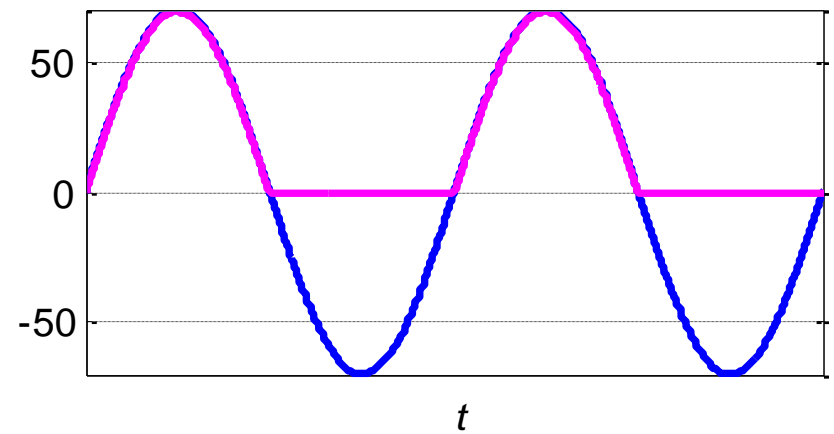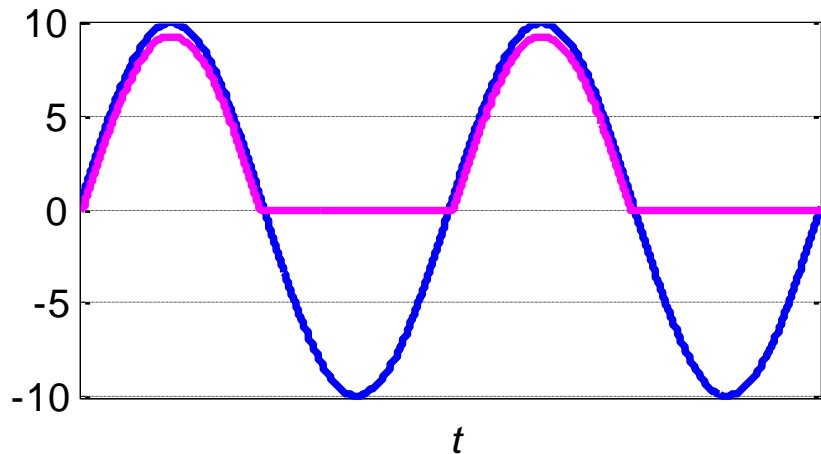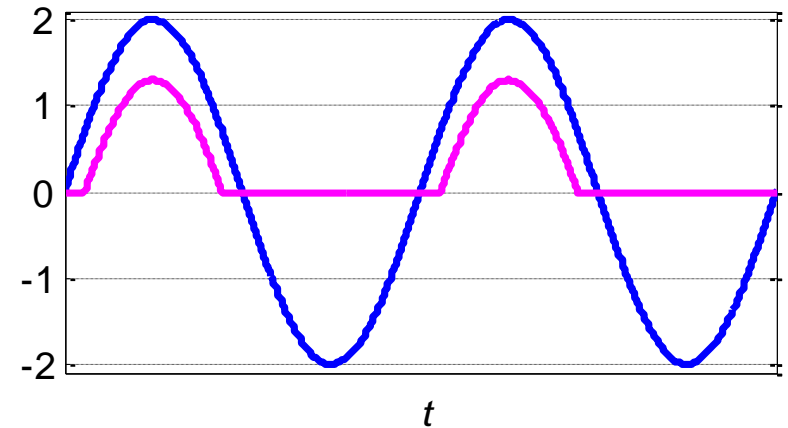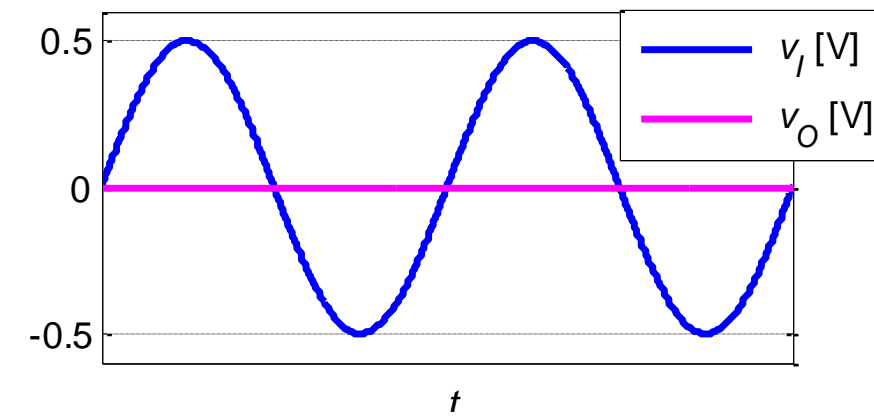
The influence of the threshold voltage and voltage drop across the diode in conduction



- ❖ If the input voltage is large enough ($\gg 0.7\text{V}$)
 - the threshold voltage can be neglected (considered 0V)
 - the voltage drop across the conducting diode can be neglected; $D - (\text{on}); v_O = v_I$


Applications of *DR* two-port networks

❖ Half-wave rectifier

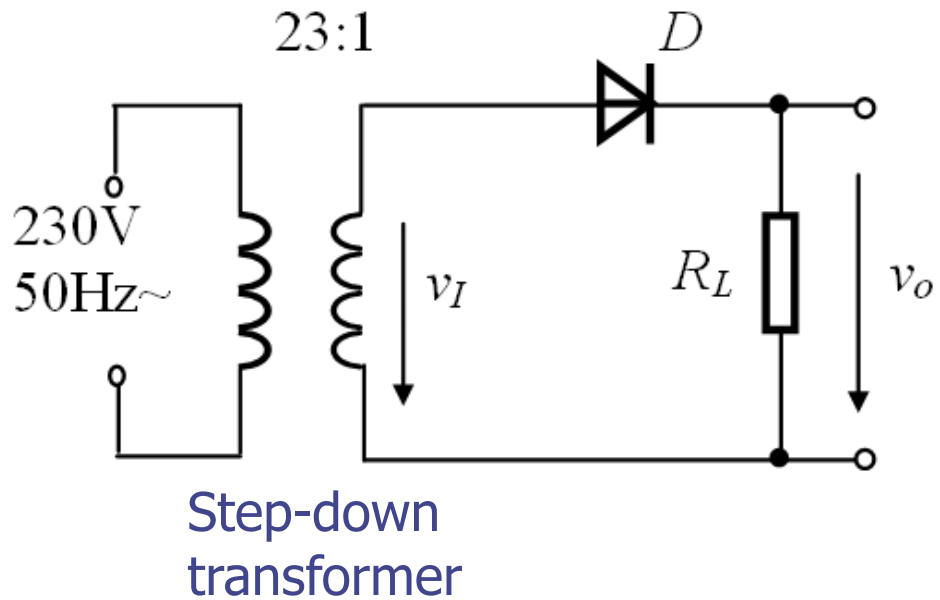



Transformers are electrical devices consisting of two or more coils of wire used to transfer electrical energy by means of a changing magnetic field.

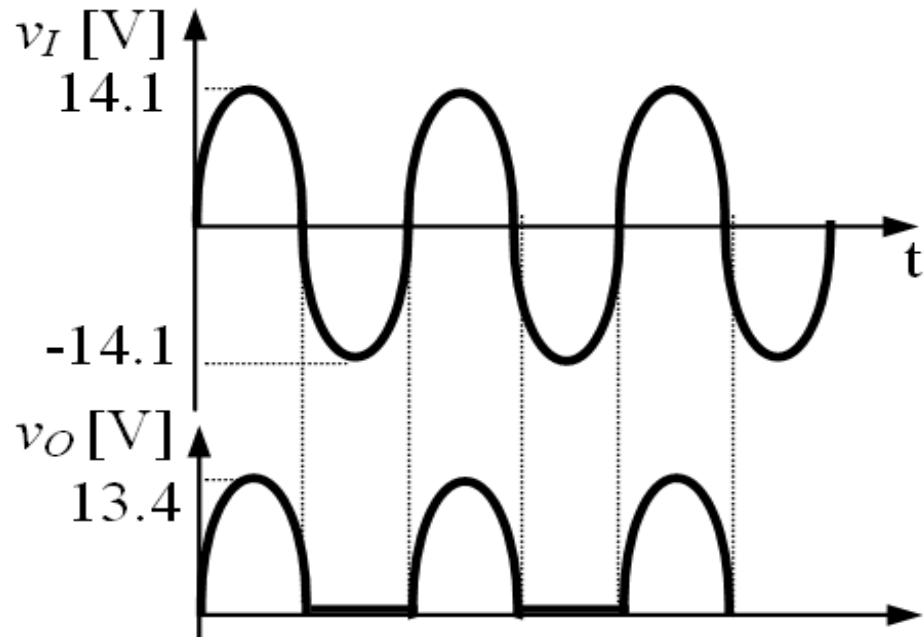The difference in voltage between the primary and the secondary windings is achieved by changing the number of coil turns in the primary winding compared to the number of coil turns on the secondary winding.



❖ Pulses selector


OPTIONAL

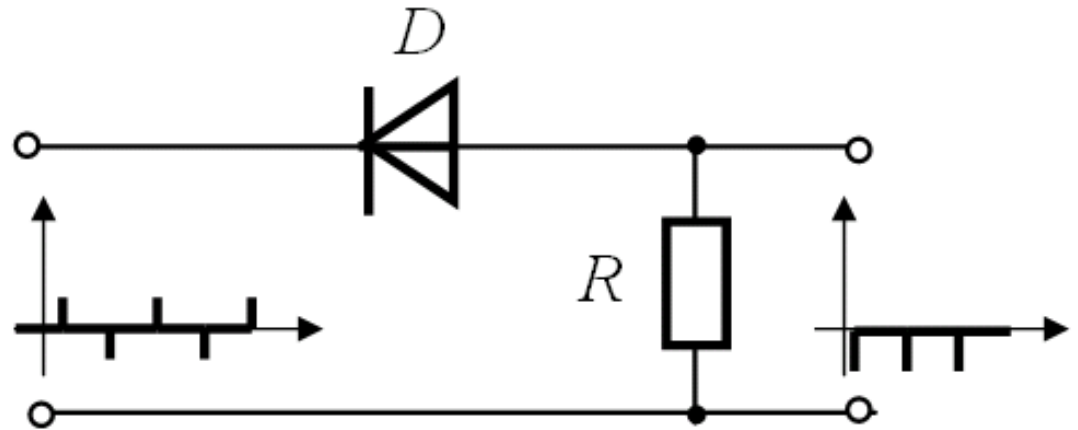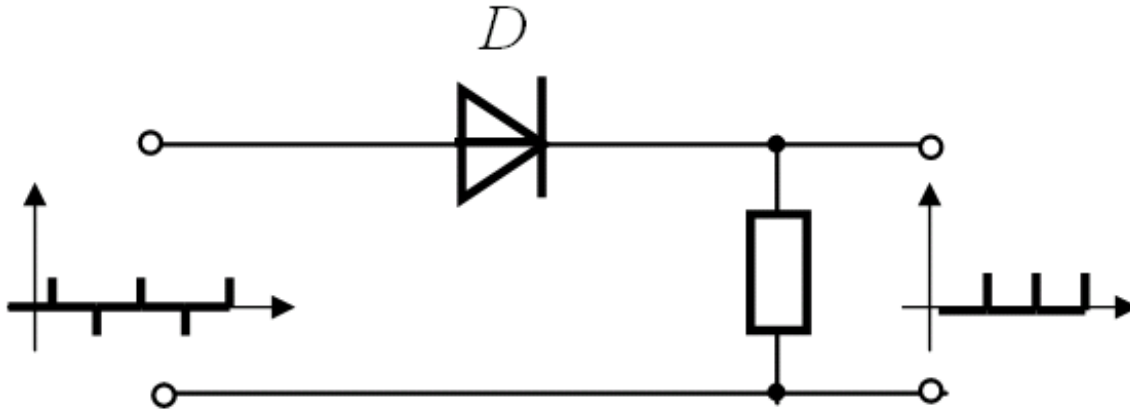





❖ Voltage limiters

❖ VTC?


simple

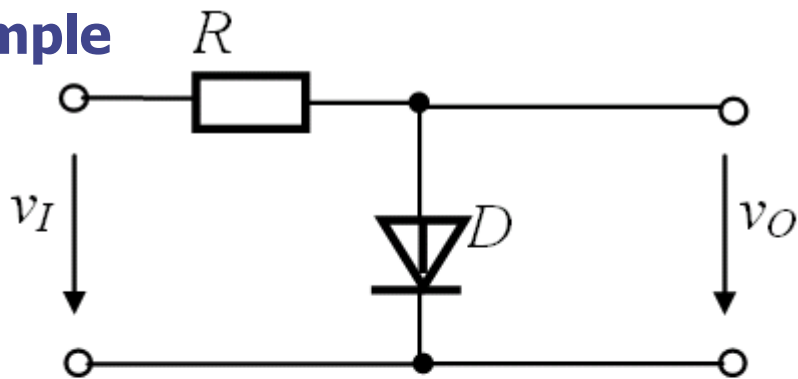

double

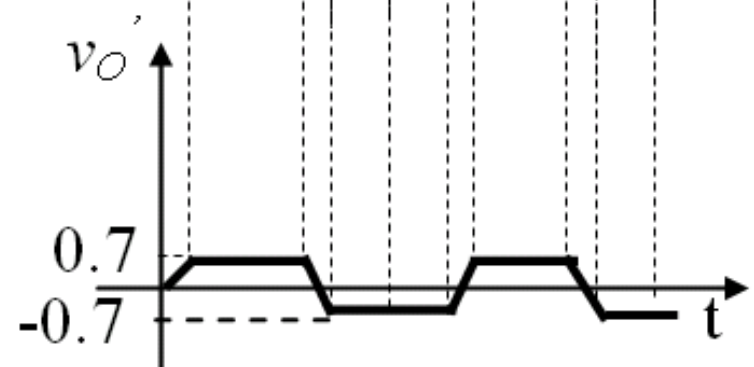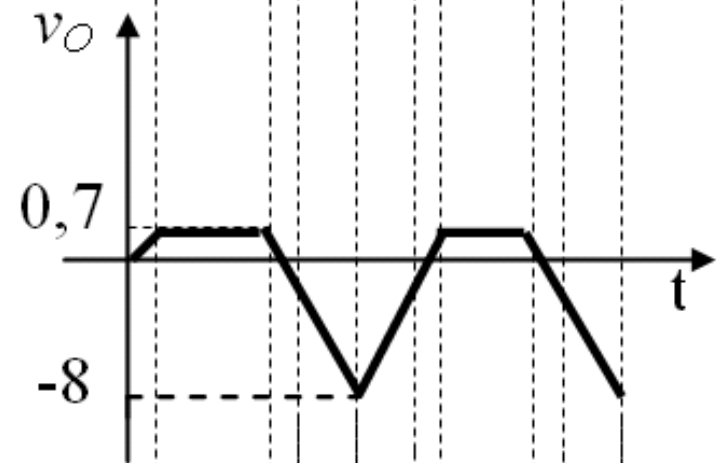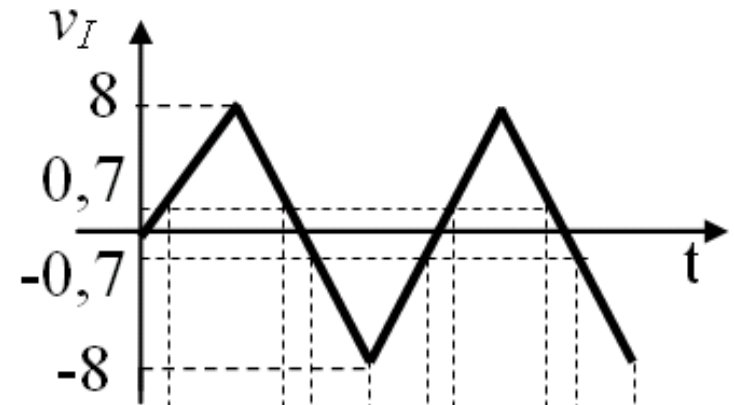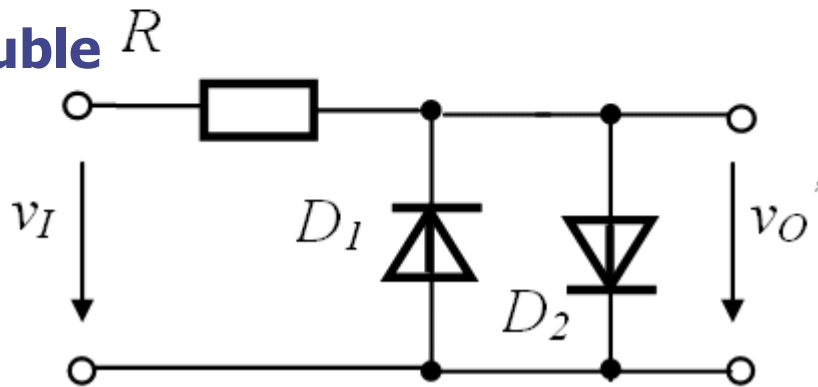

❖ Maximum multi-port networks

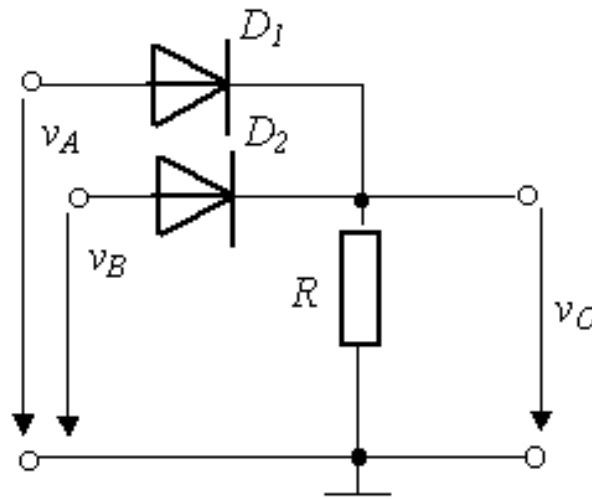

$$\begin{cases} v_A > v_B \\ v_A > 0.7\text{V} \end{cases}$$

$$D_1 - (\text{on}), D_2 - (\text{off}); \quad v_O = v_A - 0.7\text{V}$$

$$\begin{cases} v_B > v_A \\ v_B > 0.7\text{V} \end{cases}$$


$$D_1 - (\text{off}), D_2 - (\text{on}); \quad v_O = v_B - 0.7\text{V}$$

$$\begin{cases} v_A < 0.7\text{V} \\ v_B < 0.7\text{V} \end{cases}$$

$$D_1 - (\text{off}), D_2 - (\text{off}); \quad v_O = 0$$

$$v_O = \max(v_A - 0.7\text{V}; v_B - 0.7\text{V}; 0\text{V})$$

Maximum multi-port networks

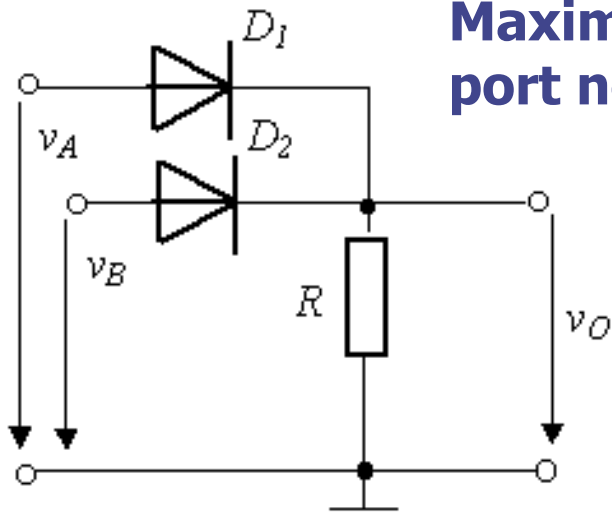


$$v_O = \max(v_A - 0.7\text{V}; v_B - 0.7\text{V}; 0)$$

$$v_O = \max(v_A; v_B; 0) \text{ neglecting } 0.7\text{V}$$


- neglecting 0.7V
- · - · - D – constant-voltage-drop

What is the peak value of the current through each circuit element if $R=5\text{k}\Omega$?

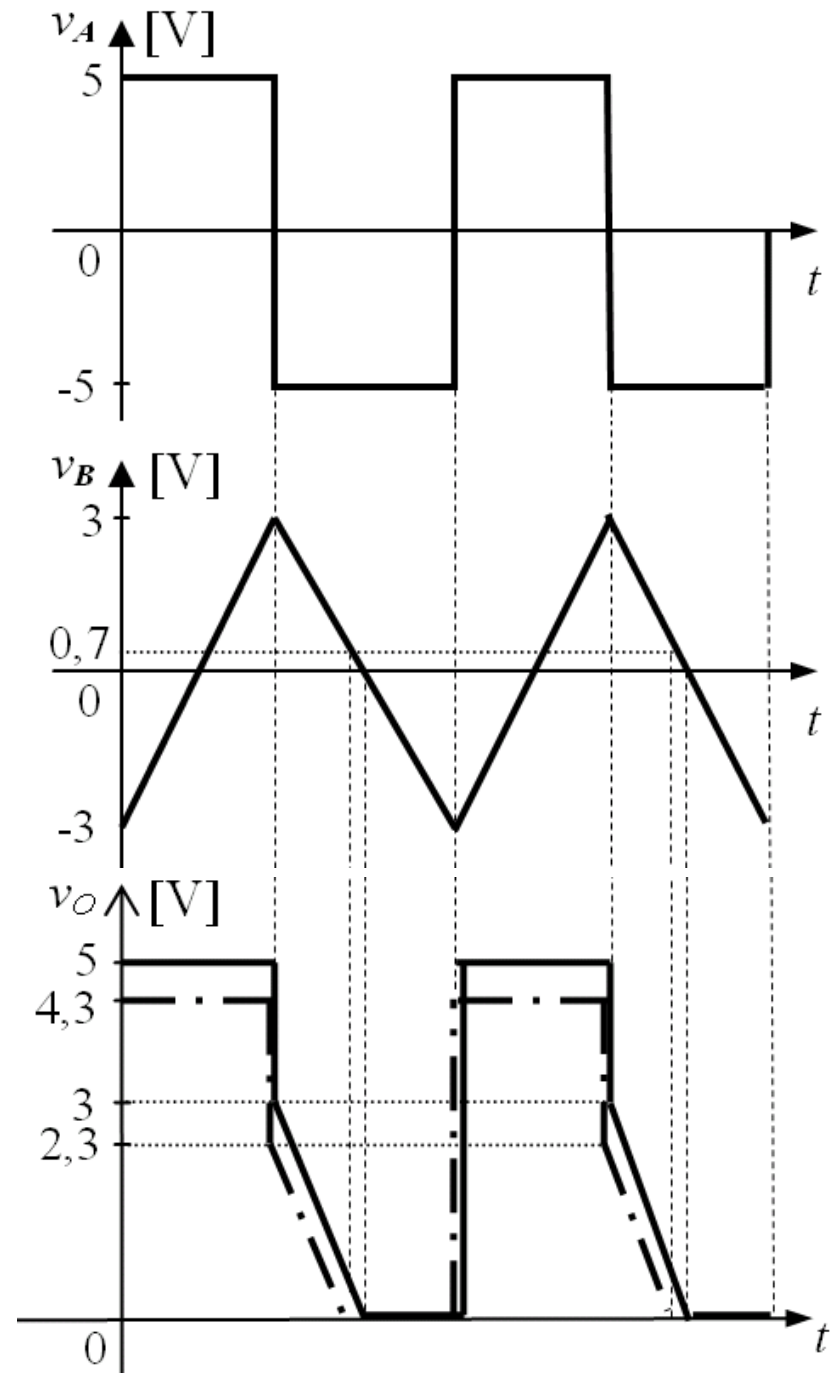What is the range of values for R , if the peak forward current through diode is 200mA?






❖ Minimum multi-port networks

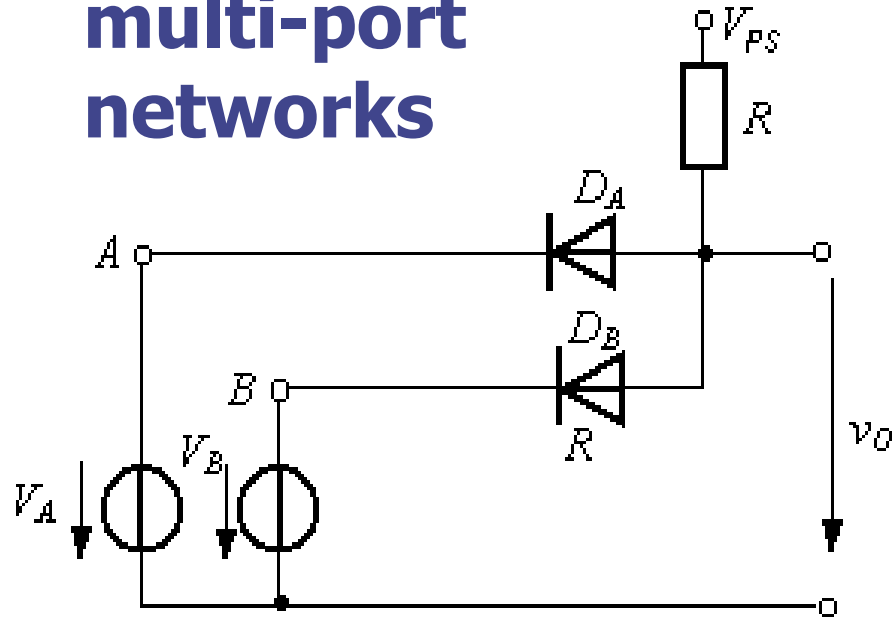

$$v_O = ?$$

$$v_O = \min(v_A + 0.7V; v_B + 0.7V; V_{PS})$$

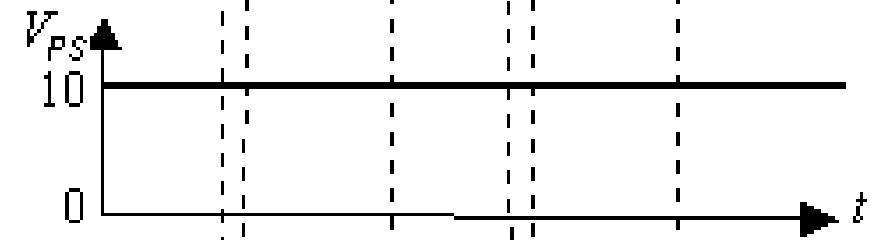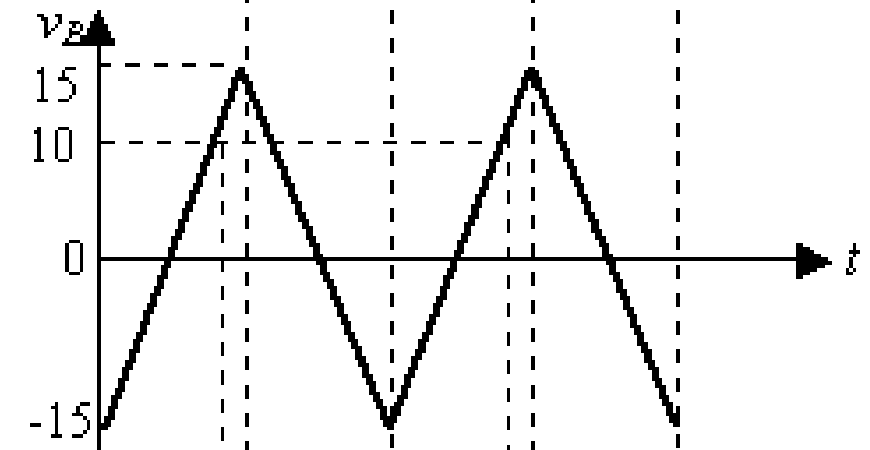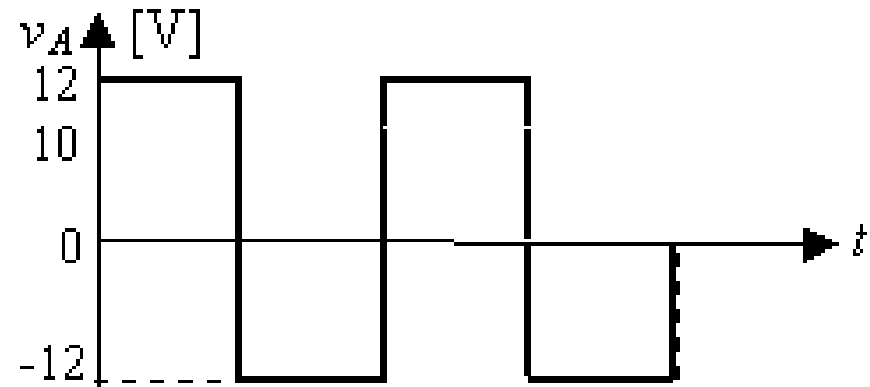
$$v_O = \min(v_A, v_B, V_{PS}) \text{ neglecting } 0.7V$$




$$v_O(t) = ?$$

DR logic circuits

analog signal

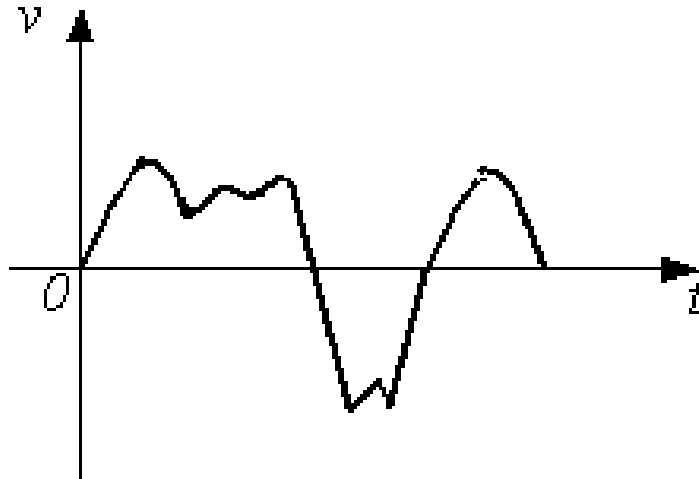

digital signal

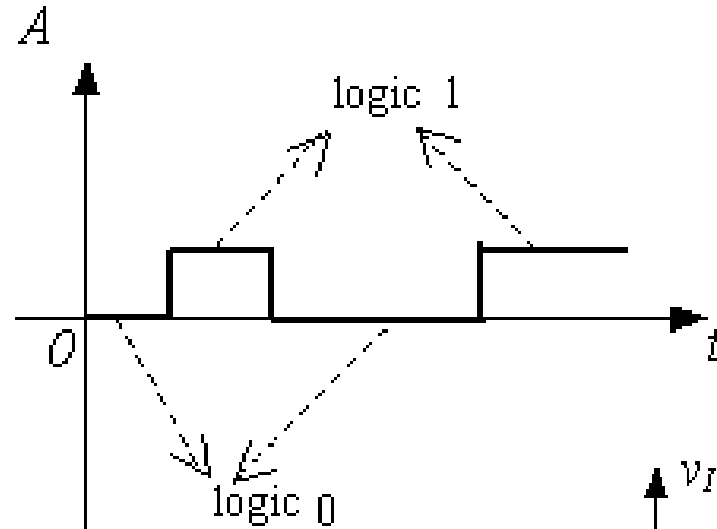

Logic 0

false

low

Logic 1


true

high


0V → logic 0

5V → logic 1

CMOS logic family
supplied at +5V

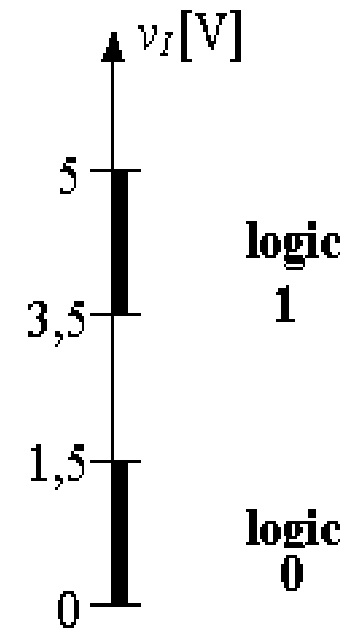

❖ two-input OR circuit

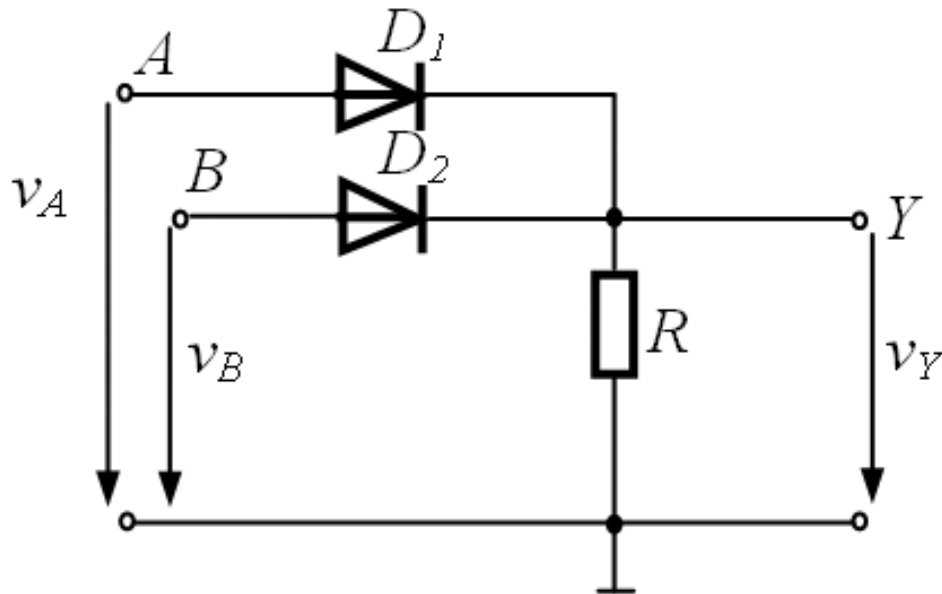

0V \rightarrow logic 0

5V \rightarrow logic 1

v_A	v_B	v_Y	D_1	D_2
0V	0V	0V	(off)	(off)
0V	5V	4.3V	(off)	(on)
5V	0V	4.3V	(on)	(off)
5V	5V	4.3V	(on)	(on)

operating table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

truth table

❖ three-input AND circuit

0V → logic 0

5V → logic 1

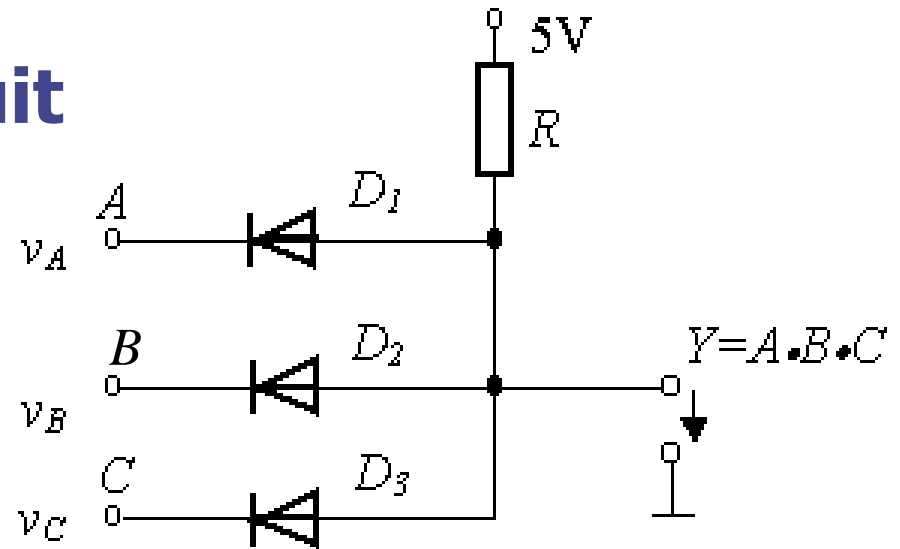

v_A [V]	v_B [V]	v_C [V]	v_Y [V]
0	0	0	0.7
0	0	5	0.7
0	5	0	0.7
0	5	5	0.7
5	0	0	0.7
5	0	5	0.7
5	5	0	0.7
5	5	5	5


operating table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

truth table


❖ Full wave rectifier - diode bridge

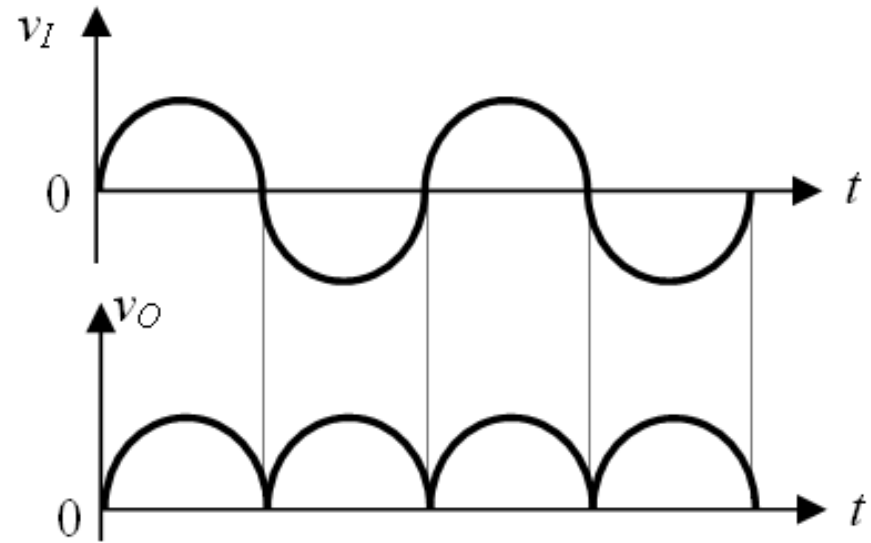neglecting 0.7V across
the conducting diode



➤ positive half, $v_I > 0$
 D_1, D_3 – (on) D_2, D_4 – (off)

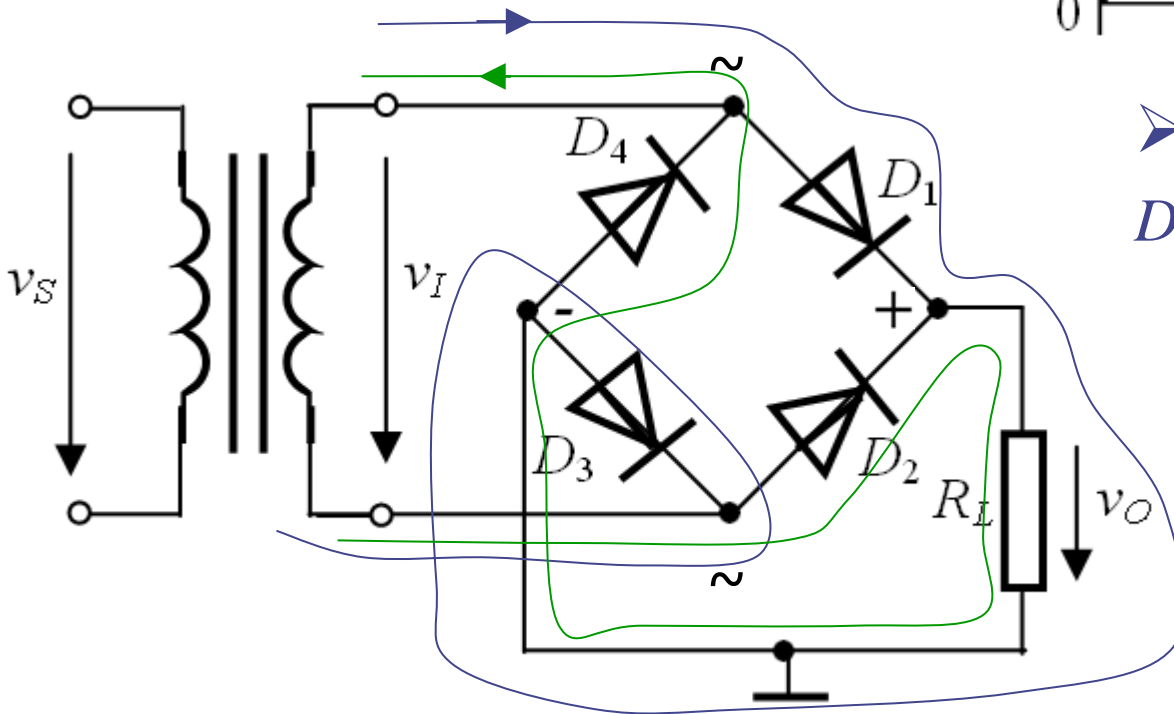
➤ negative half, $v_I < 0$
 D_1, D_3 – (off) D_2, D_4 – (on)



$v_I > 0V$


$v_I < 0V$

❖ Backup Supply

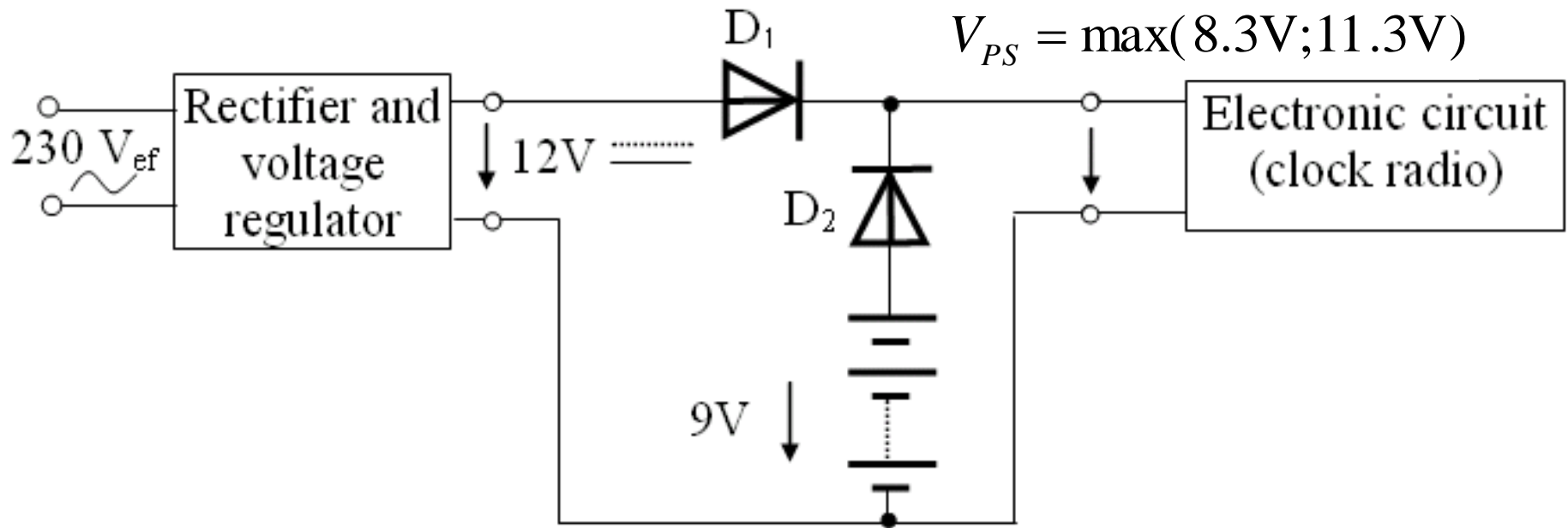

Problem

$$v_I(t) = \hat{V}_I \sin \omega t$$

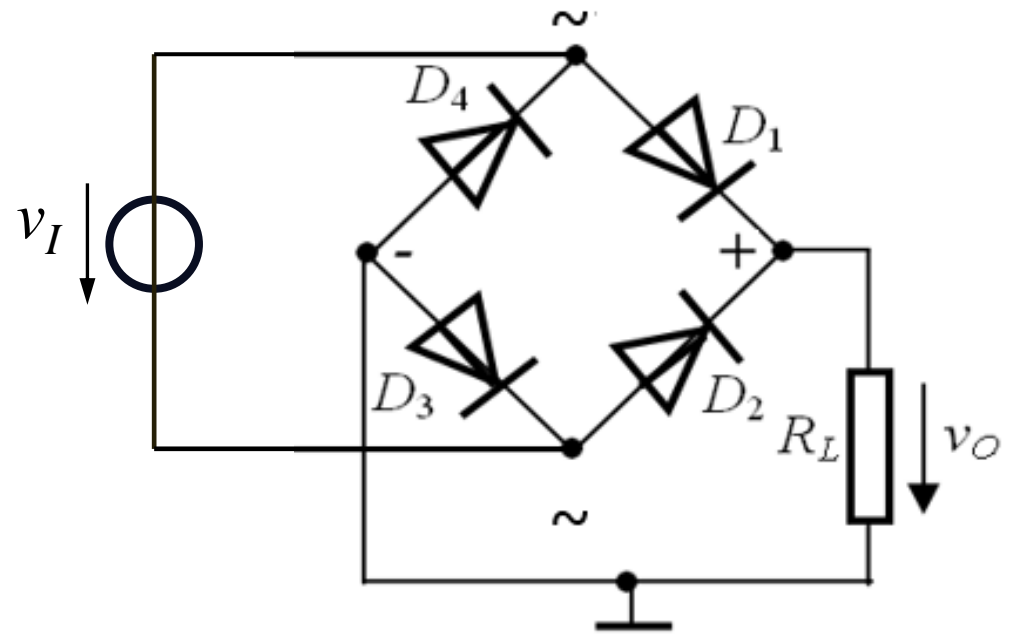


For the circuit in the figure, $R_L=50\Omega$. Assume $\hat{V}_I = 25\text{V}$

- $v_o(t)$ and $i_o(t)$
- What are the value of the maximum reverse voltage v_{DR} across each diode and the maximum forward current through each diode?
- Repeat a) and b) assuming $\hat{V}_I = 6.4\text{V}$

Power-supply filtering

v_I is the voltage in a secondary winding of a step-down line transformer.

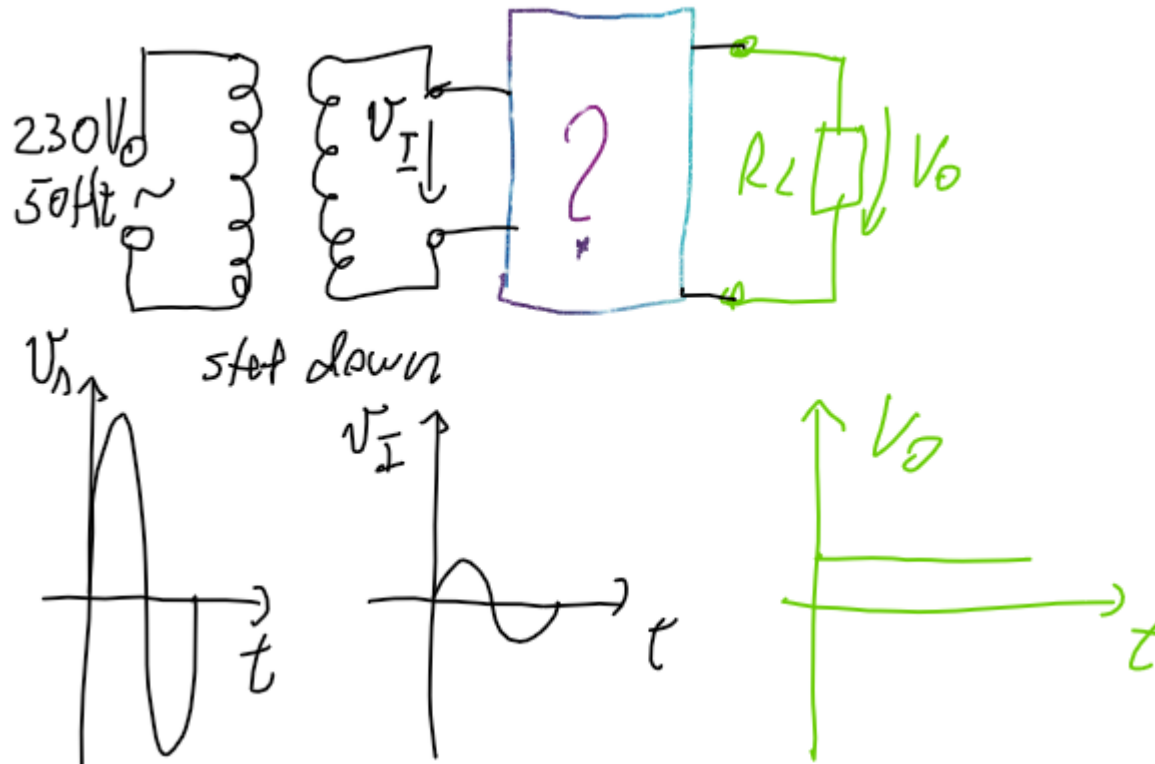It is required to obtain an almost dc voltage (on a load resistor)






How “to smooth” the output voltage (as close as possible to dc)?

Power-supply filtering - cont.

1st step





Half-wave (full wave) rectifier

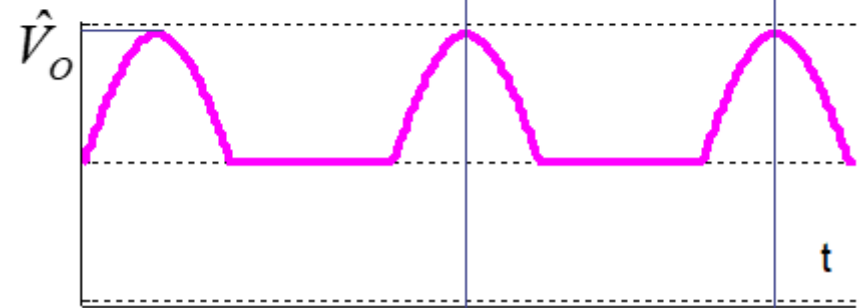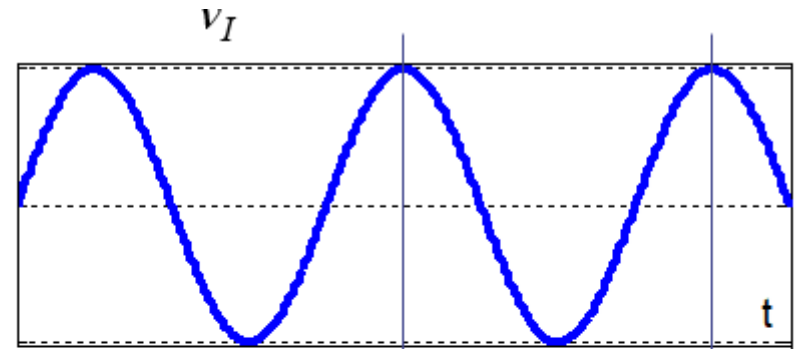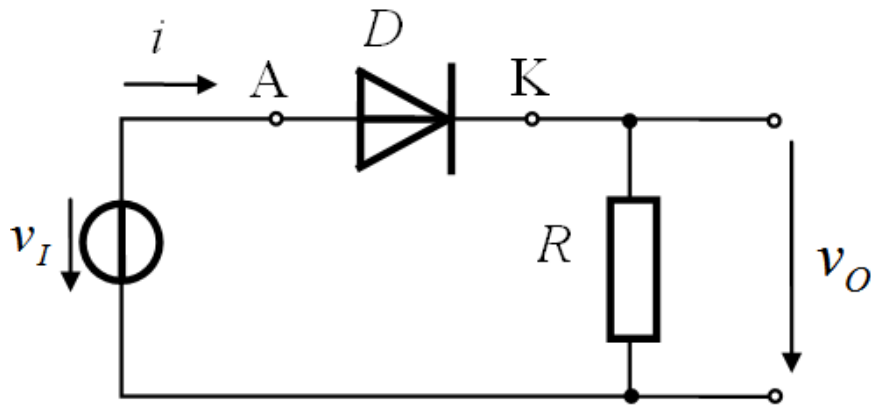


How “to smooth” the output voltage (as close as possible to dc)?

Power-supply filtering

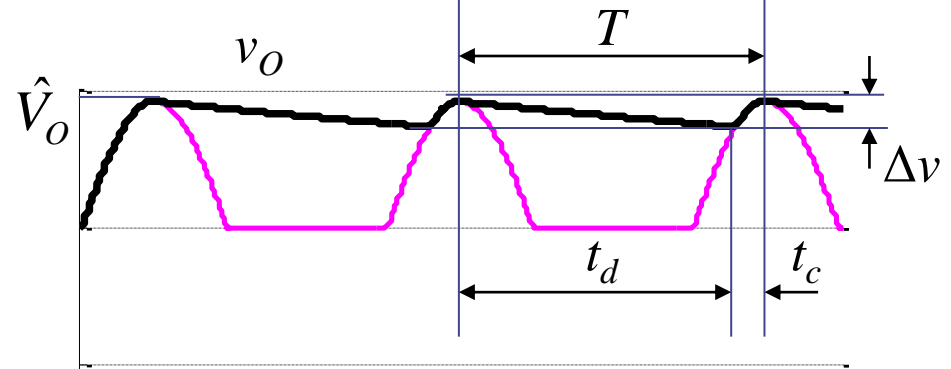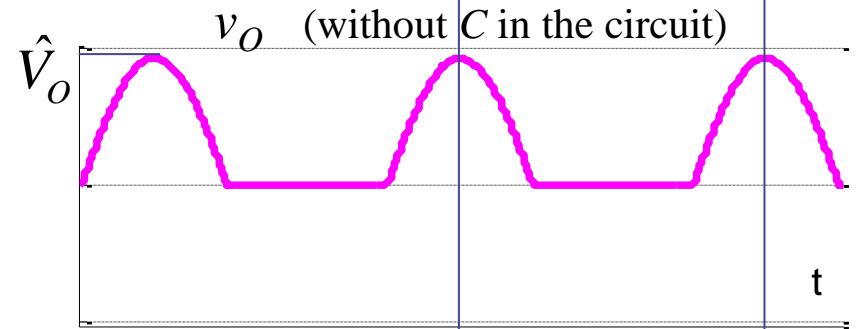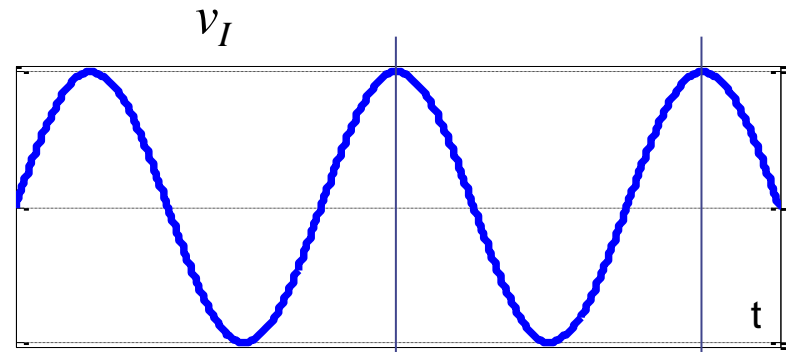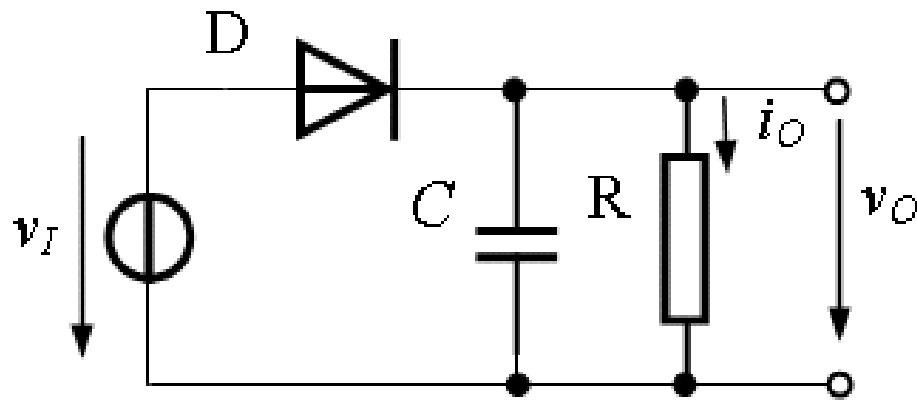Half-wave rectifier with capacitive filter (and load)



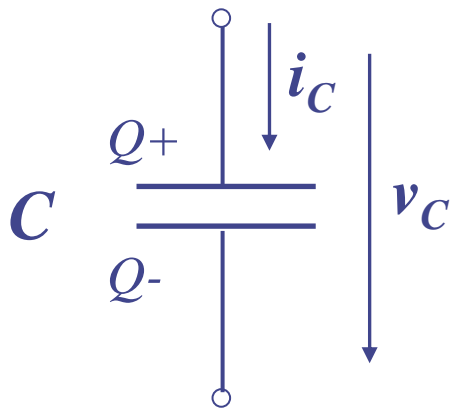Between successive peaks of input voltage (and rectified voltage), D - off, the capacitor acts as a element of electrical energy storage, providing electrical energy in the load, with a decrease of its own voltage.



$$C dv_C(t) = i_C(t) dt$$

$$v_C(t) = \frac{1}{C} \int_{t_0}^t i_C(t) dt + v_C(t_0)$$

If the **current** through the capacitor, can be approximated as being a **constant** one I_C :

$$v_C(t) = \frac{1}{C} I_C (t - t_0) + v_C(t_0)$$


$$v_C(t) - v_C(t_0) = \frac{1}{C} I_C (t - t_0)$$

$$\Delta v_C = \frac{1}{C} I_C \Delta t$$

$$C dv_C(t) = i_C(t) dt$$


$$C \Delta v_C = I_C \Delta t$$

For I_C constant

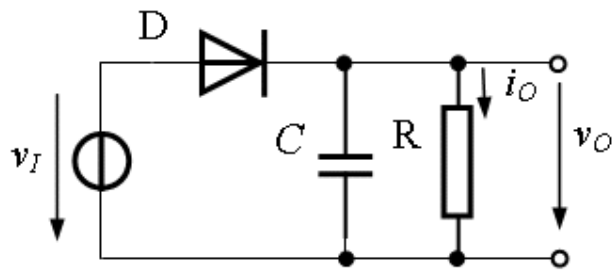

Between successive peaks of input voltage (and rectified voltage), **D - off**, the capacitor acts as a **element of electrical energy storage**, providing electrical energy in the load, with a decrease of its own voltage:

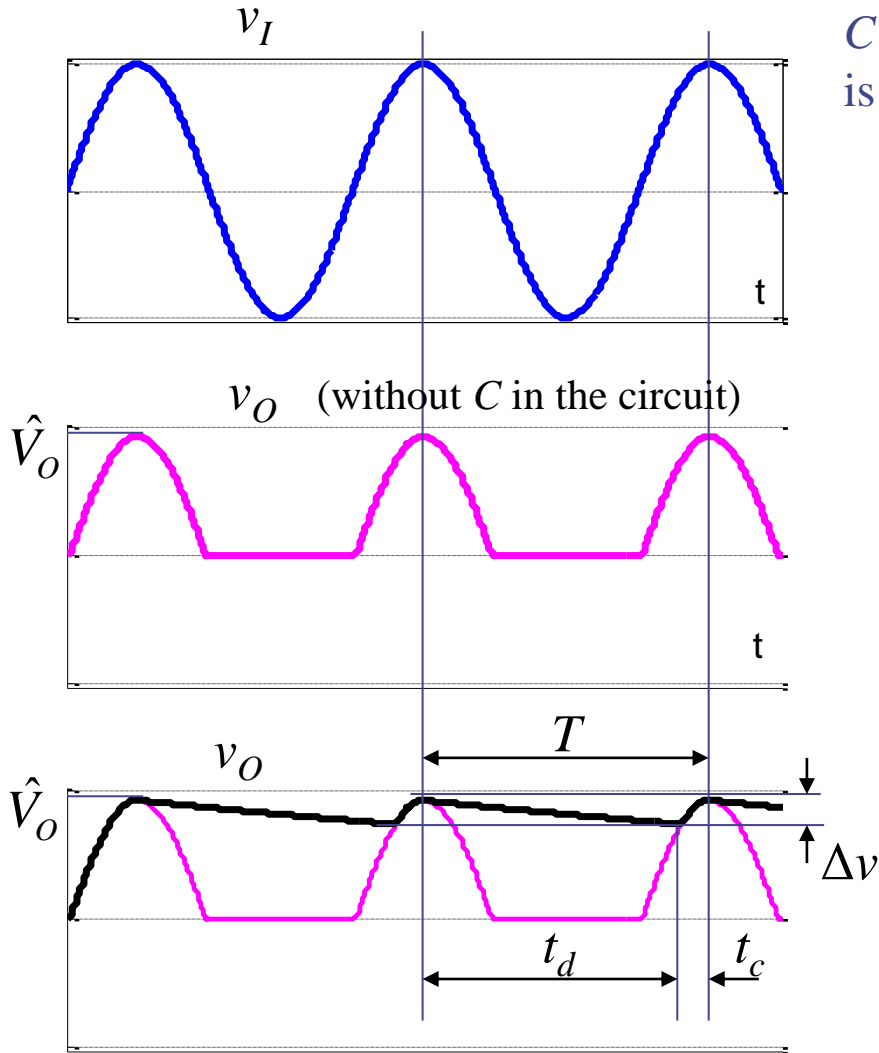C discharges through R ; the discharging current is supposed to be constant, to its maximum value.



$$\Delta v_c = \frac{1}{C} I_C \Delta t$$

$$I_C = \frac{\hat{V}_o}{R}$$

$$\Delta t = t_d = T - t_c \approx T$$


$$\Delta v_c = \Delta v = \frac{1}{C} I_C \Delta t = \frac{1}{C} \frac{\hat{V}_o}{R} T$$

$$\Delta v = \hat{V}_o \frac{T}{RC} = \frac{1}{f} \frac{\hat{V}_o}{RC}$$

RC – time constant of the circuit

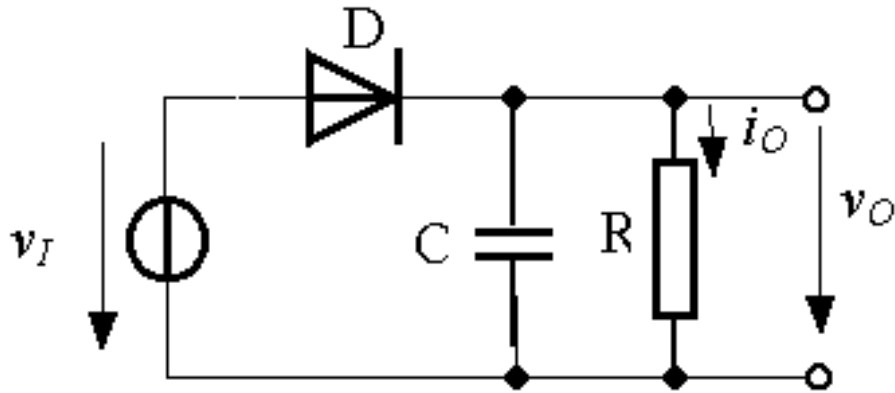Example

$$\hat{V}_I = 10.7\text{V} \quad f = 50\text{ Hz} \quad R_L = 100\Omega \quad \Delta v < 1.5\text{V} \quad C = ?$$



$$\hat{V}_O = \hat{V}_I - 0.7\text{V} = 10\text{V}$$

$$\Delta v = \frac{\hat{V}_O}{fRC} < 1.5\text{V}$$

$$C > \frac{\hat{V}_O}{1.5fR} = \frac{10}{1.5 \cdot 50 \cdot 100} = 1333\ \mu\text{F} \quad C > 1333\ \mu\text{F}$$

We chose an electrolytic capacitor $C = 1500\ \mu\text{F}/25\text{V}$

What is the actual value of the output ripple?

What should be a new value of C if the output ripple must be reduce to the half?

Solve again in the case of full-wave rectification.