

# Op-amp simple comparators




Op-amp in *switching mode*  $\Rightarrow$  *comparators* with op-amp.

The **voltage comparator** compares two input voltages and signalizes to the output what input voltage is greater.

- voltages comparison: by the sign of their difference
- according to the sign of the difference, the comparator outputs one or another of the two possible output voltages
- for op-amp comparators one can consider only one input, namely the difference between  $v^+$  and  $v^-$ , meaning  $v_D$

$$V_O \in \{V_{OL}, V_{OH}\} \quad \begin{array}{l} v_D > 0, \text{ that is } v^+ > v^-, \quad v_O = V_{OH} \\ v_D < 0, \text{ that is } v^+ < v^-, \quad v_O = V_{OL} \end{array}$$

# Op-amp model in switching regime

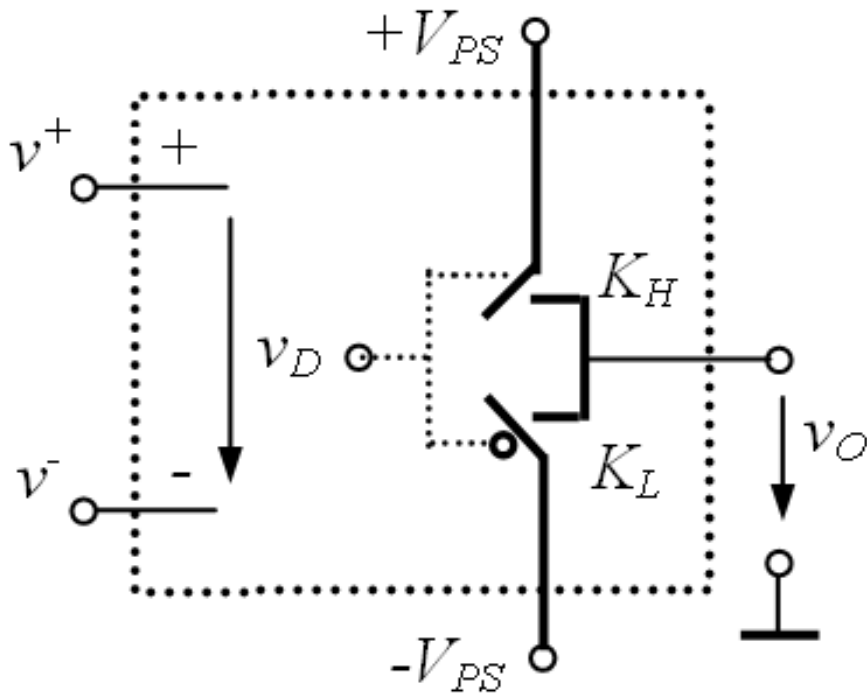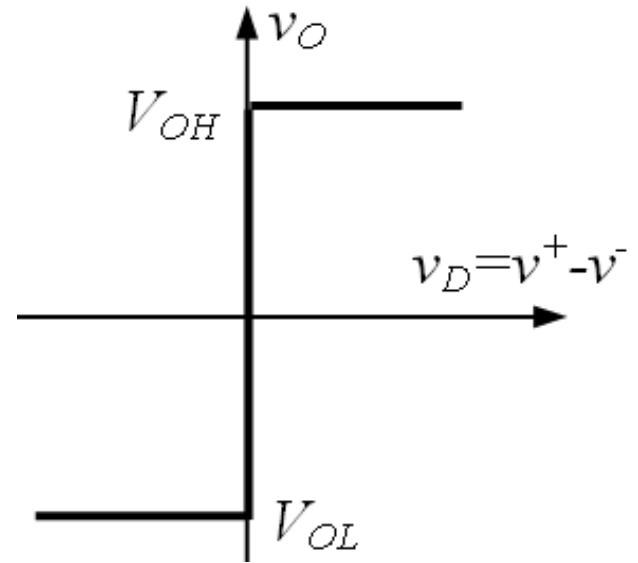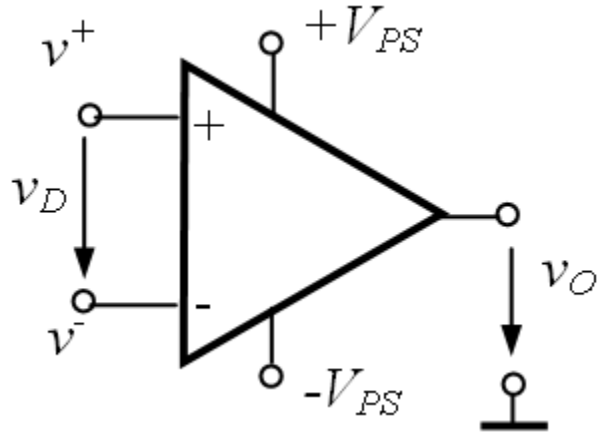

$v_D$	$K_H$	$K_L$	$v_O$
$> 0$	<i>on</i>	<i>off</i>	$V_{OH} = +V_{PS}$
$< 0$	<i>off</i>	<i>on</i>	$V_{OL} = -V_{PS}$

**Appropriate for  
rail-to-rail op-amp**

# Two types of voltage comparators:

## ➤ **simple comparators**

- ❖ no feedback,
- ❖ **one threshold** voltage.

## ➤ **hysteresis comparators**

- ❖ positive feedback,
- ❖ **two threshold** voltages

□ **threshold voltage**  $V_{Th}$ : that particular value of the input voltage  $v_I$  for which

- ✓ the output switches
- ✓  $v_D$  - crosses through zero ( $v_D = 0$ )

# Simple Comparators

- no feedback, one threshold voltage

## To find $V_{Th}$ :


- find the expression of  $v_D$
- use the condition  $v_D = 0$  and replace  $v_I$  with  $V_{Th}$
- obtain  $V_{Th}$

## Simple comparators with $V_{Th} = 0V$


- one grounded input
- $v_I$  is applied to the other input

# Comparators with $V_{Th} = 0V$

- noninverting

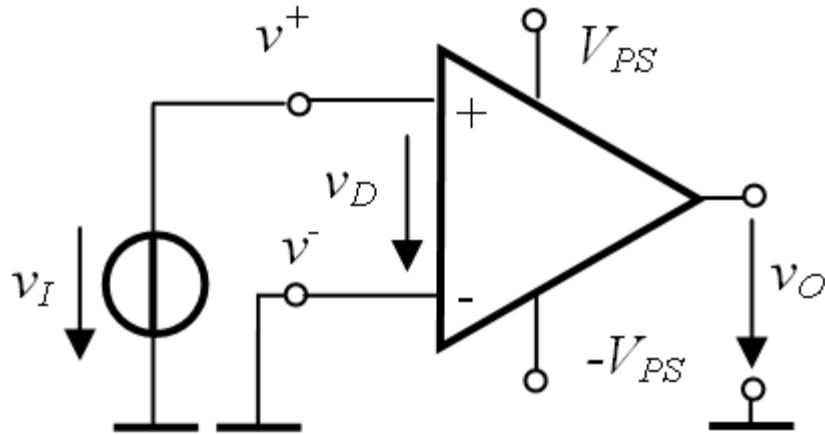
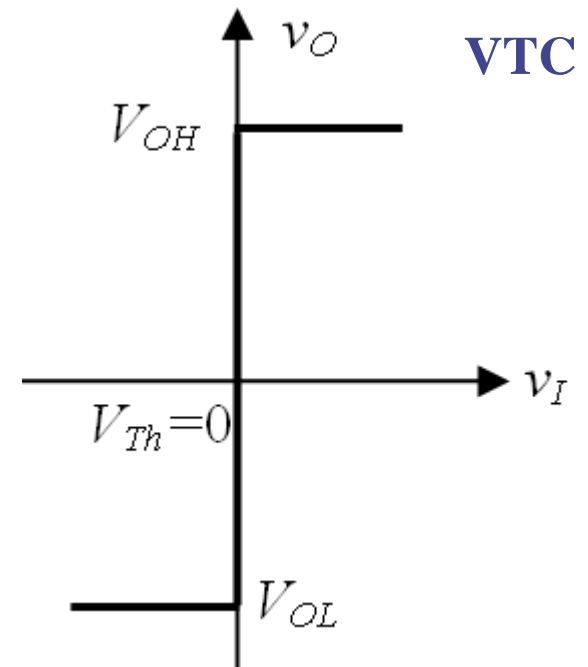
$$v_O = \begin{cases} V_{OH} & \text{if } v_D > 0, \text{ this is } v_I > 0 \\ V_{OL} & \text{if } v_D < 0, \text{ this is } v_I < 0 \end{cases}$$



$$v_D = v^+ - v^-$$

$$v^+ = v_I; \quad v^- = 0$$

$$v_D = v_I$$



$$v_D = 0; \quad V_{Th} = 0$$

How does the output voltage look like if the input voltage is a sine wave with 3 V amplitude and the supply is  $\pm V_{PS} = \pm 12 V$ ?

# Comparators with $V_{Th} = 0V$ – cont.
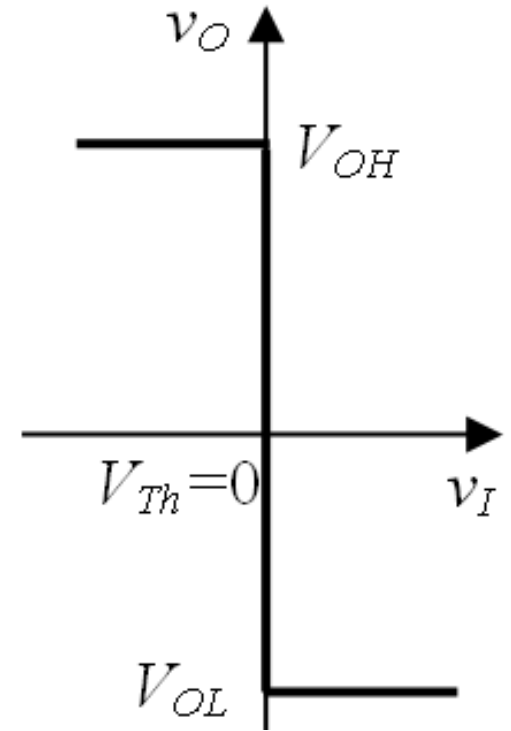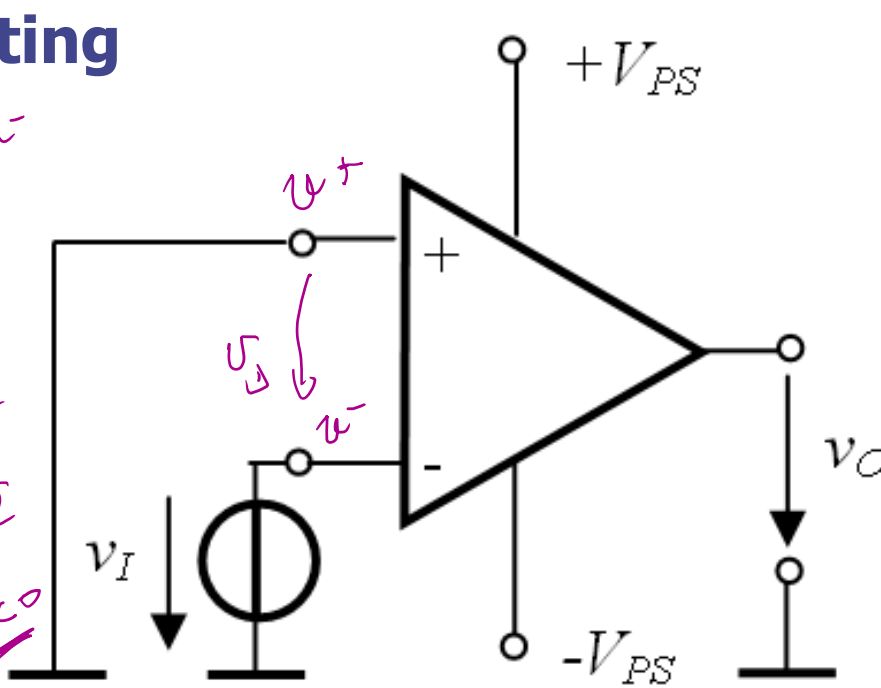
## • inverting


$v_+ = v_+ - v_-$   
 $v_+ = 0$   
 $v_- = v_i$   
 $v_+ = 0 - v_i$   
 $v_+ = -v_i$   
 $v_+ > 0: v_i < 0$   
 $v_+ < 0: v_i > 0$   
 $v_o = V_{OH}$




How does the output voltage look like if the input voltage is a sine wave with 3V amplitude and the supply is  $\pm V_{PS} = \pm 12V$ ?

# Comparators with $V_{Th} \neq 0$

noninverting




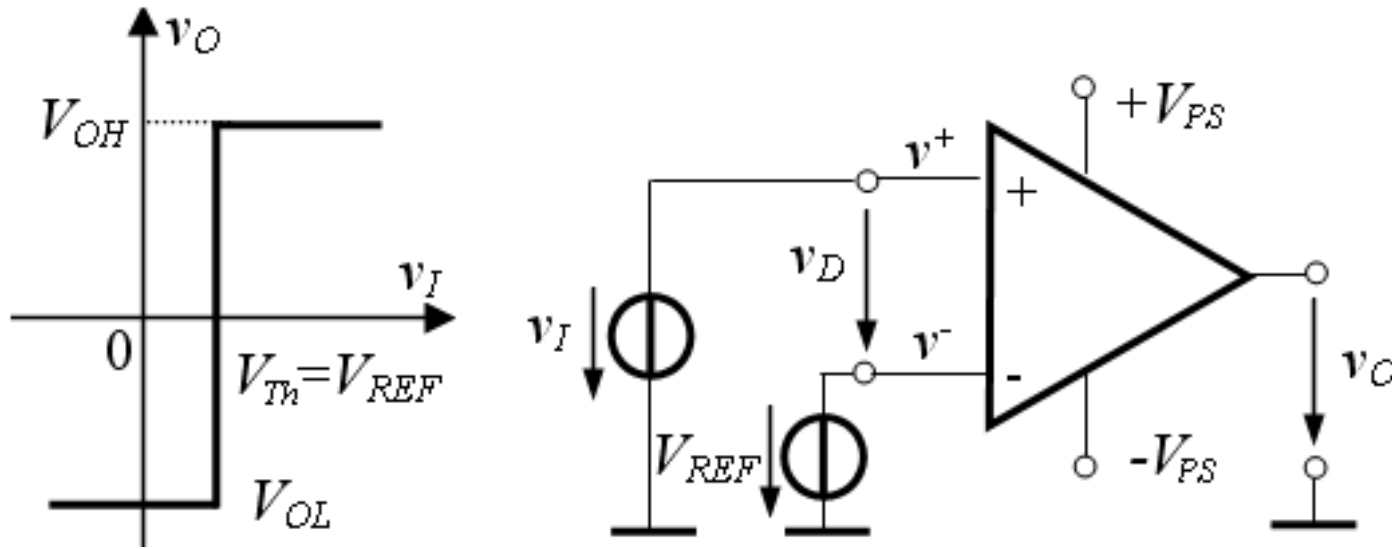


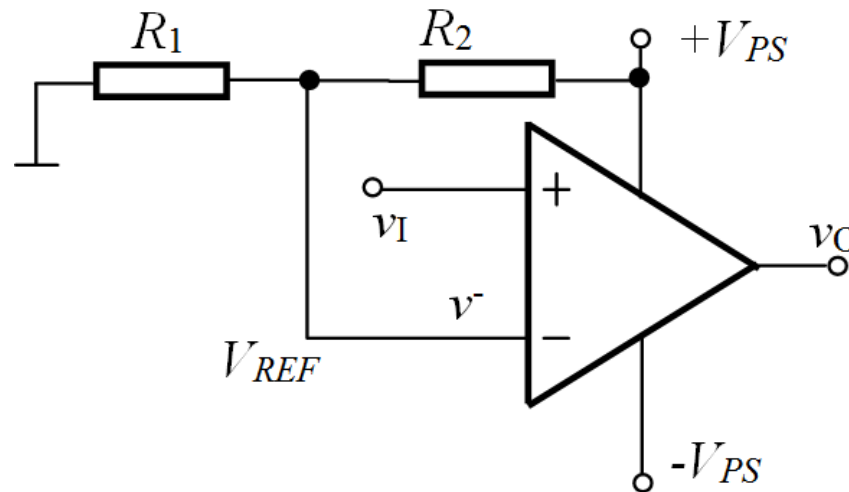How can  $V_{REF}$  be obtained from the available dc sources?



$$V_{REF} = \frac{R_1}{R_1 + R_2} V_{PS}$$

# • Example

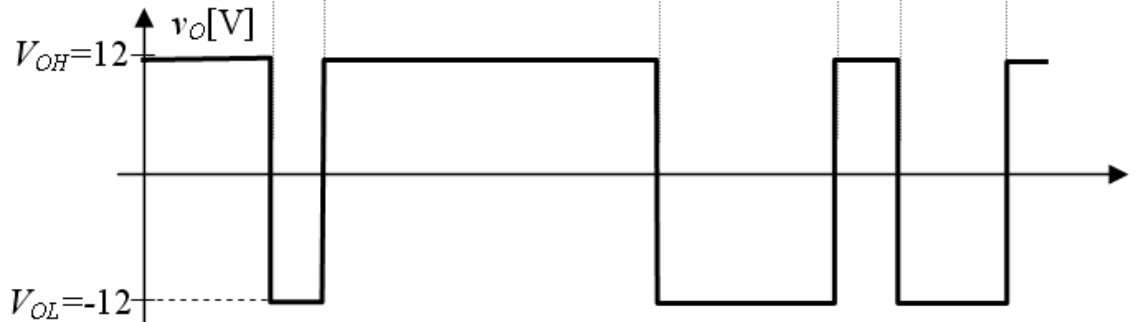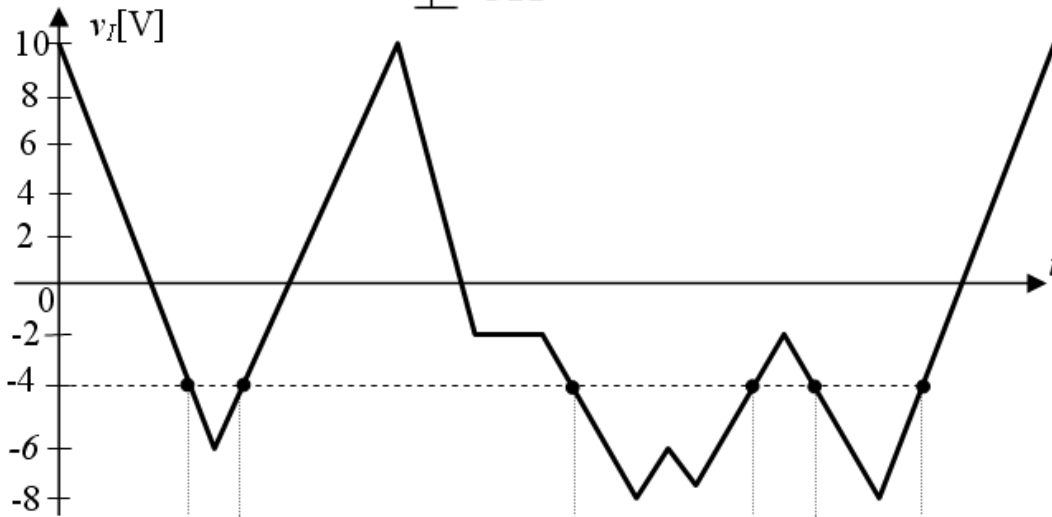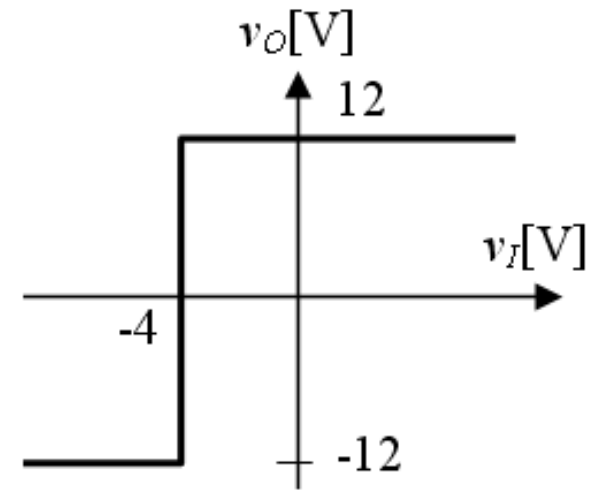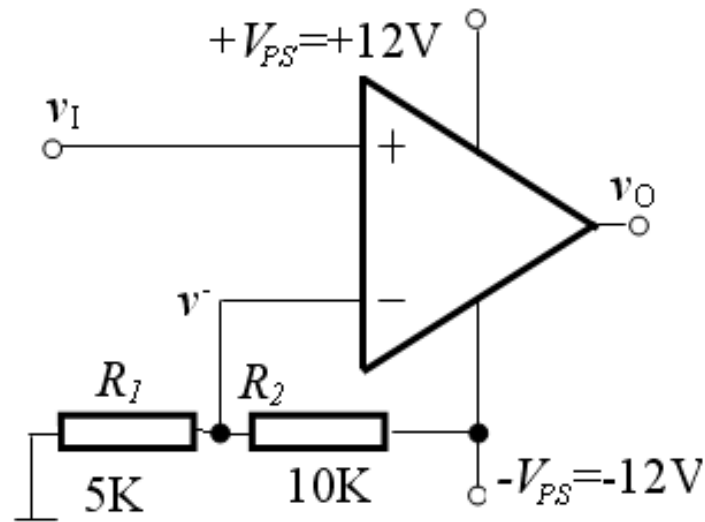

## Redesign:

✓ inverting

✓  $V_{Th} = +6V$




? VTC

?  $v_O(t)$



# Comparators with $V_{Th} \neq 0$

inverting

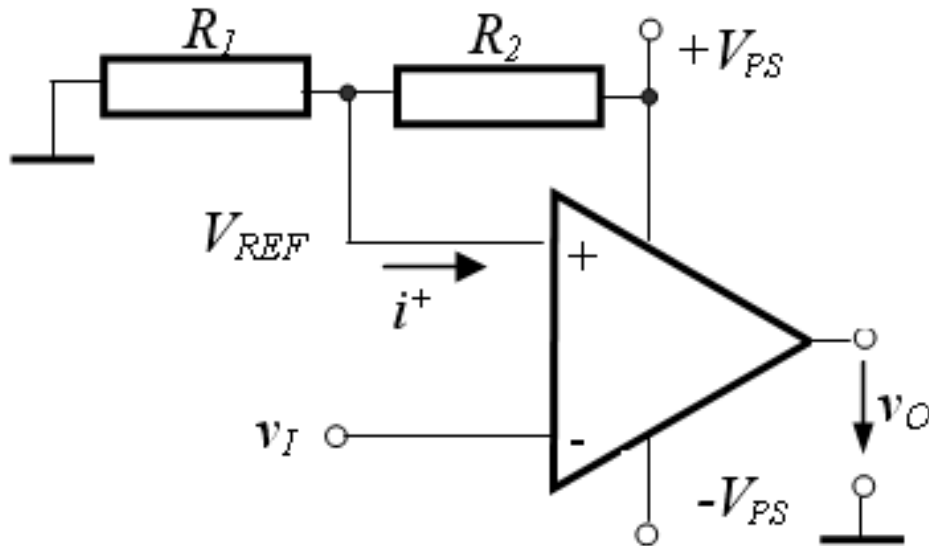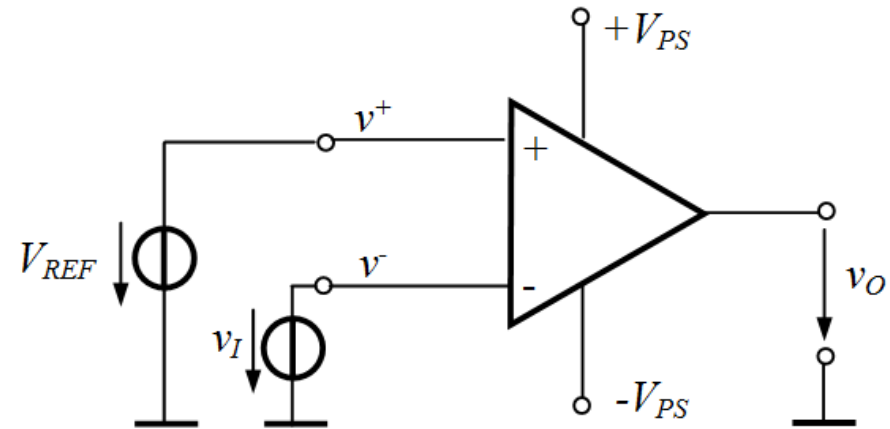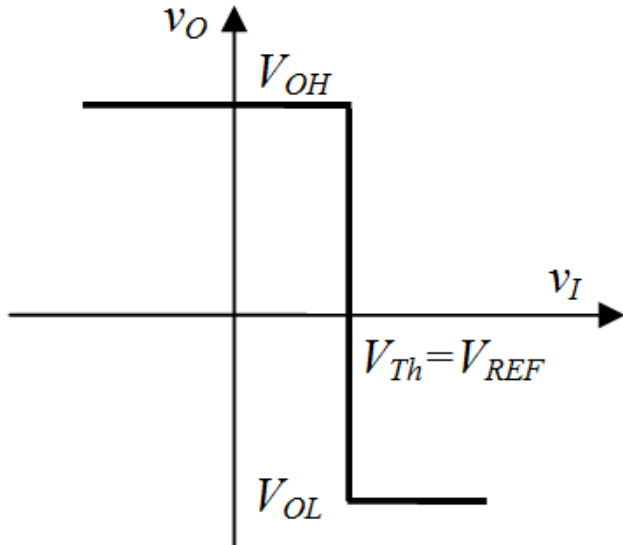

$i^+ \ll$  current through  $R_1, R_2$  divider ( $i^+ \cong 0$ )

$$V_{REF} = \frac{R_1}{R_1 + R_2} V_{PS}$$

# Op-amps specially intended for comparators

- general-purpose op-amp comparators
- **special class** of op-amp intended for comparators like: *LM306, LM 311 ,LM 399, LM 393, LM 339* :
  - **high** differential **voltages**
  - **very fast** response (very high slew rate)
  - usual comparators has **open collector** output (they necessitate an external resistor connected from the output towards a positive potential)
  - can have an extra **ground terminal** beside the usual supply terminals


# Applications of simple comparators

- **Light sensor**
- **Interface between analog and logic circuits**
- **Obtaining rectangular signal from sinusoidal (triangular) signal**
- **Optical indicator for voltage level**
- **Pulse width modulation**
- **Signalizing and control circuit**
- **Analog to digital converter**
- **.....**

# Light Sensor Circuit



Photocell *PC*  
e.g.: PDV-P8001

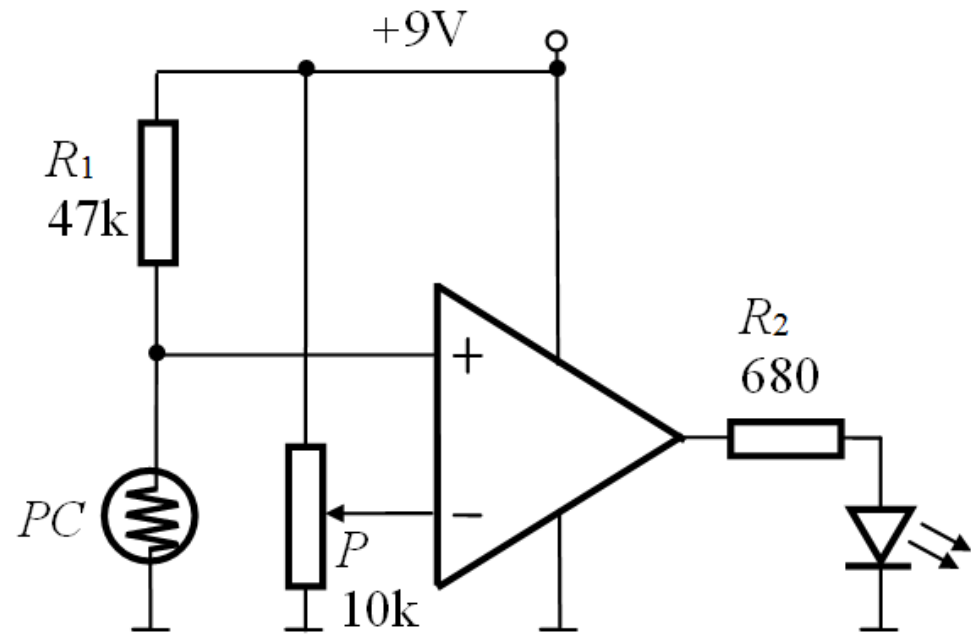

Dark resistance (big):  $R_D > 200 \text{ k}\Omega$


Illuminated resistance (small):  $R_I \in (3; 11) \text{ k}\Omega$

A photocell ( $PC$ ) is a resistor that changes resistance depending on the amount of light incident on it ( $LDR$  – light dependent resistor).

A photocell operates on semiconductor photoconductivity: the energy of photons hitting the semiconductor frees electrons to flow, decreasing the resistance.

When the amount of light increases  $\Rightarrow$  the resistance decreases

# Optical Indicator for Voltage Level

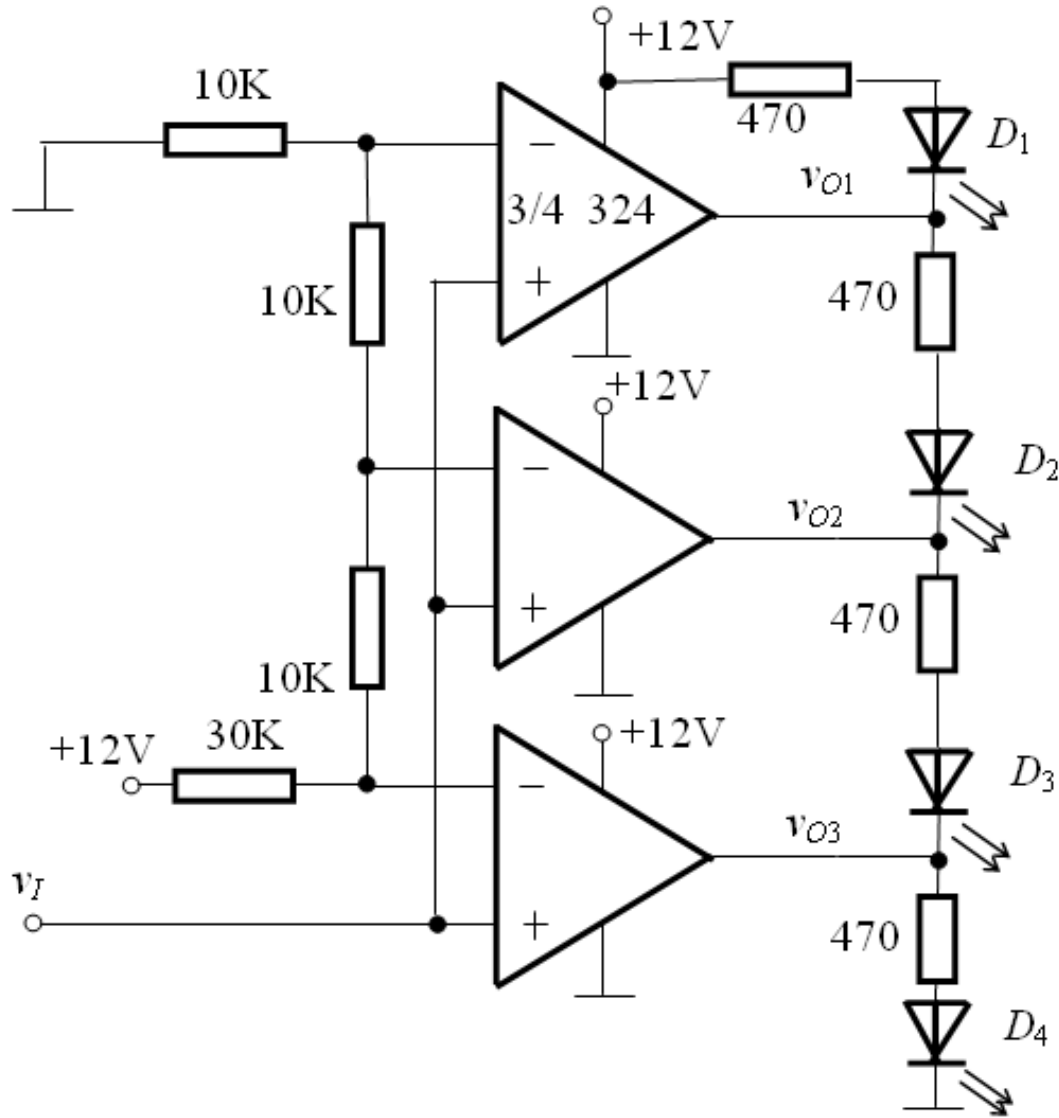

$v_I$	$v_{O1}$	$v_{O2}$	$v_{O3}$	LED State
12V	12V	12V	12V	$D_4$ -on
6V	12V	12V	0V	$D_3$ -on
4V	12V	0V	0V	$D_2$ -on
2V	0V	0V	0V	$D_1$ -on
0V	0V	0V	0V	$D_1$ -on


Design a bar graph optical indicator for the voltage level using 5 LEDs

# LED Bar Graph Dual Column Vu-meter display Decibel level 2x12

Bar graph LED indicating the audio level under 2X12 levels (stereo)

It contains 12 LEDs per side (7 green, 2 orange, 3 red).

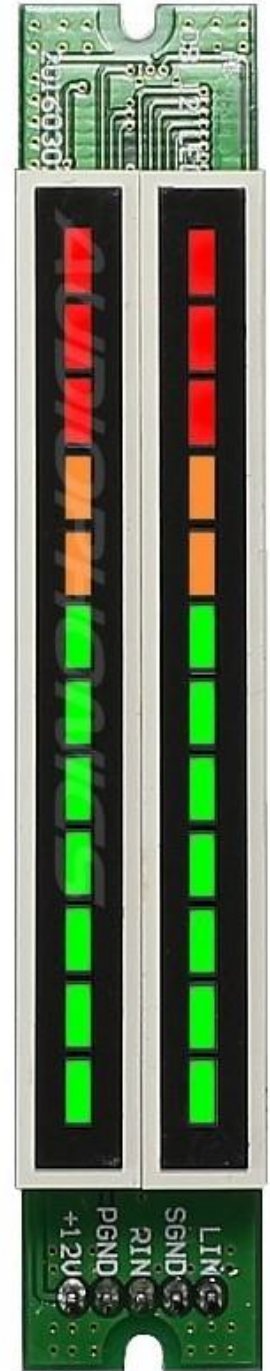The display speed and peak level can be adjusted individually by the knob on the rear panel.



# Analog to Logic Circuits Interfacing

High speed  
voltage  
comparator

