
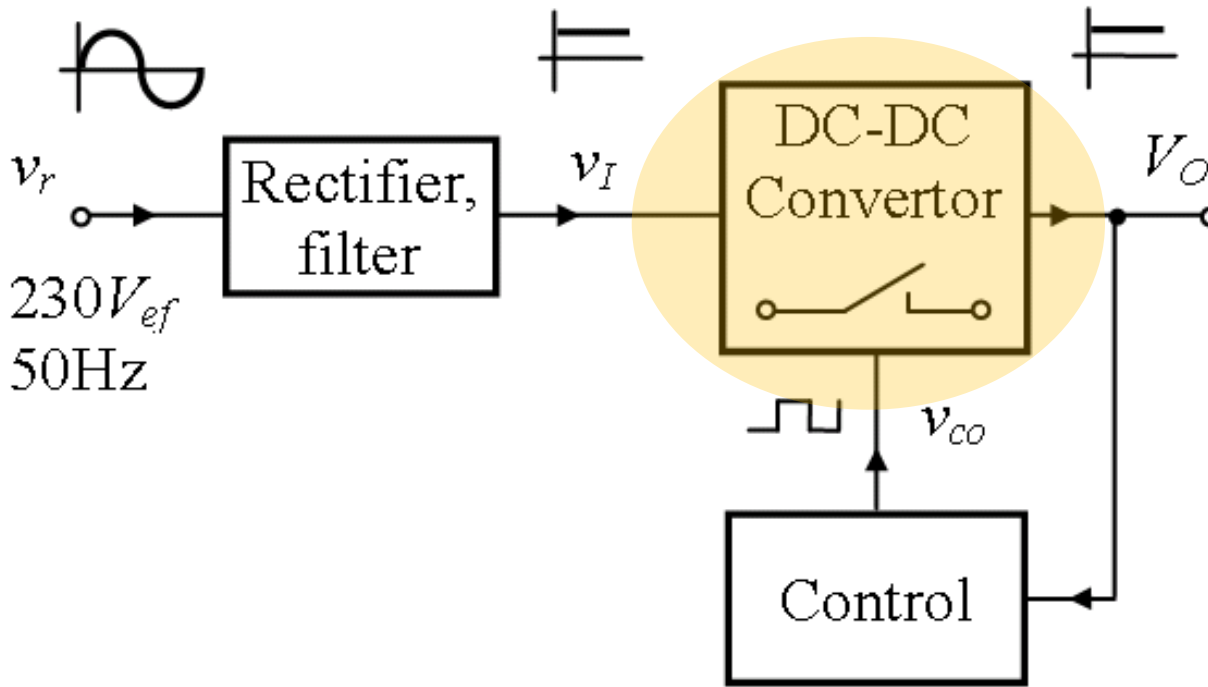


Switched Mode Power Supply

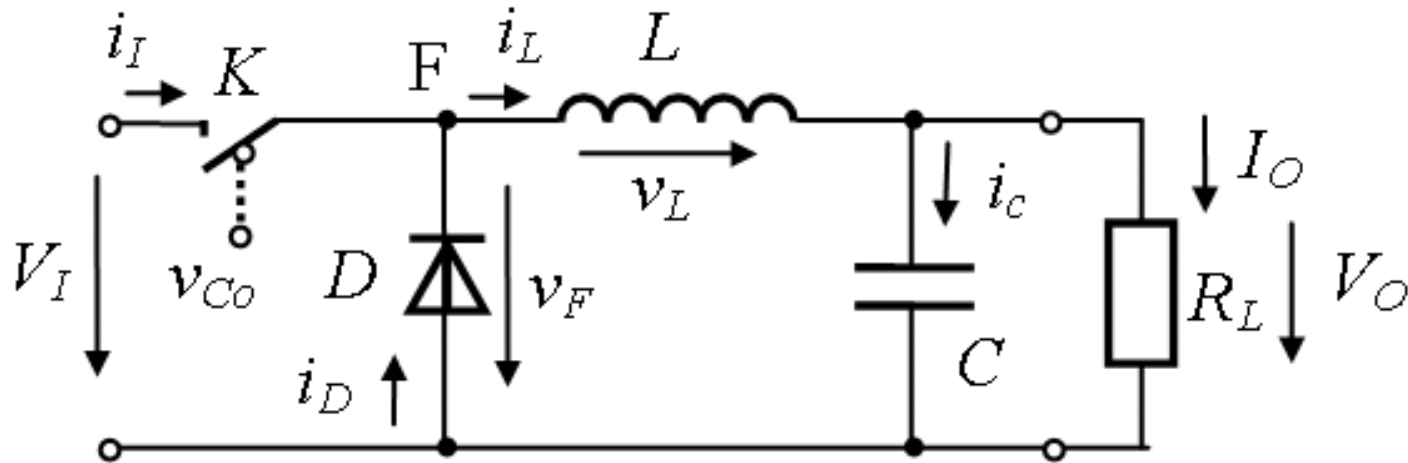

- v_I – periodically applied across an inductance for short time intervals
- energy is stored in the magnetic field $(1/2)Li_L^2$
- the energy is then transferred on a filtering capacitor, to the output
- the capacitor act like an energy reservoir and provides current into the load between the charging intervals
- the capacitor also smoothes the output voltage

Step-down Converter or Buck Converter



OPTIONAL

K is an ideal switch, p type (MOST p channel; BJT pnp) ;


All elements are lossless (except for load resistance);

The circuit operates in the steady state regime (all waveforms are periodic);


Output voltage is constant, (the ripple of the output voltage is neglected against the average value of V_O);

The input voltage is constant

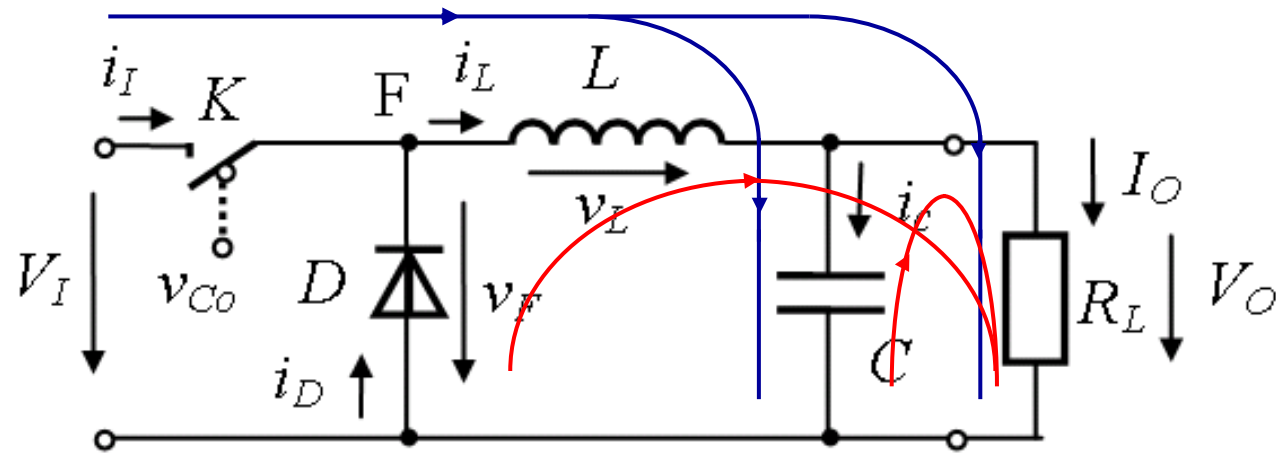Step-down Converter or Buck Converter – cont.





OPTIONAL

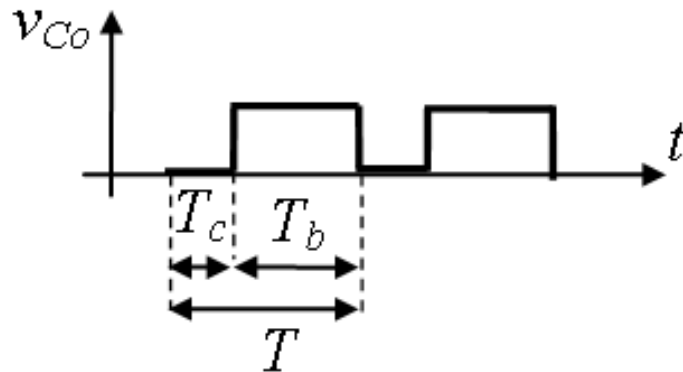

$$\frac{T_c}{T_c + T_b} = \frac{T_c}{T} = \delta$$

Duty factor

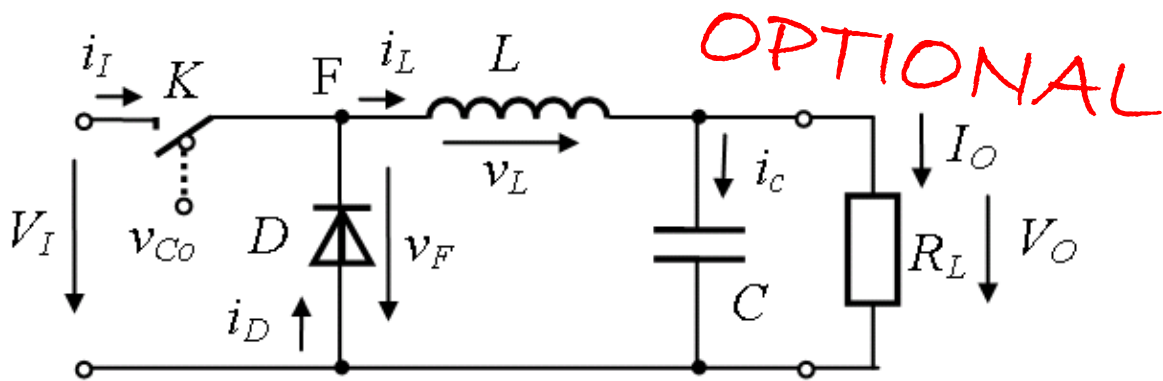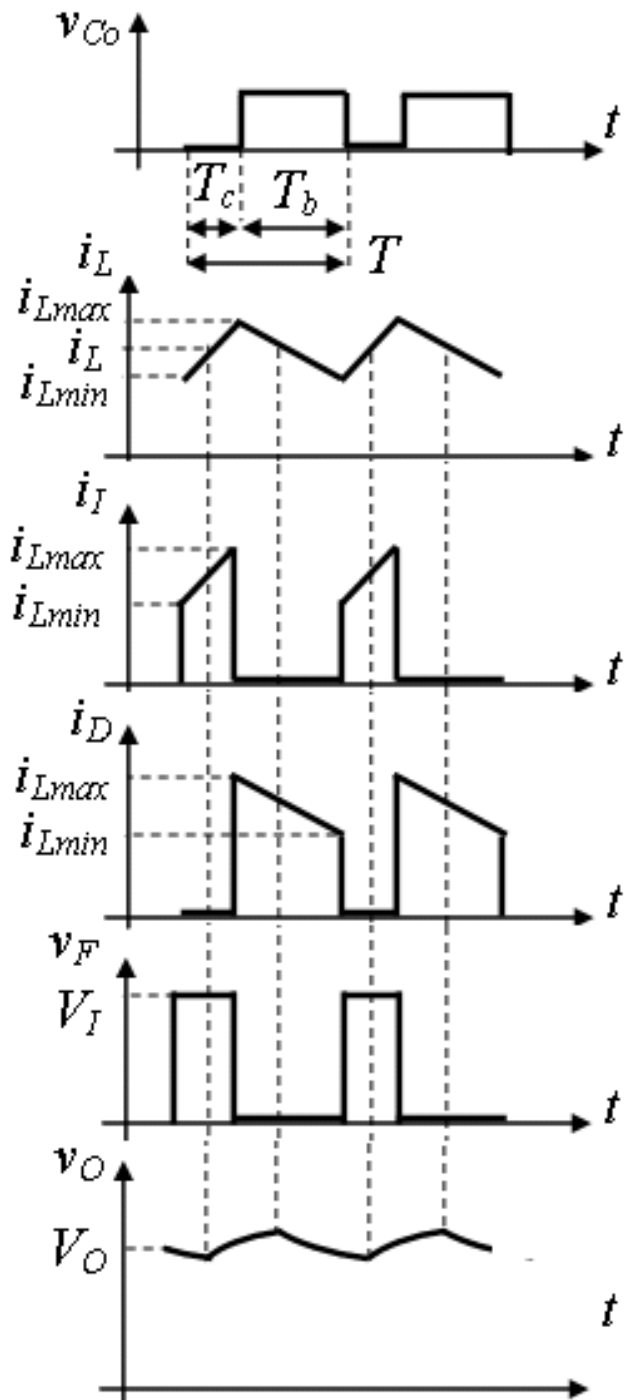- ✓ T_c - conduction interval of K - energy is stored in the magnetic field of L
- ✓ T_b - blocking interval of K – energy is released to the output



For $v_L(t) = V_L = \text{cst}$

$$i_L(t) = \frac{1}{L} \int dv_L(t) dt$$

$$\Delta i_L = \frac{1}{L} V_L \Delta t$$

$$\Delta t = T_c \quad \Delta i_L = I_{L\text{max}} - I_{L\text{min}} = \frac{1}{L} (V_I - V_O) T_c$$

$$\Delta t = T_b$$


$$-\Delta i_L = I_{L\text{min}} - I_{L\text{max}} = \frac{1}{L} (-V_O) (T_b) = -\frac{1}{L} V_O T_b$$

$$\frac{1}{L} (V_I - V_O) T_c = \frac{1}{L} V_O T_b \quad V_O = \frac{T_c}{T_c + T_b} V_I$$

$$\frac{T_c}{T_c + T_b} = \frac{T_c}{T} = \delta$$

$$V_O = \delta V_I$$

Step-up Converter or Boost Converter

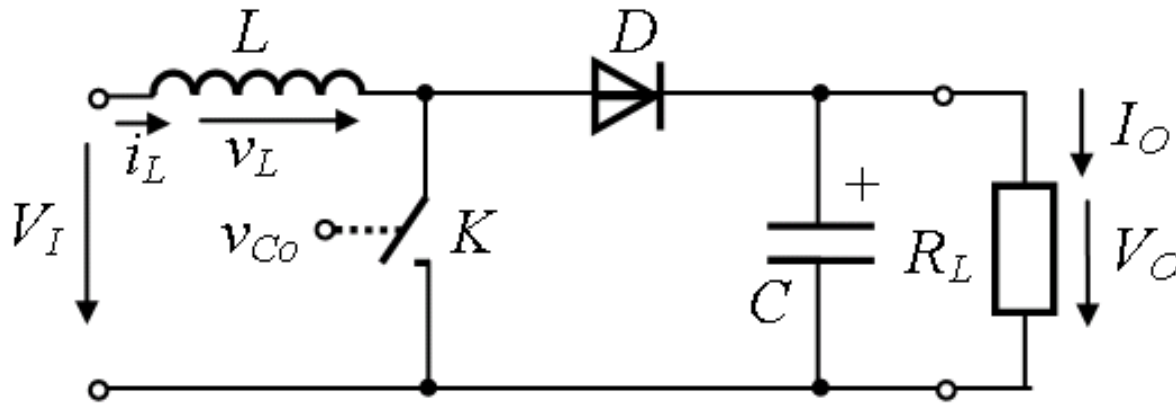


OPTIONAL

$$V_O = \frac{1}{1-\delta} V_I$$

$$\delta < 1 \quad V_O > V_I$$

Step-down/Step-up Converter or Buck-Boost Converter

OPTIONAL

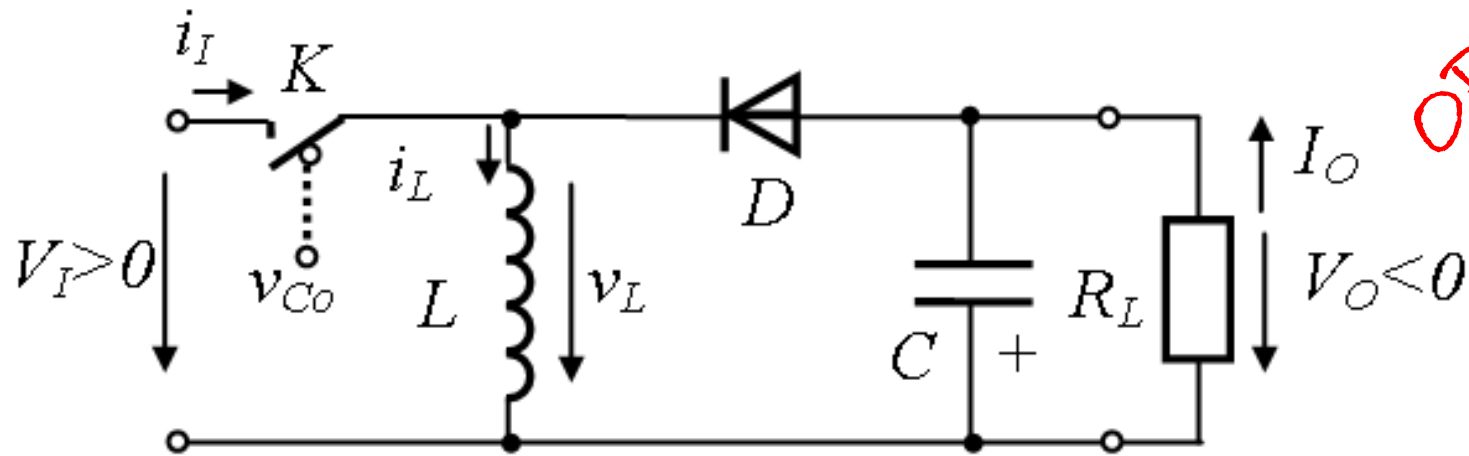

$$V_O = -\frac{\delta}{1-\delta} V_I$$

$$\delta > 0.5$$

The magnitude of the output voltage is greater than the input voltage

$$\delta < 0.5$$

The magnitude of the output voltage is less than the input voltage