

# Sinusoidal Oscillators

- Signal generators: sinusoidal, rectangular, triangular, sawtooth, etc.
- Sine wave generation: frequency selective network in a feedback loop of a PF amplifier: *sinusoidal oscillator*
  - Oscillation frequency:  $f_0$
  - Oscillation amplitude:  $\hat{V}_o$ 
    - Oscillation criterion
    - Frequency stability
    - Amplitude stability
    - Distortion coefficient

# Oscillator feedback loop


In the complex domain

For a unique  $f_0$

$$\omega_0 = 2\pi f_0$$

Signal reconstruction on  
the feedback loop

$$a(j\omega_0)r(j\omega_0) = 1$$

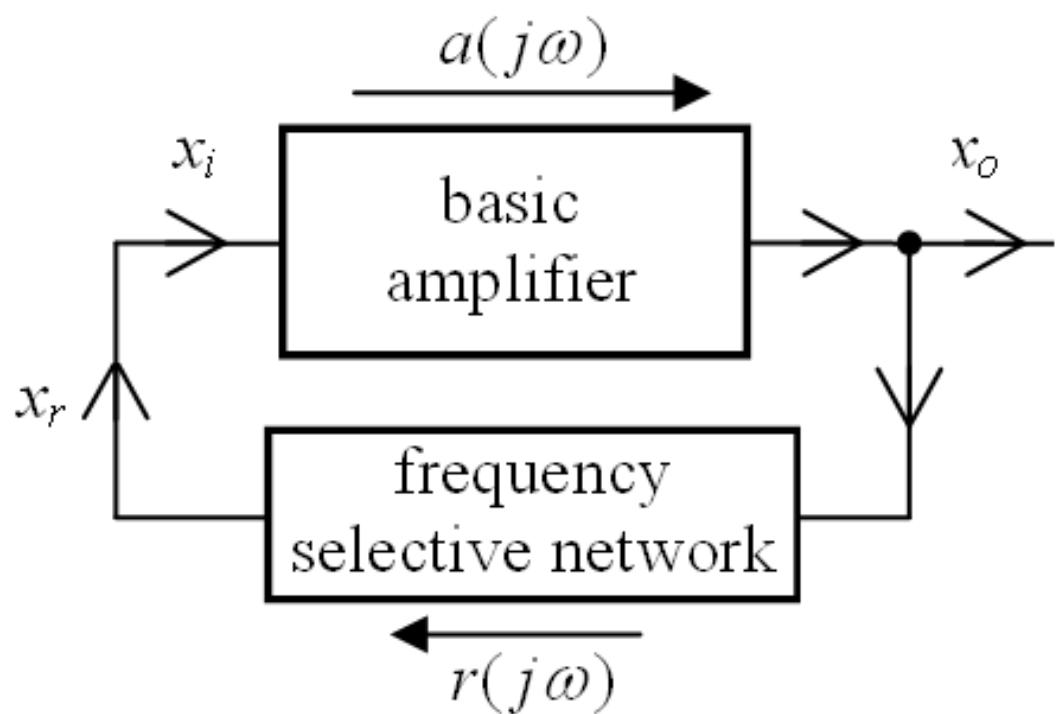

Frequency dependent  
components ( $C, L$ )

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 2\pi f C}$$

$$Z_L = j\omega L = j2\pi f L$$

Barkhausen criterion


# Complex number - short review

$$z = a + jb$$


$$\begin{cases} \operatorname{Re}(z) = a \\ \operatorname{Im}(z) = b \end{cases} \quad j = \sqrt{-1}$$

imaginary unit  
imaginary number

Cartesian complex plane

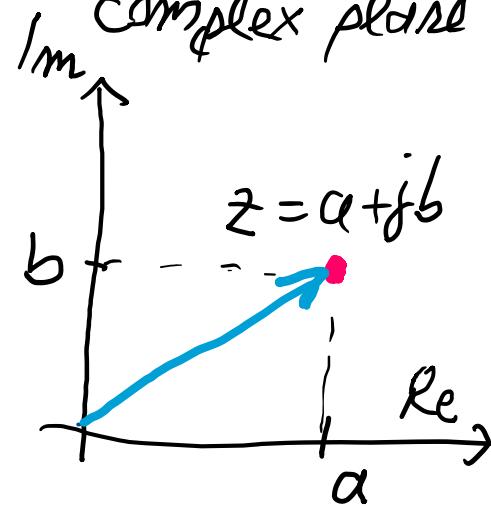

Polar complex plane

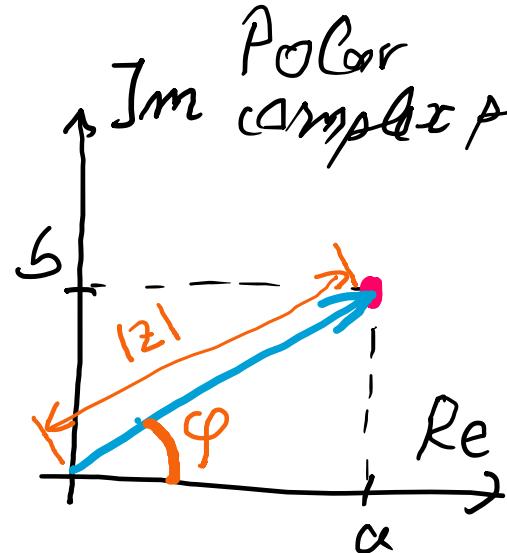

- absolute value; modulus;  
 $|z| = \sqrt{a^2 + b^2}$  magnitude
- argument; phase  
 $\varphi = \tan^{-1}\left(\frac{b}{a}\right)$


trigonometric form:

$$z = |z|(\cos \varphi + j \sin \varphi)$$

Euler's formula

$$z = |z| e^{j\varphi}$$


Unit circle

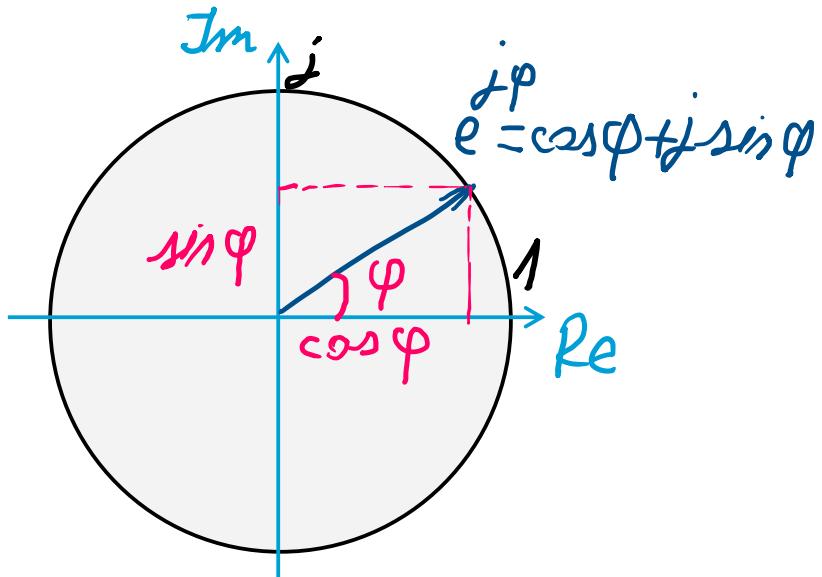

# Oscillation criteria

$$a(j\omega) = |a(j\omega)| e^{j\varphi_a}$$

$$r(j\omega) = |r(j\omega)| e^{j\varphi_r}$$

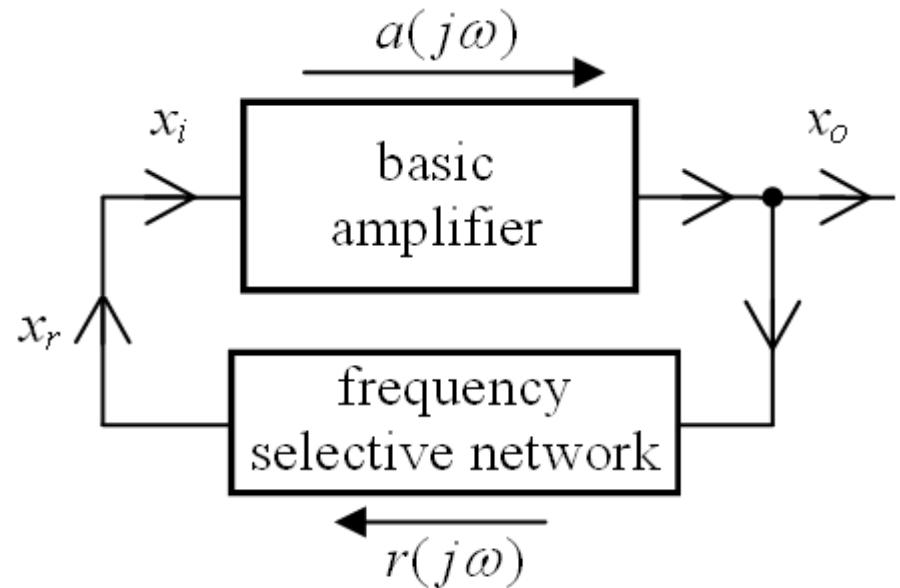

$$a(j\omega_0)r(j\omega_0) = |a(j\omega_0)| |r(j\omega_0)| e^{j(\varphi_a + \varphi_r)} = 1$$

✓ magnitude condition:  $|a(j\omega_0)| |r(j\omega_0)| = 1$  gives  $a_0$

The loop gain is equal to unity in magnitude

✓ phase condition:  $\varphi_a + \varphi_r = 2k\pi$  gives  $f_0$

The phase shift around the loop is zero or an integer multiple of  $2\pi$

# RC Oscillators

➤ **Basic amplifier** – frequency independent

- inverting       $\varphi_a = 180^\circ$
- noninverting     $\varphi_a = 0$


➤ Frequency selective **feedback network**

To fulfil the phase condition, there must be  
**a unique frequency,  $f_0$**  where the phase shift is:

$$\varphi_r = 180^\circ, \text{ if } \varphi_a = 180^\circ$$


$$\varphi_r = 0^\circ, \quad \text{if } \varphi_a = 0^\circ$$

# RC Oscillators

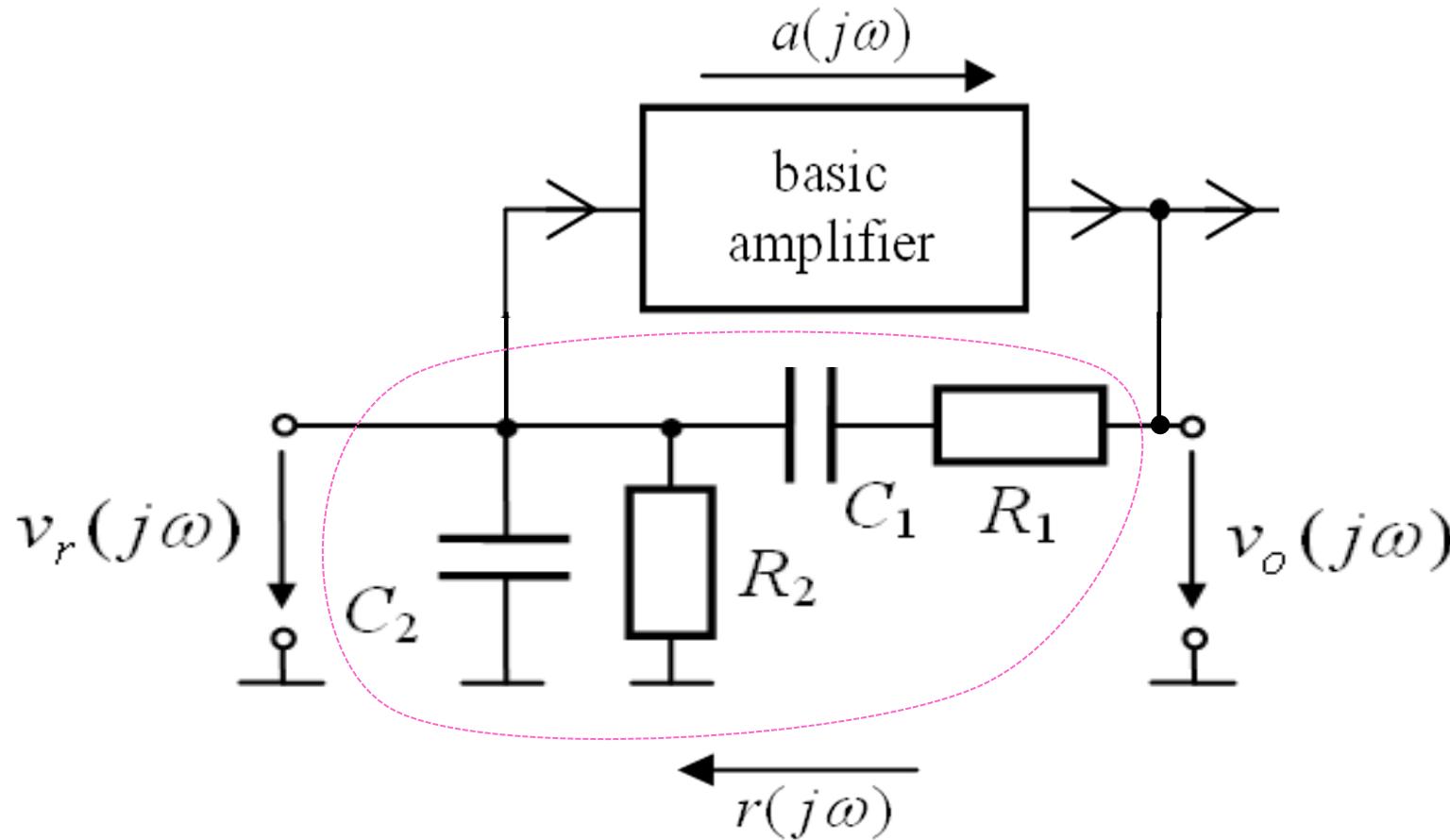

**Feedback network**  
**Frequency selective network**  
**WIEN Bridge**
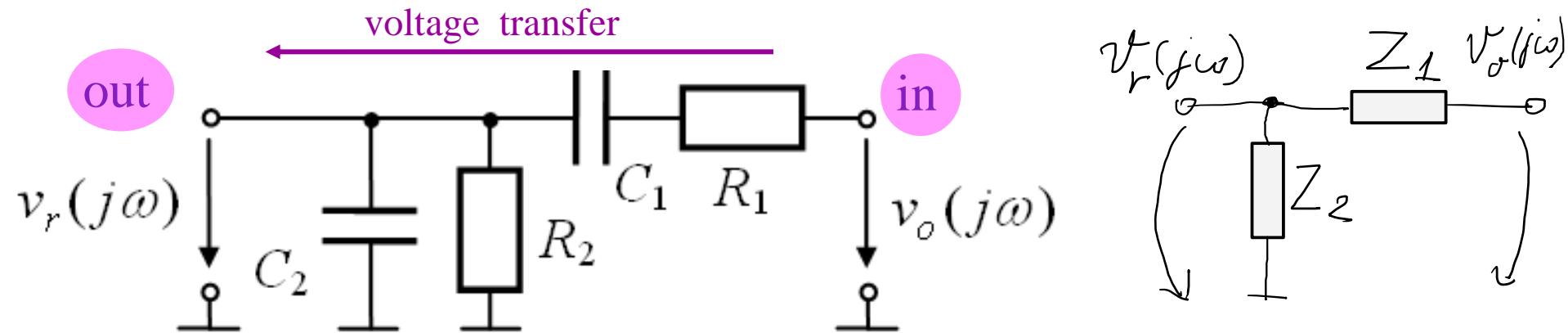
# WIEN Bridge Frequency selective network Transfer function



$$v_r(j\omega) = r(j\omega)v_o(j\omega)$$


$$r(j\omega) = \frac{v_r(j\omega)}{v_o(j\omega)}$$

$$r(j\omega) = \frac{Z_2}{Z_1 + Z_2} \quad Z_1 = R_1 + \frac{1}{j\omega C_1} \quad Z_2 = R_2 \parallel \frac{1}{j\omega C_2}$$

$$r(j\omega) = \frac{v_r(j\omega)}{v_o(j\omega)} = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1} + j\left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)}$$

complex number

# WIEN Bridge

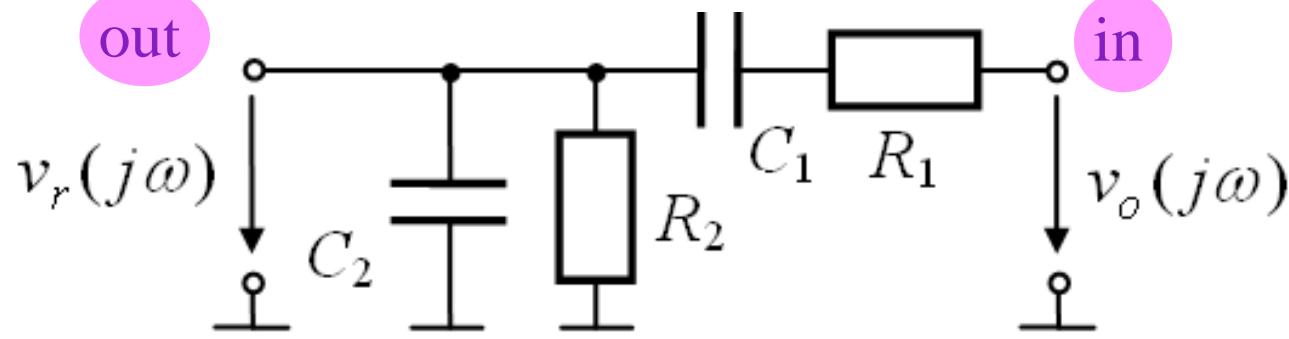

$$r(j\omega) = \frac{v_r(j\omega)}{v_o(j\omega)} = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1} + j\left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)}$$

$$r(j\omega) = |r(j\omega)| e^{j\varphi_r}$$

$$|r(j\omega)| = \frac{1}{\sqrt{\left(1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}\right)^2 + \left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)^2}}$$

$$\varphi_r = -\arctg \left( \frac{\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}} \right)$$

**modulus**

**phase**

# Modulus

WIEN  
Bridge

$$|r(j\omega)| = \frac{1}{\sqrt{\left(1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}\right)^2 + \left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)^2}}$$

$$\omega \rightarrow 0 \quad |r(j\omega)| \rightarrow 0 \quad \text{asymptote}$$

$$\omega \rightarrow \infty \quad |r(j\omega)| \rightarrow 0 \quad \text{asymptote}$$

The maximum value (as a function of  $\omega$ ):

$$\omega = \omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$|r(j\omega_0)| = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}}$$

# Modules

# WIEN Bridge


$$|r(j\omega)| = \frac{1}{\sqrt{\left(1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}\right)^2 + \left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)^2}}$$

- $\omega \rightarrow 0 \quad |r(j\omega)| \rightarrow 0 \quad \text{asymptote}$   
 $\omega \rightarrow \infty \quad |r(j\omega)| \rightarrow 0 \quad \text{asymptote}$

The maximum value:

$$\omega = \omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$r_0 = |r(j\omega_0)| = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}}$$

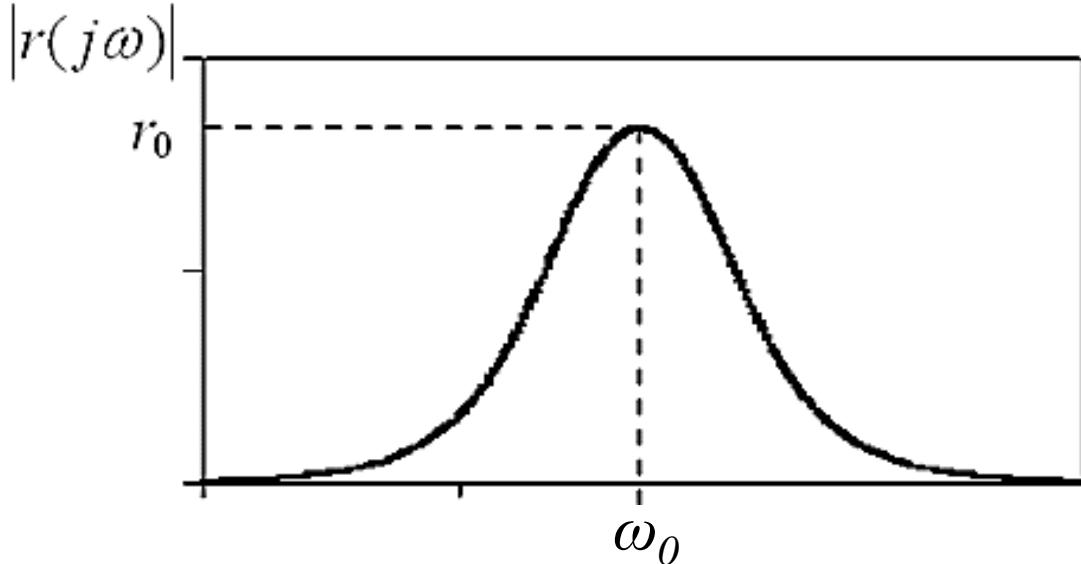

## Phase

WIEN  
Bridge

$$\varphi_r = -\arctg \left( \frac{\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}} \right)$$

$$\omega \rightarrow 0 \quad \varphi_r \rightarrow +90^\circ \quad \text{asymptote}$$

$$\omega \rightarrow \infty \quad \varphi_r \rightarrow -90^\circ \quad \text{asymptote}$$

$$\omega = \omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad \varphi_r = 0^\circ$$

intermediate  
value

# Phase

# WIEN Bridge


$$\varphi_r = -\arctg \left( \frac{\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}} \right)$$

$$\omega \rightarrow 0 \quad \varphi_r \rightarrow +90^\circ \quad \text{asymptote}$$

intermediate value

$$\omega \rightarrow \infty \quad \varphi_r \rightarrow -90^\circ \quad \text{asymptote}$$


$$\varphi_r = 0^\circ$$

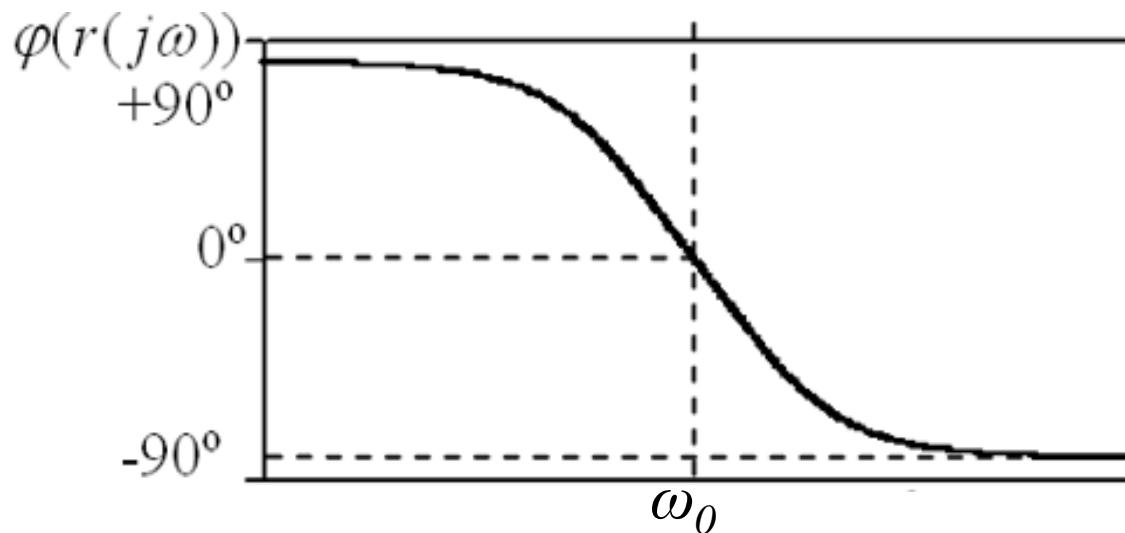

$$\omega = \omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

# WIEN Bridge

## Frequency response

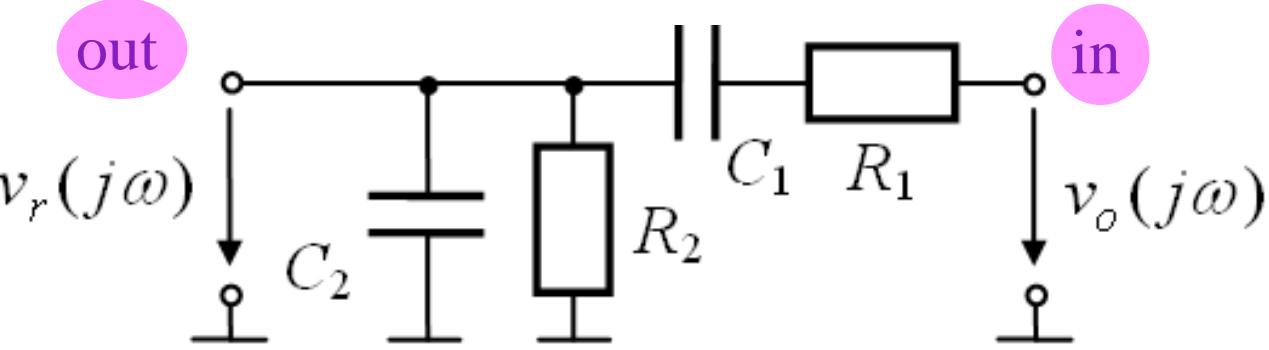


For only one **unique frequency**,  $f_0$  we have

$$\varphi_r = 0$$


For the phase condition:  
noninverting amplifier

$$\varphi_a = 0$$
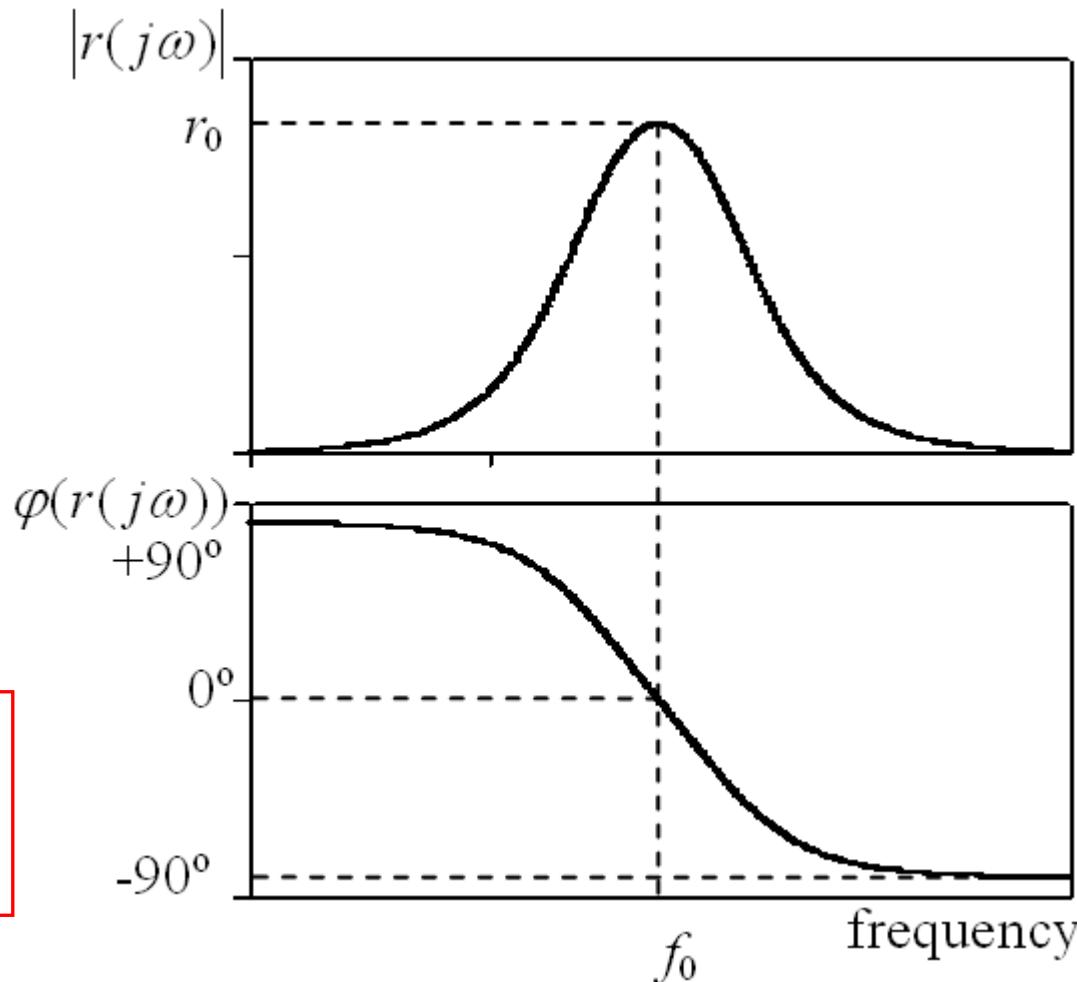
$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$



# WIEN Bridge Summary

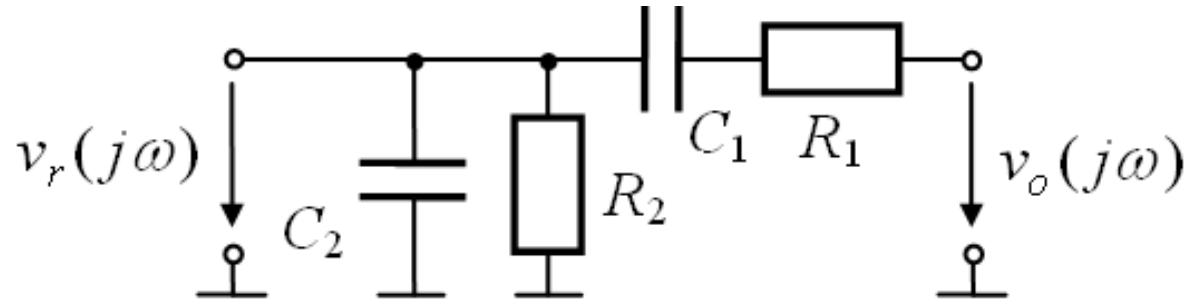

$$r(j\omega) = \frac{v_r(j\omega)}{v_o(j\omega)} = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1} + j\left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)}$$

Barkhausen criterion:  $a(j\omega_0)r(j\omega_0)=1$

Real number


Real number

$$\omega_0 R_1 C_2 - \frac{1}{\omega_0 R_2 C_1} = 0$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$f_0 = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

# WIEN Bridge Summary

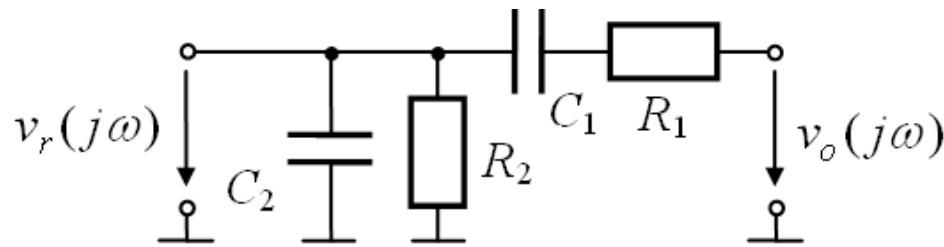

$$r(j\omega) = \frac{v_r(j\omega)}{v_o(j\omega)} = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1} + j\left(\omega R_1 C_2 - \frac{1}{\omega R_2 C_1}\right)}$$

$$f_0 = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$\varphi_r(j\omega_0) = 0$$


$$|r(j\omega_0)| = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}}$$

If  $R_1 = R_2 = R$   
 $C_1 = C_2 = C$

$$f_0 = \frac{1}{2\pi R C}$$

$$|r(j\omega_0)| = \frac{1}{3}$$


# Op amp and WIEN bridge oscillator

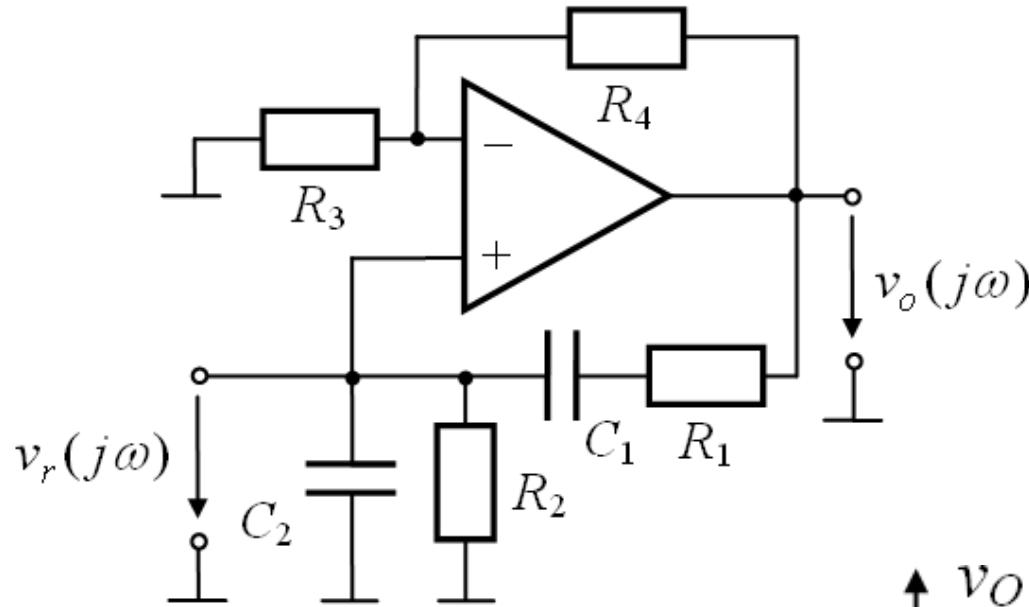


$$v_o(t) = \hat{V}_o \sin 2\pi f_0 t$$

$$f_0 = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$|r(j\omega_0)| = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}}$$

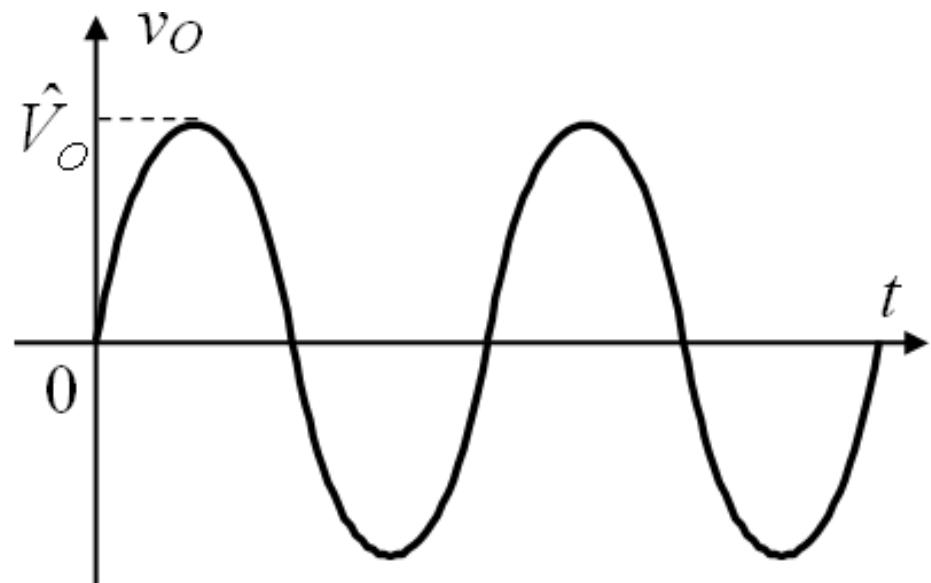

# Op amp and WIEN bridge oscillator

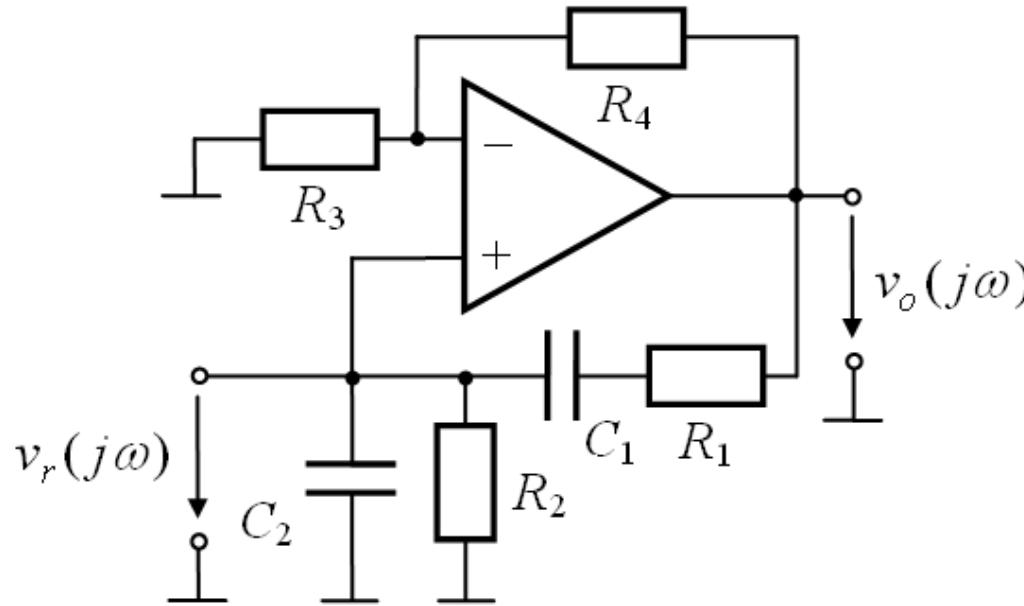

$$f_0 = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$|r(j\omega_0)| = \frac{1}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}}$$

For  $\begin{cases} C_1 = C_2 = C \\ R_1 = R_2 = R \end{cases}$

$$f_0 = \frac{1}{2\pi R C}$$

$$|r(j\omega_0)| = \frac{1}{3}$$

$$|a(j\omega_0)| = \frac{1}{|r(j\omega_0)|} = 3 \quad a = 1 + \frac{R_4}{R_3}$$

$$1 + \frac{R_4}{R_3} = 3 \quad R_4 = 2R_3$$

$$\hat{V}_o = ?$$

Nonlinearity of the gain, close to saturation

# Automatic gain control (AGC)


$|a(j\omega)| |r(j\omega)| < 1$  oscillations are attenuated - zero

$|a(j\omega)| |r(j\omega)| > 1$  oscillations are amplified - saturation

$|a(j\omega_0)| |r(j\omega_0)| = 1$  oscillations are maintained - oscillate

Stability of the oscillation amplitude

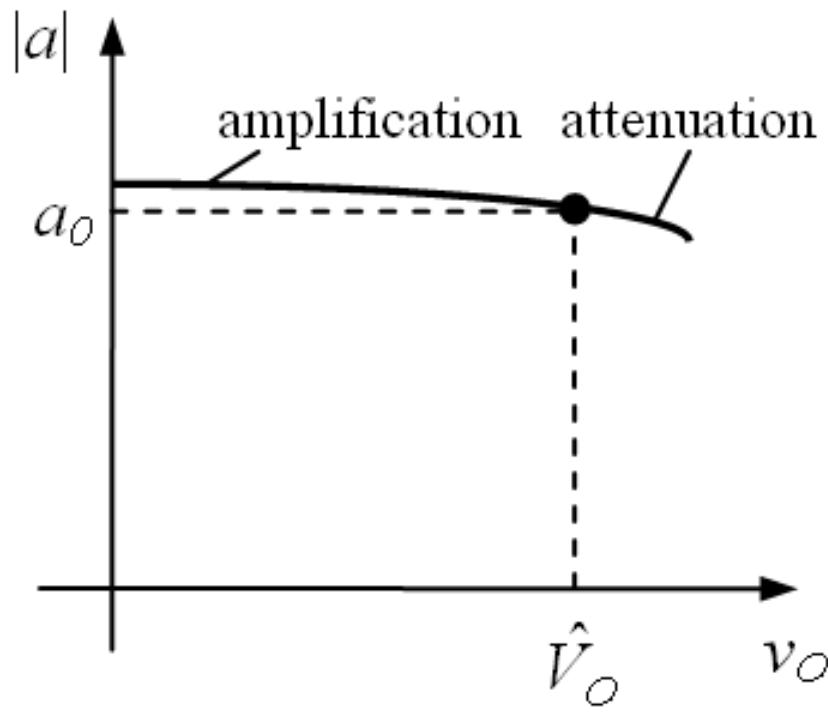Automatic gain control - depending on the output voltage magnitude  $\hat{V}_o$




$$v_o = \hat{V}_o \sin 2\pi f_0 t$$

$$|r(j\omega)| = cst$$

$$\underline{\hat{V}_o} \uparrow, |a(j\omega_0)| \downarrow, \underline{\hat{V}_0} \downarrow$$

# AGC for WIEN bridge oscillator

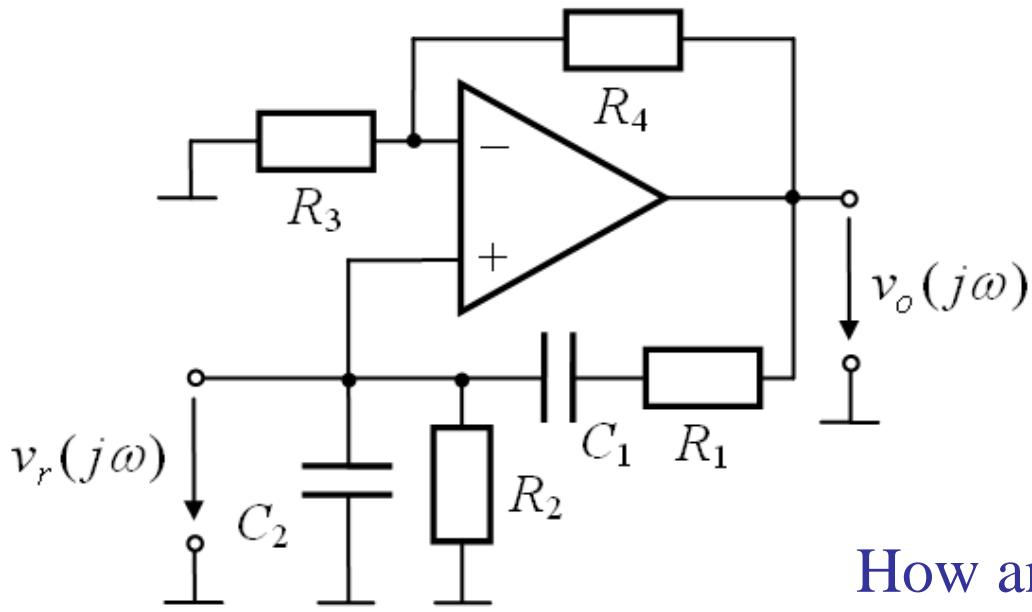

$$a = 1 + \frac{R_4}{R_3}$$


How an AGC can be implemented,  
so that  $a$  will depend on  $v_o$  value?

- $R_4$  - dependent on  $v_o$

or

- $R_3$  - dependent on  $v_o$

# Diode revisited - as variable resistor

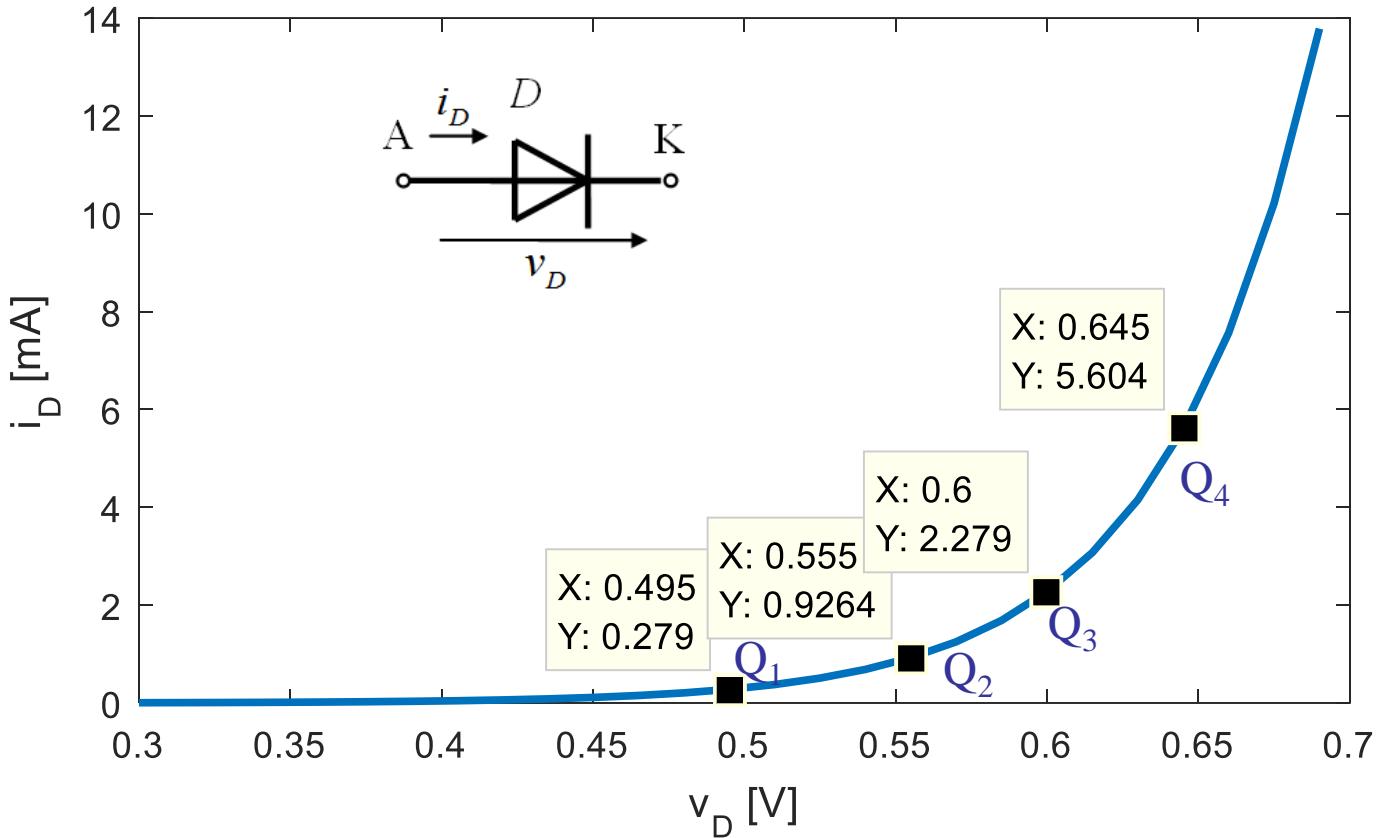

Static resistance  
of a diode in the  
operating point

$$r_D = \frac{V_D}{I_D}$$

$$r_{D1} = \frac{V_{D1}}{I_{D1}} = \frac{0.495 \text{ V}}{0.279 \text{ mA}} = 4.24 \text{ k}\Omega$$


$$r_{D3} = \frac{V_{D3}}{I_{D3}} = \frac{0.6 \text{ V}}{2.279 \text{ mA}} = 0.263 \text{ k}\Omega$$

$$r_{D2} = \frac{V_{D2}}{I_{D2}} = \frac{0.555 \text{ V}}{0.926 \text{ mA}} = 0.599 \text{ k}\Omega$$

$$r_{D4} = \frac{V_{D4}}{I_{D4}} = \frac{0.645 \text{ V}}{5.604 \text{ mA}} = 0.115 \text{ k}\Omega$$


If the voltage drops,  $V_D$  increases; the equivalent static resistance  $r_D$  decreases

# AGC using Diodes - how?

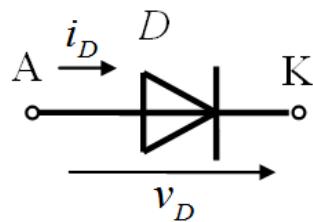

$$r_D = \frac{V_D}{I_D}$$

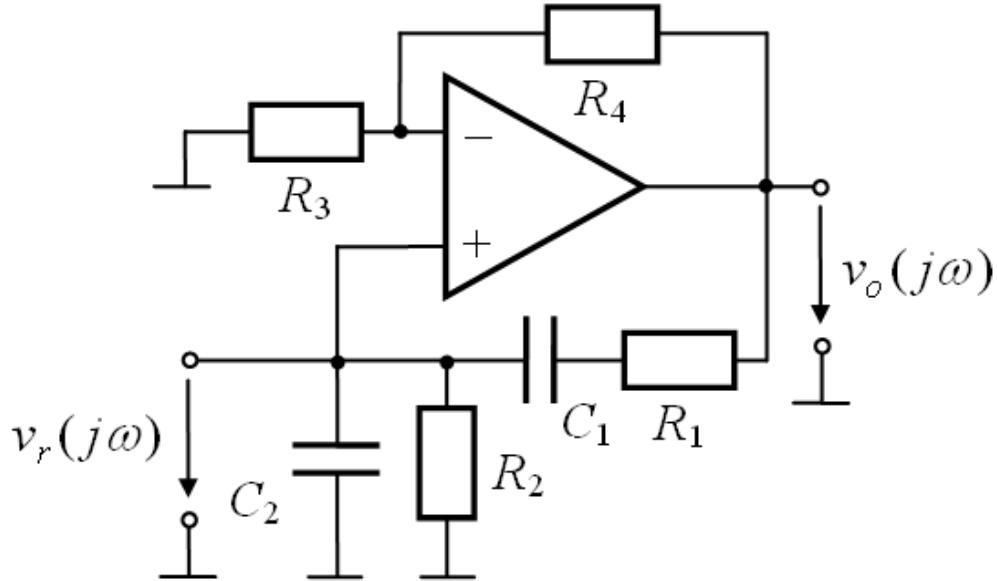
If the voltage drops,  $V_D$  increases; the equivalent static resistance  $r_D$  decreases



$$a = 1 + \frac{R_4}{R_3}$$

- $R_4$  - dependent on  $v_o$   
or
- $R_3$  - dependent on  $v_o$

# 1. AGC using diodes

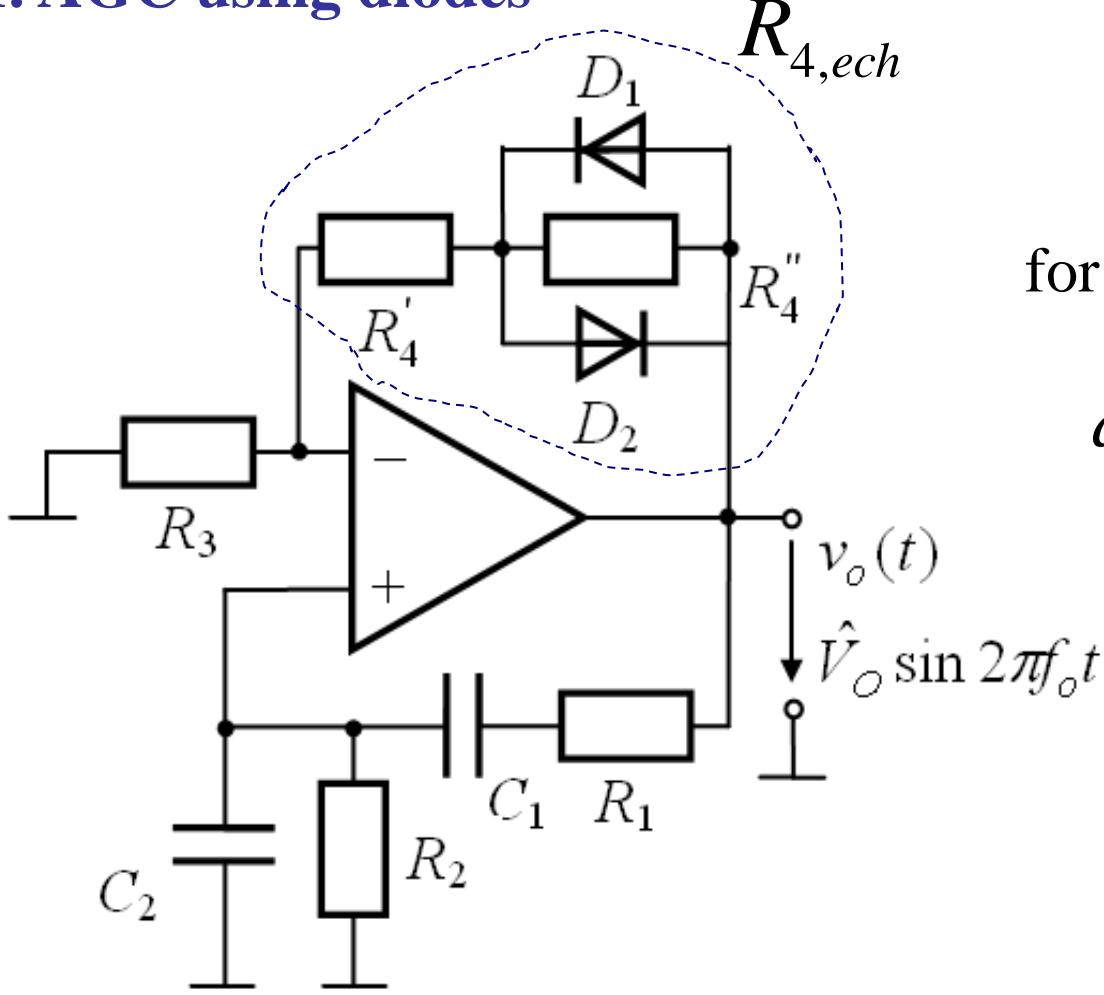

$$a_{on} = 1 + \frac{R'_4 + R''_4 \| r_D}{R_3} \quad |a_{on}(j\omega_0)|r(j\omega_0)| = 1$$

$\hat{V}_o$  is given by the value of  $r_D$

$$a = 1 + \frac{R_{4,ech}}{R_3}$$


for  $v_o(t)$  small,  $D_1, D_2 - (off)$

$$a_{off} = 1 + \frac{R'_4 + R''_4}{R_3}$$

$$|a_{off}(j\omega_0)|r(j\omega_0)| > 1$$

$v_o(t)$  increases,  
 $D_1 - (on)$  on the  
positive half-cycle  
 $D_2 - (on)$  on the  
negative half-cycle  
to maintain oscillations

# Problem



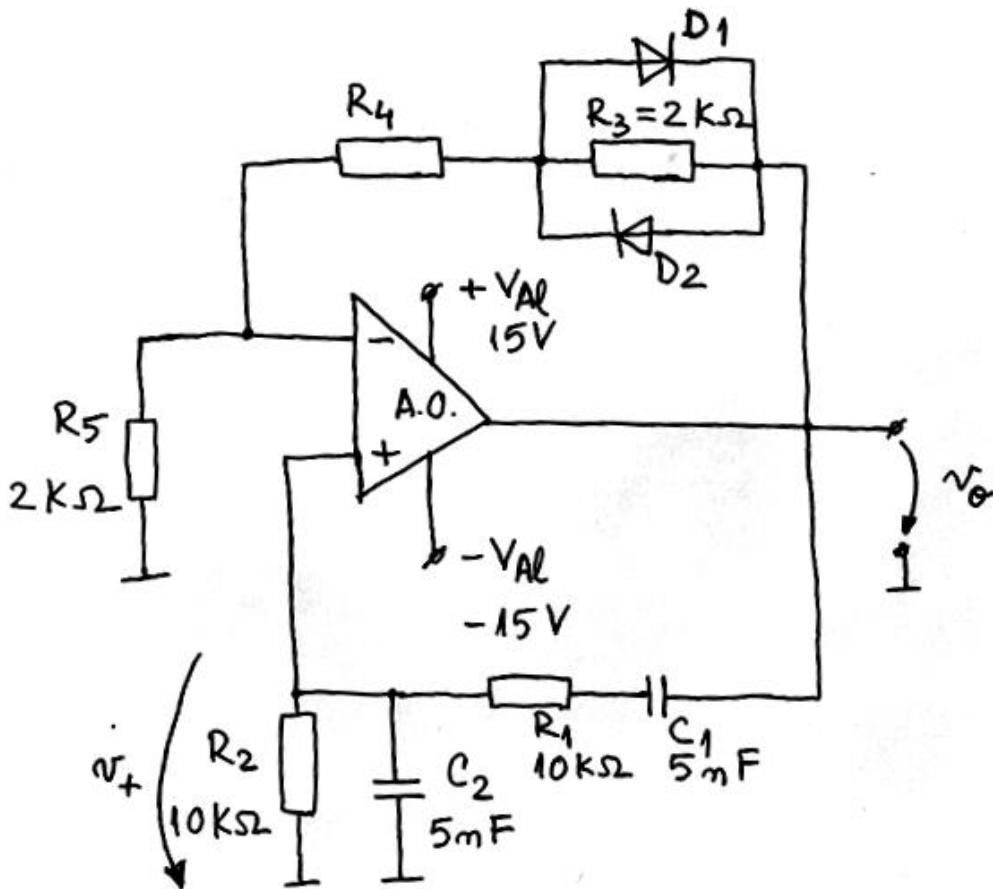


- How does the voltages  $v_o(t)$  and  $v_+(t)$  look like in the steady-state regime? What is the oscillation frequency?
- Size  $R_4$  so that the circuit will maintain the oscillation. For the maximum value (magnitude) of the sinusoidal output, consider  $r_{D1} = r_{D2} = 0.5\text{ k}\Omega$ . Verify if the oscillation can start.
- What is the magnitude of  $v_o(t)$  in the conditions of question b), if the voltage drop across one diode is  $v_D = 0.58\text{ V}$  for the equivalent resistance  $r_D = 0.5\text{ k}\Omega$
- How does the voltage  $v_o(t)$  look like in the steady-state regime if  $D_2$  diode is missing?
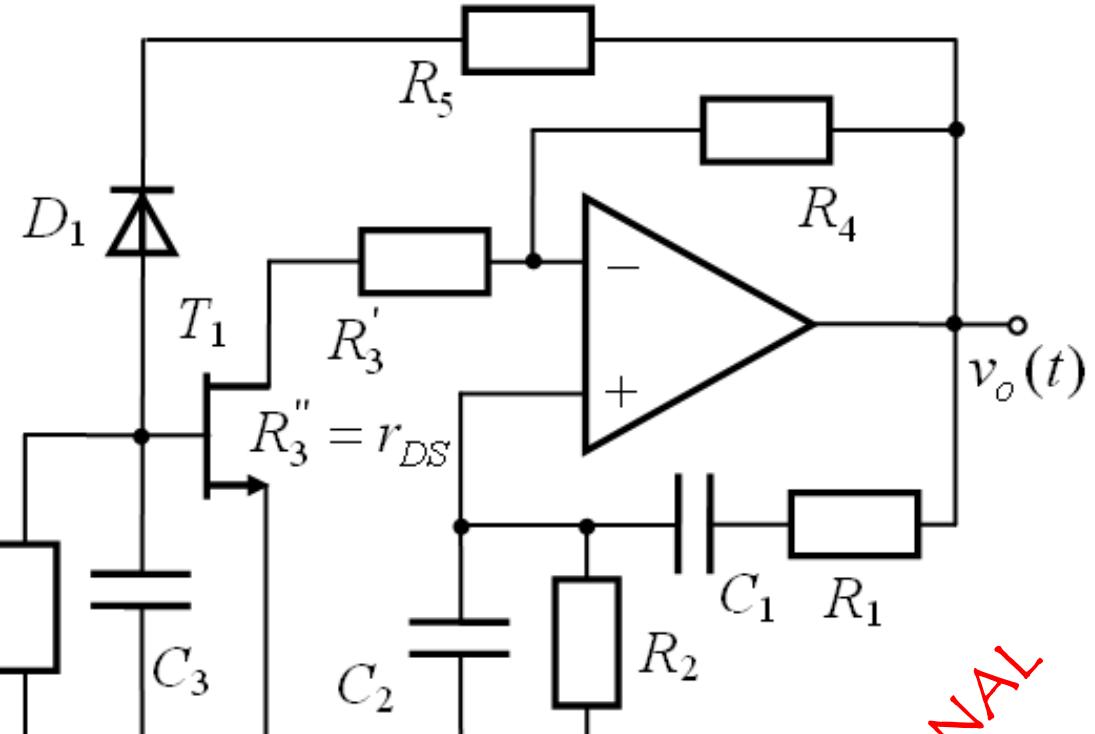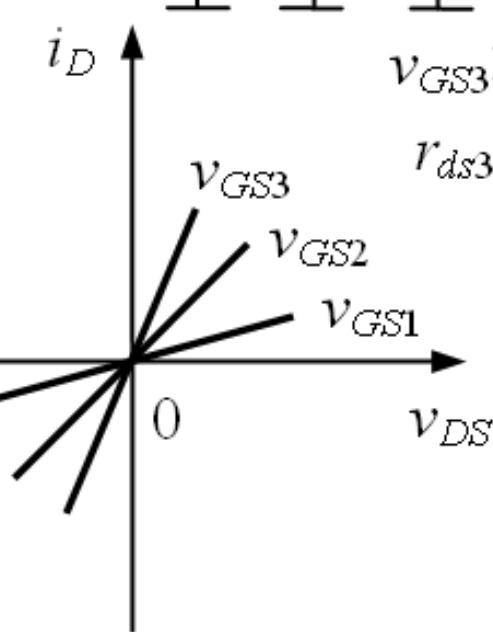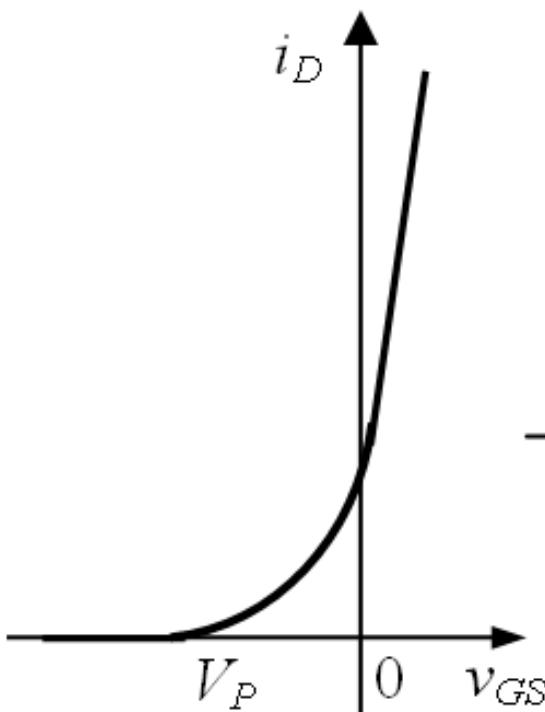
## 2. AGC using *n*-channel depletion-type MOSFET

$$a = 1 + \frac{R_4}{R_3 + r_{DS}}$$

$$r_{DS} \approx \frac{1}{2\beta(v_{GS} - V_{Th})}$$




$$\begin{aligned}v_{GS3} &> v_{GS2} > v_{GS1} \\r_{ds3} &< r_{ds2} < r_{ds1}\end{aligned}$$

**OPTIONAL**


$$\begin{aligned}v_{GS} &< 0 \\|v_{GS}| \uparrow, r_{DS} &\downarrow\end{aligned}$$

# Op amp and RC ladder network oscillator

- High pass band
- Low pass band

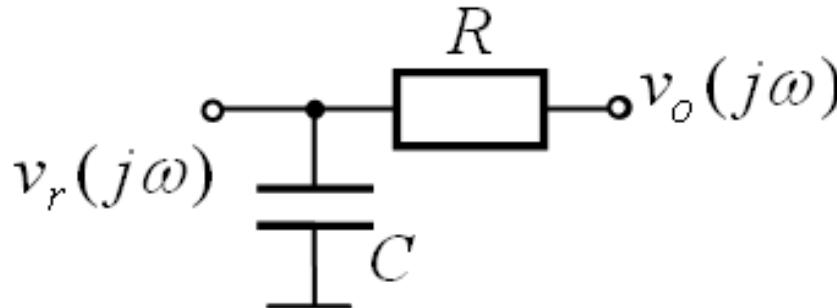


OPTIONAL

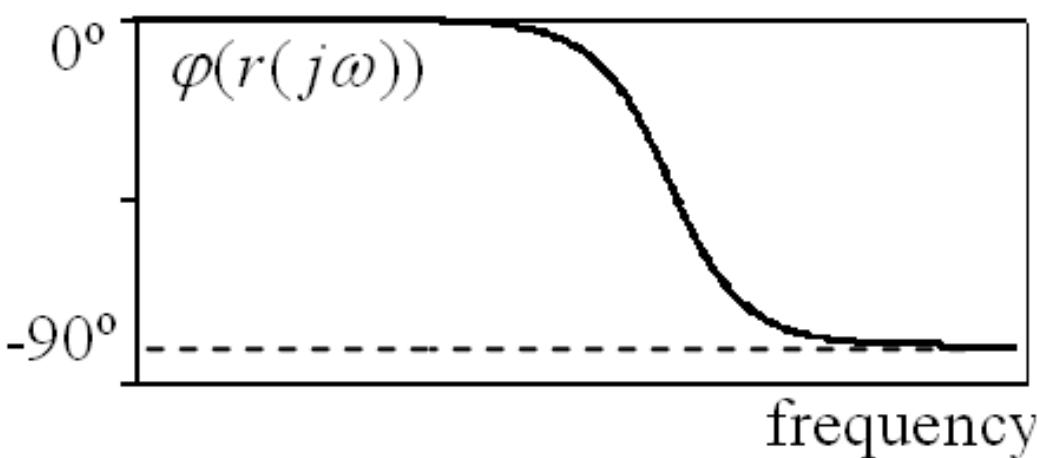


- the phase-shift is in the range of  $[0^\circ; -90^\circ]$
- inverting basic amplifier
- how many identical RC cells are necessary to build an oscillator?


## Low pass RC ladder with 3 cells

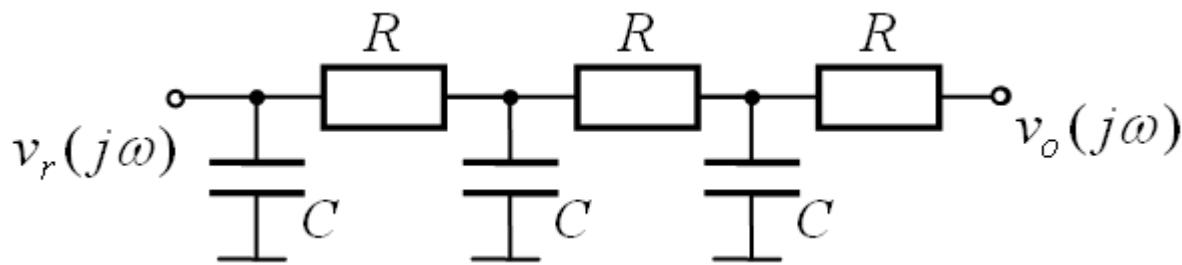
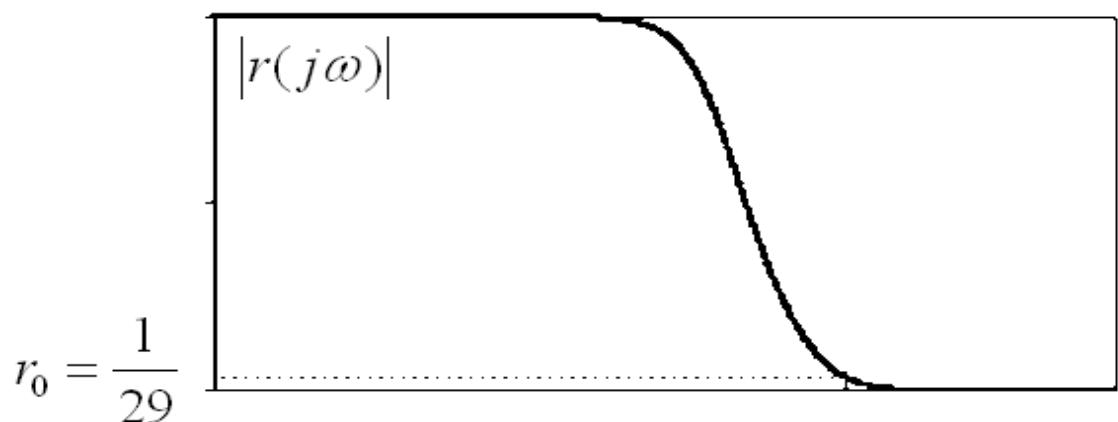
$$r(j\omega) = \frac{1}{1 - 5(\omega RC)^2 + j[6\omega RC - (\omega RC)^3]}$$



$$r_0 = \frac{1}{29}$$

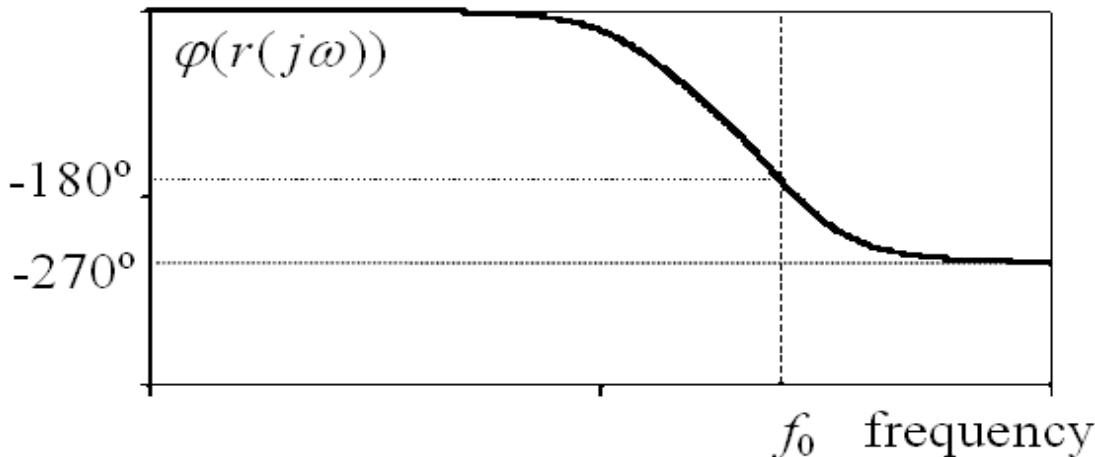

$$\varphi_r = 0$$

$$6\omega_0 RC - (\omega_0 RC)^3 = 0$$

$$f_0 = \frac{\sqrt{6}}{2\pi RC}$$

$$r(j\omega_0) = -\frac{1}{29}$$

OPTIONAL

# The circuit of RC ladder network oscillator

OPTIONAL

