


Nonsinusoidal Signal Generators

- rectangle, triangle, saw tooth, pulse, etc.

Multivibrator circuits:

- ❖ **astable** – no stable states (two quasi-stable states; it remains in each state for predetermined times)
- ❖ **monostable** – one stable state, one non-stable state
- ❖ **bistable** – two stable states
 - From one stable state the circuit switches in the other state under the action of a control signal (input signal).
 - From one non-stable state the circuit switches in the other state automatically.

C in the time domain

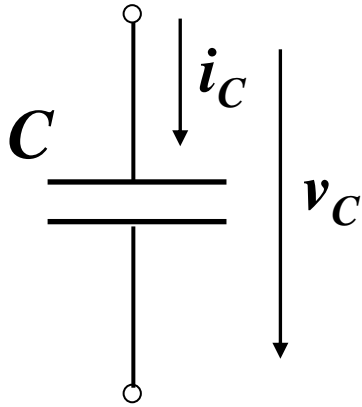


Defining relation between current and voltage

$$C dv_C(t) = i_C(t) dt$$

RC circuit – time domain analysis

❖ RC circuit with voltage source

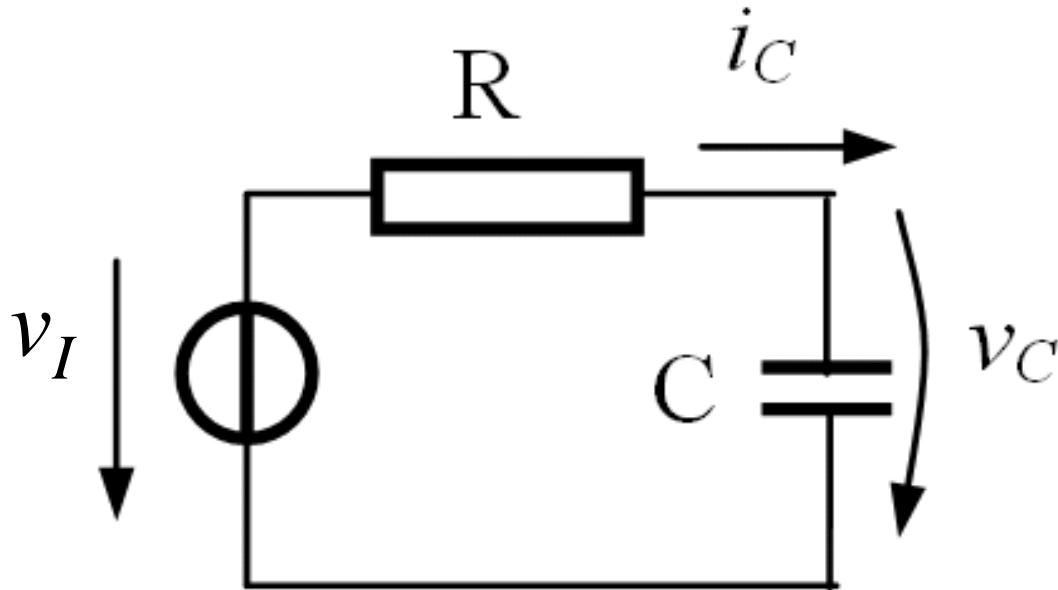

$$Ri_C(t) + v_C(t) = v_I(t)$$

$$Cdv_C(t) = i_C(t)dt$$

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_I(t)$$




$\tau = RC$ time constant of the circuit

$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$

RC circuit with dc voltage source

$$v_C(t) = v_C(0)e^{-\frac{t}{\tau}} + (1 - e^{-\frac{t}{\tau}})v_C(\infty)$$
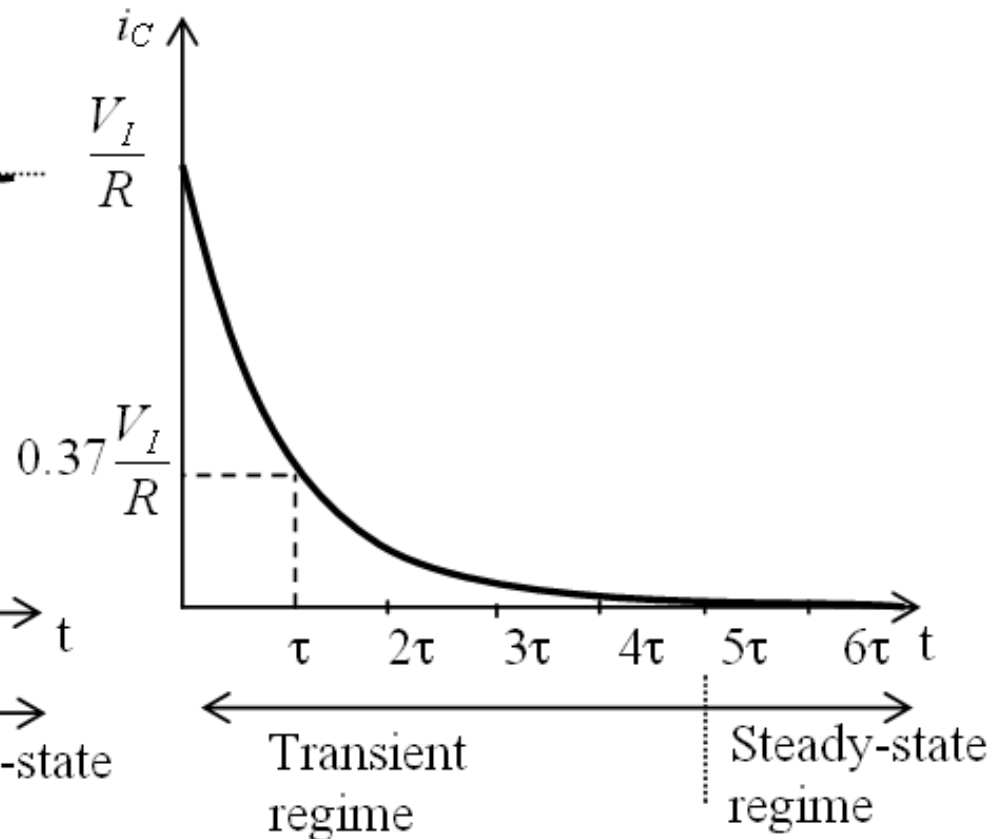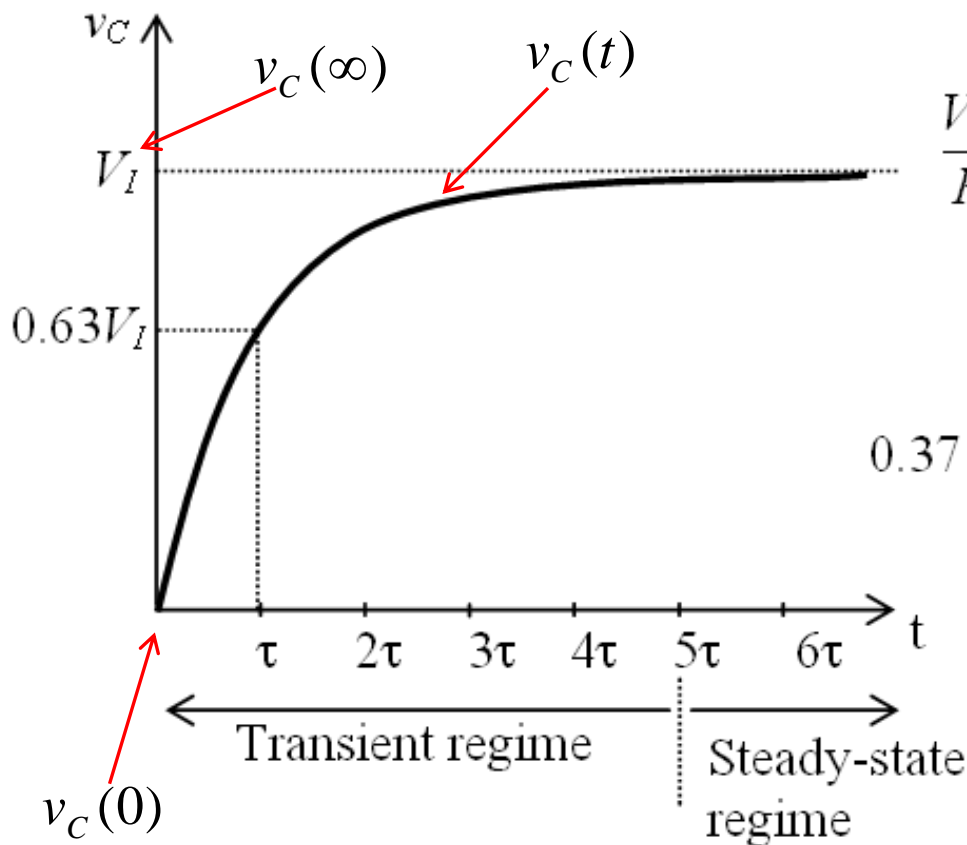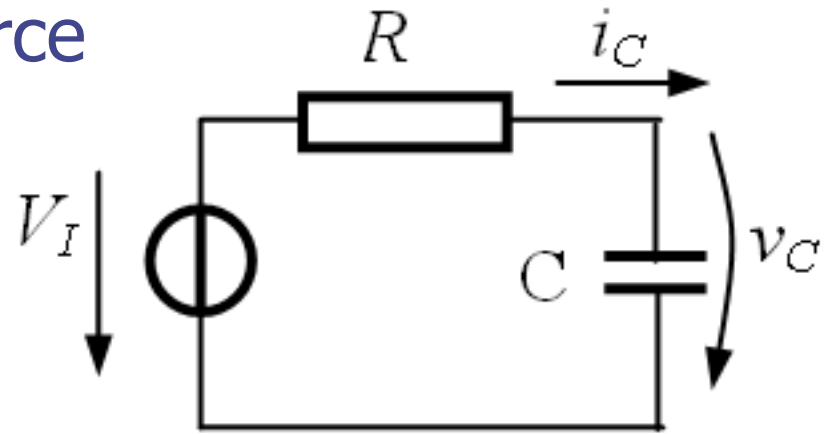
$$v_C(0) = 0; \quad v_C(\infty) = V_I; \quad \tau = RC$$





➤ Charging the C with a constant current

$$Cdv_c(t) = i_c(t)dt$$


$$v_c(t) = \frac{1}{C} \int_0^t i_c(t)dt + v_c(0)$$

$$v_c(t) = \frac{1}{C} It + v_c(0)$$

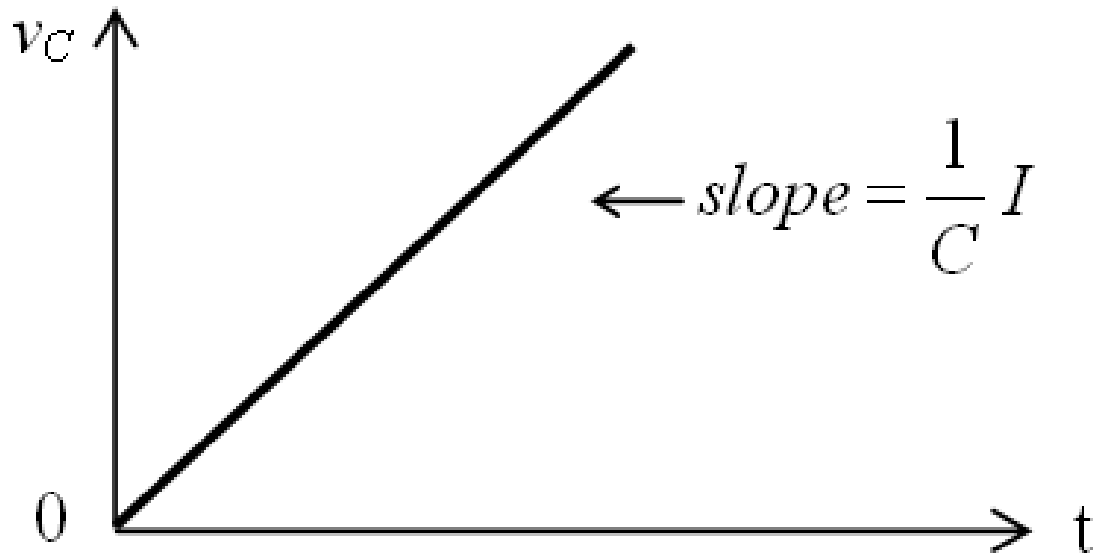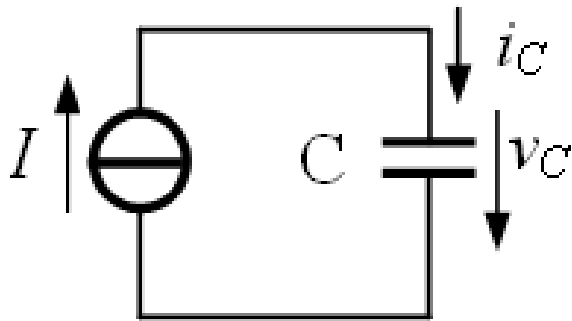


Charging the capacitor - summary


- with a R and a DC voltage source

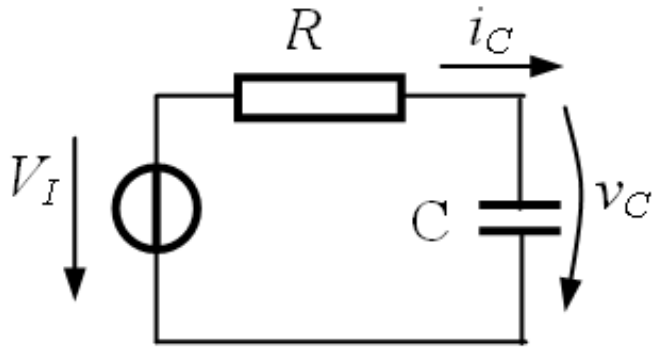

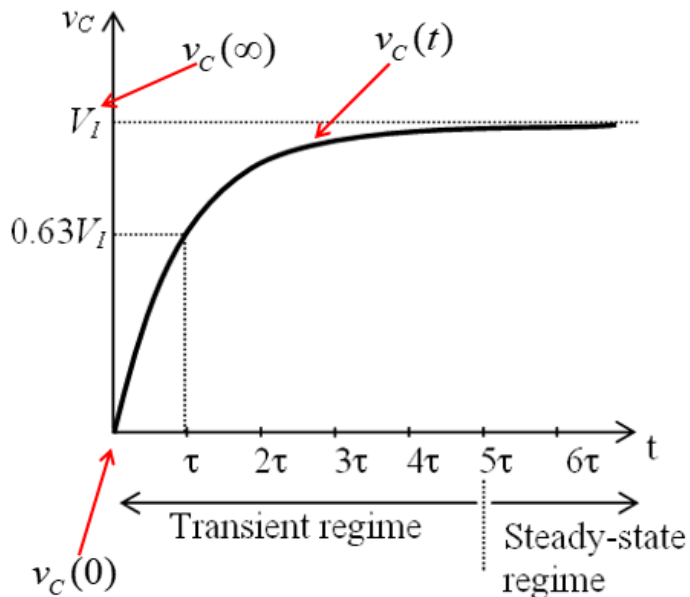
$$v_C(t) = v_C(0)e^{-\frac{t}{\tau}} + (1 - e^{-\frac{t}{\tau}})v_C(\infty)$$




- with a constant current source

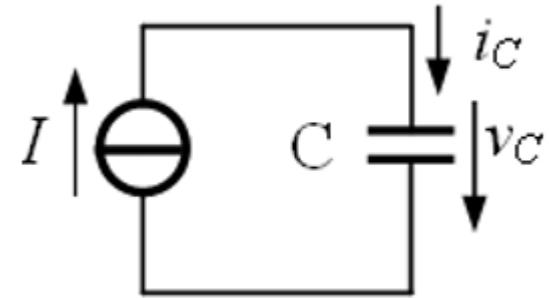


$$v_C(t) = \frac{1}{C}It + v_C(0)$$

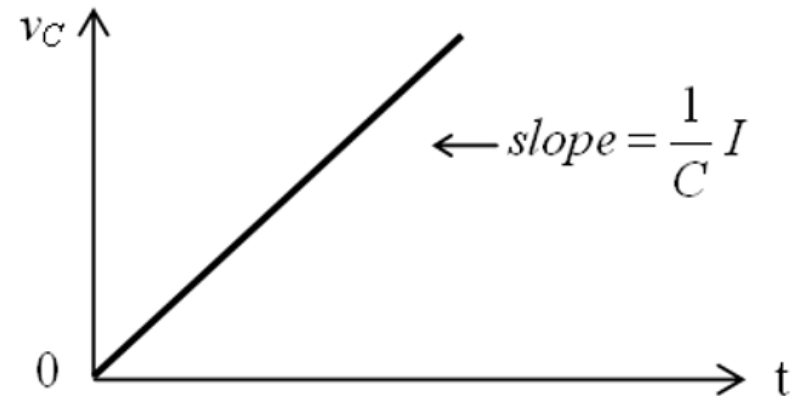

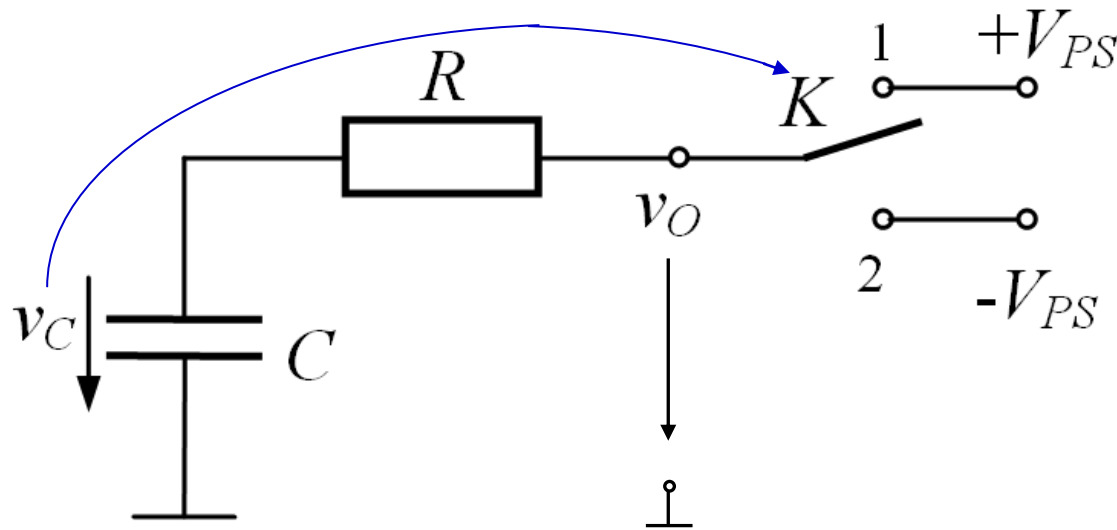Astable multivibrators (Relaxation oscillators)



Operating principle


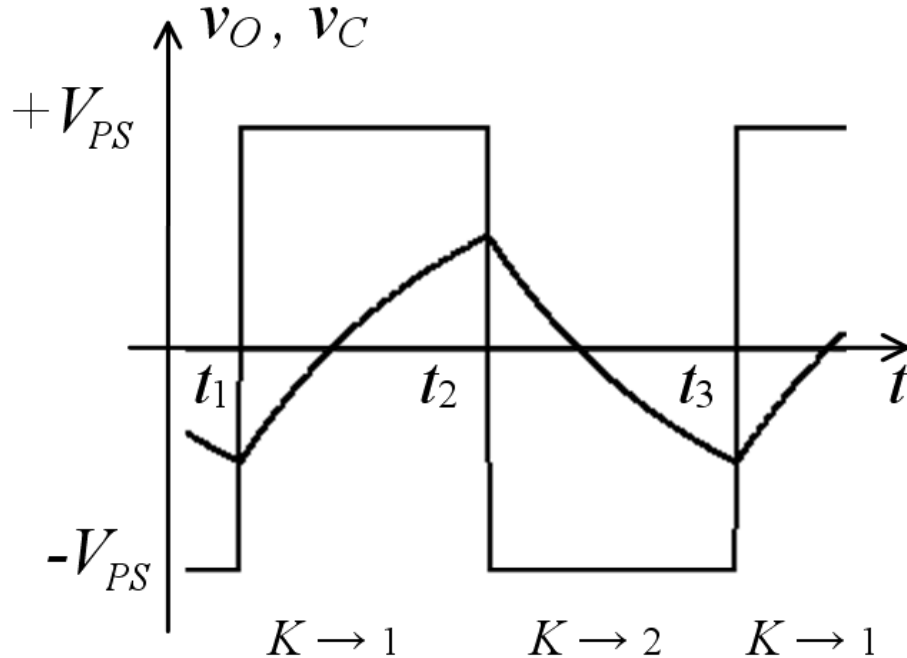


- the time variation of the voltage across the capacitor is exponential
- if the voltage across the capacitor is fed to a PF comparator, a **rectangular wave** is obtained

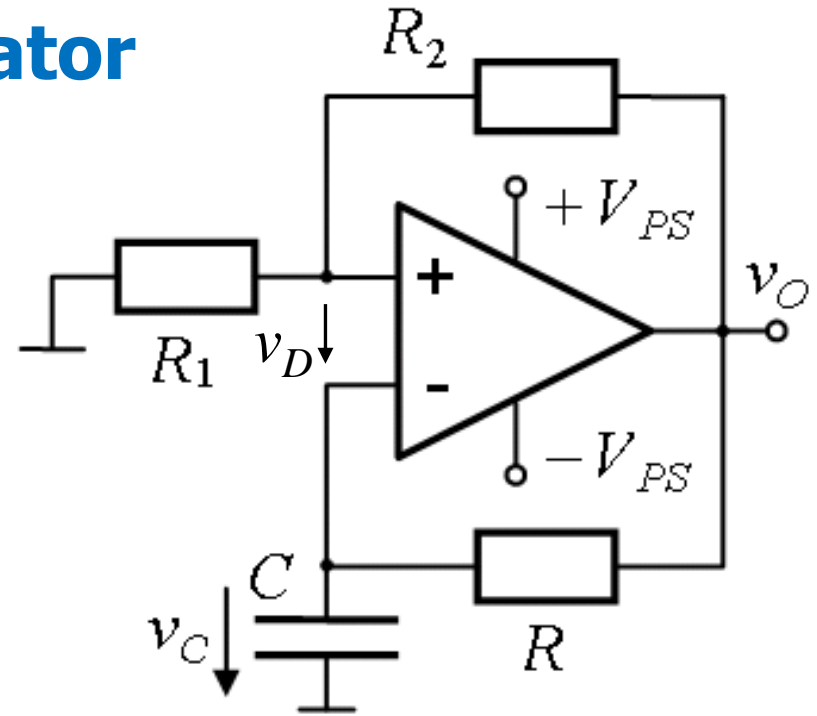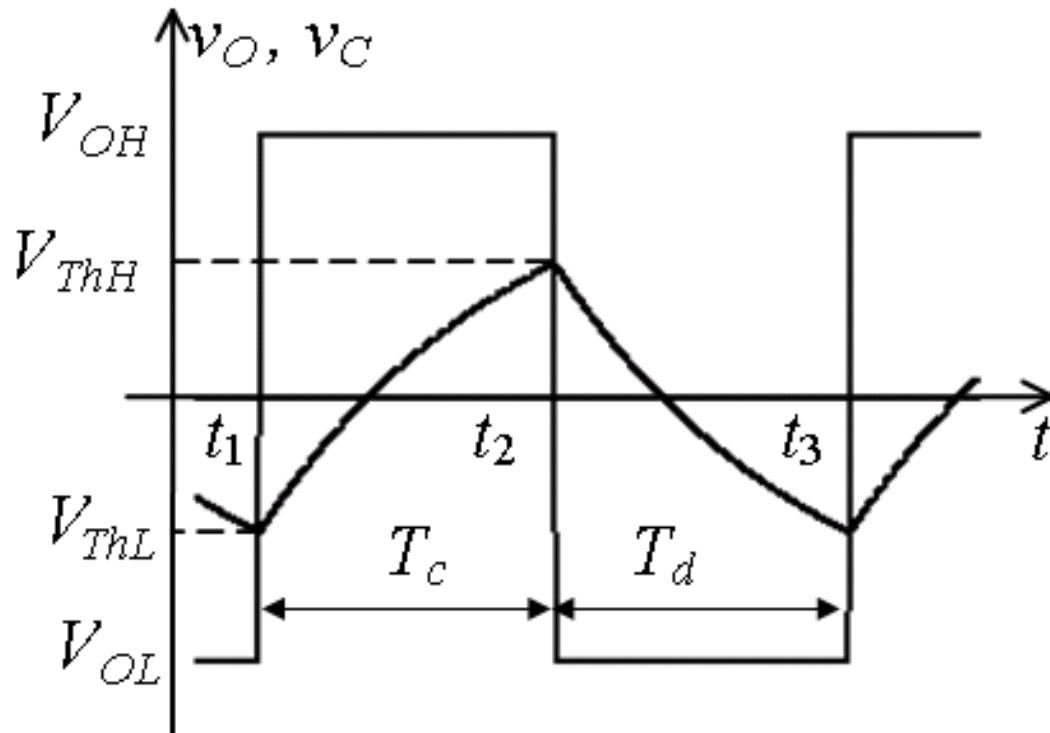1. Astable multivibrator- rectangular signal generator

$$v_C(t) = v_C(0)e^{-\frac{t}{\tau}} + \left(1 - e^{-\frac{t}{\tau}}\right)v_C(\infty)$$

$$v_D(t) = v^+ - v^- = \frac{R_1}{R_1 + R_2}v_O(t) - v_C(t)$$




$$V_{ThL} = \frac{R_1}{R_1 + R_2}V_{OL} = rV_{OL}$$

$$V_{ThH} = \frac{R_1}{R_1 + R_2}V_{OH} = rV_{OH}$$

$$t \in (t_1, t_2) \quad V_{ThH} = V_{ThL} e^{-\frac{T_c}{\tau}} + \left(1 - e^{-\frac{T_c}{\tau}}\right) V_{OH}; \quad T_c = \tau \ln \frac{V_{OH} - rV_{OL}}{(1-r)V_{OH}}$$
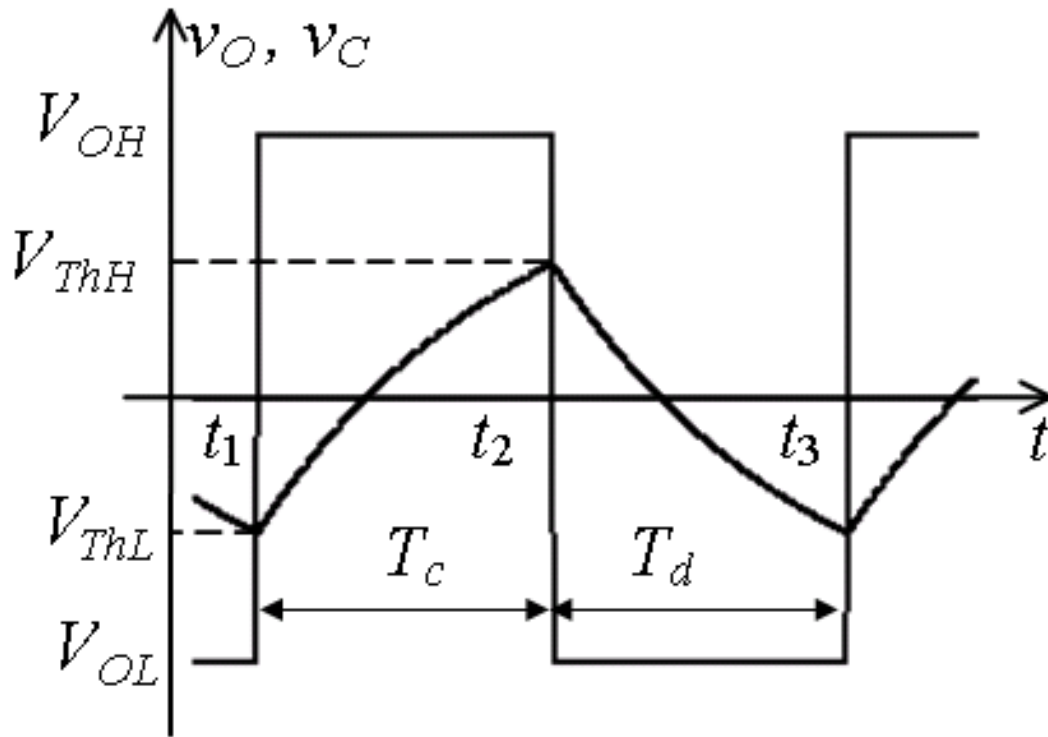
$$t \in (t_2, t_3) \quad V_{ThL} = V_{ThH} e^{-\frac{T_d}{\tau}} + \left(1 - e^{-\frac{T_d}{\tau}}\right) V_{OL}; \quad T_d = \tau \ln \frac{rV_{OH} - V_{OL}}{(r-1)V_{OL}}$$



$$T = T_c + T_d$$

Generally $V_{OH} = -V_{OL}$


$$T_c = T_d = \frac{T}{2} = \tau \ln \frac{1+r}{1-r}$$

$$T = 2RC \ln \frac{1+r}{1-r}$$

If $R_1 = R_2$

$$T = 2RC \ln 3 \approx 2,2RC$$

Problem

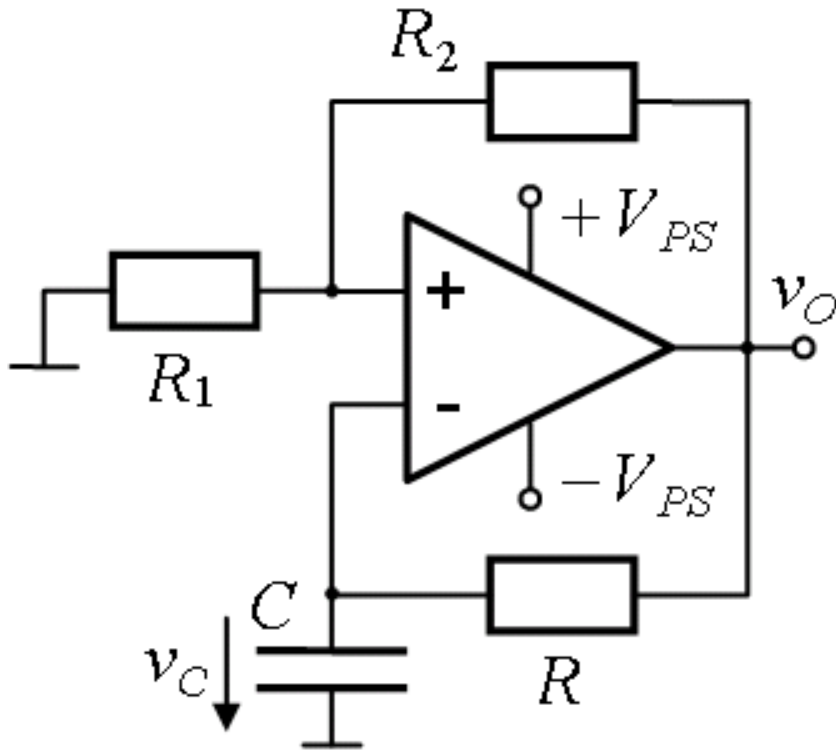

$\pm V_{PS} = \pm 12\text{V}$, $R_1 = 10\text{k}\Omega$, $R_2 = 20\text{k}\Omega$, $R = 7.5\text{k}\Omega$ and $C = 10\text{nF}$. The op amp is a rail-to-rail type.

- What are the minimum and maximum values for the voltage across the capacitor?
- What is the frequency of the rectangular signal?
- Modify the circuit for an adjustable frequency between $f_{\min} = 0.8\text{kHz}$ and $f_{\max} = 8\text{kHz}$?

a)

$$V_{ThL} = \frac{R_1}{R_1 + R_2} V_{OL} = \frac{10}{10 + 20} (-12) = -4\text{V}$$

$$V_{ThH} = \frac{R_1}{R_1 + R_2} V_{OH} = \frac{10}{10 + 20} \cdot 12 = 4\text{V}$$

$$b) \quad r = \frac{R_1}{R_1 + R_2} = \frac{10}{10 + 20} = \frac{1}{3}$$


$$T = 2RC \ln \frac{1+r}{1-r} = 2 \cdot 7.5\text{k}\Omega \cdot 10\text{nF} \cdot \ln \frac{1+1/3}{1-1/3} = 103.5\mu\text{s}$$

$$f = \frac{1}{T} = \frac{1}{166} = 9.7\text{kHz}$$

$$c) \quad T = 2RC \ln \frac{1+r}{1-r} = 2RC \ln 2 = 1.386 RC$$

$$T_{\min} = \frac{1}{f_{\max}} = 1.386 R' C$$
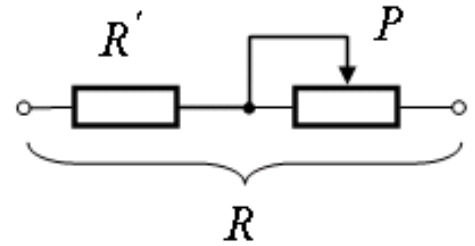
$$R' = \frac{1}{1.386 f_{\max} C} = \frac{1}{1.386 \cdot 8\text{kHz} \cdot 10\text{nF}} = 9\text{k}\Omega \quad R' = 8.87\text{k}\Omega (1\%).$$




$$T_{\max} = \frac{1}{f_{\min}} = 1.386 (R' + P) C \quad P = 9R' = 9 \cdot 8.87 = 79.8\text{k}\Omega$$

$$P = 100\text{k}\Omega$$

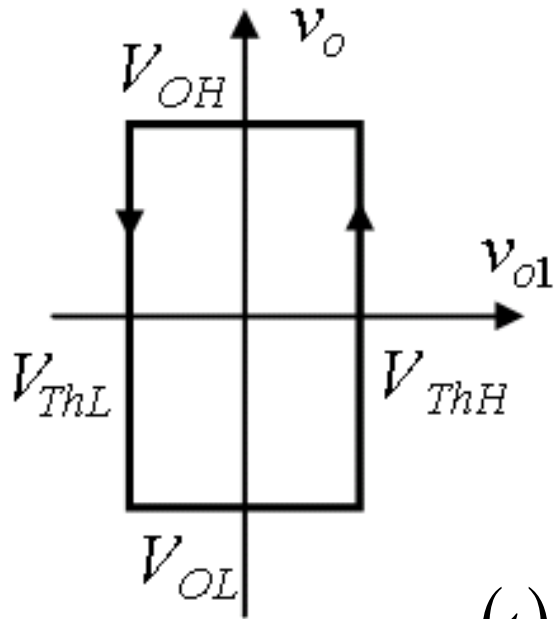2. Astable multivibrator with an integrator and a comparator



Rectangular and triangular signal generator




$$v_{o1}(t) = v_C(t)$$

$$V_{ThL} = -\frac{R_1}{R_2} V_{OH}$$

$$V_{ThH} = -\frac{R_1}{R_2} V_{OL}$$

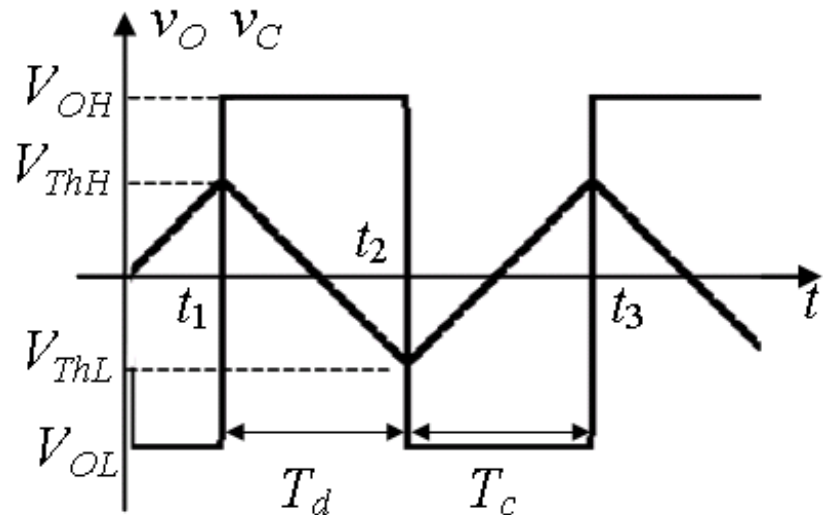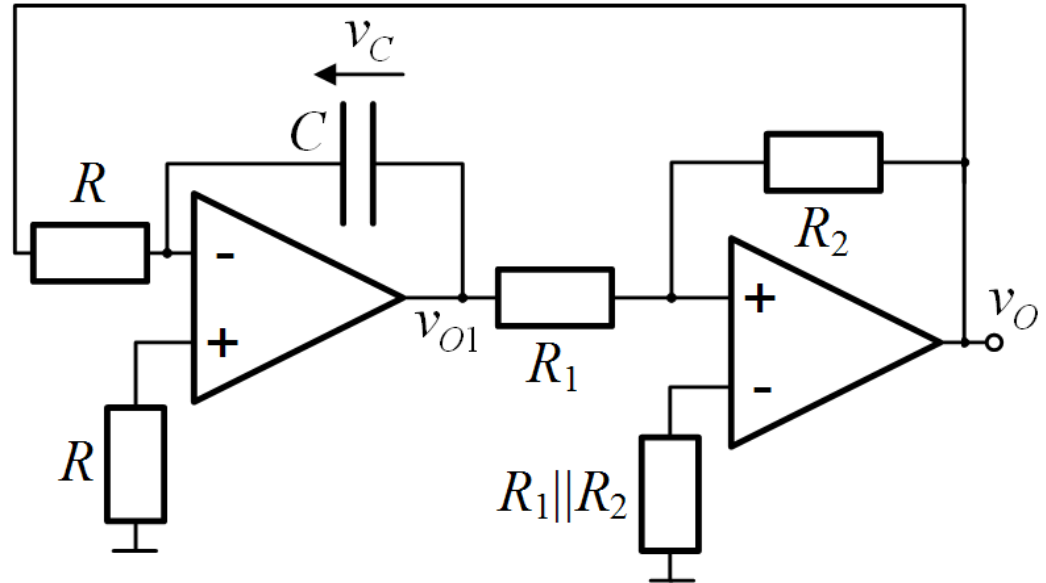

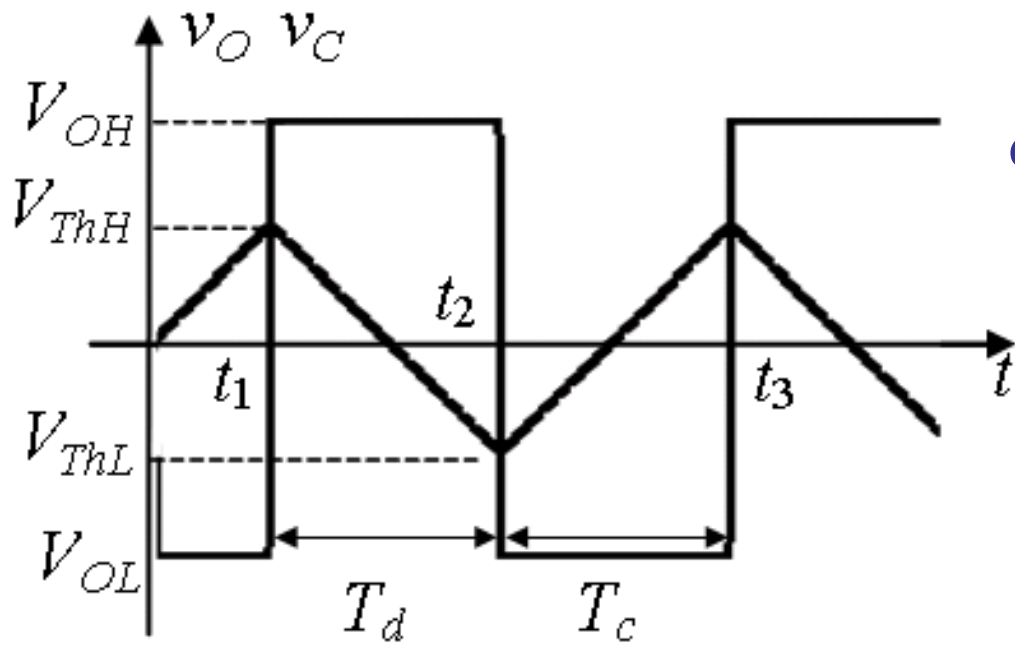

$$T = T_d + T_c$$

In general $V_{OH} = -V_{OL}$

$$T = 2RC \frac{V_{ThH} - V_{ThL}}{V_{OH}} = 4RC \frac{R_1}{R_2}$$

If $R_1 = R_2$

$$T = 4RC$$

$$C \Delta v_C = i_C \Delta t$$

discharge

$$i_C = \frac{0 - V_{OH}}{R} = -\frac{V_{OH}}{R}$$

$$\Delta v_C = V_{ThL} - V_{ThH};$$


$$\Delta t = t_2 - t_1 = T_d$$

$$T_d = RC \frac{V_{ThH} - V_{ThL}}{V_{OH}}$$

$$T_c = RC \frac{V_{ThH} - V_{ThL}}{-V_{OL}}$$

$$f = \frac{1}{4RC}$$

Problem

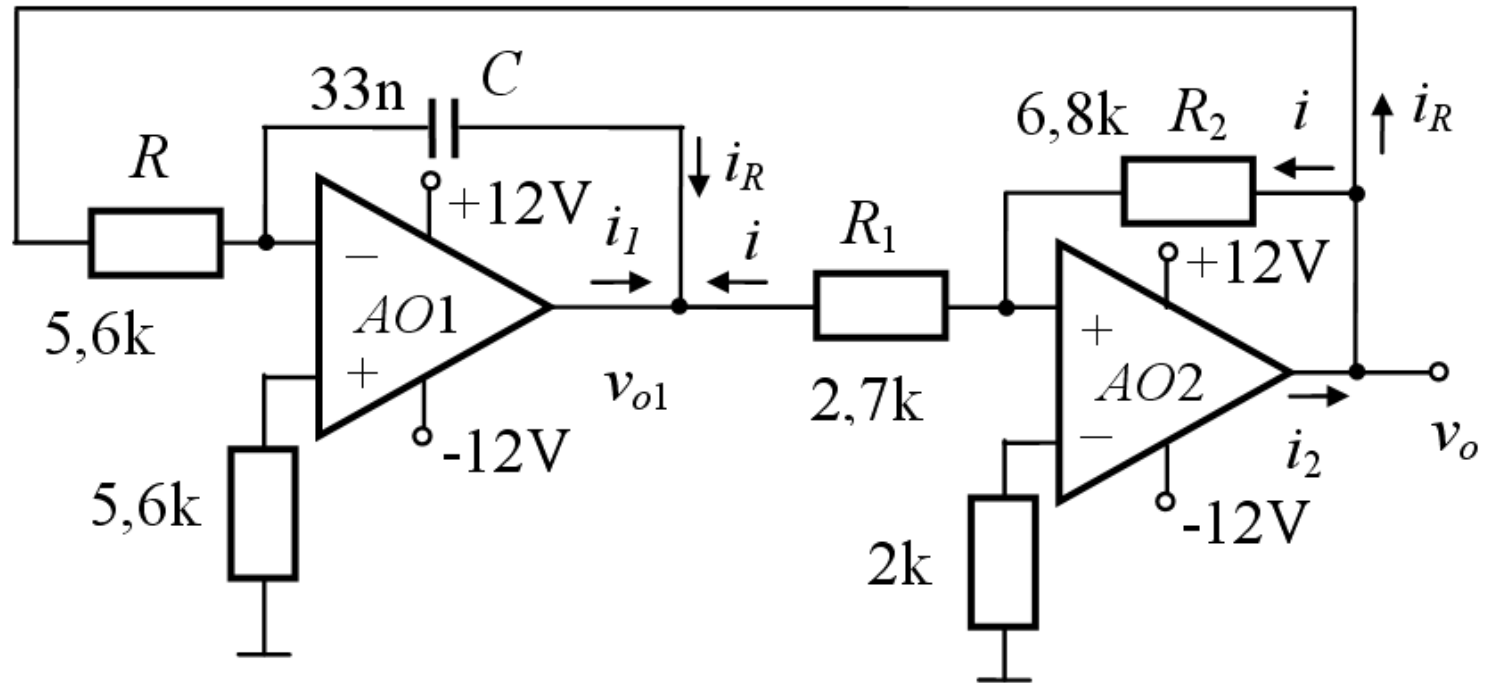


At saturation, the output voltage of op-amps is within 1V of the supply

- What is the amplitude of the triangular voltage?
- What is the oscillation frequency?
- What is the maximum value of the current to the output of each op amp?

The independence of the supply voltage

OPTIONAL

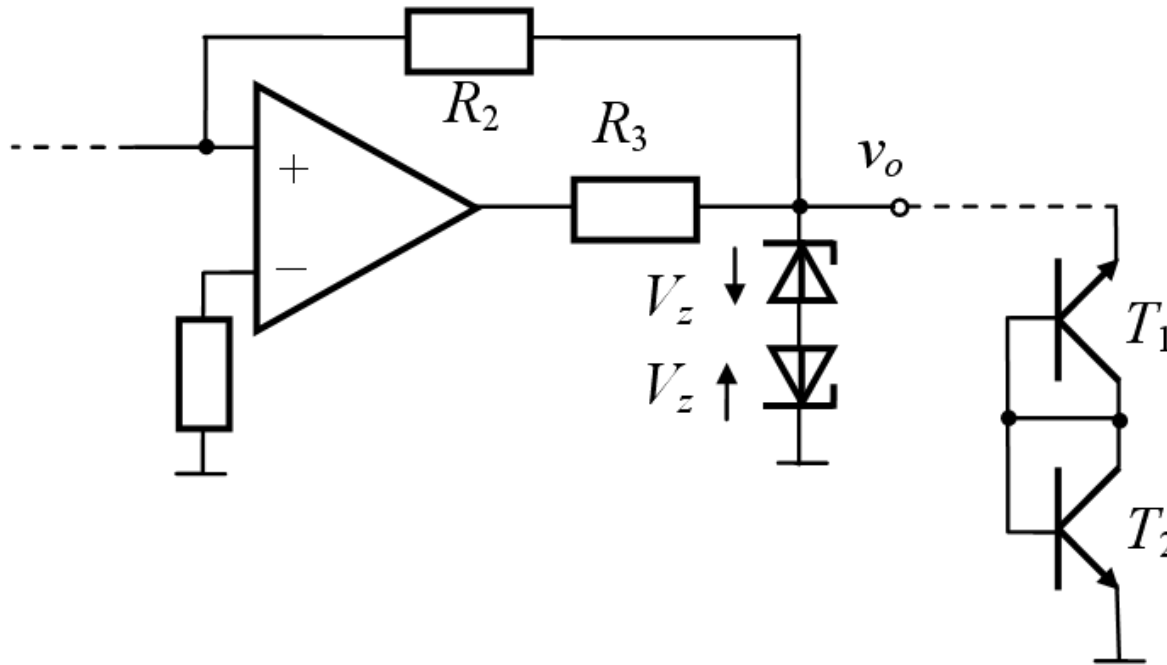


$$V_{OH} = V_Z + 0,7V;$$

$$V_{OL} = -V_Z - 0,7V$$

The reverse-biased base to emitter junction behaves as a Zener diode, regulating the voltage at a voltage dependent on the transistor type and on the emitter current (5V ... 8V) .

Frequency adjustment
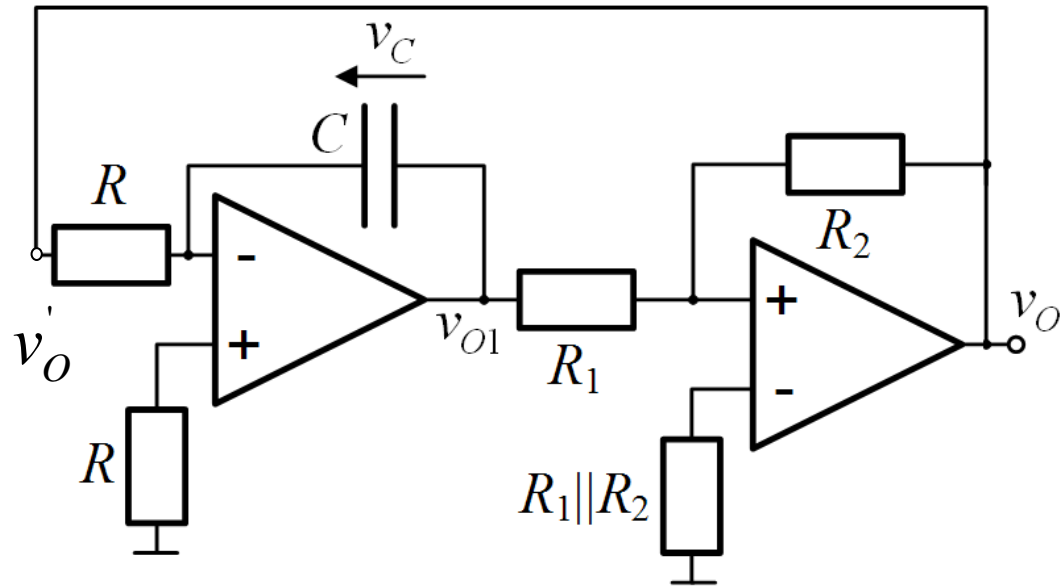
$$T = 2RC \frac{V_{ThH} - V_{ThL}}{V_{OH}}$$




$$V_{ThL} = -\frac{R_1}{R_2} V_{OH}; \quad V_{ThH} = -\frac{R_1}{R_2} V_{OL}; \quad V_{OH} = -V_{OL}; \quad V_{ThH} - V_{ThL} = 2 \frac{R_1}{R_2} V_{OH}$$

$$T = 2RC \frac{2 \frac{R_1}{R_2} V_{OH}}{V_{OH}} = 4RC \frac{R_1}{R_2} \frac{V_{OH}}{V_{OH}} \quad f = \frac{1}{4RC} \frac{R_2}{R_1} \frac{V_{OH}}{V_{OH}}$$

If V_{OH}' can be adjusted, then the period (frequency) can be adjusted

Frequency adjustment - cont.

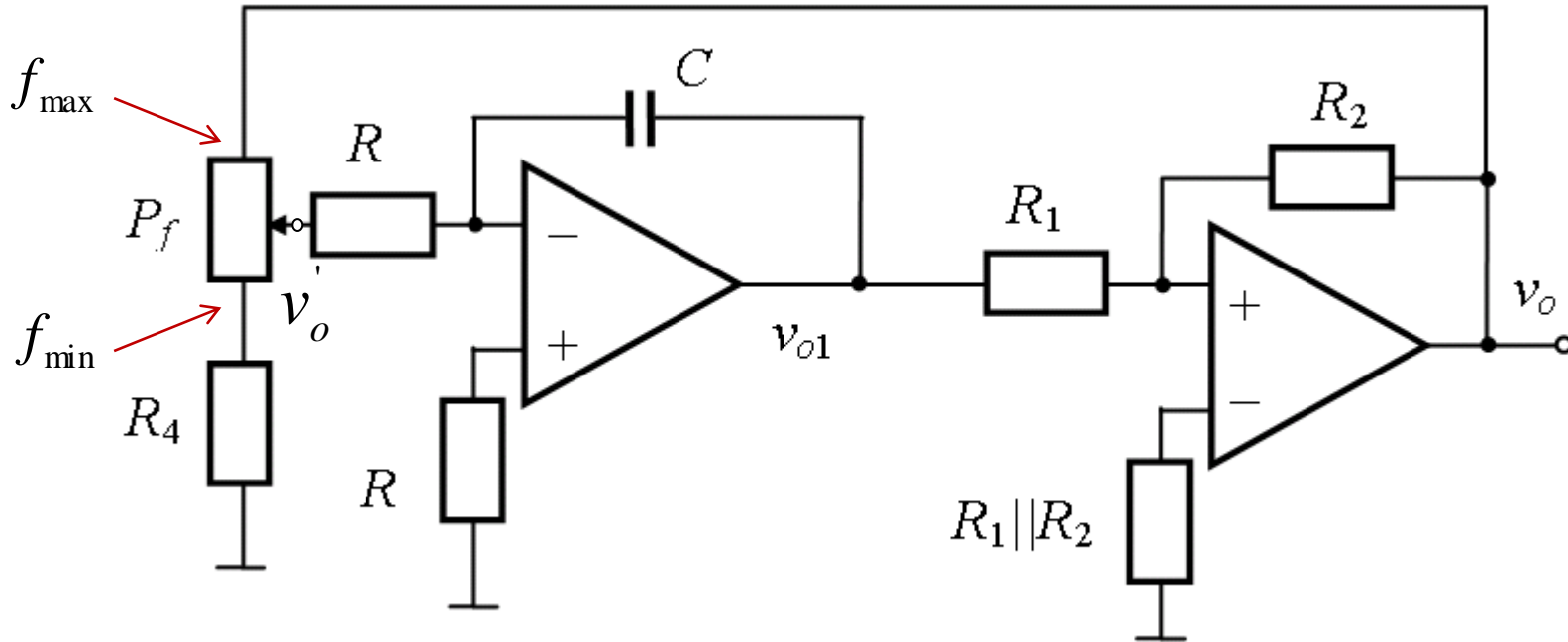


If $v'_o = v_o$;

$$f_{\max} = \frac{1}{4RC} \frac{R_2}{R_1};$$

If $v'_o = \frac{R_4}{R_4 + P_f} v_o$;

$$f_{\min} = \frac{1}{4RC} \frac{R_2}{R_1} \frac{R_4}{R_4 + P_f}$$

Problem

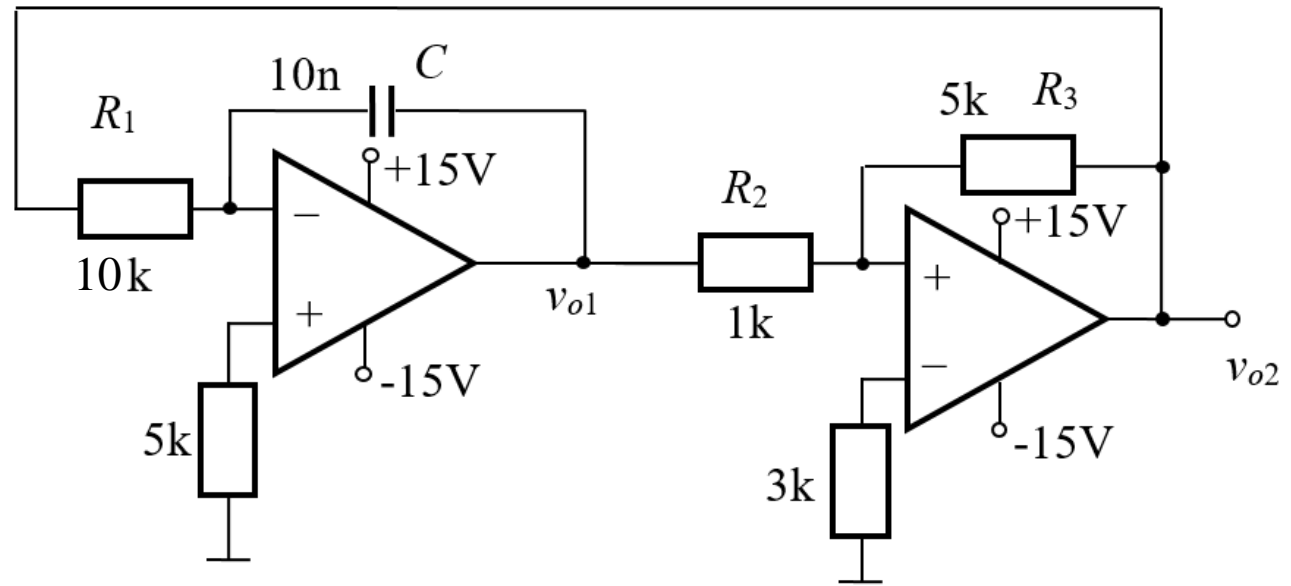


Consider rail-to-rail op-amps

- What is the oscillation frequency?
- Modify the circuit to obtain an adjustable frequency in the range of [5; 25] kHz.

Offset adjustment of the triangular voltage

OPTIONAL

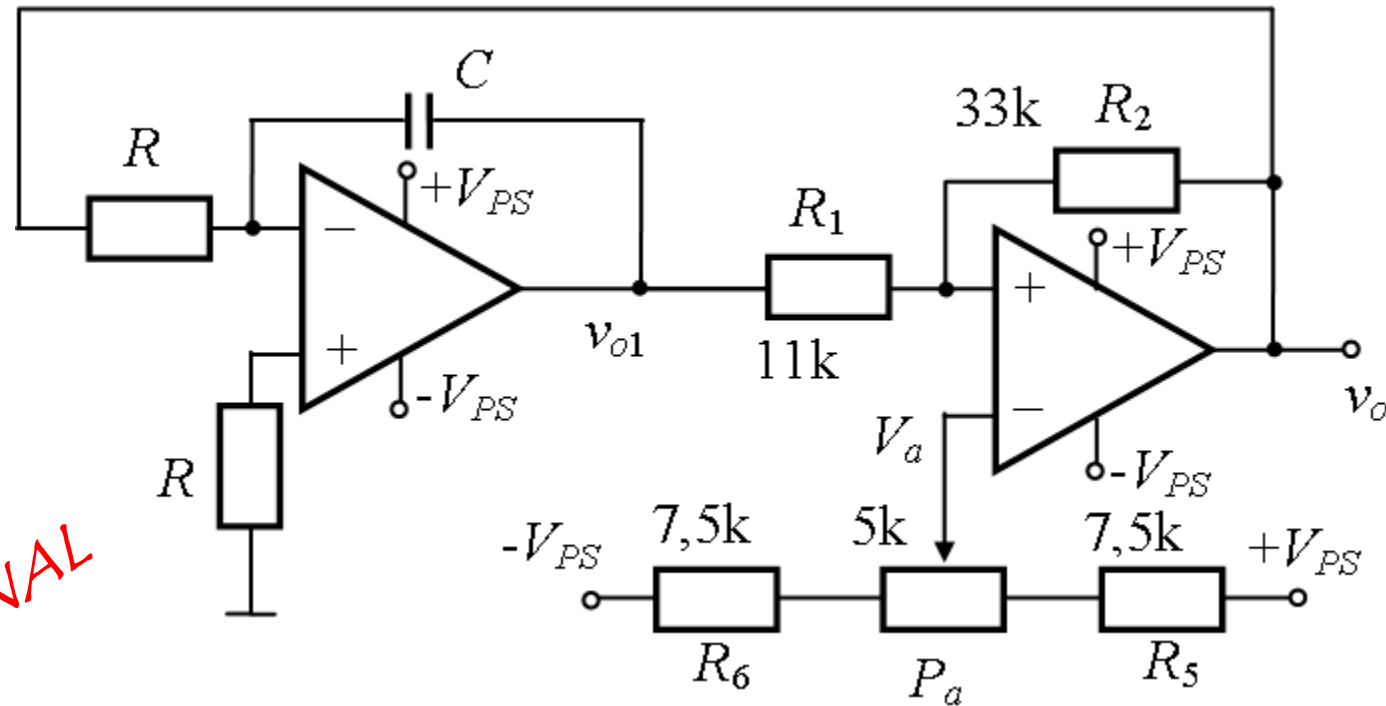


From P_a one can move the hysteresis along the horizontal axis, thus adjusting the offset (dc level) of the triangular voltage.

$$V_{ThL} = \left(1 + \frac{R_1}{R_2}\right) V_a - \frac{R_1}{R_2} V_{OH} \quad V_{ThH} = \left(1 + \frac{R_1}{R_2}\right) V_a - \frac{R_1}{R_2} V_{OL}$$

$$V_{a\max} = \frac{P_a + R_6}{R_5 + P_a + R_6} V_{PS} + \frac{R_5}{R_5 + P_a + R_6} (-V_{PS}) = 3.75V$$

OPTIONAL

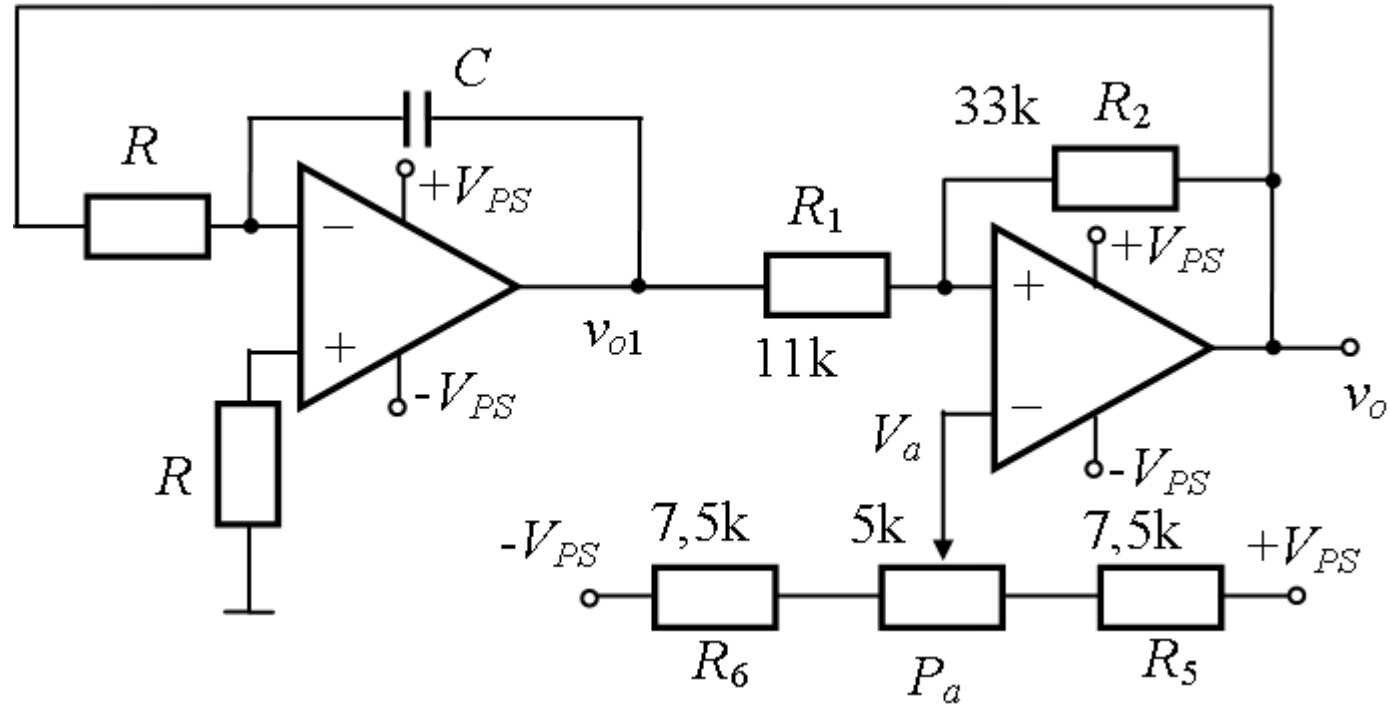Offset adjustment of the triangular voltage



$$V_{a\min} = \frac{R_6}{R_5 + P_a + R_6} V_{PS} + \frac{P + R_5}{R_5 + P_a + R_6} (-V_{PS}) = -3,75V$$

The offset can be adjusted between

$$V_{o1\max} = \left(1 + \frac{11}{33}\right) \cdot 3,75 = 5V;$$

$$V_{o1\min} = \left(1 + \frac{11}{33}\right) \cdot (-3,75) = -5V$$

Specialized integrated circuits for signals generation

- NE566 - Function generator VCO, square, triangular - 1MHz
- AD9833 - Low power, programmable waveform generator: sine, triangular, and square wave. No external components. Frequency and phase are software programmable. 3-wire serial interface. Power-down function (SLEEP). 0 MHz to 12.5 MHz output frequency range .
- 555 - highly stable device for generating accurate time delays or oscillation (astable and monostable)

Clock generators


- Quartz-crystal oscillator

$f_0 = 1, 2, 4, 5, \dots, 20\text{MHz}$

$f_0 = 14,31818\text{MHz}$ - video adapter in personal computers

$f_0 = 32,768\text{KHz}$ - digital wristwatch, divide by 2^{15} to get 1Hz

OPTIONAL

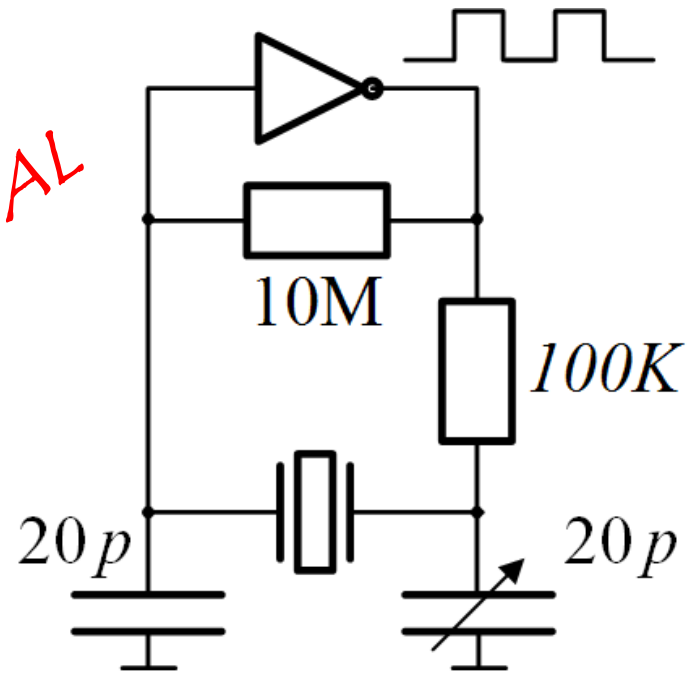

- NOT gates oscillator

