

SINUSOIDAL OSCILLATORS

I. OBJECTIVES

- a) The adjustment of the value of the forward transmission a in order to fulfill the Barkhausen criterion in Wien bridge oscillators.
- b) Understanding the amplitude stabilization mechanism of the oscillations, using amplitude stabilization circuits with diodes.

II. COMPONENTS AND INSTRUMENTATION

For the experiments, we use a breadboard and a 741 operational amplifier, two 1N4148 diodes, resistors and capacitors. In order to supply the experimental assembly, we use a dc voltage source. We will also need a sine wave signal generator. To visualize the ac voltages, we use a dual channel oscilloscope.

III. PREPARATIONS

P.1. The Wien bridge sinusoidal oscillator

The oscillator circuit is presented in Fig.2.

- Which is the frequency of the sine wave signal generated by the oscillator? What is the value of $|r|$ at the frequency of oscillation? What about the phase of r ?
- What should be the value of the forward transmission (basic amplifier's gain) a in order to ensure the oscillation? What happens with the output signal v_O if a decreases under this value? What if a increases over this value?
- As you can see from the scheme in Fig. 2, the circuit doesn't have an input signal, only the power supply. Despite this, we will obtain a sine wave signal at the output of the circuit. Explain the mechanism by which the sine wave signal v_O at the output of the oscillator is generated.
- In order to obtain at the output of the oscillator a sine wave signal in the absence of an external input signal, is it sufficient to set a at the value specified in the Barkhausen criterion, a_0 ? How must the value a be with respect to a_0 after powering up the supply? Why? How does the waveform $v_O(t)$ look like if a takes this value different from a_0 ? How must the value a

be modified after the oscillations have appeared in order to obtain at the output a sine wave signal?

- The condition for oscillation start-up and then for maintaining the oscillation after start-up implies the achievement of a:
 - Constant and infinite gain in the circuit.
 - Constant and finite gain, given by the Barkhausen criterion.
 - Larger gain than the one from the Barkhausen criterion, at start-up (after power up), followed by the decrease of the gain until it reaches the value from the Barkhausen criterion.

P.2. The amplitude stabilization in Wien bridge oscillators

- On the oscillator with Wien Bridge from Fig.2, we will study now the amplitude stabilization mechanism.

In a sinusoidal oscillator with OpAmp there is no input signal, and the sinusoidal oscillation is generated when the circuit is powered up.

- For the circuit in Fig. 2, plot the waveform of the differential input signal $v_{OUT\ WIEN}(t)$ after the circuit's power up. Also plot the output signal, if the basic amplifier's gain is $a > a_0$, where a_0 is the basic amplifier's gain that fulfils the Barkhausen criterion.

P.2.1. Amplitude stabilization with diodes

- The oscillator circuit with OpAmp and Wien Bridge, for which the amplitude stabilization is done using two anti-parallel diodes, is presented in Fig. 3.
- In what state (on or off) are the diodes D_1 and D_2 during the transient regime, just after the power up? Compute the gain of the basic amplifier a , in this case. Plot $v_O(t)$ and $v_{OUT\ WIEN}(t)$ in this case.
- In permanent regime, when we already have at the output a sine wave signal $v_O(t)$, are D_1 and D_2 on? Which is the condition for D_1 and D_2 to be on? Compute the basic amplifier's gain a in this case.
- Why is it necessary the use of two anti-parallel diodes in the circuit from Fig. 3?
- What is the role of the resistor R_5 in parallel with D_1 and D_2 in the circuit?

IV. EXPLORATIONS AND RESULTS

1. The Wien Bridge sinusoidal oscillator

Explorations

- Build the circuit from Fig. 1. Supply the assembly with $\pm 15\text{V}$ dc.
- Apply at the input of the Wien bridge a sine wave signal $v_I(t)$ from the signal generator, $v_I(t) = 9\sin 2\pi v_0 t$ [V], where $v_0 = 1.6\text{KHz}$, frequency where the absolute value of the Wien Bridge transfer function is maximum ($1/3$).
- Using the oscilloscope visualize the signals $v_I(t)$ and $v_O(t)$ (between OUT and the ground).
- Using potentiometer POT, adjust the value of the forward transmission a until the amplitude of the signal $v_O(t)$, \hat{V}_O , equals the amplitude of the signal $v_I(t)$, \hat{V}_I .

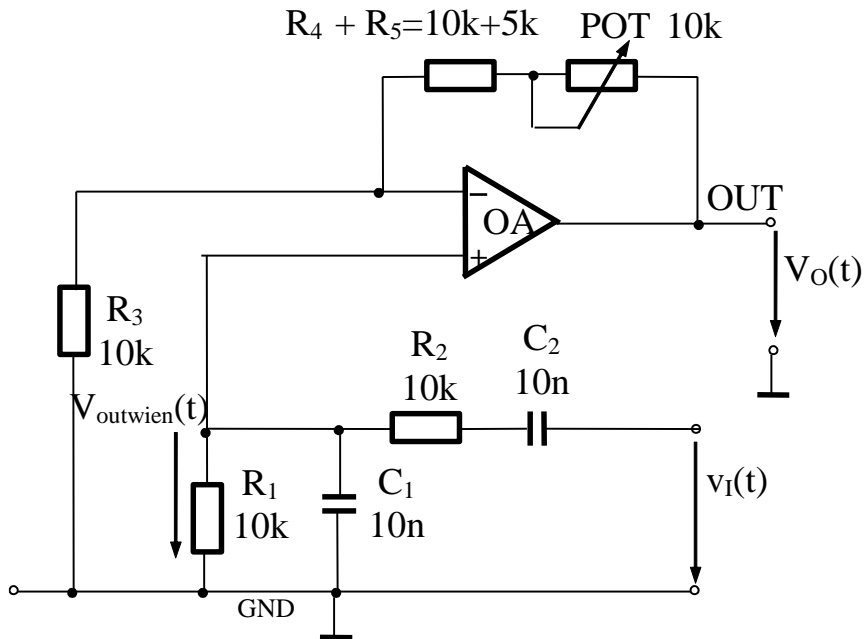


Fig. 1. OpAmp and Wien bridge circuit

- From this point on, no signal will be applied from the signal generator. The new circuit (Fig. 2) is obtained by connecting capacitor C_2 with the output of the OpAmp – the feedback loop is now closed.
- Modify the position of the cursor of POT in order to obtain at the output a sine wave signal $v_o(t)$, visualizing simultaneously $v_o(t)$ and $v_{OUT\ WIEN}(t)$ on the oscilloscope.
- Plot the signals $v_o(t)$ and $v_{OUT\ WIEN}(t)$. Measure and write down:
 - the amplitude and frequency of $v_o(t)$;
 - the amplitude and frequency of $v_{OUT\ WIEN}(t)$.

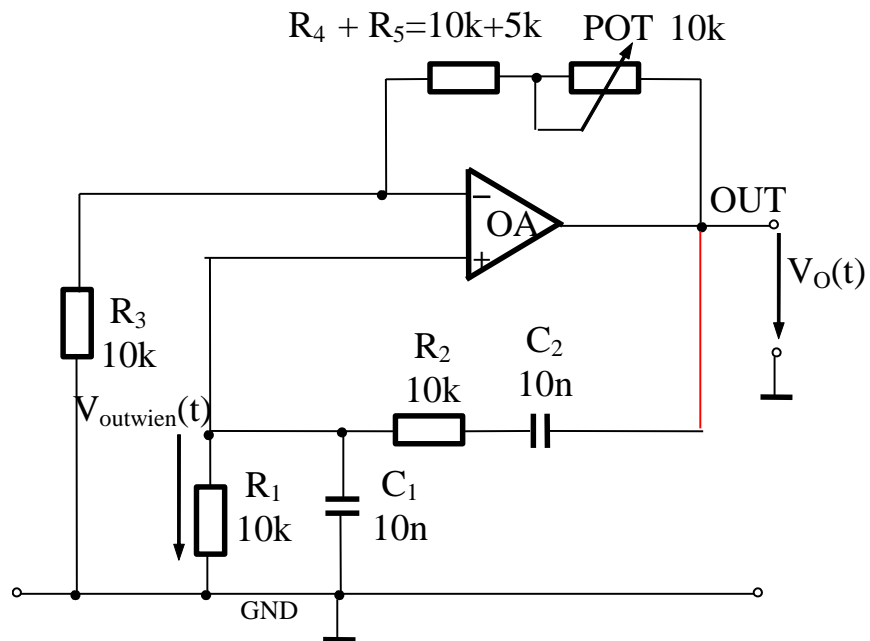


Fig. 2. Wien bridge oscillator

Results

- Determine r from the plots of $v_{OUT\ WIEN}(t)$ and $v_o(t)$.
- Determine the value of the phase shift between $v_{OUT\ WIEN}(t)$ and $v_o(t)$. Using your measurements, check the fulfillment of the Barkhausen criterion.

2. The amplitude stabilization in Wien Bridge oscillators

2.1. Amplitude stabilization with diodes

Explorations

- Use the circuit in Fig. 3 by adding two diodes.
- Visualize $v_o(t)$ on the oscilloscope. If needed, modify the cursor position of Pot until you obtain a sine wave on the output. Plot $v_o(t)$ and measure the amplitude and frequency of $v_o(t)$;
- Visualize and plot $v_{OUT\ WIEN}(t)$. Measure its amplitude and frequency.
- Now visualize $v_o(t)$ while you decrease the value of Pot, and notice the change in $v_o(t)$. Plot $v_o(t)$ for a randomly selected position of the cursor of POT, other than the one in the previous exploration step.
- Increase the value of POT and notice the change in $v_o(t)$. Redraw $v_o(t)$ for a randomly selected value of Pot, other than the ones in the previous exploration steps.
- Visualize the voltage across the group D_1 , D_2 , R_5 , and $-v_o(t)$ with the oscilloscope and plot them.

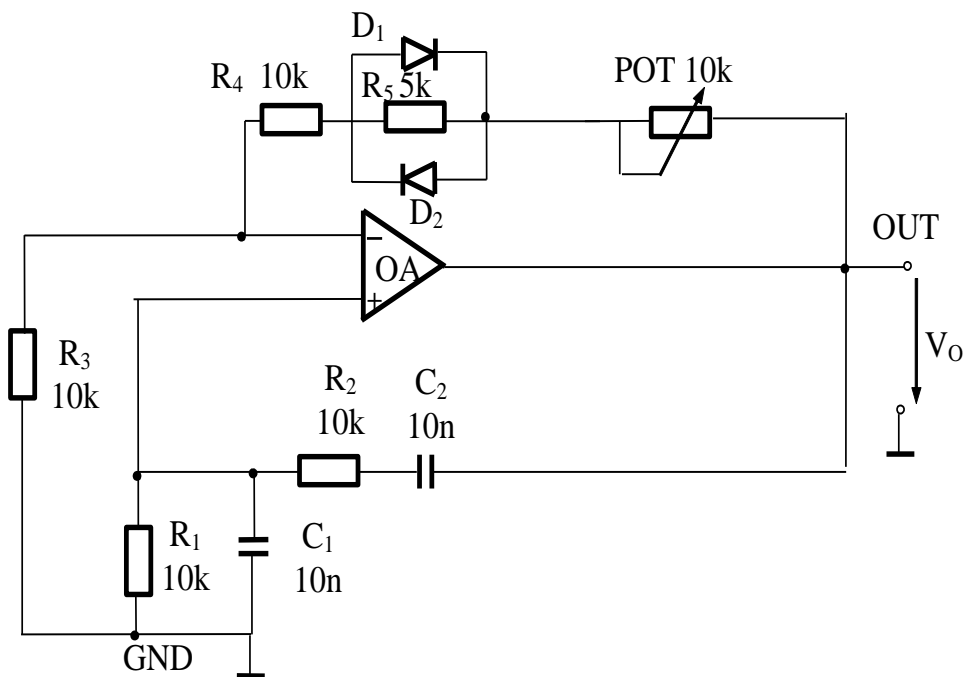


Fig. 3. Wien bridge oscillator: amplitude stabilization with diodes

Results

- Compare the frequency ν_0 of the signal $v_o(t)$ in this Wien Bridge oscillator with amplitude stabilization with the frequency of $v_o(t)$ in the basic Wien bridge oscillator measured before.
- How can you modify $v_o(t)$ amplitude, \hat{V}_o at the oscillator output? Give an approximate expression of \hat{V}_o .
- Is $v_o(t)$ a “clean” sine wave (without any distortions)? Why?
- Find the value of the phase shift between $v_{OUT\ WIEN}(t)$ and $v_o(t)$.
- How could you determine, using only the plots of $v_o(t)$ and $v_{OUT\ WIEN}(t)$, the value of the forward transmission a of the circuit? Compute it.
- What process takes place in the circuit if the value of Pot decreases and how does it influence the output $v_o(t)$? Answer the same question if the value of POT increases.

REFERENCES

1. Oltean, G., Circuite Electronice, UT Pres, Cluj-Napoca, 2007, ISBN 978-973-662-300-4
2. Sedra, A. S., Smith, K. C., Microelectronic Circuits, Fifth Edition, Oxford University Press, ISBN: 0-19-514252-7, 2004
3. http://www.bel.utcluj.ro/dce/didactic/fec_aai/