

## SEMINAR 5

### Contents:


- OA Voltage Amplifiers

#### 1. OA – ideal



a) Find the expression  $v_O(v_{I1})$  assuming the range of  $v_{I1}$  small enough to keep OA in the active region. What is the application of the circuit?

b) Plot  $v_O(t)$  for  $v_{I1}(t)=3\sin\omega_0t$  [V]

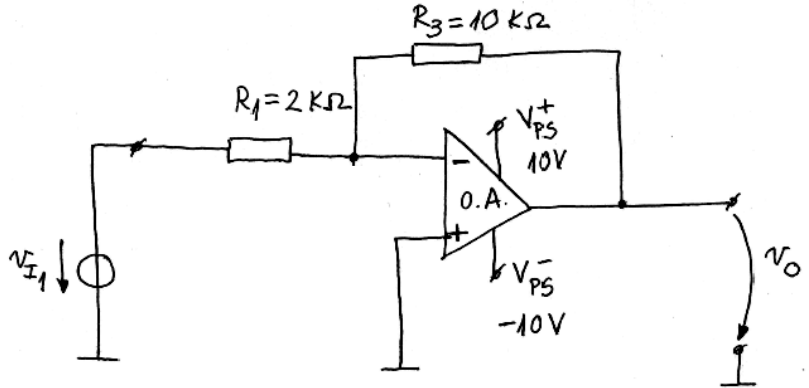c) What are the values of : the input resistance  $R_{i1}$  seen by  $v_{I1}$  and the output resistance  $R_o$  of the amplifier?



#### 2.

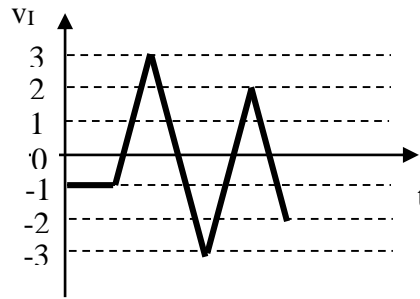
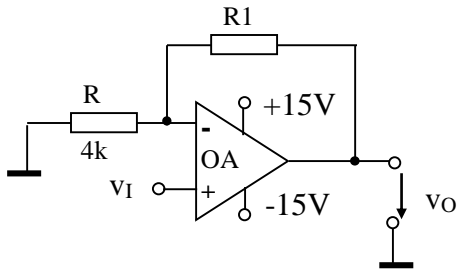


a) For  $R_1=12K$  find the values of the voltage gain, the input resistance and plot VTC  $v_O(v_I)$ .

b) How does the  $v_O(t)$  look like for  $v_I(t)$  in the above figure?

c) Redesign the circuit to obtain the adjustable voltage gain  $A_v \in [5;10]$ .

#### 3.

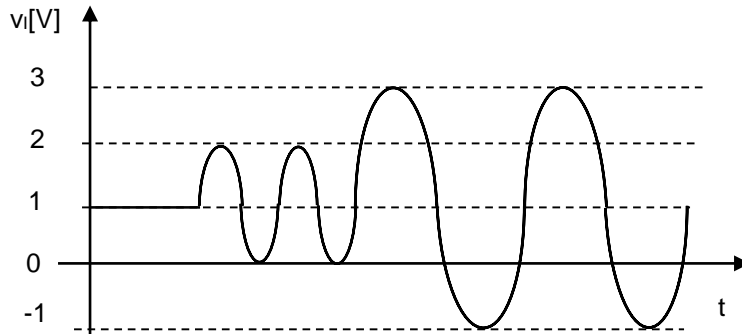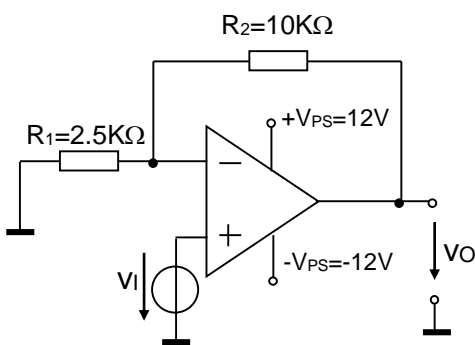

Assume a rail-to-rail op amp.

a) What is the expression and the value of the gain and how does the VTC,  $v_O(v_I)$  look like considering  $v_I \in [-5V;5V]$ ? What is the  $v_I$  range for that the amplifier remains in its active region?

b) What are the values of the input and output resistances. What is the application of the circuit?

c) How does the  $v_O(t)$  look like for  $v_I(t)$  in the above figure?

d) Where another source  $v_{I1}$  should be connected to obtain  $v_O=5v_I-4v_{I1}$ ?


4. Assume OA – ideal.

a) Prove that the above circuit has negative feedback.

b) Assuming suitable values for  $v_{I1}$ ,  $v_{I2}$  to have always the O.A. in the active region, what is the expression of  $v_O(v_{I1}, v_{I2})$ ? What is the application of the circuit? Plot  $v_O(t)$  for  $v_{I1}(t) = 3 \sin \omega t$  [V] and  $v_{I2}(t) = -v_{I1}(t)$ .

c) What should be the relationship between  $R_1, R_2, R_3, R_4$  to obtain the following expression:  $v_O = 5(v_{I1} - v_{I2})$ ?

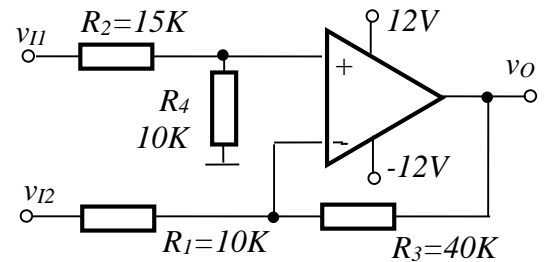d) For  $R_1, R_2, R_3, R_4$  in the original schematic, compute the input resistance seen by  $v_{I1}$ .




5. Assume OA – ideal

a) What is the expression of  $v_O(v_{I1}, v_{I2}, v_{I3})$  assuming OA in the active region for  $R_1 = R_2 = R_3 = R_4 = 15K\Omega$ ?

b) Now consider  $v_{I3} = 0$ . Find the relationship between  $R_1, R_2, R_3, R_4$  in order to obtain the expression:  $v_O = 3(v_{I2} - v_{I1})$ ? For what range of values of  $(v_{I2} - v_{I1})$  does OA work in the active region? Deduce the expressions for input resistances considering the input only  $v_{I1}$  (with  $v_{I2}$  set to zero), respectively only  $v_{I2}$  (with  $v_{I1}$  set to zero), and the output resistance of the circuit.

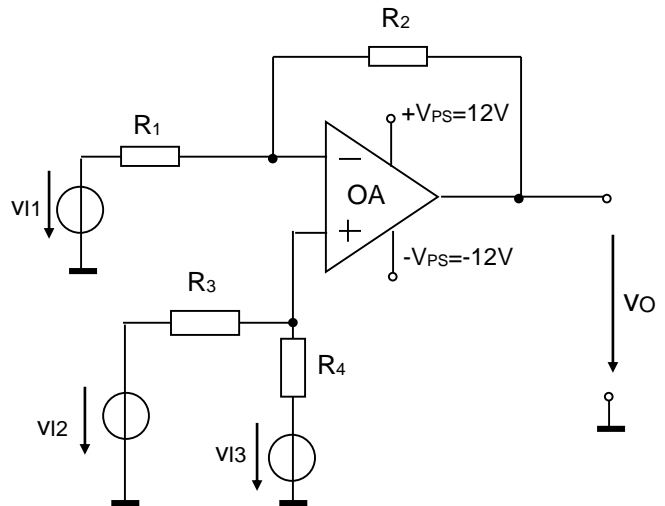c) If  $v_{I3} = 0$  and  $v_O = 3(v_{I2} - v_{I1})$  plot  $v_O(t)$  assuming  $v_{I1}(t) = 2 \sin \omega_0 t$  [V] + 1V si  $v_{I2}(t) = -3 \sin \omega_0 t$  [V] + 4V. What is the application of the circuit?



6. OA – ideal

a) Find the expression  $v_O(v_{I1}, v_{I2})$  assuming the ranges of  $v_{I1}, v_{I2}$  small enough to keep OA in the active region. What is the application of the circuit?

b) Plot  $v_O(t)$  for  $v_{I1}(t) = 3 \sin \omega_0 t$  [V] and  $v_{I2}(t) = 3V - 2 \sin \omega_0 t$  [V].

c) What are the values of: the input resistance  $R_{i1}$  seen by  $v_{I1}$ ; the input resistance  $R_{i2}$  seen by  $v_{I2}$ ; the output resistance  $R_o$  of the amplifier?

d) What should be the relationship between  $R_1, R_2$  and  $R_3$  to obtain the function:  $v_O = -(v_{I1} + v_{I2})$ ?

