


SEMINAR 5

Contents:

- Voltage regulators
- Integrated voltage regulators

1.

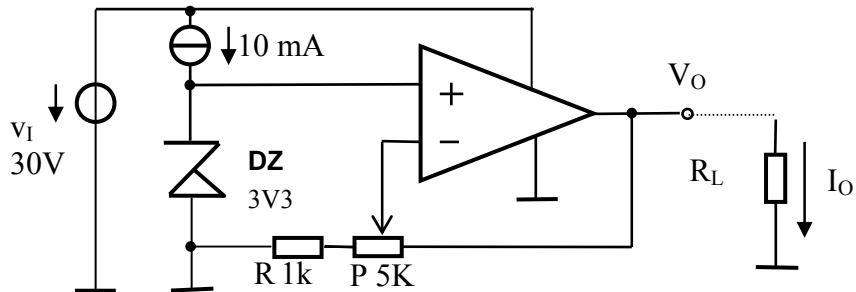
- a) What is the application of the circuit?
- b) At what end should be the tap of the potentiometer to obtain the minimum output voltage? Justify your answer.
- b) What is the adjustment range of V_O ?



2.


For op amp the maximum output current is $I_{O,OpAmp}=25\text{mA}$. Now consider $V_{Ref}=5\text{V}$, $v_I=20\text{V}$, $P=5\text{K}\Omega$, $R_1=12\text{K}\Omega$, $R_2=5\text{K}\Omega$, $R_3=4\text{K}\Omega$ and $R_L=0.75\text{K}\Omega$.

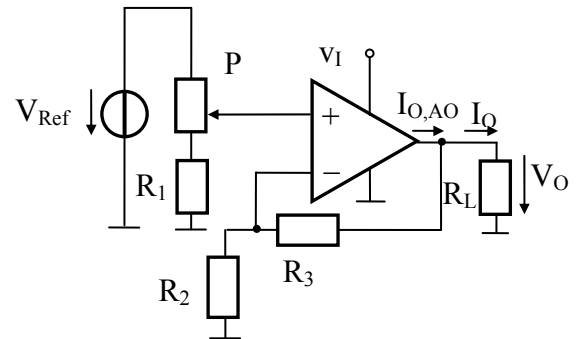- a) Find the expression and the possible range of values of v_O depending on the position of the tap of the potentiometer P.
- b) Considering R_2 an open-circuit, is the V_O range modified? If yes, recompute the V_O values.
- c) Considering R_2 an open-circuit, find the minimum value of the load resistance to maintain the operation of the circuit as voltage regulator.



3.

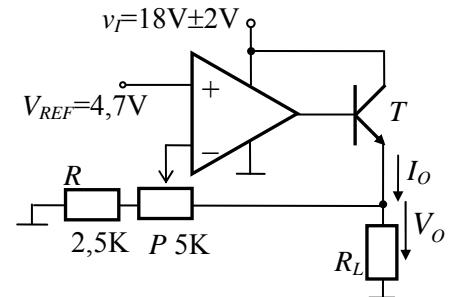
- a) What is the application of the circuit? What are the expressions and values of V_{Omax} , V_{Omin} ?
- b) How can be modified the circuit so that I_O will be limited to $I_{Omax}=750\text{mA}$?
- c) Consider the circuit in the previous question ($I_{Omax}=750\text{mA}$) and the tap of the potentiometer on the middle position. What is the maximum power dissipated by the transistor T considering $R_L=70\Omega$?



4.

For T_1 and T_2 , $V_{BE,on} = 0.6\text{V}$

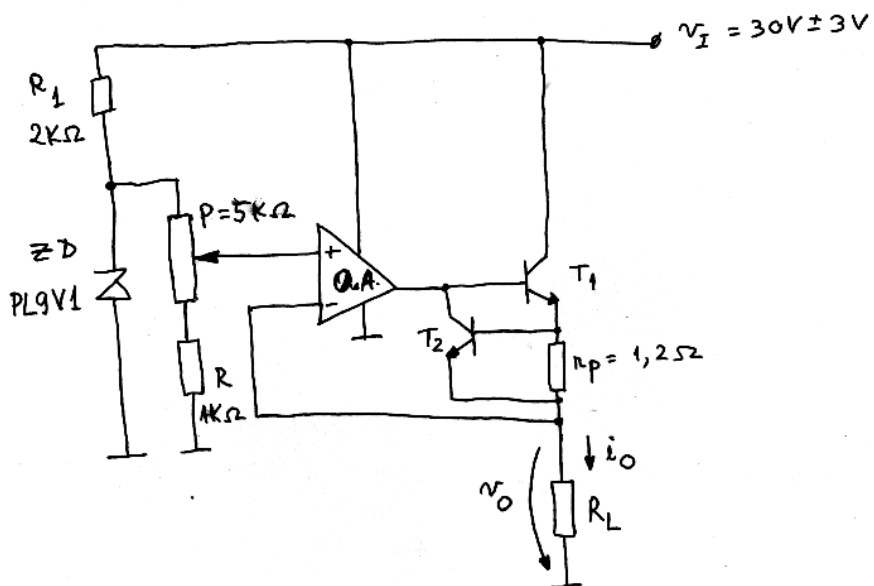- b) Find the expression and the possible range of values of v_O depending on the position of the tap of the potentiometer P.
- c) Plot the $v_O(i_O)$ output characteristic of this voltage regulator for the position of the tap of the potentiometer in the lower end, for R_L from ∞ to 0.
- d) What components form the short-circuit protection for this voltage regulator? Explain the short-circuit protection mechanism.
- e) For $R_L=50\Omega$, compute the maximum power dissipation on T_1 .



5.

$V_{REF} = 7V$ and $v_I = 14V$ are known.

- What are the expressions and the values for the minimum and maximum output voltage?
- What should be the value for the R_p resistance such that the maximum output current is limited at $0,8A$?
- Considering the conditions from b), what is the value of the power dissipated by the T transistor in short-circuit regime?
- Considering the conditions from b), what are the values for the output voltage, output current, collector-emitter voltage of the T transistor and the power dissipated by T for $R_L = 3\Omega$?

