

DESIGN ILLUSTRATION OF A SYMMETRIC OTA USING MULTIOBJECTIVE GENETIC ALGORITHMS

OUTLINE

- Motivation and related work
- Symmetric OTA
- Multiobjective optimization using genetic algorithms
- Design optimization method
- Simulations and results
- Conclusions and future development


MOTIVATION AND RELATED WORK

- **Manual analog circuit design:**
 - very difficult and complex task
 - large number of conflicting requirements
- **Automatic circuit design:**
 - great development over the past decade
 - includes **GAs** in the design process
 - industrial simulator to close the loop
 - **multiobjective optimization**

SYMMETRIC OTA

CIRCUIT DESCRIPTION

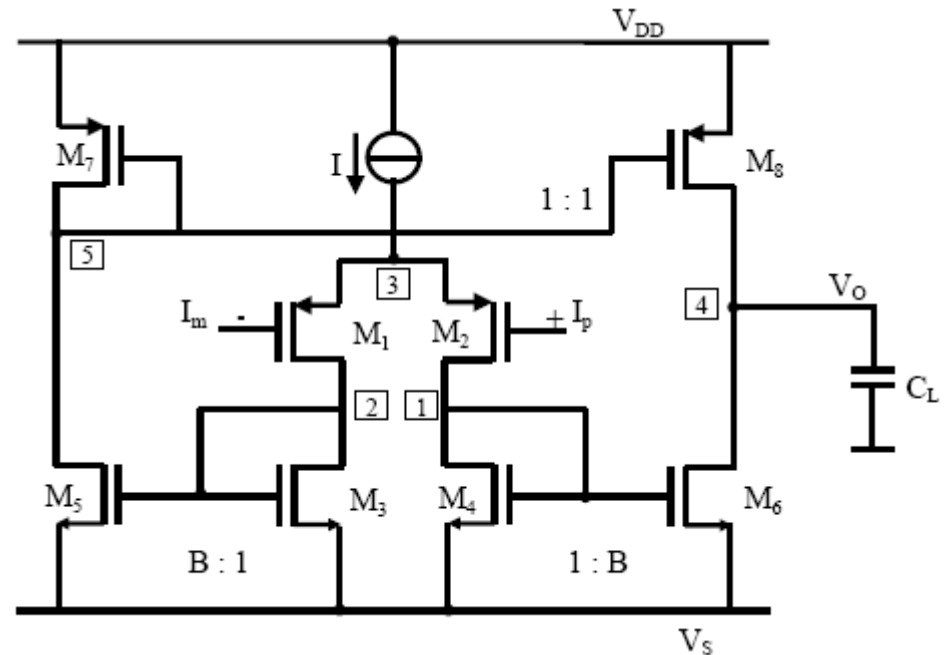- a differential pair
 M_1, M_2
- three current mirrors
 $M_7-M_8, M_3-M_5, M_4-M_6$
- two identical current mirrors
to load the input differential pair
- current gain B



- **design parameters** : the channel size (W and L) of all transistors
the biasing current I
the gain of the current mirror B

SYMMETRIC OTA

OPERATING EQUATIONS

$$A_{v0} = \frac{v_o}{v_i} = \frac{i_6 R_{N4}}{v_i} = \frac{B i_2 R_{N4}}{v_i} = \frac{B g_{m1} v_i R_{N4}}{v_i} = B g_{m1} R_{N4}$$

$$A_{v0} = 2\sqrt{K_p} \frac{V_{Ep} L_8 V_{En} L_6}{V_{Ep} L_8 + V_{En} L_6} \sqrt{\left(\frac{W}{L}\right)_1} \frac{1}{\sqrt{I}}$$

$$BW = \frac{1}{2\pi R_{N4} C_L}$$


$$BW = \frac{1}{4\pi C_L} \frac{V_{Ep} L_8 + V_{En} L_6}{V_{Ep} L_8 V_{En} L_6} IB$$

$$Area = \sum_{i=1}^N W_i L_i$$

$$P = (V_{DD} - V_{SS})(I + BI) = (V_{DD} - V_{SS})(1 + B)I$$

Simplifying assumptions: fixed Length (L) and
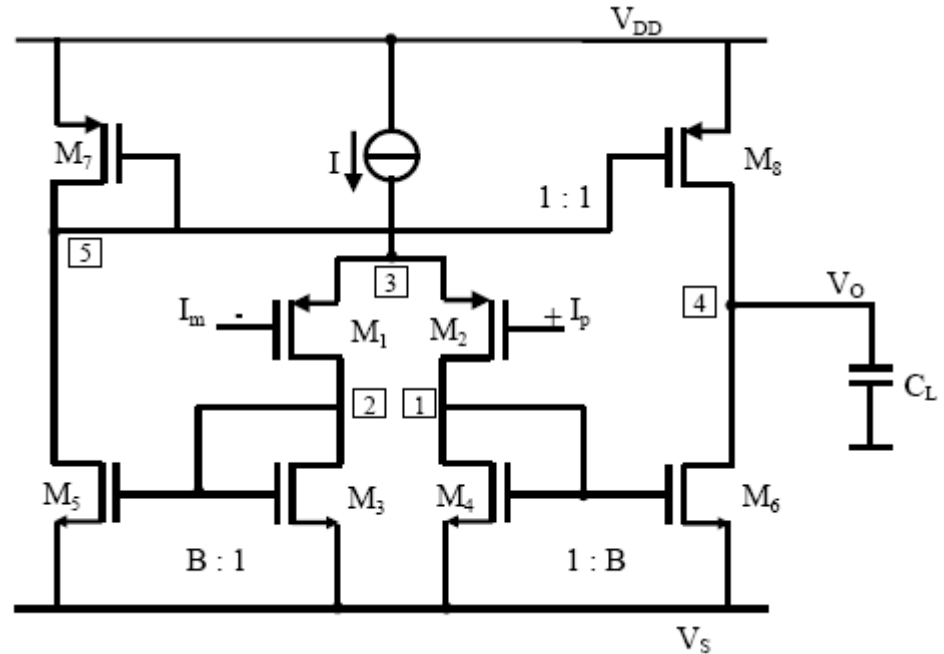
$$\left\{ \begin{array}{l} (W/L)_1 = (W/L)_2 \\ (W/L)_3 = (W/L)_4 \\ (W/L)_7 = (W/L)_8 \end{array} \right.$$



MULTIOBJECTIVE OPTIMIZATION USING GENETIC ALGORITHMS

- General Multiobjective Optimization Problem (MOP):

Find a vector x that optimizes

$$f(x) = (f_1(x), f_2(x), \dots, f_N(x))^T$$

subject to the following constraints:


$$g_j(x) < 0, j = \overline{1, \dots, M}$$

$$h_k(x) = 0, k = \overline{1, \dots, K}$$

$$a(l) \leq x(l) \leq b(l), 1 \leq l \leq n$$

Result: several optimal objective vectors (the **Pareto front**)

DESIGN OPTIMIZATION METHOD

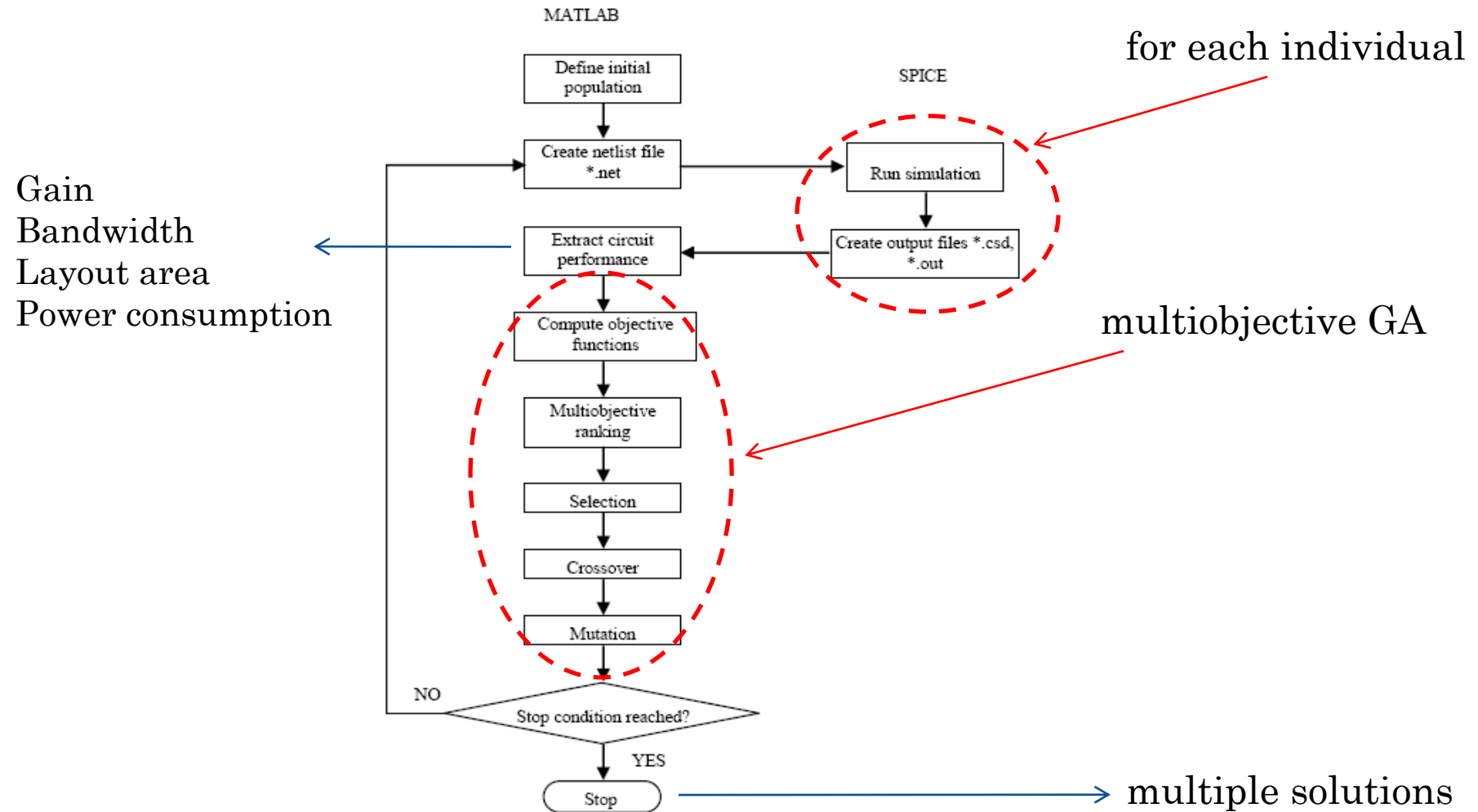

SIMULATIONS AND RESULTS

SIMULATION CONDITIONS

- Chromosome: $[W_1 W_3 W_7 I]$

- Design specifications:

No.	Specification	Desired value
1	Gain	>200
2	Bandwidth	>150KHz
3	Layout area	Minimized
4	Power consumption	Minimized

- Objective functions: absolute errors, with respect to the desired values

- Settings and constraints: $L_1 = L_2 = 1\mu m$


$$L_3 = L_4 = L_5 = L_6 = 10\mu m$$

$$(W / L)_1 > 0.036I$$

SIMULATIONS AND RESULTS

RESULTS – RANK HISTOGRAM

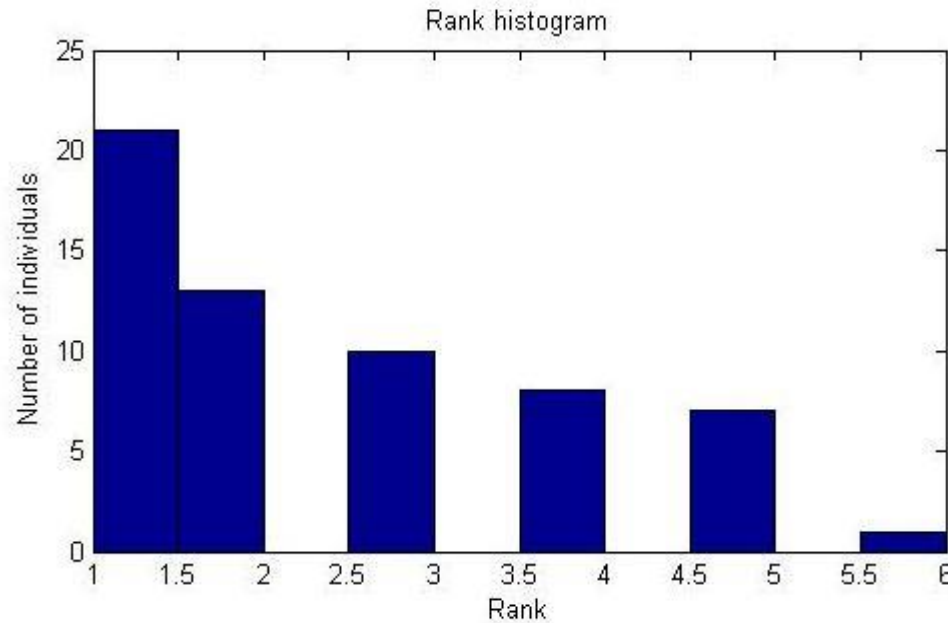
- 60 individuals, 100 generations
- 21 individuals on the final Pareto front



Rank histogram for the final Pareto front

SIMULATIONS AND RESULTS


RESULTS – BANDWIDTH VS. GAIN

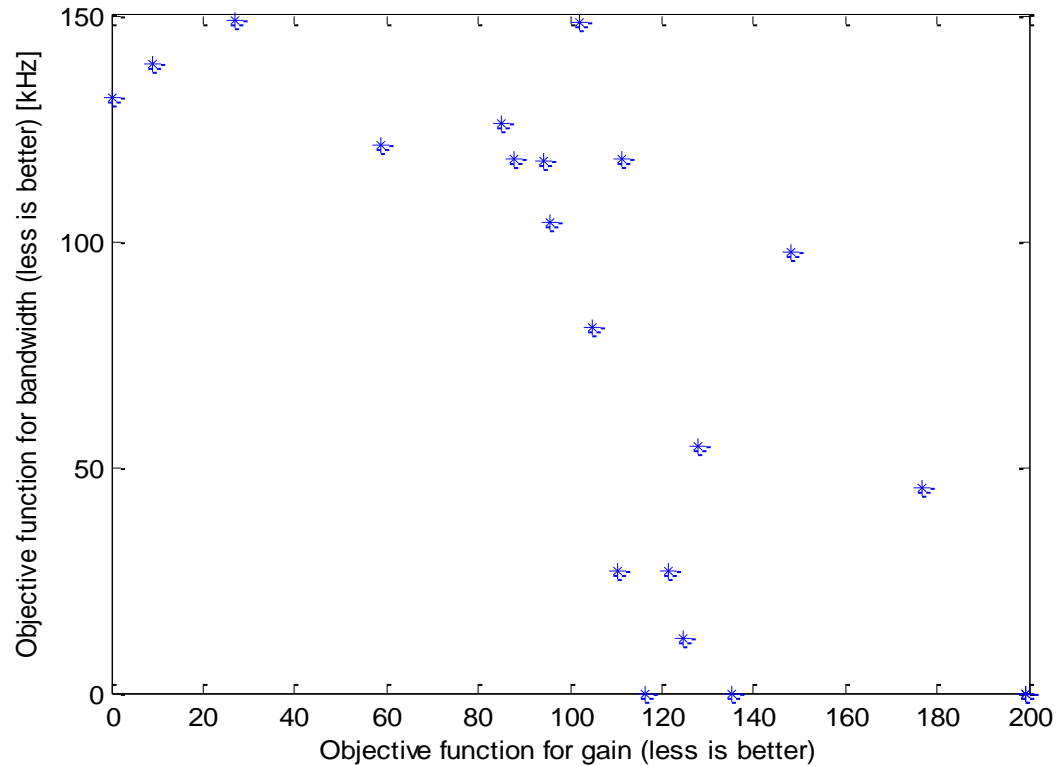

Trade-off between bandwidth and gain

SIMULATIONS AND RESULTS

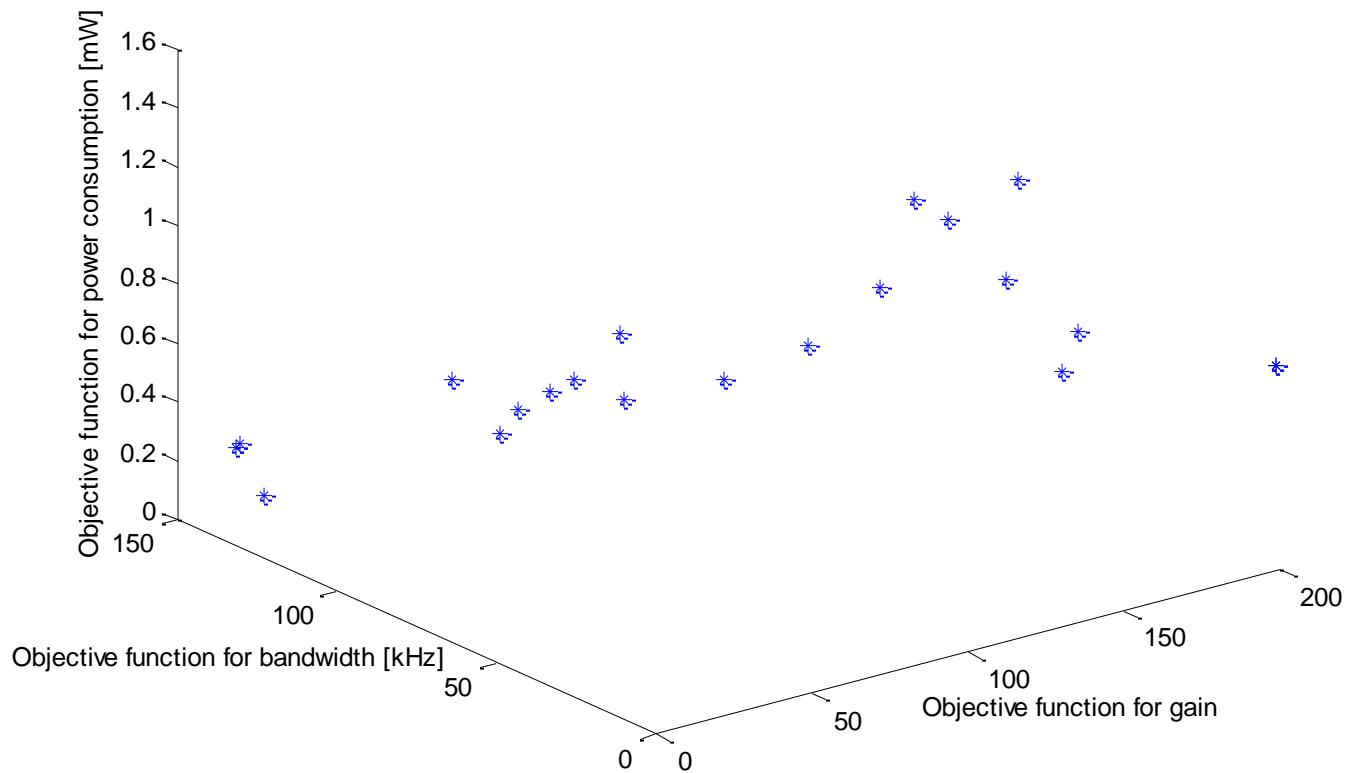RESULTS – GAIN VS. BANDWIDTH VS. POWER CONSUMPTION



3D plot for gain, bandwidth and power consumption

CONCLUSIONS AND FUTURE DEVELOPMENT

- design illustration of a multiobjective optimization method
- “greater than” and “minimum” type design specifications
- Matlab/Spice based implementation
- solutions located on the Pareto front



time consuming



modular structure



the designer makes the final choice

- adjustments and testing on more complex circuits