

## Table of Contents

Preface .....	5
Experiment No.II.1 BJT and MOSFET Static Characteristics.....	7
Experiment No.II.2 Single–Stage BJT Amplifiers. The CE, CC and CB Configurations .....	19
Experiment No.II.3 The Frequency Response of the Single Stage BJT Amplifier in CE Configuration .....	25
Experiment No.II.4 The Influence of the Feedback’s Sign and Feedback’s Amount on Circuit Functions.....	33
Experiment No.II.5 NF Effects on an Amplifier’s Parameters.....	43
Experiment No.II.6 DC Linear Voltage Regulator.....	53
Experiment No.II.7 Sinusoidal Oscillators .....	61
Experiment No.II.8 Multivibrator Circuits using the IC-555 Timer.....	69
Experiment No.II.9 The Differential Stage .....	77
Experiment No.II.10 Class B Amplifier .....	87
Experiment No.II.11 Class D Amplifier.....	95
Appendix .....	101
References .....	103