

## Table of Contents

Preface .....	5
Experiment No.1	
Lab Instrumentation.....	7
Experiment No.2	
DR Switching Circuits, Two-Port and Multi-Port Networks.....	19
Experiment No.3	
Switching Two-Port DC Networks .....	27
Experiment No.4	
Single-Phase Rectifiers with Capacitive Filter.....	35
Experiment No.5	
Semiconductor Diodes.....	43
Experiment No.6	
The Silicon Controlled Rectifier (SCR) .....	55
Experiment No.7	
Voltage Comparators with Operational Amplifiers-Simple Comparators..	63
Experiment No.8	
Voltage Comparators with Operational Amplifiers-Hysteresis Comparators.....	71
Experiment No.9	
Basic Amplifiers with Op-Amp.....	77
Experiment No.10	
Three-Port TR Network.....	87
Experiment No.11	
CMOS Transmission Gate Circuits .....	95
Experiment No.12	
Logic Circuits with BJT.....	103
Appendix .....	109
References .....	111